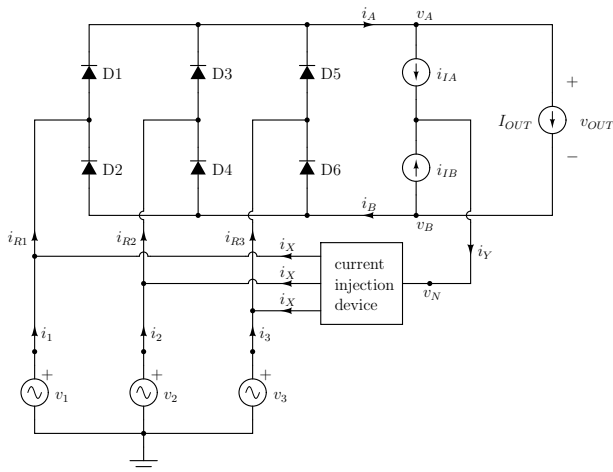


how to improve the THD?

The Third Harmonic Current Injection

1. patch the gaps in the input currents
2. do some shaping

what is this all about?



current injection device


a magnetic device that provides:

$$i_X = \frac{1}{3} i_Y$$

$$v_N = \frac{1}{3} (v_1 + v_2 + v_3) = 0$$

- patching even where not needed ...
- more to be said about the device ...
- hard to put parallel events into a sequence ...
- but, let's take a closer look ...

let's complicate a little bit

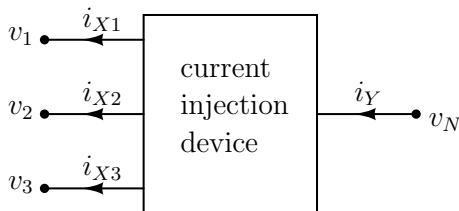

some circuit theory ...

8 variables introduced

4 element equations needed

the remaining 4 will be covered by KCL and KVL

$$i_{X1} = \frac{1}{3} i_Y$$

$$i_{X2} = \frac{1}{3} i_Y$$

$$i_{X3} = \frac{1}{3} i_Y$$


$$v_N = \frac{1}{3} (v_1 + v_2 + v_3)$$

the device is **resistive**, please remember

$$v_N i_Y - v_1 i_1 - v_2 i_2 - v_3 i_3 = 0$$

the device is **non-dissipative**, please remember this

back to the circuit ...

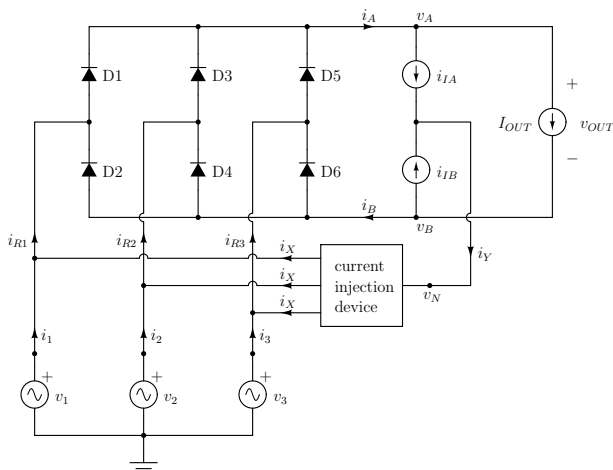

some equations, KCL, ...

$$i_k = i_{Rk} - i_X, \quad k \in \{1, 2, 3\}$$

$$i_X = \frac{1}{3} i_Y$$

$$i_{IA} = i_{IB} = \frac{1}{2} i_Y$$

$$i_A = I_{OUT} + i_{IA} = I_{OUT} + \frac{1}{2} i_Y$$

$$i_B = I_{OUT} - i_{IB} = I_{OUT} - \frac{1}{2} i_Y$$

some equations normalized

$$j_X \triangleq \frac{i_X}{I_{OUT}}$$

$$j_k = j_{Rk} - j_X, \quad k \in \{1, 2, 3\}$$

$$j_X = \frac{1}{3} j_Y$$

$$j_{IA} = j_{IB} = \frac{1}{2} j_Y$$

$$j_A = 1 + j_{IA} = 1 + \frac{1}{2} j_Y$$

$$j_B = 1 - j_{IB} = 1 - \frac{1}{2} j_Y$$

how to get j_{Rk} , $k \in \{1, 2, 3\}$?

$$j_{R1} = d_1 j_A - d_2 j_B$$

$$j_{R2} = d_3 j_A - d_4 j_B$$

$$j_{R3} = d_5 j_A - d_6 j_B$$

or, in general terms

$$j_{Rk} = d_{2k-1} j_A - d_{2k} j_B$$

for

$$k \in \{1, 2, 3\}$$

some symmetry

since

$$d_1(\omega_0 t) = d_3\left(\omega_0 t + \frac{2\pi}{3}\right) = d_5\left(\omega_0 t + \frac{4\pi}{3}\right)$$

$$d_2(\omega_0 t) = d_4\left(\omega_0 t + \frac{2\pi}{3}\right) = d_6\left(\omega_0 t + \frac{4\pi}{3}\right)$$

to have

$$j_1(\omega_0 t) = j_2\left(\omega_0 t + \frac{2\pi}{3}\right) = j_3\left(\omega_0 t + \frac{4\pi}{3}\right)$$

we need

$$j_Y(\omega_0 t) = j_Y\left(\omega_0 t + \frac{2\pi}{3}\right) = j_Y\left(\omega_0 t + \frac{4\pi}{3}\right)$$

let's assume i_Y

$$i_Y = k I_{OUT} \cos(3\omega_0 t - \phi)$$

$j_Y = k \cos(3\omega_0 t - \phi)$

range:

1. for the continuous conduction mode $-2 < k < 2$
2. let us assume $-\pi < \phi < \pi$

which couple (k, ϕ) minimizes the THD?

j_Y limitations

for the continuous conduction mode (CCM):

$$j_A > 0 \quad \Rightarrow \quad 1 + \frac{1}{2} j_Y > 0$$

$$j_B > 0 \quad \Rightarrow \quad 1 - \frac{1}{2} j_Y > 0$$

$$-2 < j_Y < 2$$

or

$$-2 I_{OUT} < i_Y < 2 I_{OUT}$$

the input currents

plugging in expressions for i_{Rk} and i_X

$$j_k = d_{2k-1} \left(1 + \frac{1}{2} j_Y\right) - d_{2k} \left(1 - \frac{1}{2} j_Y\right) - \frac{1}{3} j_Y$$

there are three cases to be considered:

$$j_k = \begin{cases} 1 + \frac{1}{6} j_Y & \text{for } d_{2k-1} = 1 \text{ and } d_{2k} = 0 \\ -1 + \frac{1}{6} j_Y & \text{for } d_{2k-1} = 0 \text{ and } d_{2k} = 1 \\ -\frac{1}{3} j_Y & \text{for } d_{2k-1} = 0 \text{ and } d_{2k} = 0 \end{cases}$$

more about j_Y

to get

$$j_Y(\omega_0 t) = j_Y\left(\omega_0 t + \frac{2\pi}{3}\right) = j_Y\left(\omega_0 t + \frac{4\pi}{3}\right)$$

we need

$$j_Y(\omega_0 t) = j_Y\left(\omega_0 t + \frac{2\pi}{3}\right)$$

meaning that j_Y is periodic with $\frac{1}{3} T_0$, i.e. the fundamental frequency of i_Y is $3 f_0$!

thus, **the third-harmonic current injection** is the simplest case

optimization over k and ϕ

$$j_1 = \begin{cases} 1 + \frac{1}{6} j_Y & \text{for } d_1 = 1 \text{ and } d_2 = 0 \\ -1 + \frac{1}{6} j_Y & \text{for } d_1 = 0 \text{ and } d_2 = 1 \\ -\frac{1}{3} j_Y & \text{for } d_1 = 0 \text{ and } d_2 = 0 \end{cases}$$


and

$$j_Y = k \cos(3\omega_0 t - \phi)$$


let's go to work!

goal: minimize the THD


numerical optimization, 1, THD [%]

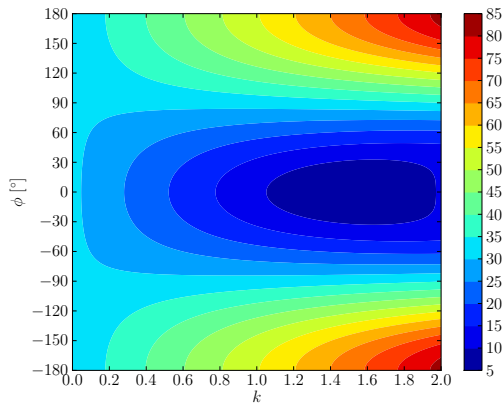


numerical optimization, 2, THD [%]

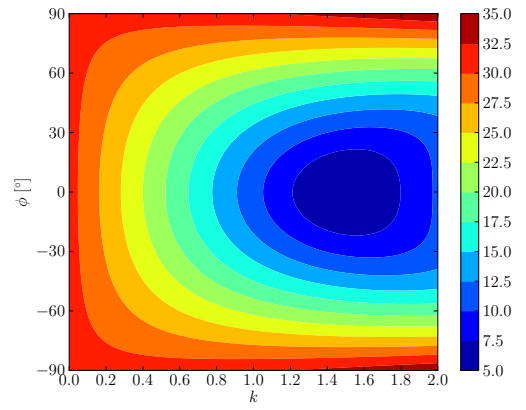


numerical optimization, 3, THD [%]

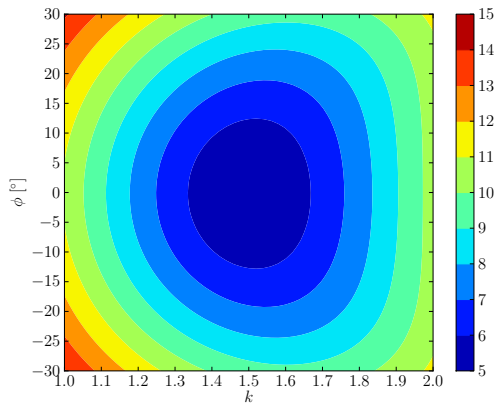

numerical optimization, 4, THD [%]

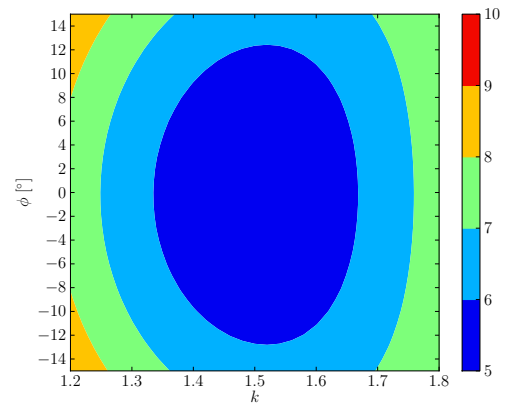

numerical optimization, 5, THD [%]

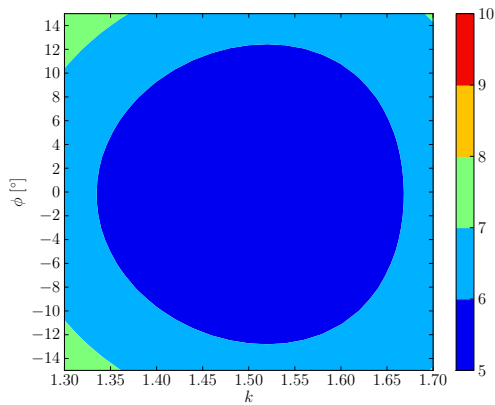

numerical optimization, conclusions

- improvement possible!
- $5\% < THD < 6\%$ achievable
- $k \approx 1.5$, $\phi \approx 0$
- it is promising to continue
- analytical optimization?
- circuit?
- let's continue ...

analytical optimization, start

$$j_1 = \begin{cases} 1 + \frac{1}{6} j_Y & \text{for } d_1 = 1 \text{ and } d_2 = 0 \\ -1 + \frac{1}{6} j_Y & \text{for } d_1 = 0 \text{ and } d_2 = 1 \\ -\frac{1}{3} j_Y & \text{for } d_1 = 0 \text{ and } d_2 = 0 \end{cases}$$

and

$$j_Y = k \cos(3\omega_0 t - \phi)$$

analytical optimization, rms and the fundamental

after lots of work (fortunately, wxMaxima's):

$$J_{RMS} = \frac{\sqrt{k^2 + 24}}{6}$$

$$J_{1Cm} = \frac{3k \cos \phi + 48}{8\sqrt{3}\pi}$$

$$J_{1Sm} = \frac{3\sqrt{3}k \sin \phi}{8\pi}$$

$$J_{1RMS} = \sqrt{\frac{J_{1Cm}^2 + J_{1Sm}^2}{2}}$$

$$J_{1RMS} = \frac{\sqrt{768 + 27k^2 + 96k \cos \phi - 24k^2 (\cos \phi)^2}}{8\sqrt{2}\pi}$$

analytical optimization, make it simple


$$THD = \sqrt{\left(\frac{J_{RMS}}{J_{1RMS}}\right)^2 - 1}$$

make it simple: to minimize THD is to minimize

$$y\left(k,\phi\right)\triangleq\left(\frac{J_{RMS}}{J_{1RMS}}\right)^2$$

$$y\left(k,\phi\right)=\frac{2\pi^2\left(16k^2+384\pi^2\right)}{6912+243k^2+864k\cos\phi-216k^2\left(\cos\phi\right)^2}$$

$$k_{opt}\left(\phi\right)$$

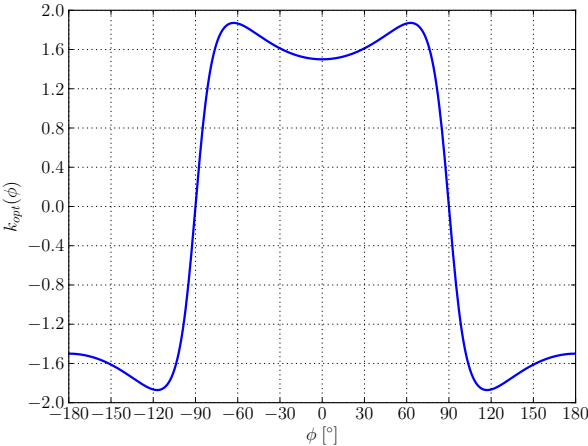

$$THD_{MIN},\phi_{OPT},\phi_{OPT}$$

$$THD_{MIN}=\min\left(THD\left(k_{opt}\left(\phi\right),\phi\right)\right)=THD\left(k_{OPT},\phi_{OPT}\right)$$

$$\phi_{OPT}=0$$

$$k_{OPT}=k_{opt}(0)=\frac{3}{2}$$

$$THD_{MIN}=\sqrt{\frac{32\pi^2}{315}-1}\approx 5.12\%$$

and that’s all the third harmonic current injection can do

$$PF\left(k_{OPT},\phi_{OPT}\right)$$

$$PF\left(k,\phi\right)=\frac{\sqrt{6}\left(3k\cos\phi+48\right)}{8\pi\sqrt{k^2+24}}$$

$$PF\left(\frac{3}{2},0\right)=\frac{3\sqrt{70}}{8\pi}\approx 0.9987$$


we could have optimized $PF\left(k,\phi\right)\dots$

analytical optimization, let’s fix ϕ


$$\frac{\partial y\left(k,\phi\right)}{\partial k}=0$$

$$k_{opt}\left(\phi\right)=\frac{\sqrt{576\left(\cos\phi\right)^4+624\left(\cos\phi\right)^2+25}-24\left(\cos\phi\right)^2-5}{4\cos\phi}$$

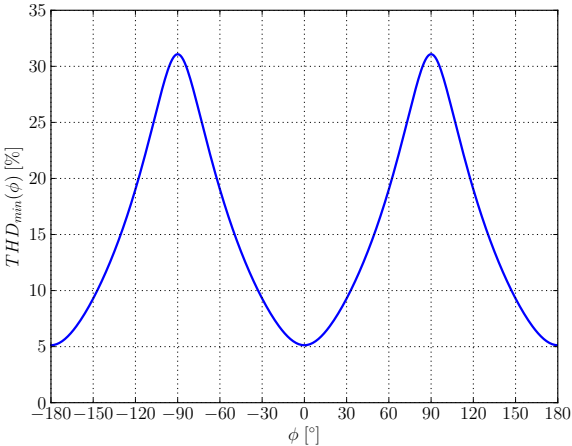
$$THD\left(k_{opt}\left(\phi\right),\phi\right)$$


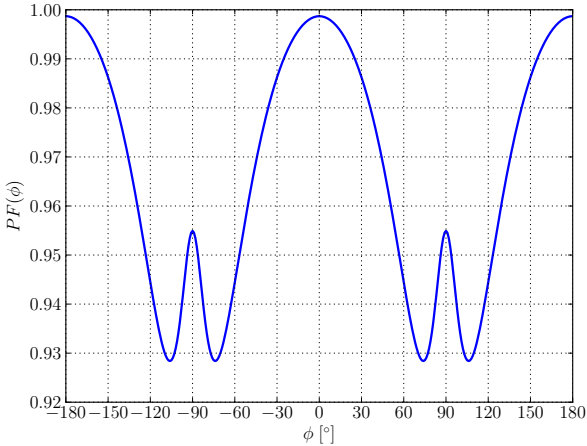
$$PF\left(k_{opt}\left(\phi\right),\phi\right)$$


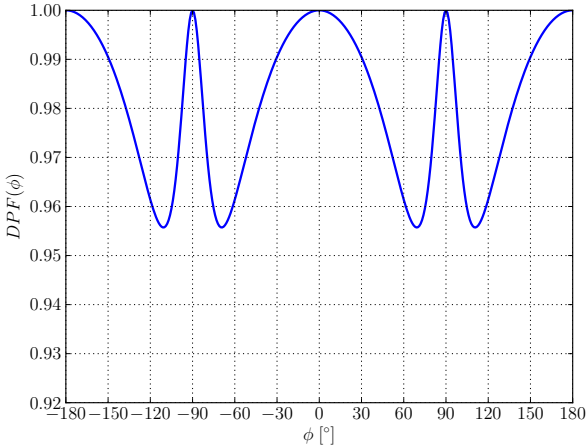
$$DPF\left(k_{opt}\left(\phi\right),\phi\right)$$



$$DPF\left(k_{OPT},\phi_{OPT}\right)$$

$$DPF\left(k,\phi\right)=\frac{\sqrt{3}\left(k\cos\phi+16\right)}{\sqrt{768+27k^2+96k\cos\phi-24k^2\left(\cos\phi\right)^2}}$$

$$DPF\left(\frac{3}{2},0\right)=1$$


$$\eta\left(k_{OPT},\phi_{OPT}\right)$$

$$\eta\left(k,\phi\right)=\frac{48}{3k\cos\phi+48}$$


$$\eta\left(\frac{3}{2},0\right)=\frac{32}{35}\approx91.43\%$$

optimizing $\eta\left(k,\phi\right)$?

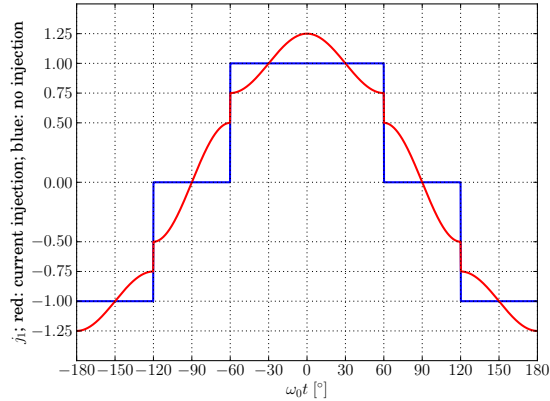
$$j_1, \text{ with and without injection}$$



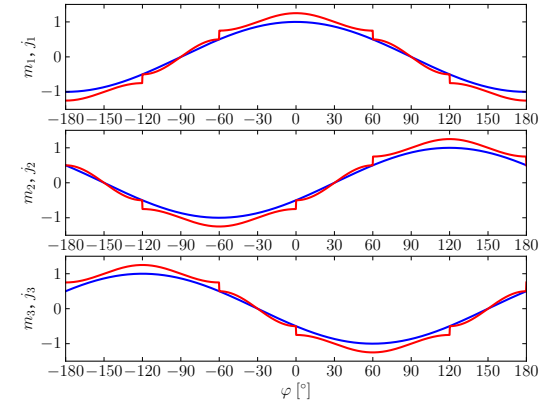
$$m_k \text{ and } j_k, \; k \in 1, 2, 3$$



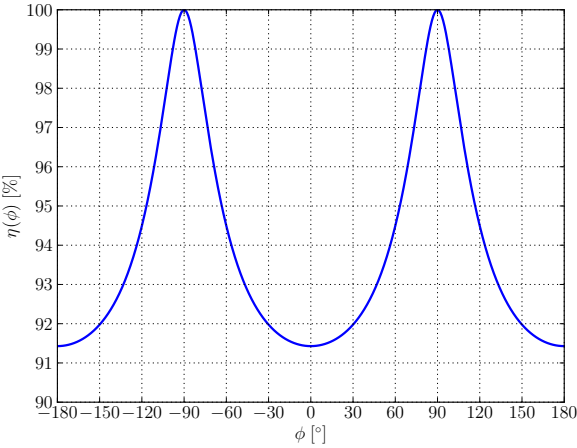
$$\eta\left(k_{opt}\left(\phi\right),\phi\right)$$



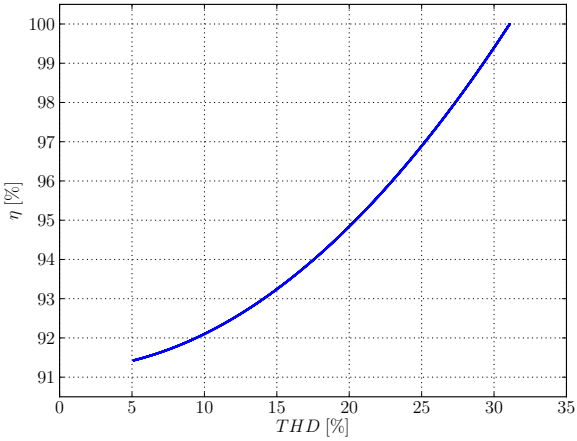
$$\eta\left(THD\right), \text{ the tradeoff}$$




$$\left|J_{1,k}\right|, \text{ with and without injection}$$

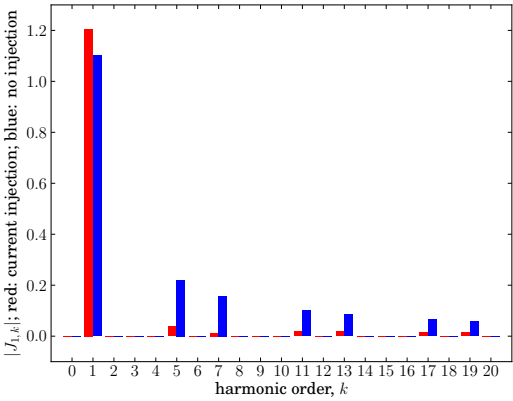


$$j_k, \text{ with ideal waveforms}$$

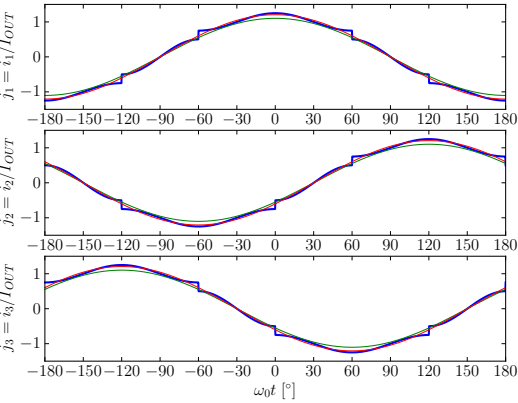

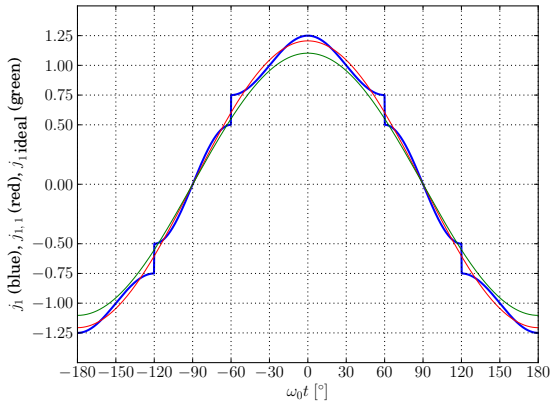
j_k , with ideal waveforms, a closer look




j_A and j_B

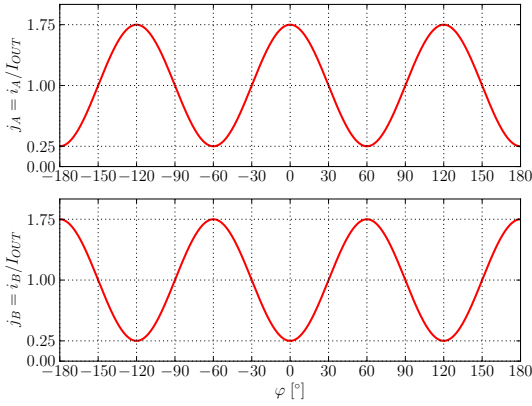

j_{IA} and j_{IB}

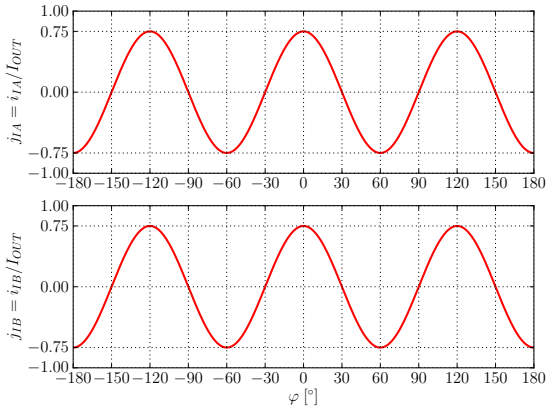

the cost ...

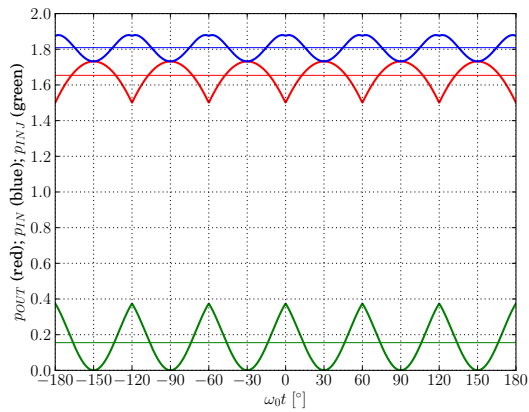

increase in the amplitude

$$J_{1m} = \frac{35\sqrt{3}}{16\pi} \approx 1.2060$$

$$J_{1m\,ideal} = \frac{2\sqrt{3}}{\pi} \approx 1.1027$$

$$J_{RMS} = \frac{\sqrt{105}}{12} \approx 0.8539$$

$$J_{1RMS} = \frac{35\sqrt{6}}{32\pi} \approx 0.8528$$

$$J_{1RMS\,ideal} = \frac{\sqrt{6}}{\pi} \approx 0.77970$$

j_A and j_B , mean and rms

$$J_A = \overline{j_A} = \langle j_A \rangle = 1$$

$$J_B = \overline{j_B} = \langle j_B \rangle = 1$$


as it was before, but

$$J_{ARMS} = \sqrt{\frac{41}{32}} \approx 1.1319 > 1$$

$$J_{BRMS} = \sqrt{\frac{41}{32}} \approx 1.1319 > 1$$

$v_D = V_D + R_D i_D$, somewhat increased losses in the diodes

j_Y and j_X

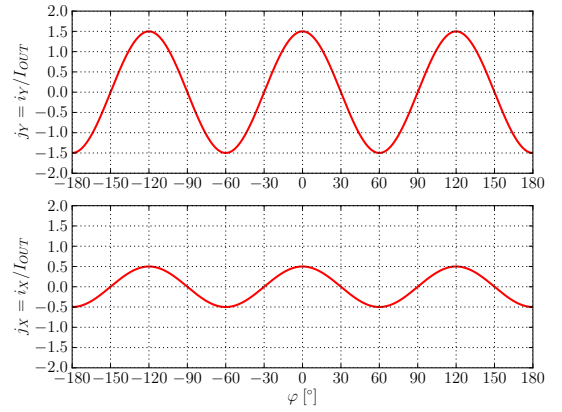

achieved


$$THD = \sqrt{\frac{32\pi^2}{315}} - 1 \approx 5.12\%$$

$$PF = \frac{3\sqrt{70}}{8\pi} \approx 0.9987$$


$$DPF = 1$$

$$\eta = \frac{32}{35} \approx 91.43\%$$


a common misconception ...

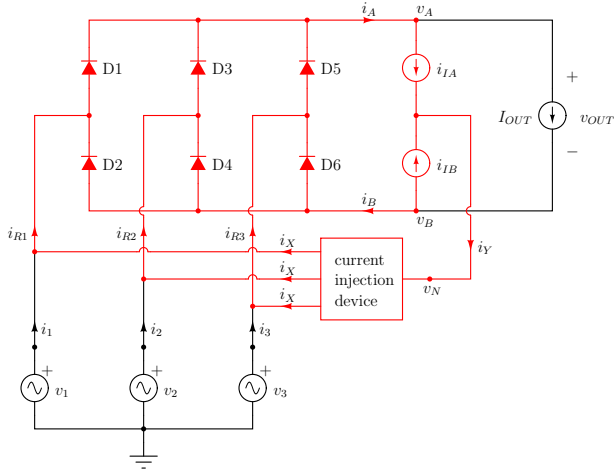

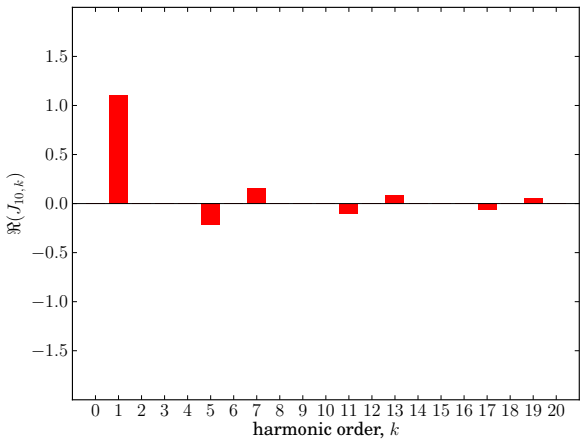
let's walk around, j_{10} , real (cosine) part



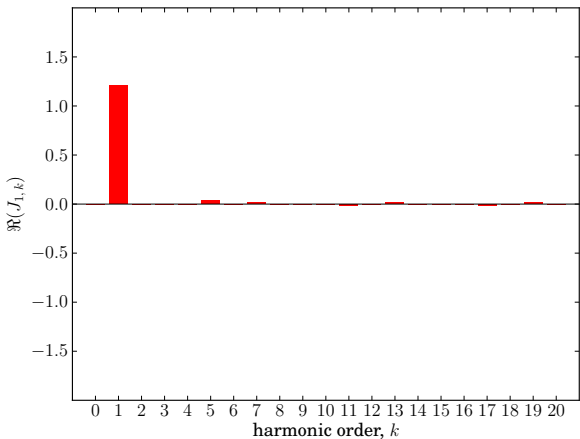
let's walk around, j_1 , real (cosine) part



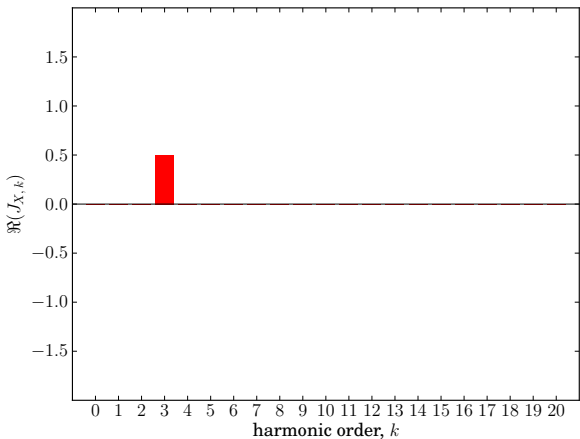
let's walk around, j_X , real (cosine) part



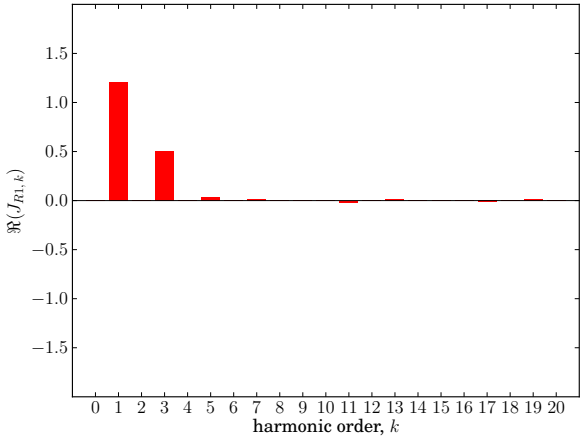
let's walk around, j_{R1} , real (cosine) part




how j_1 is fixed?

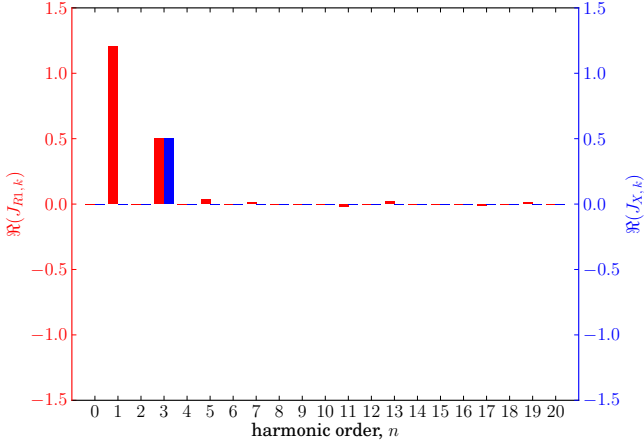

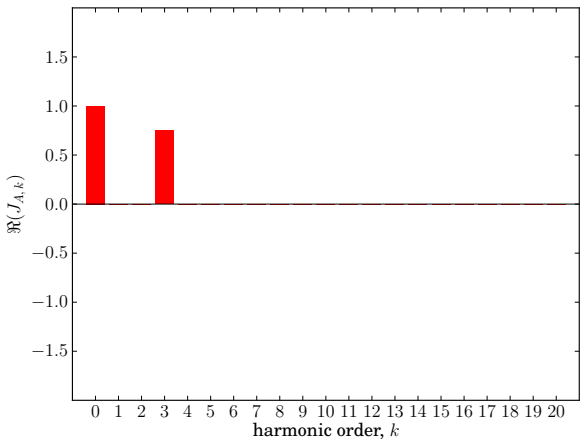
let's walk around, j_A , real (cosine) part



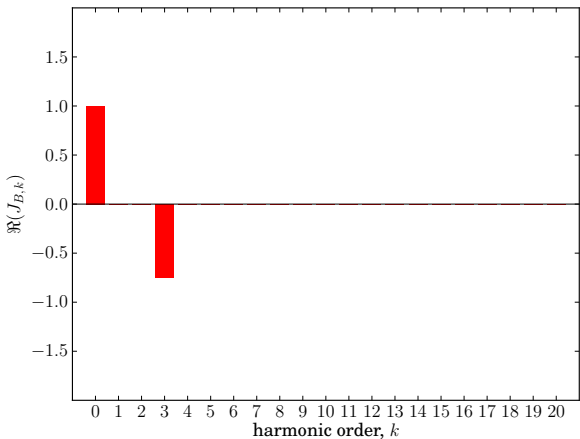
let's walk around, j_B , real (cosine) part



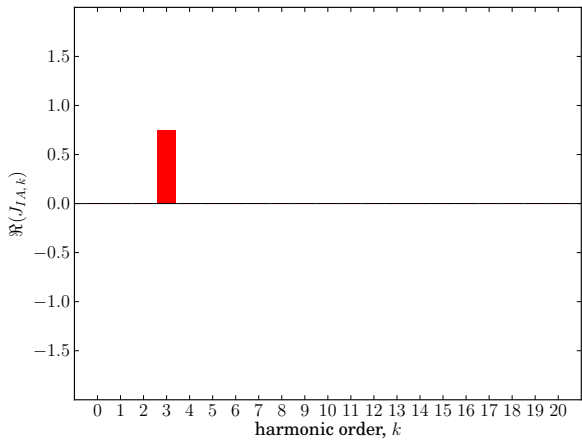
let's walk around, j_{IA} , real (cosine) part



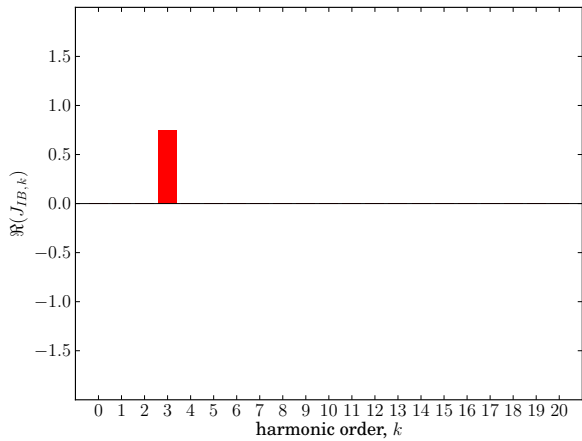let's walk around, j_{IB} , real (cosine) part



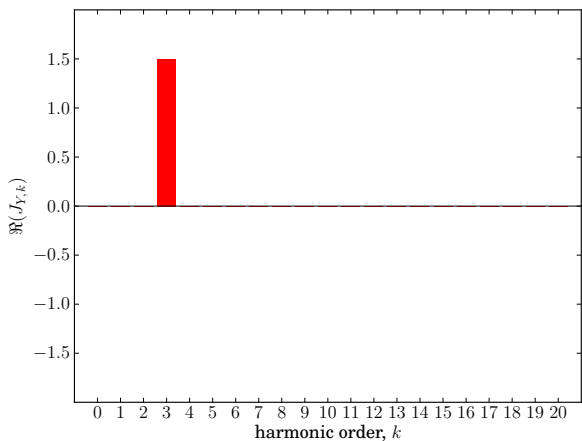let's walk around, j_Y , real (cosine) part



what the 3rd harmonic current injection is not ...

- ▶ the third harmonic current injection is not a compensation for the third harmonics in the rectifier input currents
- ▶ there were **no** third harmonics in the input currents **before** the injection was applied
- ▶ **neither** there are **any** third harmonics in the input currents **after** the injection was applied
- ▶ the third harmonics circle through and around the diode bridge
- ▶ the diode bridge creates the third harmonics and “consumes” them
- ▶ the diode bridge is a nonlinear system, capable of creating harmonics

“future work”

- ▶ only currents focused; how to get them?
- ▶ how to improve the efficiency?
- ▶ is there a way to lower the $THD = 5.12\%$ further?

published in ...

Predrag Pejović, Žarko Janda

“An Analysis of Three Phase Low Harmonic Rectifiers Applying the Third Harmonic Current Injection”

IEEE Transactions on Power Electronics,
vol. 14, no. 3, pp. 397–407, May 1999

but this research was initiated by a comparison of two circuits ...
which is our next topic ...