

RF Power Amplifier

Amplifier design: Danny de Gans



Speaker: Ruben Pellicer-Guridi



22nd of September, 2023

Berlin / Online



OSI² ONE
Build Workshop

Info sources


<https://gitlab.com/osii/rf-system/rf-power-amplifier>

The screenshot shows a web browser displaying the GitLab repository page for the '1kW peak RFPA' project. The browser's address bar shows the URL: https://gitlab.com/osii/rf-system/rf-power-amplifier/1kw-peak-rfpa/-/tree/main?ref_type=heads. The page header includes the GitLab logo, navigation links (Why GitLab, Pricing, Contact Sales, Explore), and a 'Get free trial' button. The main content area shows the repository structure for the '1kW peak RFPA' project, with a table listing files and folders, their last commit status, and the time since the last update.

Name	Last commit	Last update
PCB	Intial commit	1 year ago
assembly	Intial commit	1 year ago
enclosure	Intial commit	1 year ago
measurements	Intial commit	1 year ago
ordering	Intial commit	1 year ago
other docs	Intial commit	1 year ago
pictures	Intial commit	1 year ago
DISCLAIMER.pdf	Intial commit	1 year ago
README.md	add test document	1 year ago
RFPA_12MHz.pdf	add test document	1 year ago
cern_ohL_w_v2.pdf	Intial commit	1 year ago



Working principle

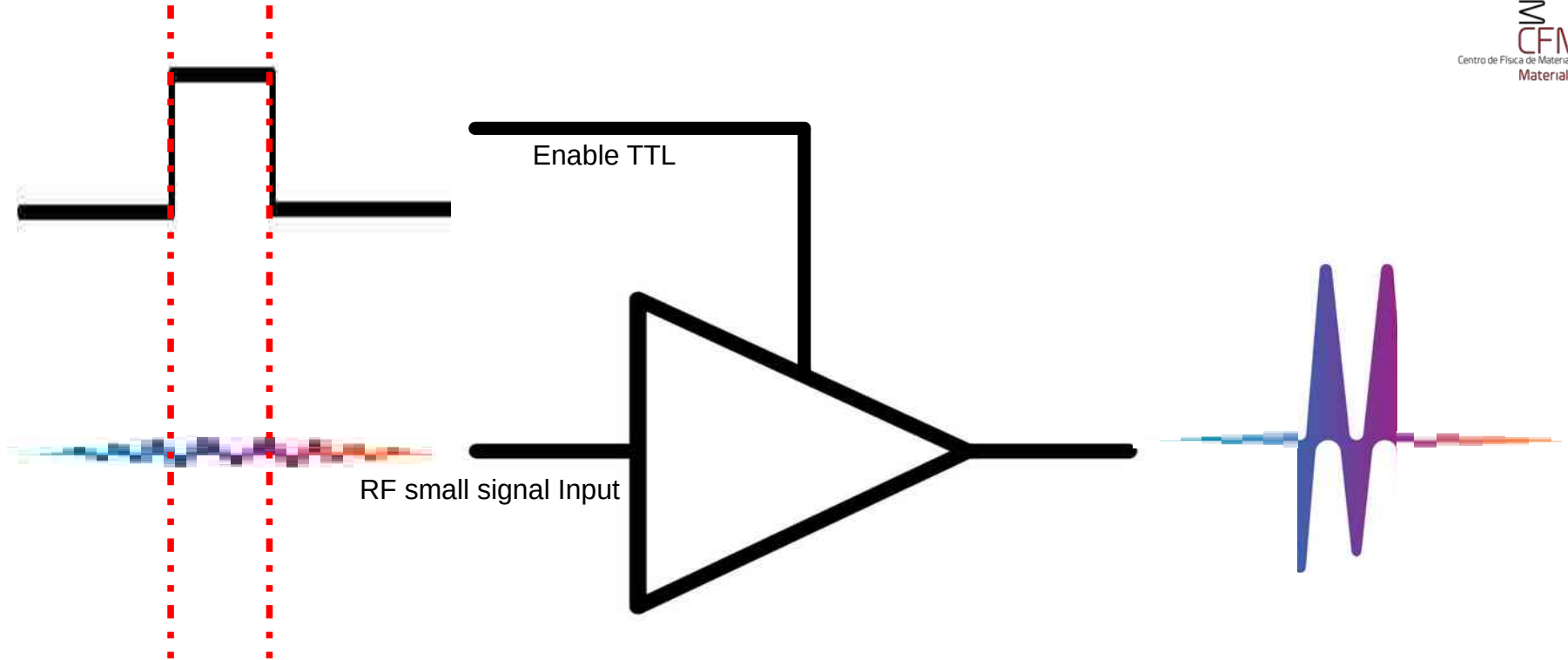


Construction

- PCBs
- Heatsink
- Transformer
- Capacitor bank
- Enclosure




Shopping

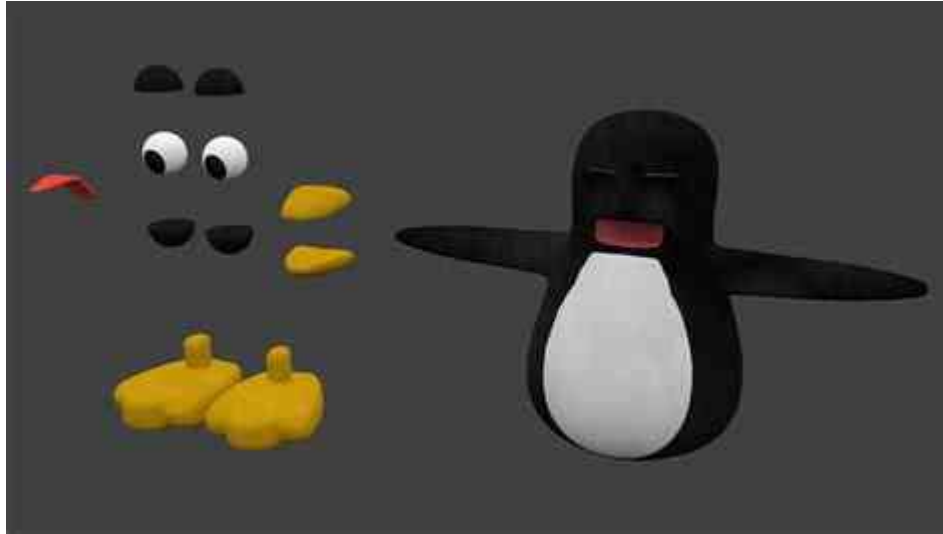




- BOM_MRlamp2.pdf
- BOM_enclosure.pdf
- PCBs
- 3D printed capacitor holders
- Copper plates for the capacitor holders
- Cables for transformer and enclosure peripherals

Budget ~1 k€



PCBs

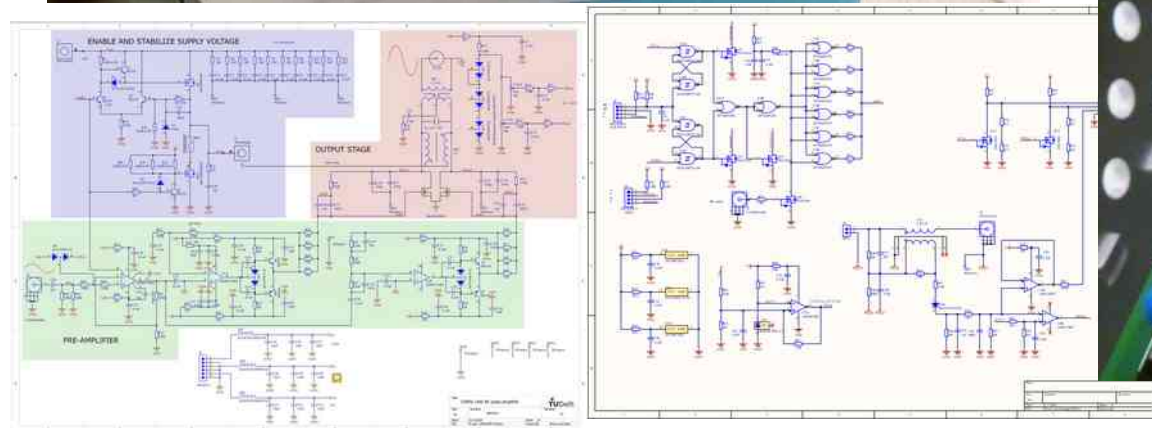

Transformer

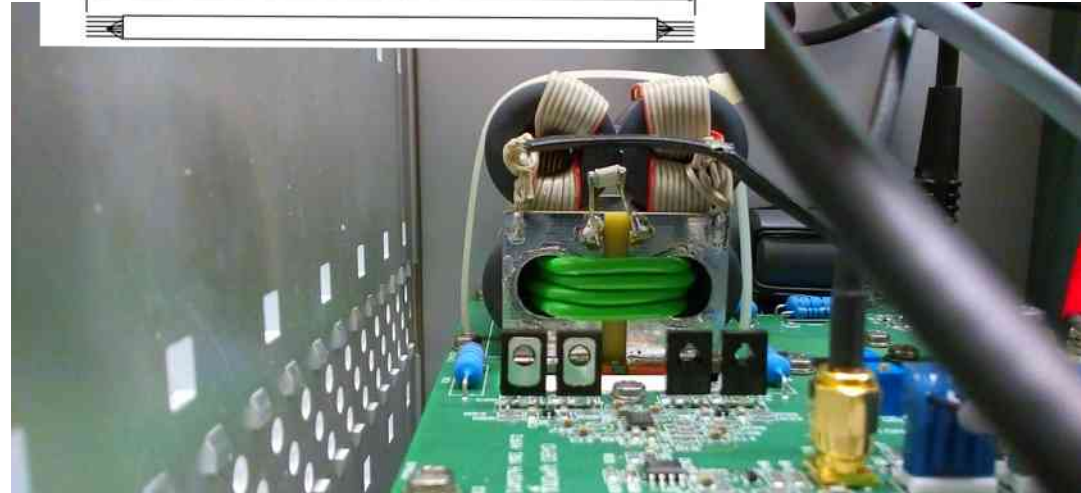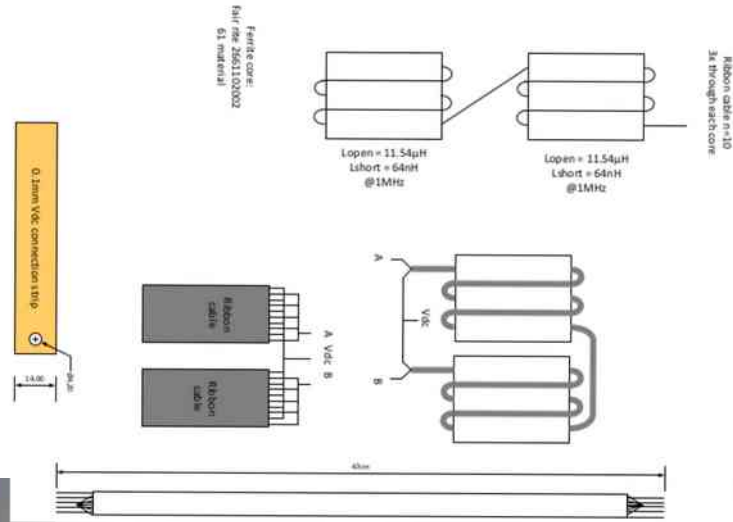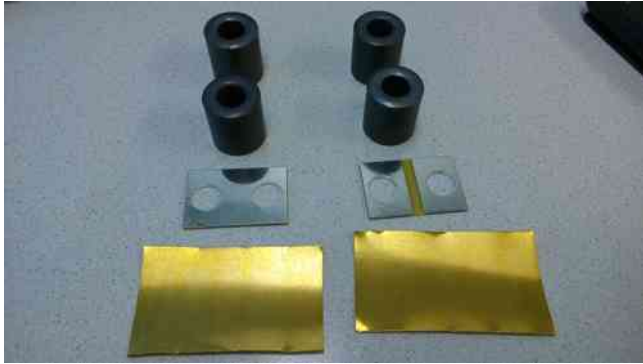

Heatsink

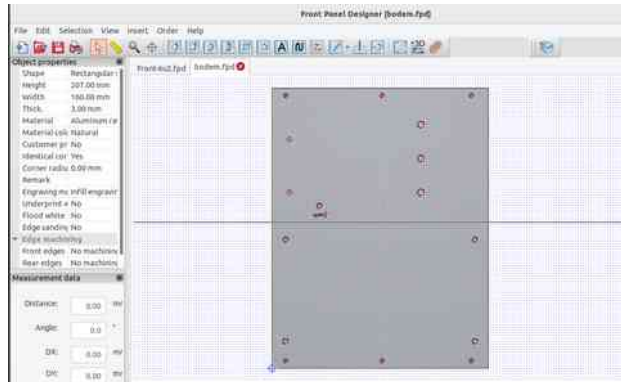
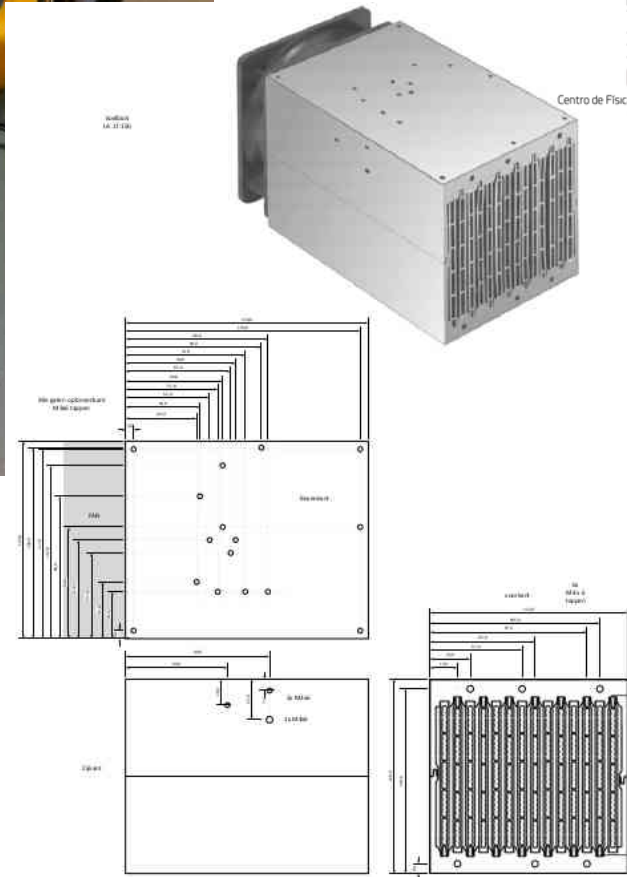


Caution

High energy capacitors → Long time to discharge



Enclosure

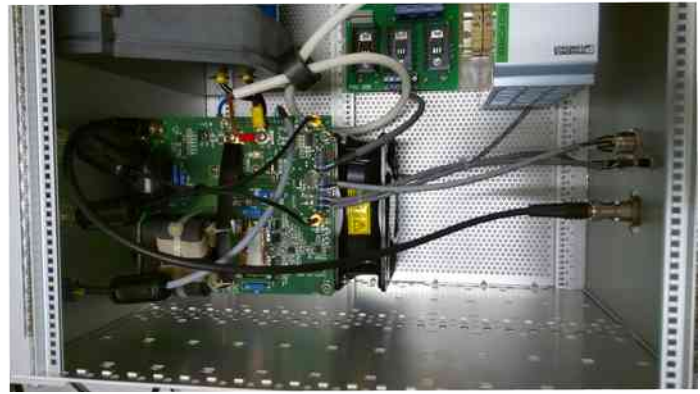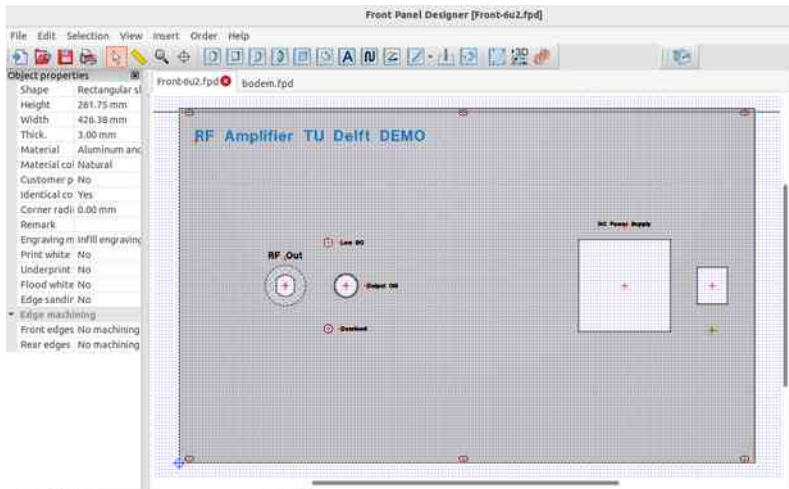


Time to test the amplifier!



Kurzschluss- Reaktion

Biassing and testing (1)

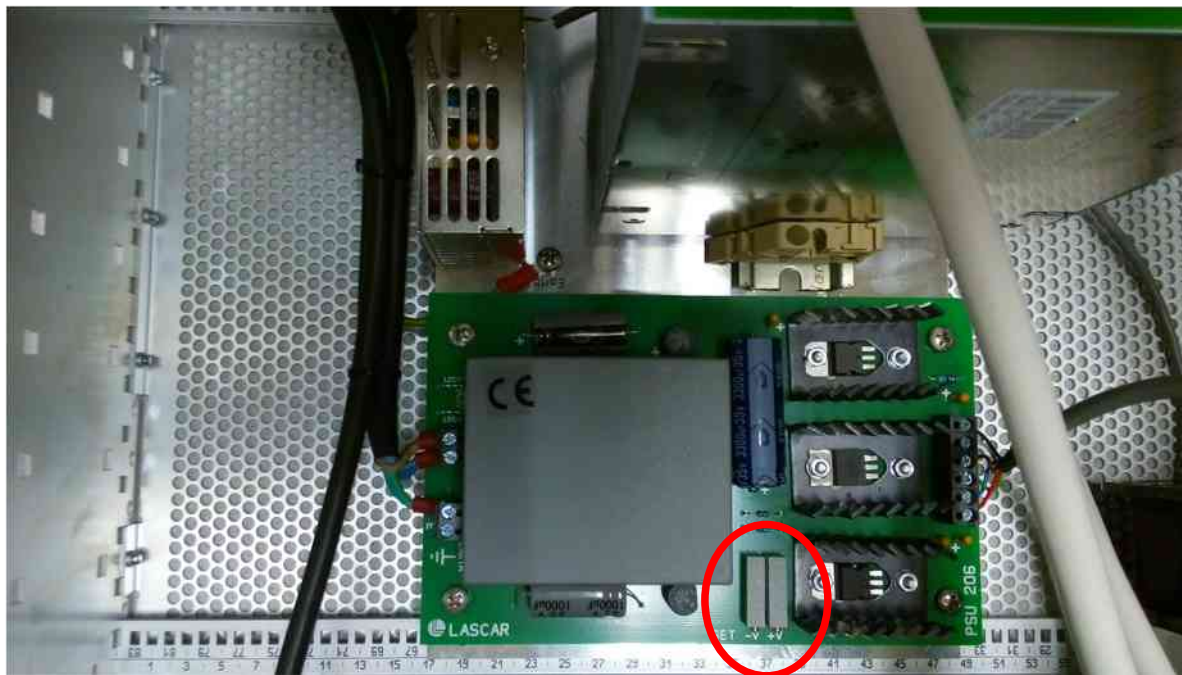- Before connecting the Lascar power supply adjust its voltages to 8V, -5V (-4V for AD8017) and +5V



Biasing and testing (2)

- Turn the Phoenix voltage adjustment potentiometer to its lowest setting




Biasing and testing (3)

- Connect a 50 Ω /100W..1kW load to the output of the amplifier.



Biassing and testing (4)

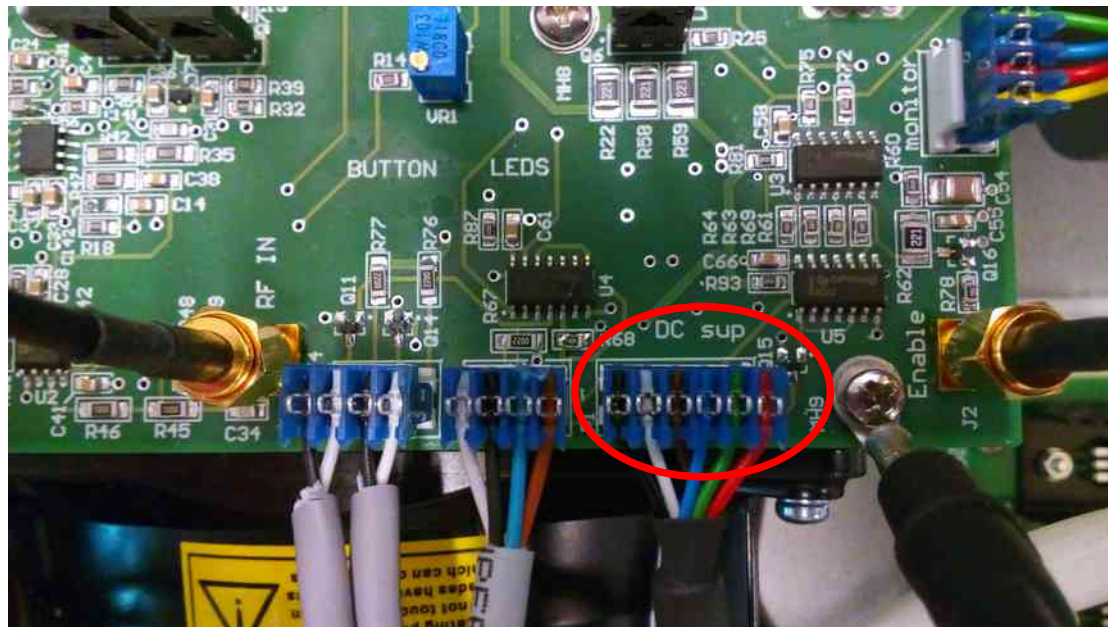- Connect P1 and switch on the power, the LOW voltage indicator LED will be on




Biasing and testing (5)

- Increase the voltage of the Phoenix power supply to about 34V



Biassing and testing (6)

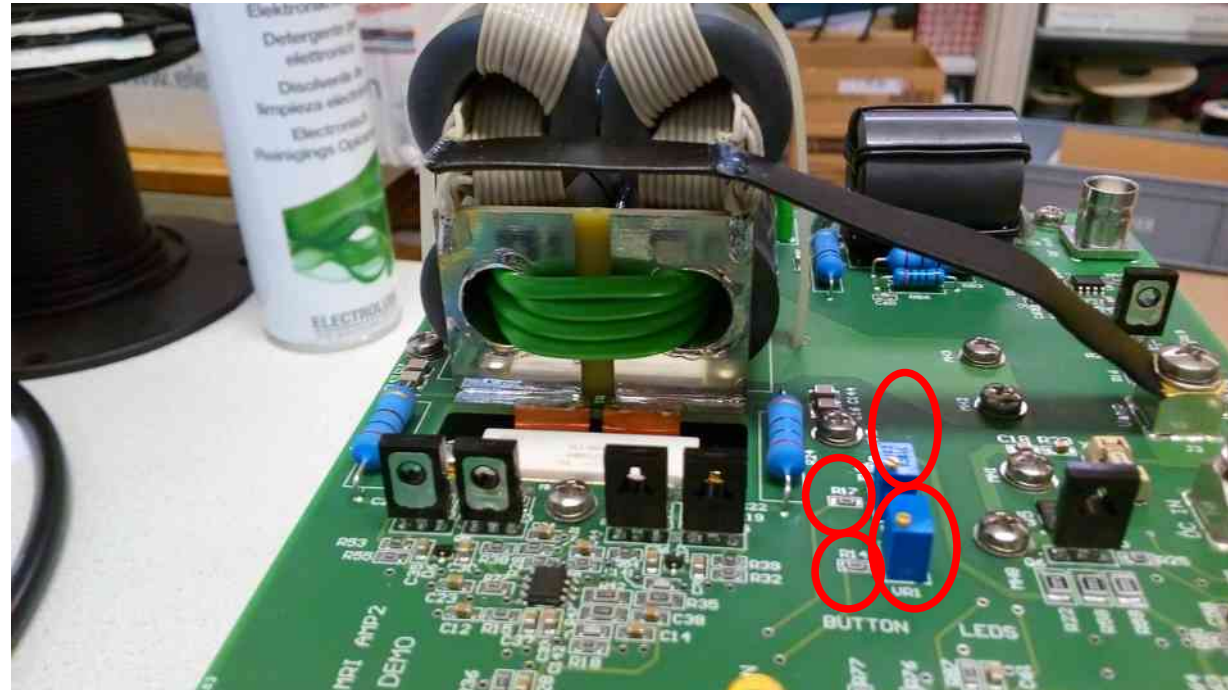- Increase the voltage at VR1,2 to 2.0V. This can be measured at R14 and R17.




Biasing and testing (7)

- Press the Output ON button on the front of the amplifier to enable the amplifier.






Biasing and testing (8)

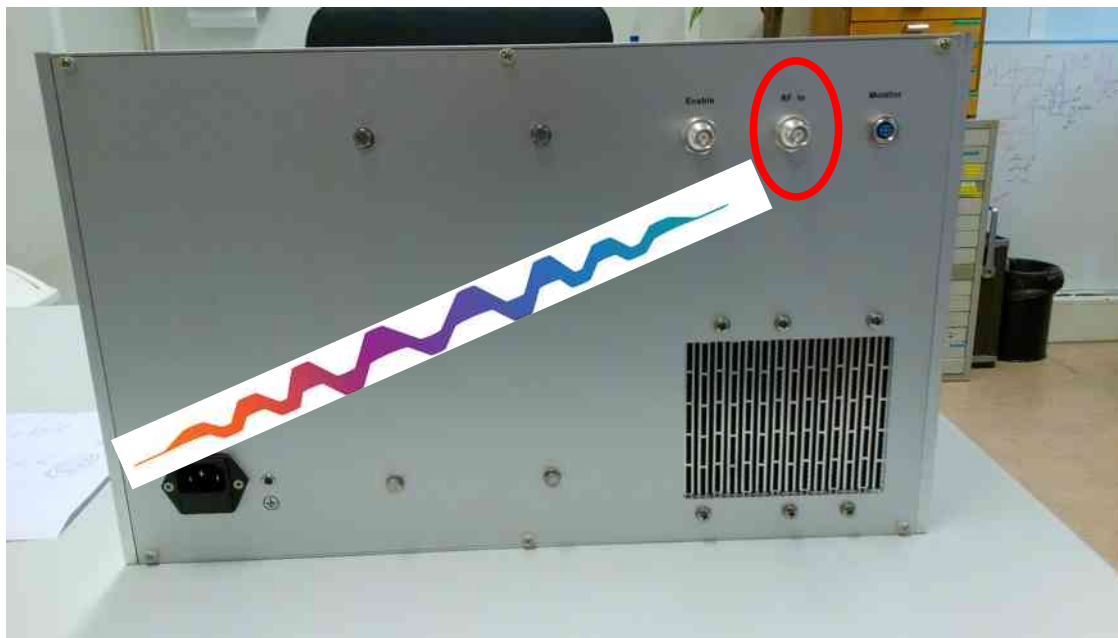- Apply a 10mV signal of 1MHz at the RF In input.



Biassing and testing (9)

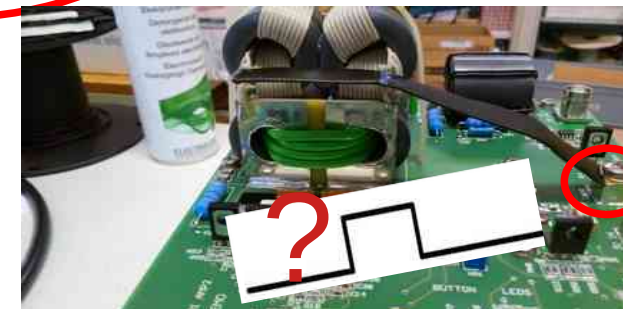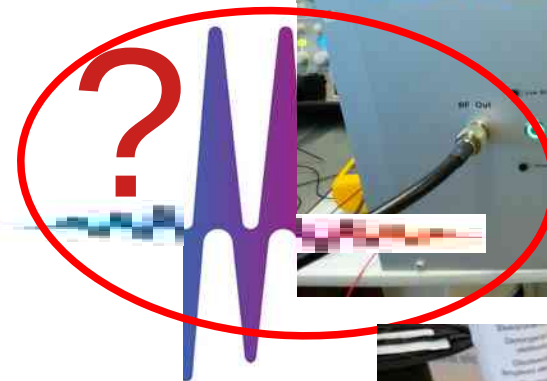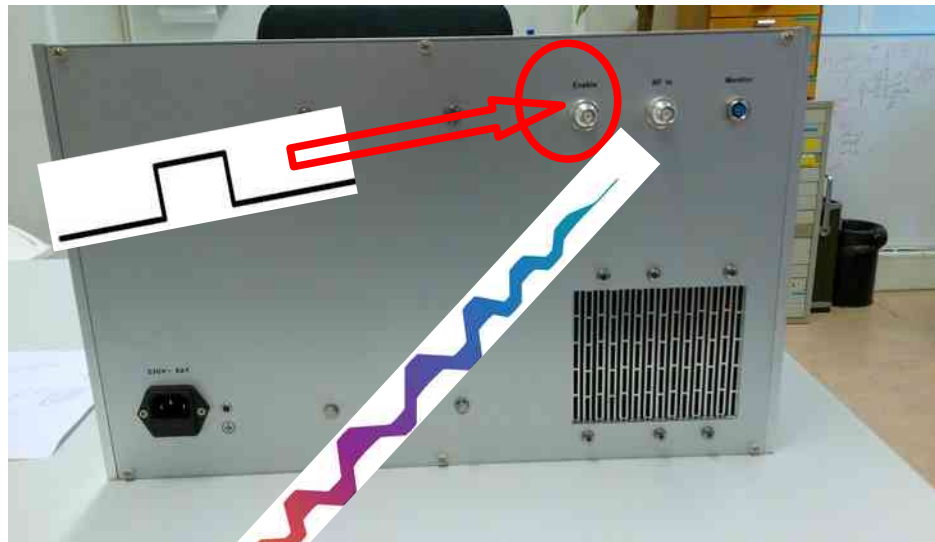- Apply a single pulse with a **pulse time of 10 μ s** and a level of 1.5..5V at the Enable input and check if a signal is present at the load resistor and see if the voltage at J3 switches on and off.



Common mistake

- ONLY short RF pulses! No Continuous wave.




Biassing and testing (10)

- Increase the voltage out of the phoenix power supply to 56V and the bias voltage potentiometers to 2.5V.




Biasing and testing (11)

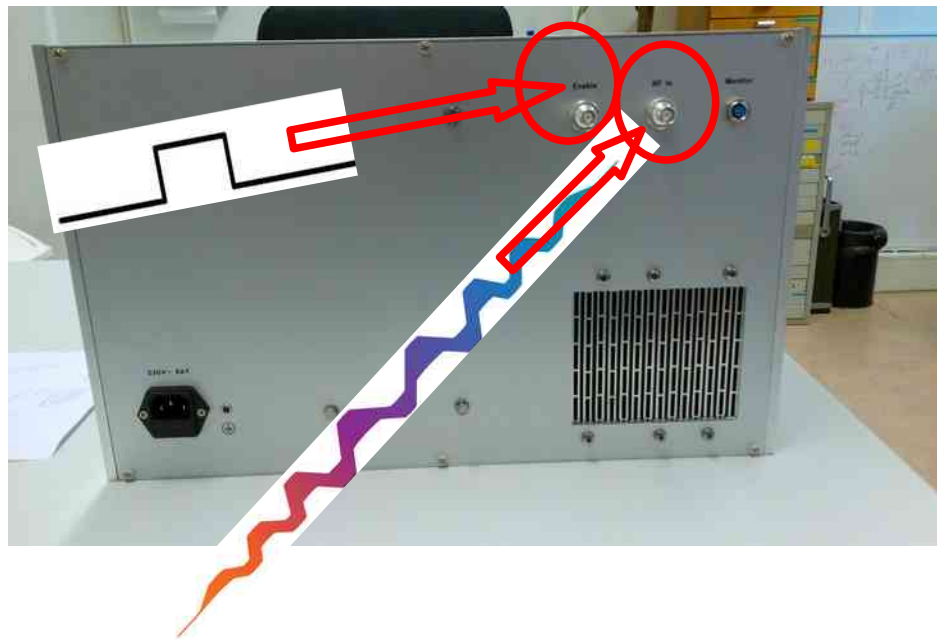- Test with 250mV amplitude input signal while checking the sine wave at the load with single enable pulses.




Biassing and testing (11)

Slowly increase the input signal amplitude and see if the peaks of the sine wave become distorted. The maximum output signal is 632Vpp at 1.1Vpp input signal. Increase the bias voltage to just the value at which the signal looks undistorted at full power (1kW). This takes a bias voltage of around 2.7V. Make sure that both potentiometers are set to the same voltage while tuning before applying an enable pulse.

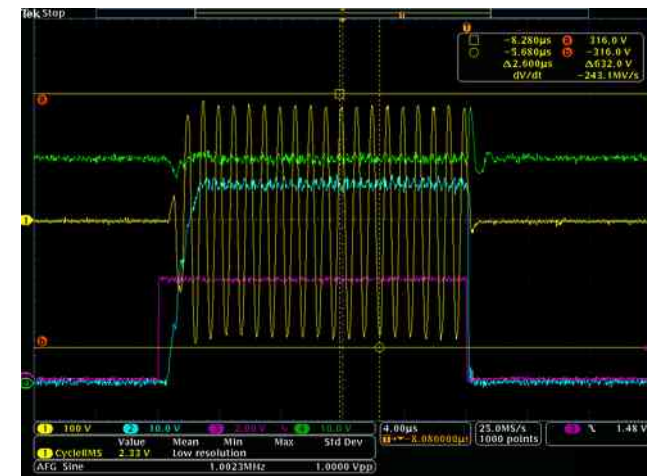

Thank you!

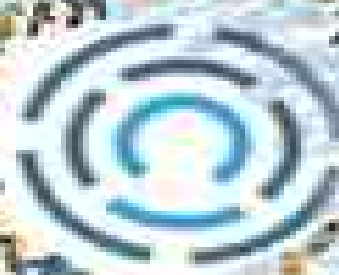

Special thanks to **Danny de Gans** <D.H.deGans@tudelft.nl>

Speaker **Ruben Pellicer-Guridi** <ruben.pellicer@ehu.eus>

