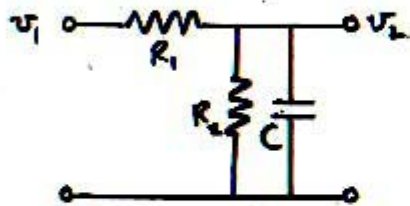


3. NORMAL AND INVERTED POLES AND ZEROS

How to choose the gain at any frequency as the Reference Gain


"Flat gain"



The hard way:

$$\begin{aligned}\frac{v_2}{v_1} &= \frac{R_2 \parallel \frac{1}{sC}}{R_1 + R_2 \parallel \frac{1}{sC}} = \frac{\frac{R_2}{1+sCR_2}}{R_1 + \frac{R_2}{1+sCR_2}} \\ &= \frac{R_2}{R_1 + R_2 + sCR_1R_2}\end{aligned}$$

"Flat gain"

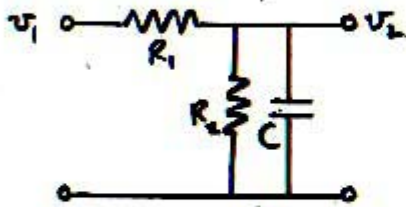


The hard way:

$$\frac{v_2}{v_1} = \frac{R_2 \parallel \frac{1}{sC}}{R_1 + R_2 \parallel \frac{1}{sC}} = \frac{\frac{R_2}{1 + sCR_2}}{R_1 + \frac{R_2}{1 + sCR_2}} = \frac{R_2}{R_1 + R_2 + sCR_1R_2}$$

This format is commonly considered to be "the answer."

However, it is much better to extract the constant term from both the numerator and denominator polynomials in s :

"Flat gain"

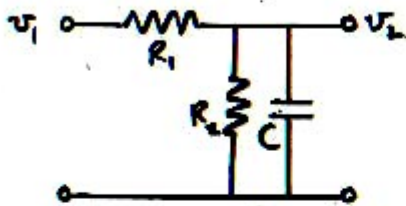

The hard way:

$$\begin{aligned}\frac{v_2}{v_1} &= \frac{R_2 \parallel \frac{1}{sC}}{R_1 + R_2 \parallel \frac{1}{sC}} = \frac{\frac{R_2}{1+sCR_2}}{R_1 + \frac{R_2}{1+sCR_2}} \\ &= \frac{R_2}{R_1 + R_2 + sCR_1R_2} \\ &= \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + sC(R_1 \parallel R_2)}\end{aligned}$$

This *normalizes* the polynomials, and exposes a zero-frequency gain and a corner frequency.

This is a special case of the general result as a ratio of polynomials in complex frequency s :

$$A = \frac{b_0 + b_1s + b_2s^2 + b_3s^3 + \dots}{a_0 + a_1s + a_2s^2 + a_3s^3 + \dots}$$

Extraction of the constant term from numerator and denominator defines the zero-frequency reference gain A_{ref} and normalizes the polynomials:

$$A = A_{\text{ref}} \frac{1 + \frac{b_1}{b_0}s + \frac{b_2}{b_0}s^2 + \frac{b_3}{b_0}s^3 + \dots}{1 + \frac{a_1}{a_0}s + \frac{a_2}{a_0}s^2 + \frac{a_3}{a_0}s^3 + \dots}$$


Factorization of the polynomials defines the poles and zeros, and hence the final (preferred) "factored pole-zero" form:

$$\mathbf{A} = \mathbf{A}_{\text{ref}} \frac{\left(1 + \frac{s}{\omega_{z1}}\right)\left(1 + \frac{s}{\omega_{z2}}\right)\left(1 + \frac{s}{\omega_{z3}}\right)\dots}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)\left(1 + \frac{s}{\omega_{p3}}\right)\dots}$$

The reference gain and the poles and zeros should, of course, be low entropy expressions in terms of the circuit elements.

Return to the example:


"Flat gain"

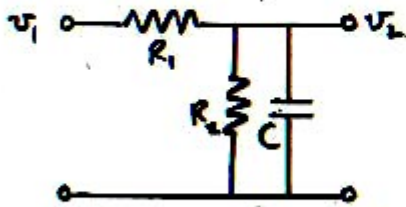

The hard way:

$$\begin{aligned}\frac{v_2}{v_1} &= \frac{R_2 \parallel \frac{1}{sC}}{R_1 + R_2 \parallel \frac{1}{sC}} = \frac{\frac{R_2}{1+sCR_2}}{R_1 + \frac{R_2}{1+sCR_2}} \\ &= \frac{R_2}{R_1 + R_2 + sCR_1R_2} \\ &= \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1+sC(R_1 \parallel R_2)}\end{aligned}$$

"Flat gain"

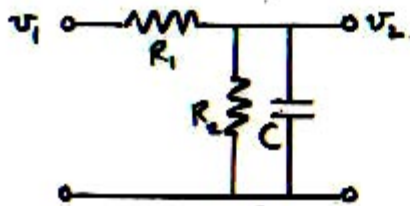


The hard way:

$$\frac{v_2}{v_1} = \frac{R_2 \parallel \frac{1}{sC}}{R_1 + R_2 \parallel \frac{1}{sC}} = \frac{\frac{R_2}{1 + sCR_2}}{R_1 + \frac{R_2}{1 + sCR_2}}$$

$$= \frac{R_2}{R_1 + R_2 + sCR_1R_2}$$


$$= \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + sC(R_1 \parallel R_2)}$$

The easy way:

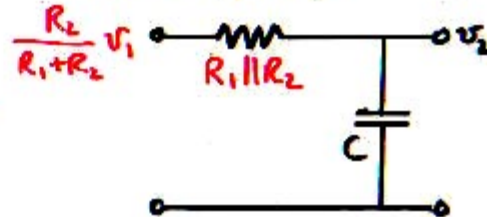

$$\frac{v_2}{v_1} = \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + sC(R_1 \parallel R_2)}$$

"Flat gain"

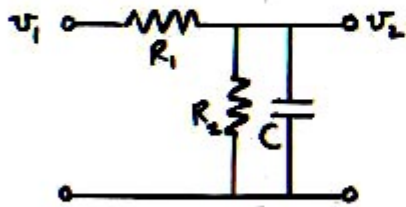


The hard way:

$$\frac{v_2}{v_1} = \frac{R_2 \parallel \frac{1}{sC}}{R_1 + R_2 \parallel \frac{1}{sC}} = \frac{\frac{R_2}{1 + sCR_2}}{R_1 + \frac{R_2}{1 + sCR_2}}$$

$$= \frac{R_2}{R_1 + R_2 + sCR_1R_2}$$

$$= \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + sC(R_1 \parallel R_2)}$$

The easy way:

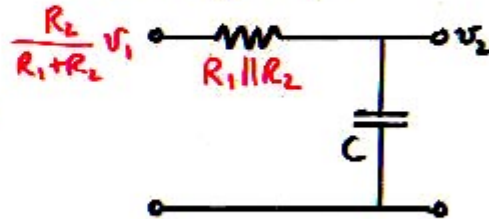

$$\frac{v_2}{v_1} = \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + sC(R_1 \parallel R_2)}$$


Result:

$$\frac{v_2}{v_1} \equiv A = A_1 \frac{1}{1 + \frac{s}{\omega_1}} \quad \text{where } A_1 \equiv \frac{R_2}{R_1 + R_2} \quad \omega_1 \equiv \frac{1}{C(R_1 \parallel R_2)}$$

Single-pole response:

$$A = A_1 \frac{1}{1 + \frac{s}{\omega_1}}$$

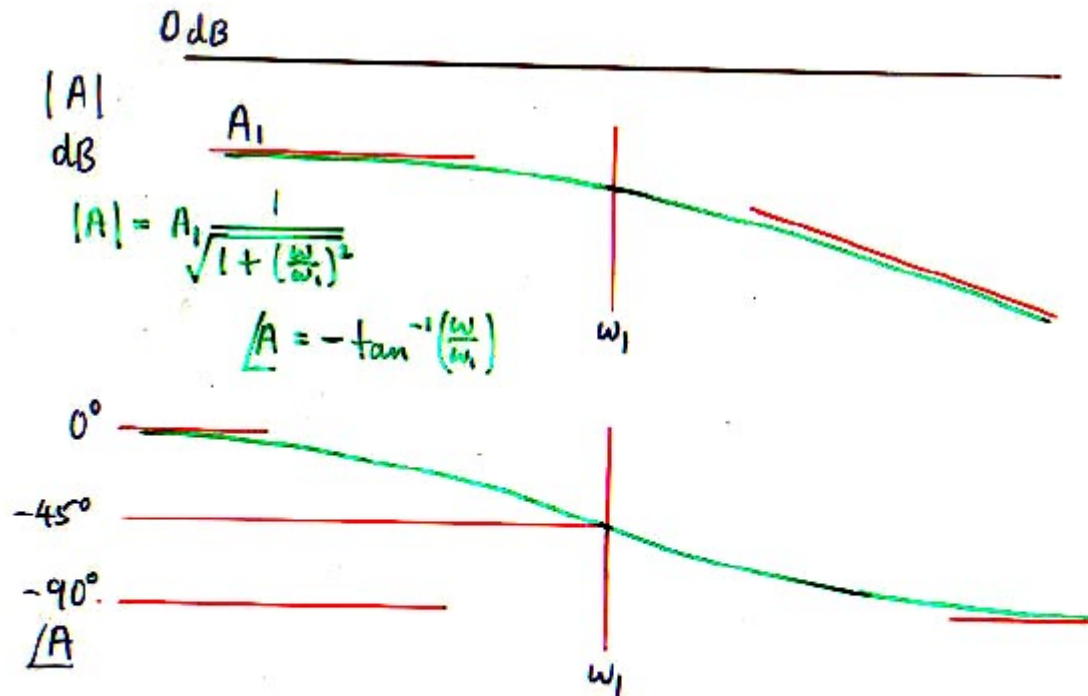
flat gain \nearrow \leftarrow normal pole



Single-pole response:

$$A = A_1 \frac{1}{1 + \frac{s}{\omega_1}}$$

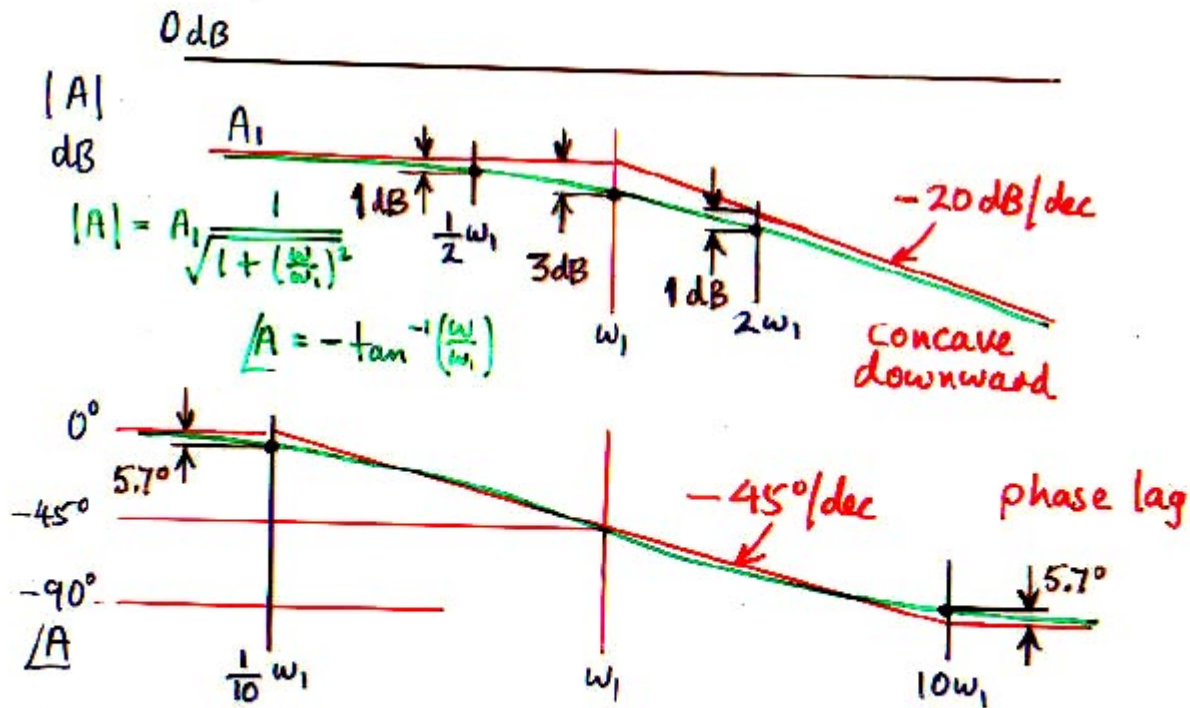flat gain \nearrow A_1 \longleftarrow normal pole





Single-zero response:

$$A = A_1 \left(1 + \frac{s}{\omega_1} \right)$$

flat gain \nearrow \nwarrow normal zero

$$|A| = A_1 \sqrt{1 + \left(\frac{\omega}{\omega_1} \right)^2}$$

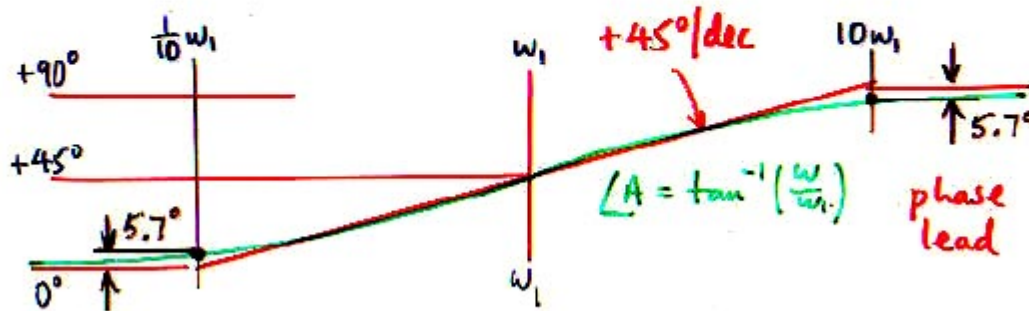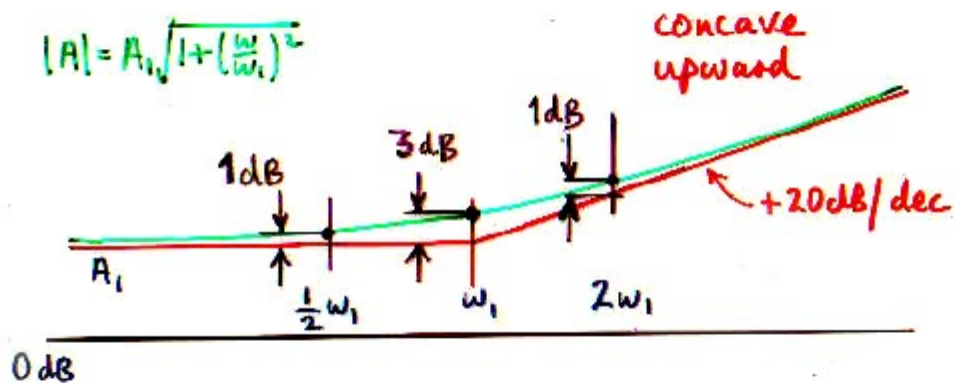


Generalization: Property of Magnitude and Phase Graphs

A corner can be "seen" from further away on the phase graph than on the magnitude graph.

OR:


The phase gives a more accurate value of a nearby corner frequency than does the magnitude.

Normal and Inverted poles and zeros

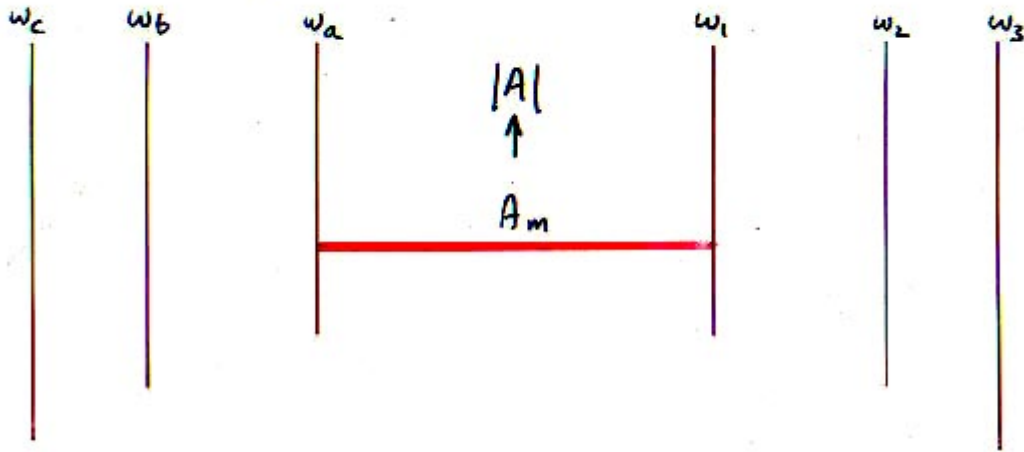


$$A = A_m$$

Normal and Inverted poles and zeros

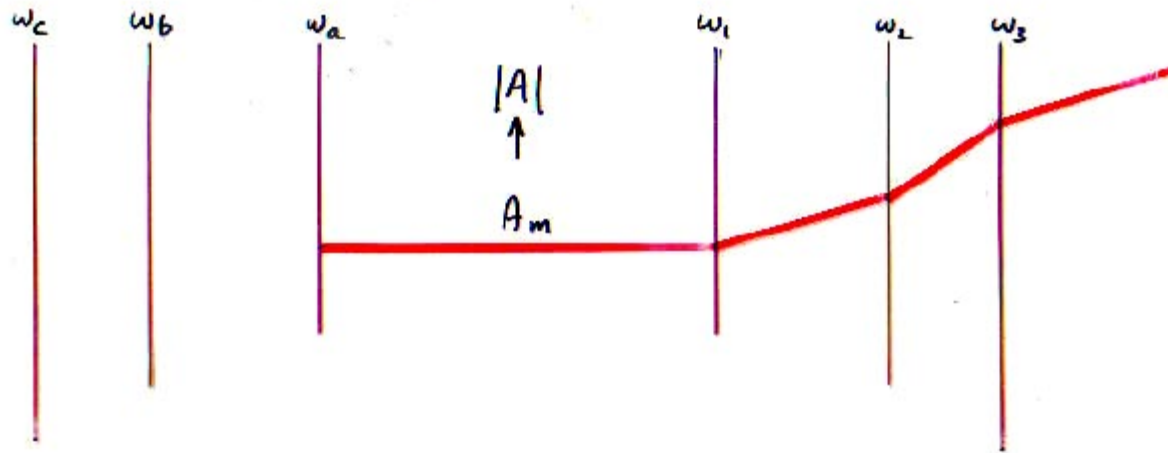

$$A = A_m$$


Normal and Inverted poles and zeros

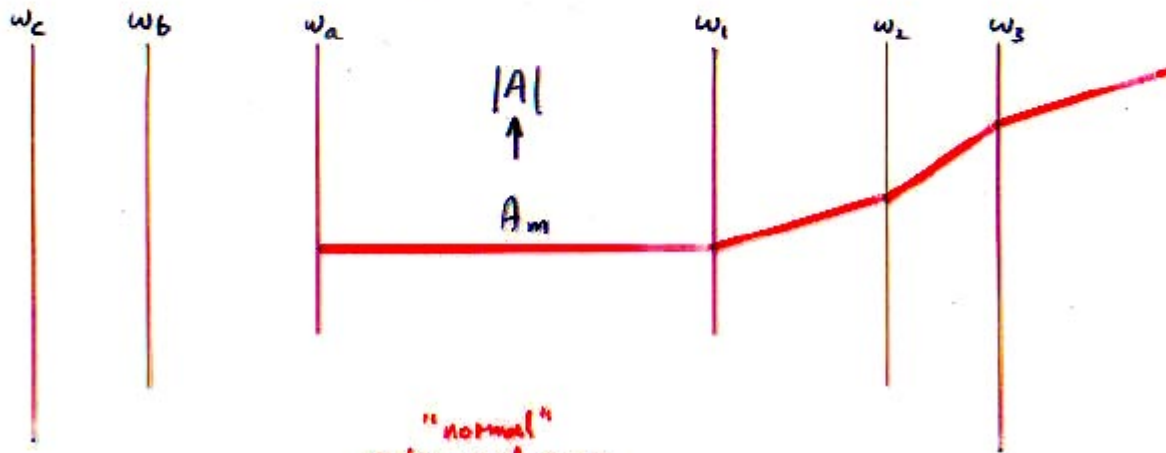

"normal"
poles and zeros


$$A = A_m \frac{(1 + \frac{s}{\omega_1})(1 + \frac{s}{\omega_2})}{(1 + \frac{s}{\omega_3})}$$

Normal and Inverted poles and zeros

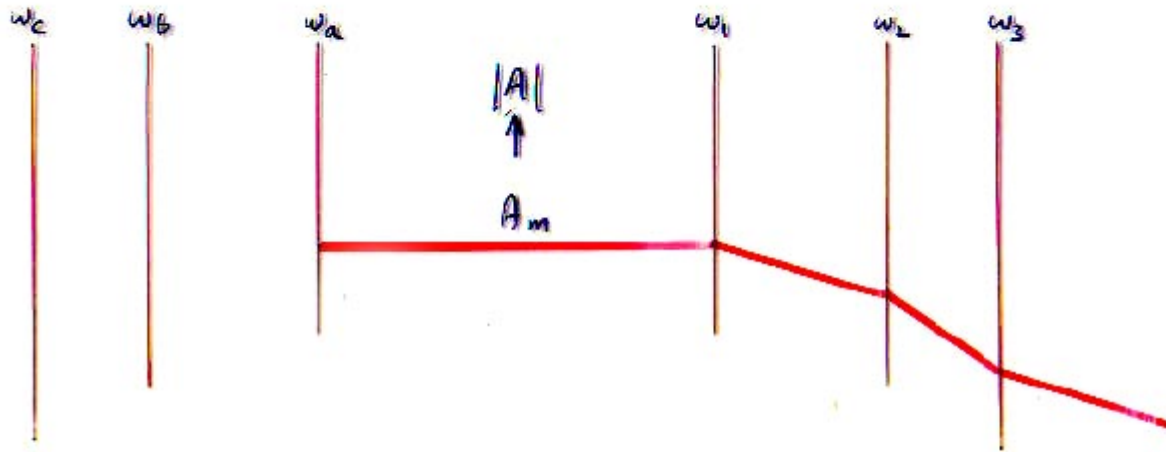

$$A = A_m$$

Normal and Inverted poles and zeros

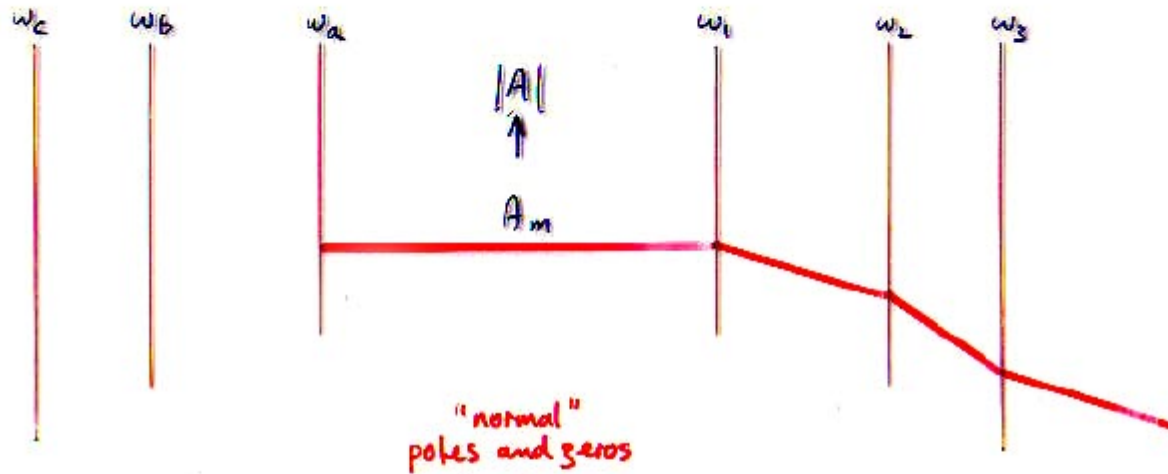


"normal"
poles and zeros

$$A = A_m \frac{(1 + \frac{s}{\omega_3})}{(1 + \frac{s}{\omega_1})(1 + \frac{s}{\omega_2})}$$


Inversion of pole-zero factors \Leftrightarrow vertical inversion of magnitude graph

Normal and Inverted poles and zeros

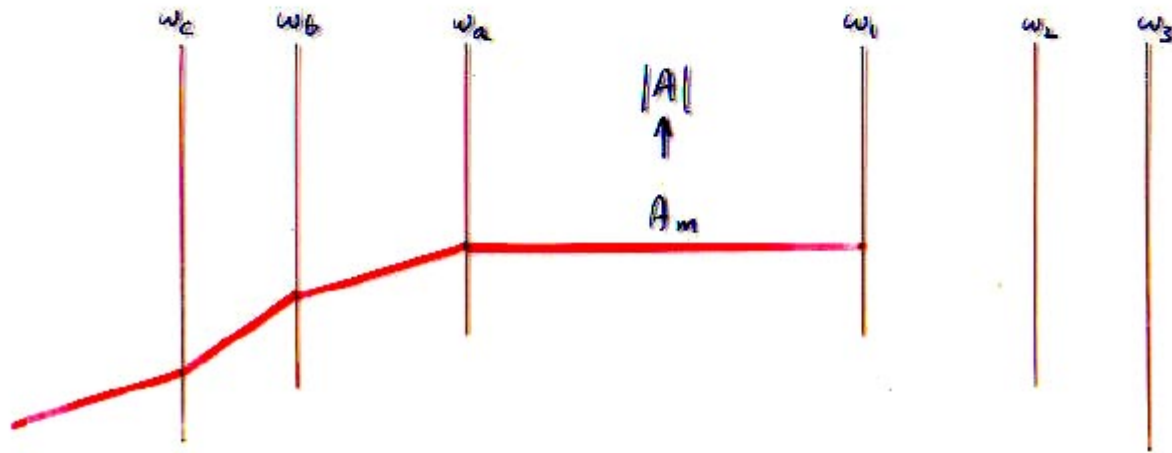

$$A = A_m$$

Normal and Inverted poles and zeros

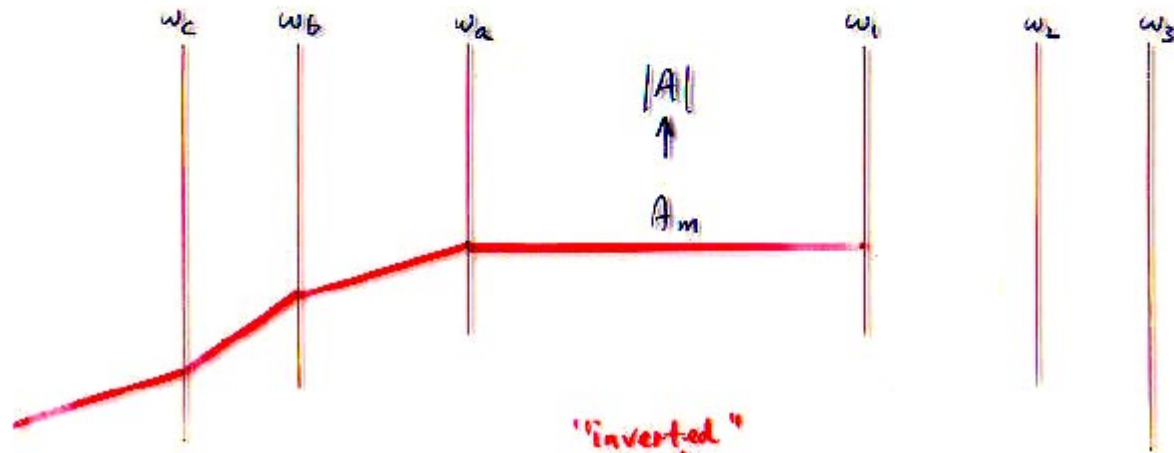


"inverted"
poles and zeros

$$A = A_m \frac{\left(1 + \frac{\omega_c}{s}\right)}{\left(1 + \frac{\omega_a}{s}\right)\left(1 + \frac{\omega_b}{s}\right)}$$


Inversion of frequency terms \Leftrightarrow horizontal reversal of magnitude graph

Normal and Inverted poles and zeros

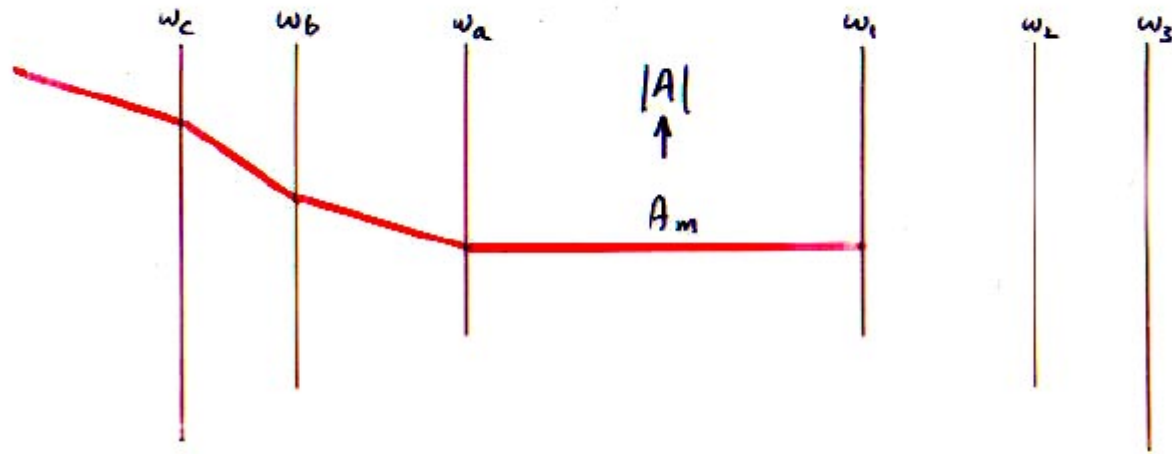


$$A = A_m$$

Normal and Inverted poles and zeros

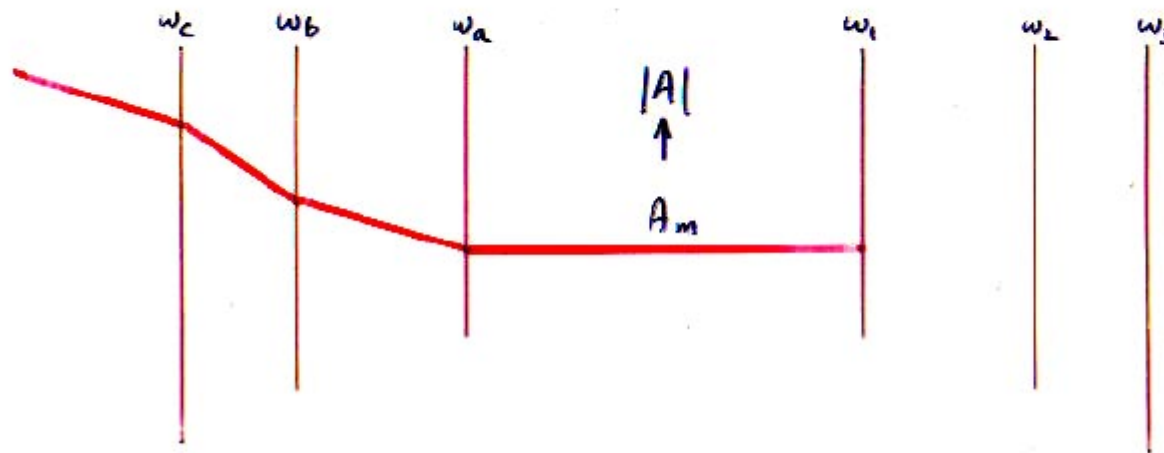

$$A = A_m \frac{\left(1 + \frac{\omega_a}{s}\right) \left(1 + \frac{\omega_b}{s}\right)}{1 + \frac{\omega_c}{s}}$$

Normal and Inverted poles and zeros

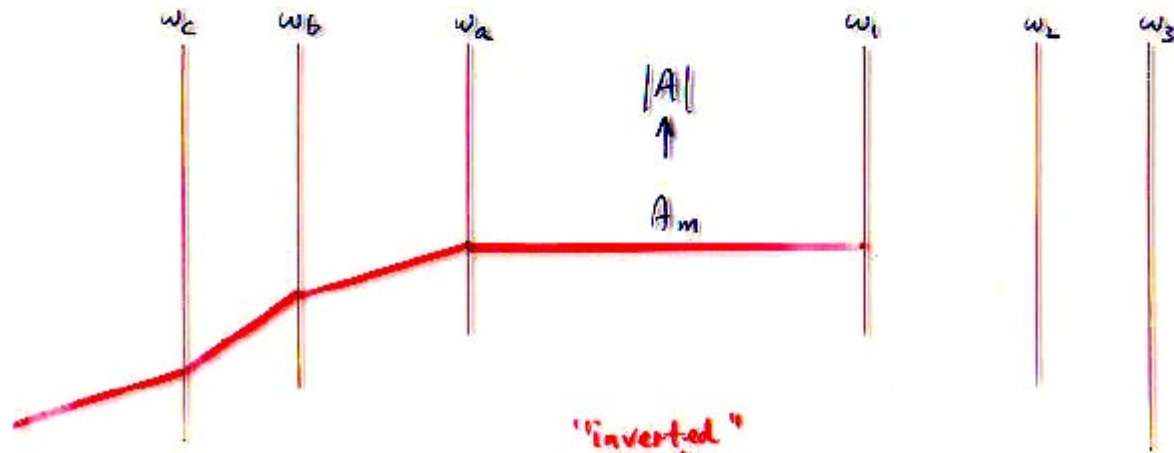


"inverted"
poles and zeros

$$A = A_m \frac{\left(1 + \frac{\omega_c}{s}\right)}{\left(1 + \frac{\omega_a}{s}\right)\left(1 + \frac{\omega_b}{s}\right)}$$


Inversion of frequency terms \Leftrightarrow horizontal reversal of magnitude graph

Normal and Inverted poles and zeros

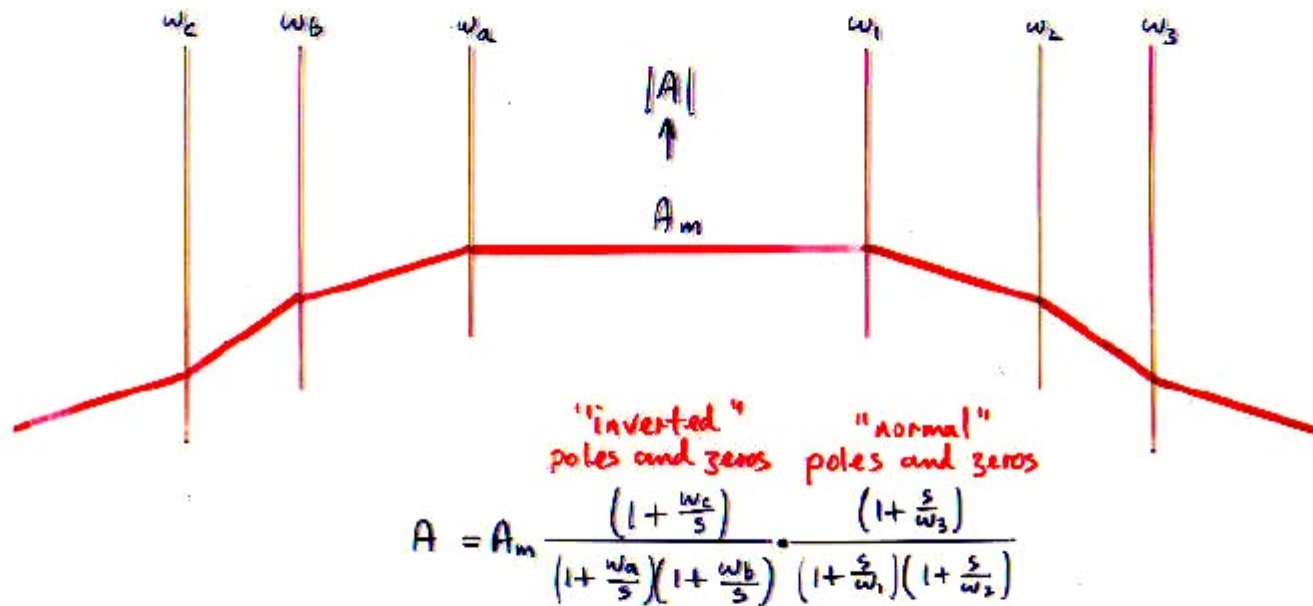

Inversion of frequency terms \Leftrightarrow horizontal reversal of magnitude graph

Relationships to conventional forms:

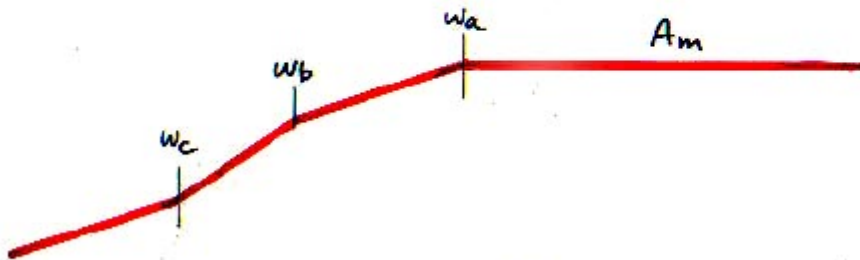

$$A = A_m \frac{\left(1 + \frac{\omega_c}{s}\right)}{\left(1 + \frac{\omega_a}{s}\right)\left(1 + \frac{\omega_b}{s}\right)} = A_m \frac{\frac{\omega_c}{s}}{\frac{\omega_a}{s} \frac{\omega_b}{s}} \frac{\left(\frac{s}{\omega_c} + 1\right)}{\left(\frac{s}{\omega_a} + 1\right)\left(\frac{s}{\omega_b} + 1\right)}$$


$$= \frac{A_m \omega_c s}{\omega_a \omega_b} \frac{\left(1 + \frac{s}{\omega_c}\right)}{\left(1 + \frac{s}{\omega_a}\right)\left(1 + \frac{s}{\omega_b}\right)} = \frac{s}{\omega_x} \frac{\left(1 + \frac{s}{\omega_c}\right)}{\left(1 + \frac{s}{\omega_a}\right)\left(1 + \frac{s}{\omega_b}\right)}$$

conventional form
(normal poles and zeros)

Where is ω_x on the graph? Where is A_m in the formula?

ω_x is not a useful parameter.

Relationships to conventional forms:

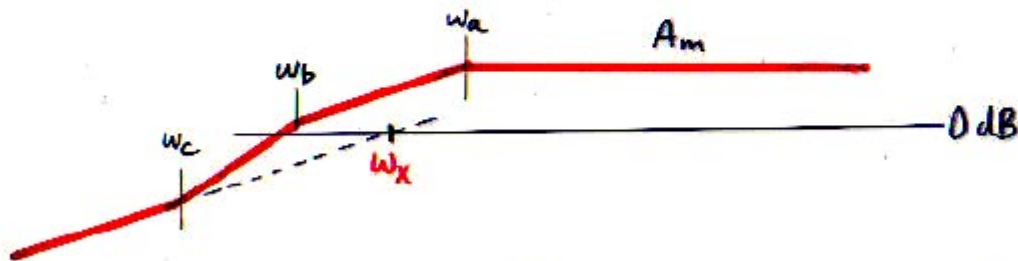


$$A = A_m \frac{\left(1 + \frac{w_c}{s}\right)}{\left(1 + \frac{w_a}{s}\right)\left(1 + \frac{w_b}{s}\right)} = A_m \frac{\frac{w_c}{s}}{\frac{w_a}{s} \frac{w_b}{s}} \frac{\left(\frac{s}{w_c} + 1\right)}{\left(\frac{s}{w_a} + 1\right)\left(\frac{s}{w_b} + 1\right)}$$

$$= \frac{A_m w_c s}{w_a w_b} \frac{\left(1 + \frac{s}{w_c}\right)}{\left(1 + \frac{s}{w_a}\right)\left(1 + \frac{s}{w_b}\right)} = \frac{s}{w_x} \frac{\left(1 + \frac{s}{w_c}\right)}{\left(1 + \frac{s}{w_a}\right)\left(1 + \frac{s}{w_b}\right)}$$

conventional form (normal poles and zeros)

Where is w_x on the graph? Where is A_m in the formula?


w_x is not a useful parameter.

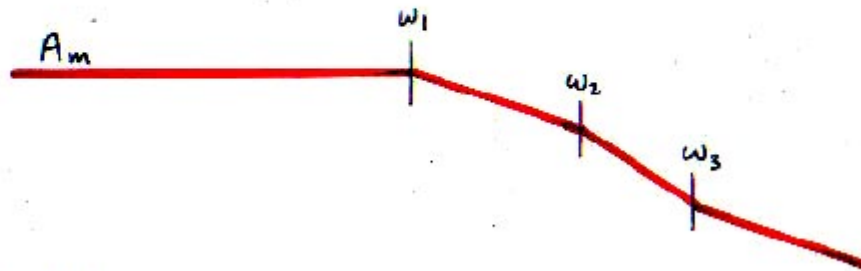

$$\begin{aligned}
 A &= A_m \frac{\left(1 + \frac{s}{w_3}\right)}{\left(1 + \frac{s}{w_1}\right)\left(1 + \frac{s}{w_2}\right)} = A_m \frac{\frac{1}{w_3}}{\frac{1}{w_1} \frac{1}{w_2}} \frac{(w_3 + s)}{(w_1 + s)(w_2 + s)} \\
 &= \frac{A_m w_1 w_2}{w_3} \frac{(s + w_3)}{(s + w_1)(s + w_2)} = w_y \cdot \frac{(s + w_3)}{(s + w_1)(s + w_2)} \quad \leftarrow \text{conventional form}
 \end{aligned}$$

Where is w_y on the graph? Where is A_m in the formula?

w_y is not a useful parameter.

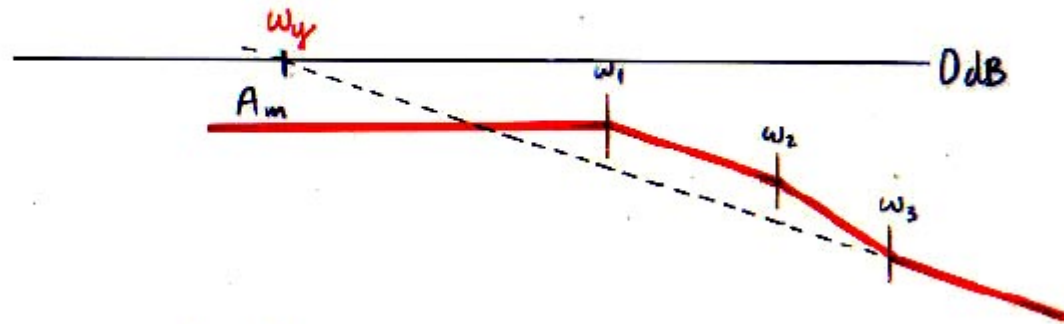

$$\begin{aligned}
 A &= A_m \frac{\left(1 + \frac{s}{w_3}\right)}{\left(1 + \frac{s}{w_1}\right)\left(1 + \frac{s}{w_2}\right)} = A_m \frac{\frac{1}{w_3}}{\frac{1}{w_1} \frac{1}{w_2}} \frac{(w_3 + s)}{(w_1 + s)(w_2 + s)} \\
 &= \frac{A_m w_1 w_2}{w_3} \frac{(s + w_3)}{(s + w_1)(s + w_2)} = w_y \frac{(s + w_3)}{(s + w_1)(s + w_2)} \quad \leftarrow \text{conventional form}
 \end{aligned}$$


Where is w_y on the graph? Where is A_m in the formula?

w_y is not a useful parameter.

If there is no "flat gain", use a reference value:




$|A|$
↑

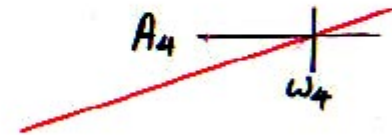


$$A = A_3 \frac{1}{\frac{s}{\omega_3}} = A_3 \frac{\omega_3}{s}$$

$$A = A_4 \frac{s}{\omega_4}$$

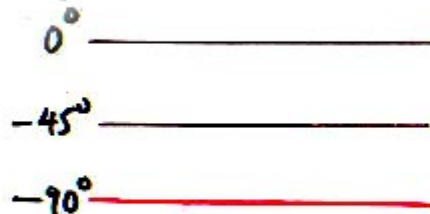

$\angle A$
↑

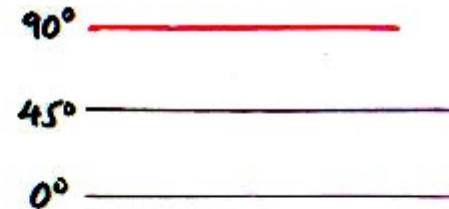


Exercise 3.1

Write factored pole-zero forms from asymptotes

Exercises


Express the gains in factored pole-zero form

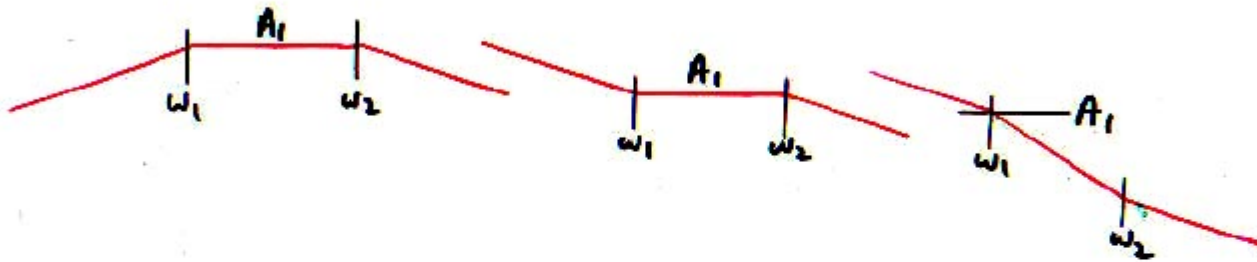

Exercise 3.1 - Solution

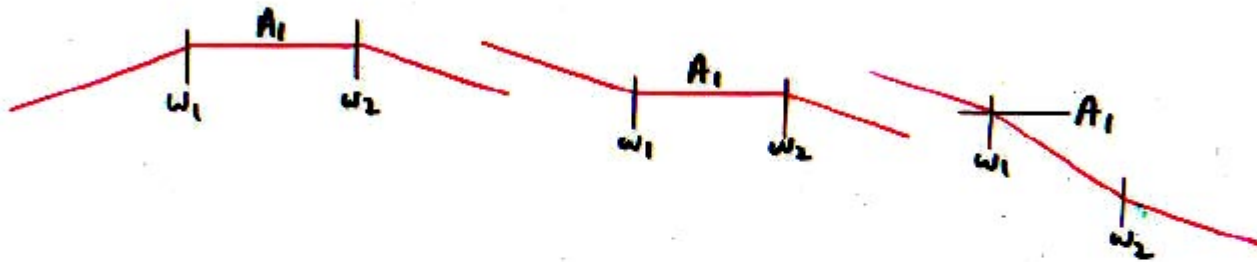Exercises

Express the gains in factored pole-zero form




$$A = A_1 \frac{1}{\left(1 + \frac{\omega_1}{s}\right) \left(1 + \frac{s}{\omega_2}\right)}$$

Exercise 3.1 - Solution

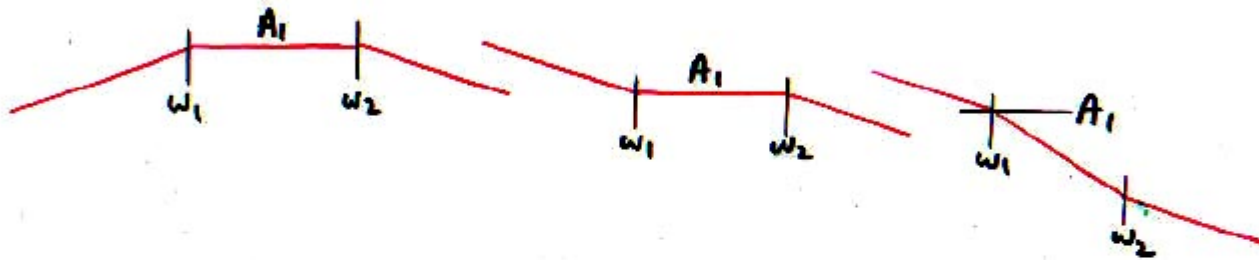Exercises

Express the gains in factored pole-zero form




$$A = A_1 \frac{1}{\left(1 + \frac{\omega_1}{s}\right)\left(1 + \frac{s}{\omega_2}\right)}$$

$$A = A_1 \frac{1 + \frac{\omega_1}{s}}{1 + \frac{s}{\omega_2}}$$

Exercise 3.1 - Solution

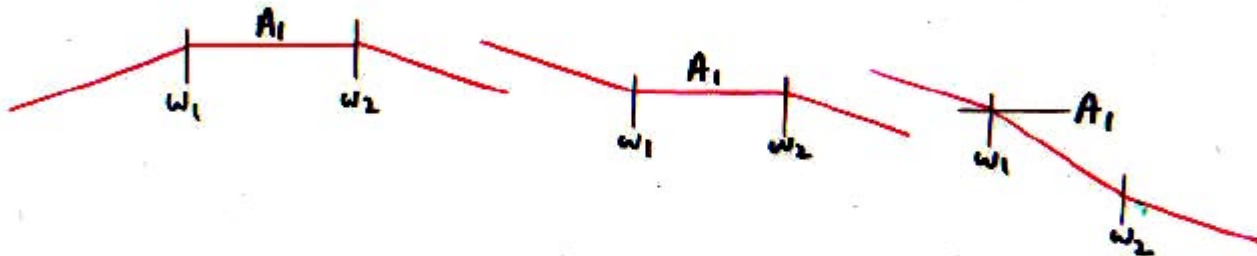Exercises

Express the gains in factored pole-zero form



$$A = A_1 \frac{1}{\left(1 + \frac{\omega_1}{s}\right)\left(1 + \frac{s}{\omega_2}\right)}$$


$$A = A_1 \frac{1 + \frac{\omega_1}{s}}{1 + \frac{s}{\omega_2}}$$

$$A = A_1 \left(\frac{\omega_1}{s}\right) \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}}$$

Exercise 3.1 - Solution

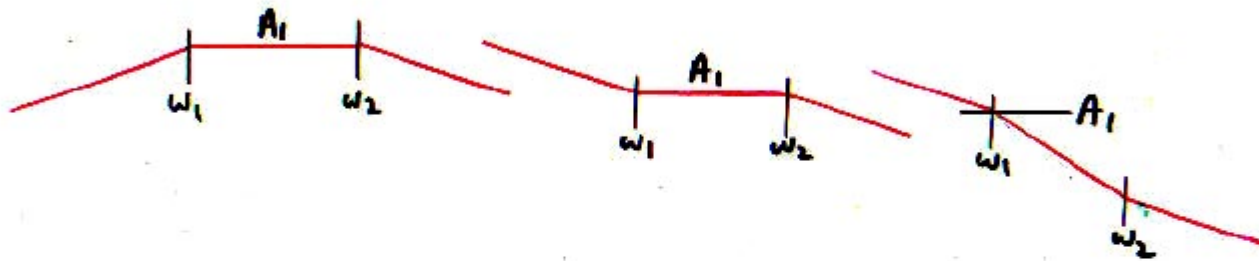Exercises

Express the gains in factored pole-zero form




$$A = A_1 \frac{1}{\left(1 + \frac{\omega_1}{s}\right)\left(1 + \frac{s}{\omega_2}\right)}$$

$$A = A_1 \frac{1 + \frac{\omega_1}{s}}{1 + \frac{s}{\omega_2}}$$

$$A = A_1 \left(\frac{\omega_1}{s}\right) \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}}$$


$$A = A_1 \left(\frac{\omega_1}{s}\right)^2 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}}$$

Lag-lead network

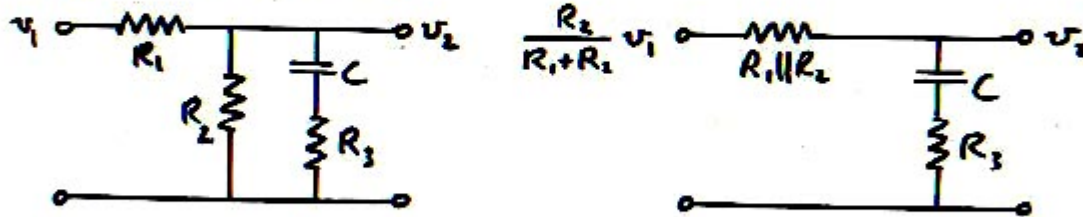

$$\frac{v_2}{v_1} = A = \frac{R_2}{R_1 + R_2} \cdot \frac{\frac{1}{sC} + R_3}{\frac{1}{sC} + R_3 + R_1 || R_2}$$

$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} \quad \text{where} \quad A_1 \equiv \frac{R_2}{R_1 + R_2} \quad \omega_1 \equiv \frac{1}{C(R_3 + R_1 || R_2)} \quad \omega_2 \equiv \frac{1}{CR_3}$$

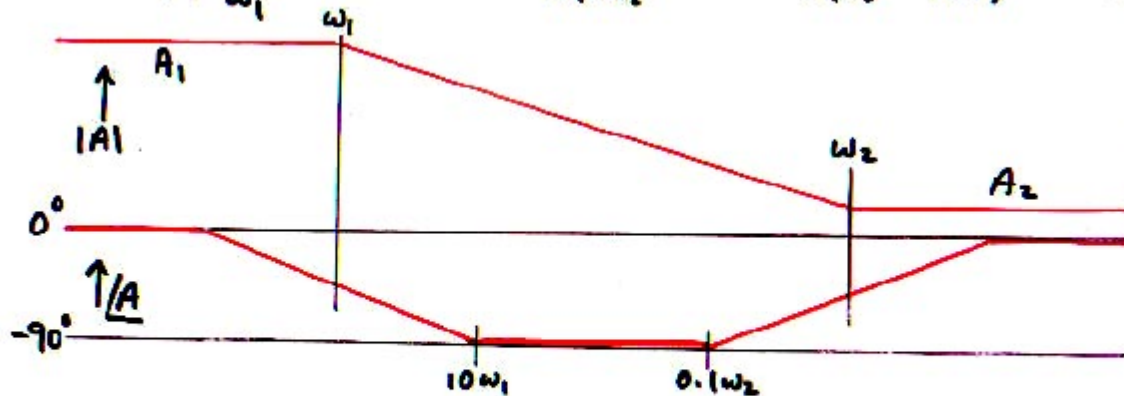

In this case, there are two flat gains. As derived, the low-frequency flat gain A_1 appears as coefficient, together with normal pole and zero:

$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}}$$

Equally well, directly from the $|A|$ asymptotes, the result could be written with the high-frequency flat gain A_2 as coefficient, together with inverted zero and pole:

$$A = A_2 \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

What is the relation between A_1 and A_2 ? One form of the result can be derived from the other algebraically:

$$A = \underbrace{A_1}_{\substack{\uparrow \\ \text{This is } A|_{s \rightarrow 0}}} \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} = A_1 \frac{\frac{s}{\omega_2}}{\frac{s}{\omega_1}} \frac{\frac{\omega_2}{s} + 1}{\frac{\omega_1}{s} + 1} = A_1 \frac{\omega_1}{\omega_2} \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

In this case, there are two flat gains. As derived, the low-frequency flat gain A_1 appears as coefficient, together with normal pole and zero:

$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}}$$

Equally well, directly from the $|A|$ asymptotes, the result could be written with the high-frequency flat gain A_2 as coefficient, together with inverted zero and pole:

$$A = A_2 \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

What is the relation between A_1 and A_2 ? One form of the result can be derived from the other algebraically:

$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} = A_1 \frac{\frac{s}{\omega_2} \frac{\omega_2}{s} + 1}{\frac{s}{\omega_1} \frac{\omega_1}{s} + 1} = A_1 \frac{\omega_1}{\omega_2} \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

↑
This is $A|_{s \rightarrow 0}$

↑
This is $A|_{s \rightarrow \infty}$, so must be A_2

Result:

$$\frac{A_2}{A_1} = \frac{\omega_1}{\omega_2}$$

For the lag-lead network:

$$A_2 = A_1 \frac{\omega_1}{\omega_2} = \frac{R_2}{R_1 + R_2} \frac{\cancel{R_3}}{\cancel{C}(R_3 + R_1 \parallel R_2)}$$

which is obvious from the reduced model.

Generalization: Gain-Bandwidth Trade-Off

For a single-slope ($\pm 20\text{dB/dec}$)

Ratio of flat gains = Ratio of corner frequencies
that separate them

This is a form of gain-bandwidth trade-off.

More than one flat gain




$$A = A_1 \frac{1 + \frac{s}{w_1}}{1 + \frac{s}{w_2}} = A_1 \frac{w_2}{w_1} \frac{1 + \frac{w_1}{s}}{1 + \frac{w_2}{s}} = A_2 \frac{1 + \frac{w_1}{s}}{1 + \frac{w_2}{s}}$$

Hence: "gain-bandwidth tradeoff":

$$\frac{A_2}{A_1} = \frac{w_2}{w_1}$$


Either flat gain can be used as "reference" gain.

Lag-lead network

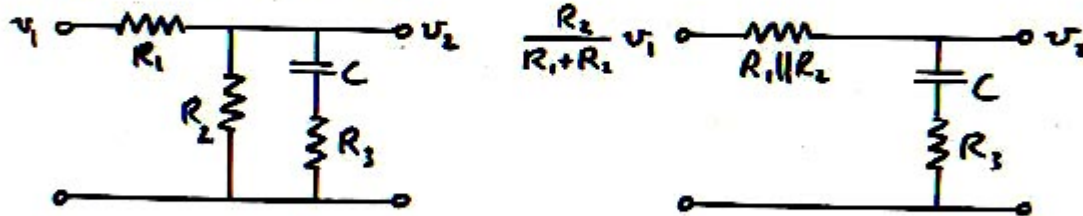

$$\frac{v_2}{v_1} = A = \frac{R_2}{R_1 + R_2} \cdot \frac{\frac{1}{sC} + R_3}{\frac{1}{sC} + R_3 + R_1 || R_2}$$


$$A = A_1 \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} \quad \text{where} \quad A_1 \equiv \frac{R_2}{R_1 + R_2} \quad \omega_1 \equiv \frac{1}{C(R_3 + R_1 || R_2)} \quad \omega_2 \equiv \frac{1}{CR_3}$$

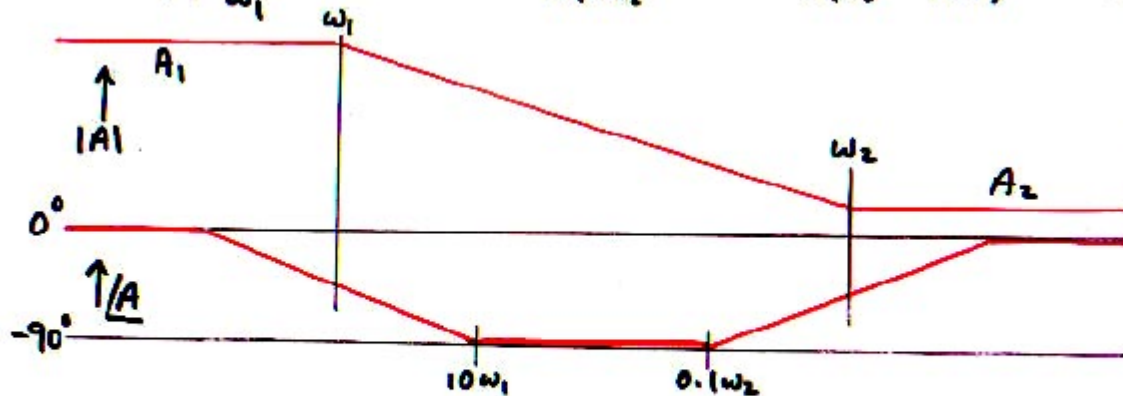

If $\omega_2 > 100\omega_1$, phase asymptotes do not overlap and the phase lag reaches 90° before returning to zero.

If $\omega_2 < 100\omega_1$, the phase asymptotes do overlap, and the phase lag reaches a maximum, less than 90° , which is a function of the ratio of the flat gains.

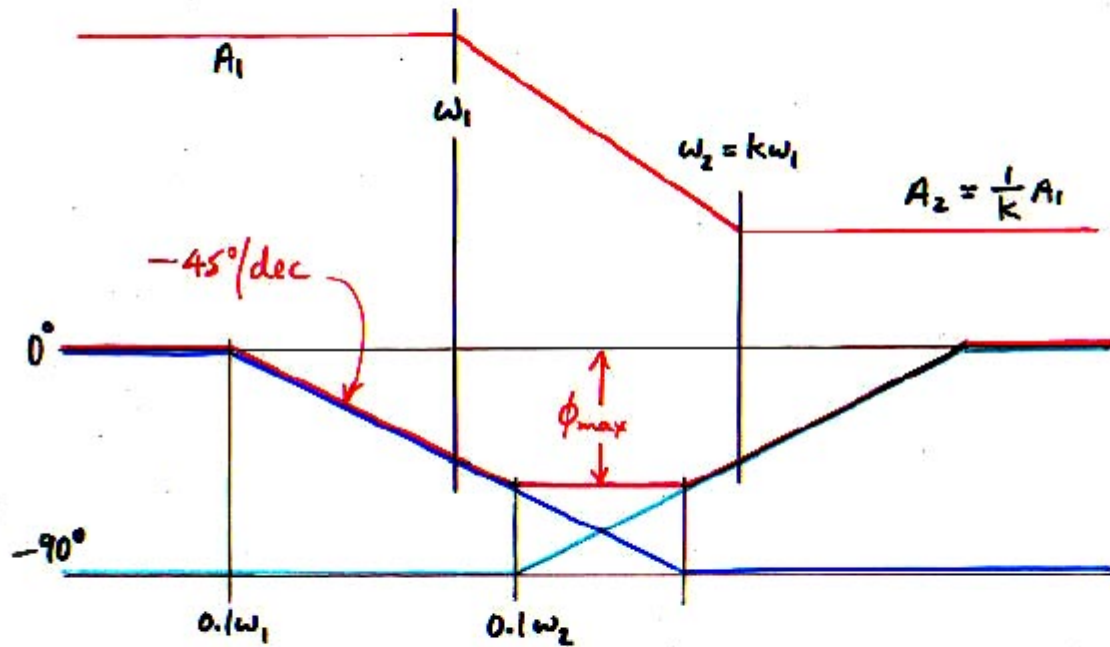Find the maximum phase lag ϕ_{max} as a function of the gain ratio $k \equiv A_1/A_2 = \omega_2/\omega_1$



$$\phi_{max} = -45^\circ \log \frac{0.1\omega_2}{0.1\omega_1} = -45^\circ \log k \quad (k < 100)$$


Exercise 3.2

Write factored pole-zero forms for different Reference Gains, and write A_2 and A_3 in terms of A_1 .

Exercise:

No flat gain

Identify the gain at any chosen frequency as "reference" gain

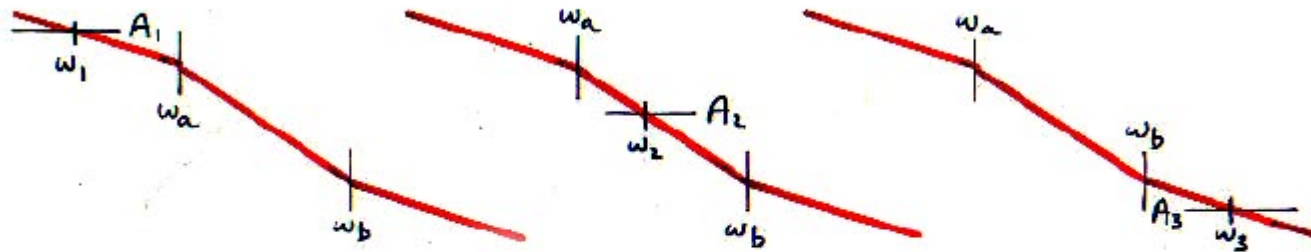


Exercise 3.2 - Solution

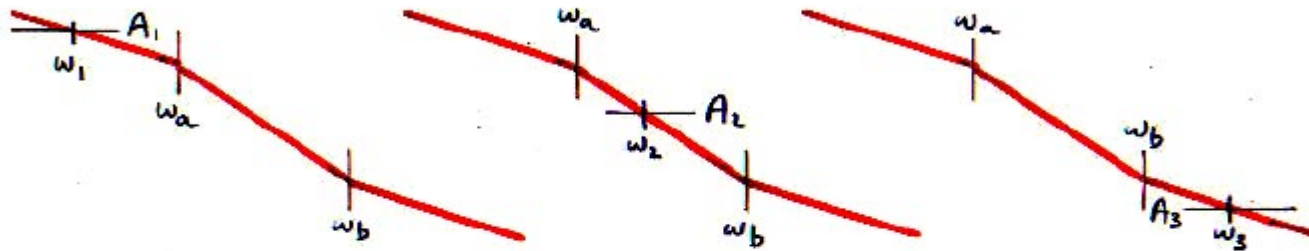Exercise:

No flat gain

Identify the gain at any chosen frequency as "reference" gain



$$A = A_1 \frac{w_1}{s} \frac{1 + \frac{s}{w_b}}{1 + \frac{s}{w_a}}$$

$$A = A_2 \left(\frac{w_2}{s}\right)^2 \frac{1 + \frac{s}{w_b}}{1 + \frac{w_a}{s}}$$


$$A = A_3 \frac{w_3}{s} \frac{1 + \frac{w_b}{s}}{1 + \frac{w_a}{s}}$$

Exercise 3.2 - Solution

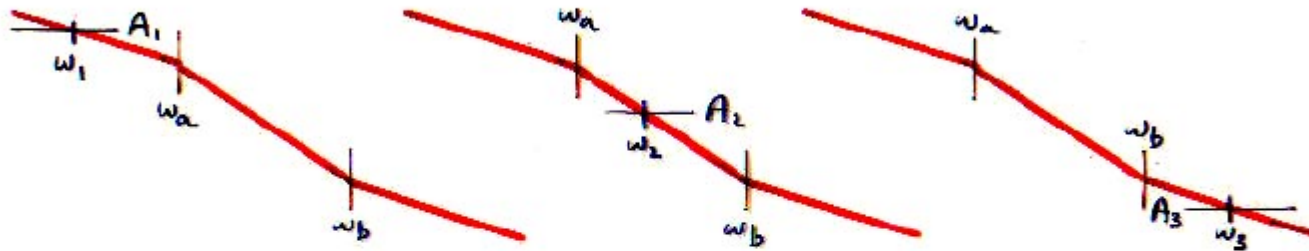Exercise:

No flat gain

Identify the gain at any chosen frequency as "reference" gain



$$A = A_1 \frac{w_1}{s} \frac{1 + \frac{s}{w_b}}{1 + \frac{s}{w_a}}$$

$$A = A_2 \left(\frac{w_2}{s}\right)^2 \frac{1 + \frac{s}{w_b}}{1 + \frac{s}{w_a}}$$

$$A = A_3 \frac{w_3}{s} \frac{1 + \frac{s}{w_b}}{1 + \frac{s}{w_a}}$$


Exercise: Express A_2 and A_3 in terms of A_1 .

Exercise 3.2 - Solution

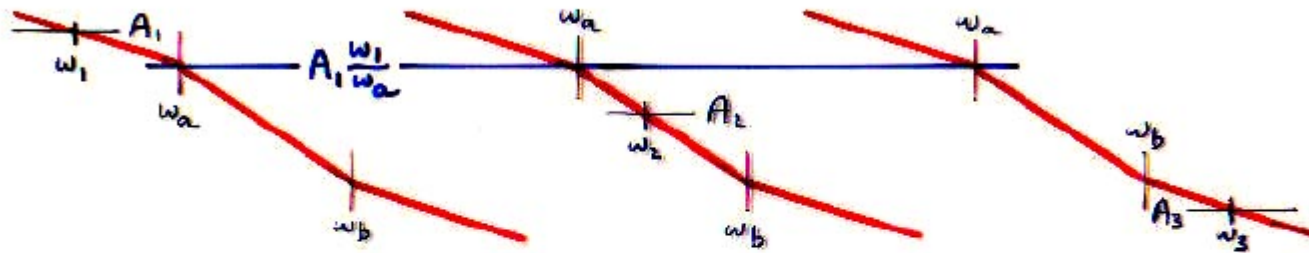Exercise:

No flat gain

Identify the gain at any chosen frequency as "reference" gain



$$A = A_1 \frac{\omega_1}{s} \frac{1 + \frac{s}{\omega_b}}{1 + \frac{s}{\omega_a}}$$

$$A = A_2 \left(\frac{\omega_2}{s}\right)^2 \frac{1 + \frac{s}{\omega_b}}{1 + \frac{s}{\omega_a}}$$

$$A = A_3 \frac{\omega_3}{s} \frac{1 + \frac{\omega_b}{s}}{1 + \frac{\omega_a}{s}}$$

Exercise: Express A_2 and A_3 in terms of A_1 .


$$\begin{aligned} A_2 &= \left(A_1 \frac{\omega_1}{\omega_a}\right) \left(\frac{\omega_a}{\omega_2}\right)^2 \\ &= A_1 \frac{\omega_1 \omega_a}{\omega_2^2} \end{aligned}$$

Exercise 3.2 - Solution

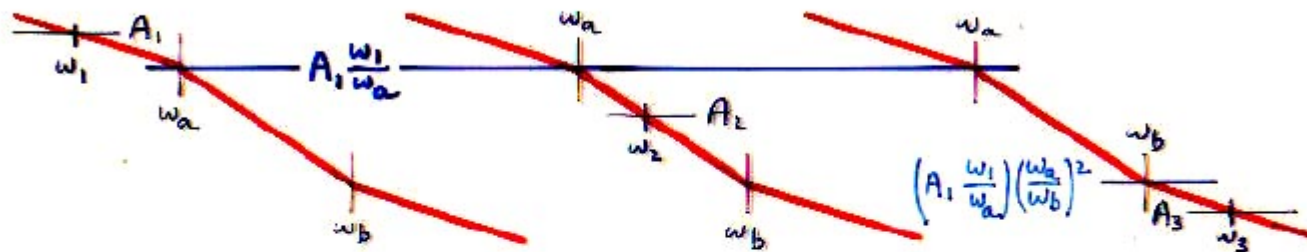Exercise:

No flat gain

Identify the gain at any chosen frequency as "reference" gain



$$A = A_1 \frac{w_1}{s} \frac{1 + \frac{s}{w_b}}{1 + \frac{s}{w_a}}$$

$$A = A_2 \left(\frac{w_2}{s}\right)^2 \frac{1 + \frac{s}{w_b}}{1 + \frac{w_a}{s}}$$


$$A = A_3 \frac{w_3}{s} \frac{1 + \frac{w_b}{s}}{1 + \frac{w_a}{s}}$$

Exercise: Express A_2 and A_3 in terms of A_1 .

$$\begin{aligned} A_2 &= \left(A_1 \frac{w_1}{w_a}\right) \left(\frac{w_a}{w_2}\right)^2 \\ &= A_1 \frac{w_1 w_a}{w_2^2} \end{aligned}$$

$$\begin{aligned} A_3 &= \left[\left(A_1 \frac{w_1}{w_a}\right) \left(\frac{w_a}{w_b}\right)^2\right] \frac{w_b}{w_3} \\ &= A_1 \frac{w_1 w_a}{w_3 w_b} \end{aligned}$$

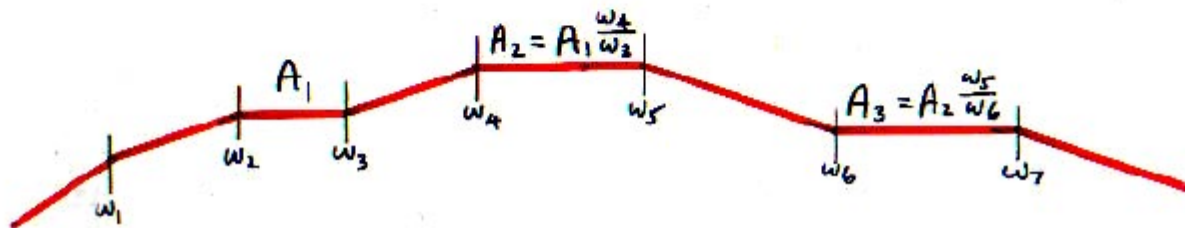Any flat gain can be used as "reference" gain A_{ref} .
 With respect to A_{ref} , poles and zeros above A_{ref}
 are normal, those below A_{ref} are inverted.



$$A = A_1 \frac{(1 + \frac{s}{w_3})(1 + \frac{s}{w_6})}{(1 + \frac{s}{w_2})(1 + \frac{s}{w_4})(1 + \frac{s}{w_5})(1 + \frac{s}{w_7})}$$

$$A = A_2 \frac{(1 + \frac{s}{w_3})(1 + \frac{s}{w_6})}{(1 + \frac{s}{w_4})(1 + \frac{s}{w_5})(1 + \frac{s}{w_7})}$$


$$A = A_3 \frac{(1 + \frac{s}{w_6})(1 + \frac{s}{w_3})}{(1 + \frac{s}{w_5})(1 + \frac{s}{w_4})(1 + \frac{s}{w_7})}$$

If you don't use inverted poles and zeros, you are stuck with the zero-frequency gain as the reference gain.


The principal benefit of using inverted poles and zeros is that you can choose the gain at *any* frequency as the reference gain.

Impedance asymptotes
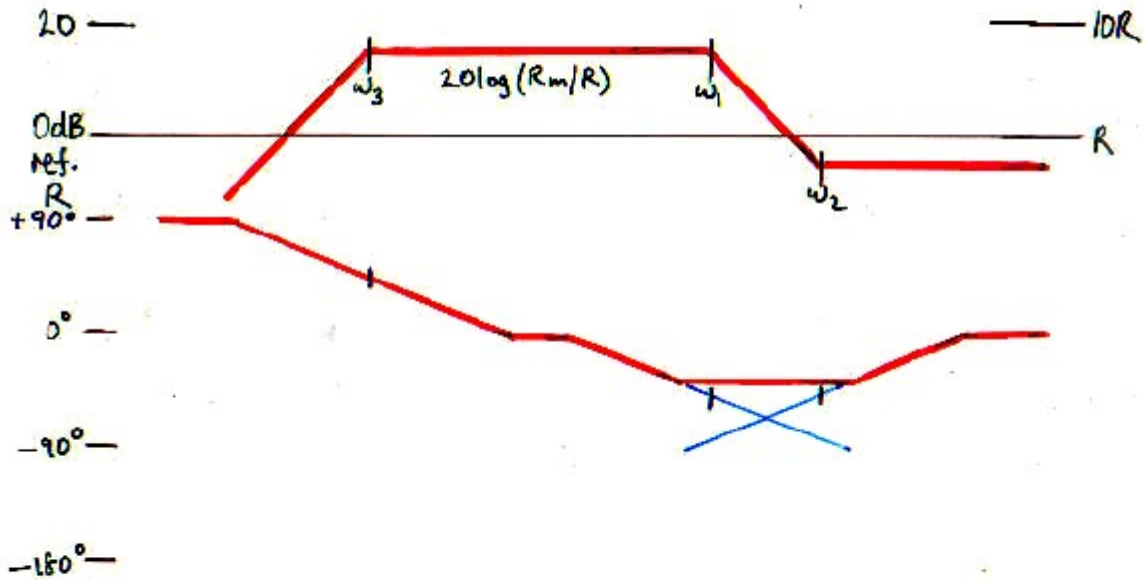
$$Z = R_m \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} \frac{1}{1 + \frac{\omega_3}{s}}$$




Input and output impedances

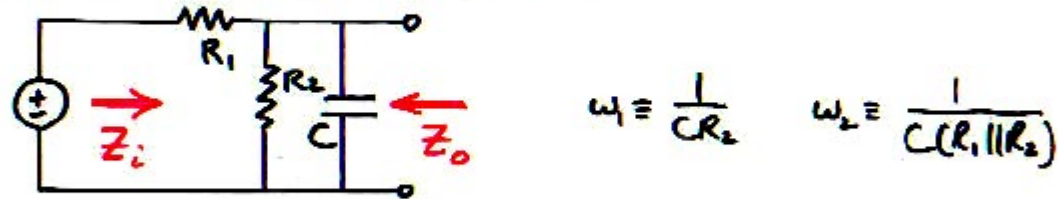

$$Z_i = R_1 + \frac{R_2}{1 + sCR_2} = (R_1 + R_2) \frac{1 + \frac{s}{\omega_2}}{1 + \frac{s}{\omega_1}} = R_1 \frac{1 + \frac{\omega_2}{s}}{1 + \frac{\omega_1}{s}}$$

$$Z_o = R_1 \parallel R_2 \parallel \frac{1}{sC} = R_1 \parallel R_2 \frac{1}{1 + \frac{s}{\omega_2}}$$


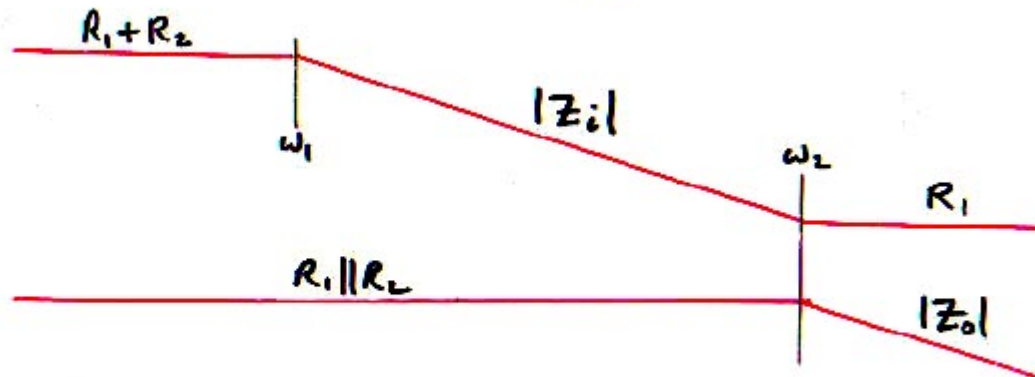


Exercise 3.3

Write input and output impedances Z_i and Z_o in factored pole-zero forms.

Exercise



Find the input and output impedances Z_i and Z_o in factored pole-zero form, and sketch the magnitude and phase asymptotes, for each of the two networks:

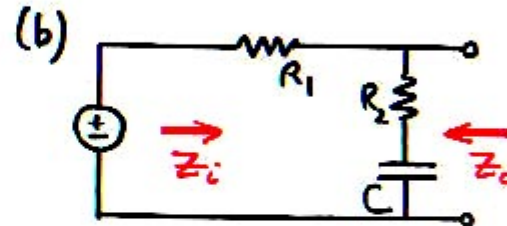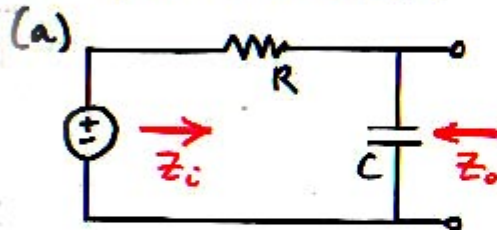

Exercise 3.3 - Solution

Exercise


Find the input and output impedances Z_i and Z_o in factored pole-zero form, and sketch the magnitude and phase asymptotes, for each of the two networks:

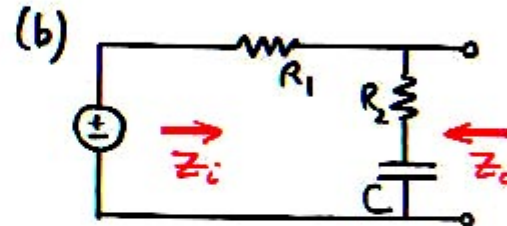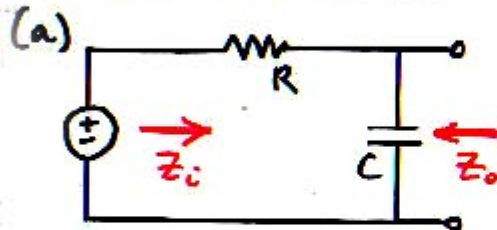

Exercise 3.3 - Solution

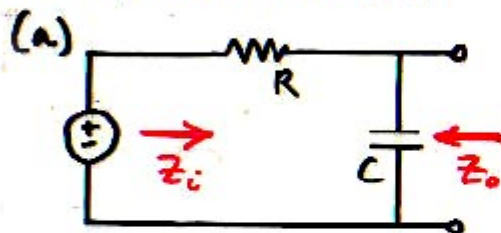
Exercise

Find the input and output impedances Z_i and Z_o in factored pole-zero form, and sketch the magnitude and phase asymptotes, for each of the two networks:




$$\begin{aligned} Z_i &= R + \frac{1}{sC} \\ &= R \left(1 + \frac{\omega_1}{s} \right) \quad \omega_1 = \frac{1}{CR} \end{aligned}$$

$$\begin{aligned} Z_o &= R \parallel \frac{1}{sC} \\ &= R \frac{1}{1 + \frac{s}{\omega_1}} \end{aligned}$$

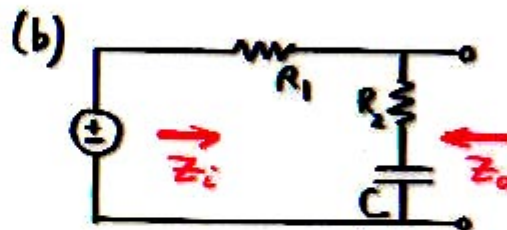

Exercise 3.3 - Solution

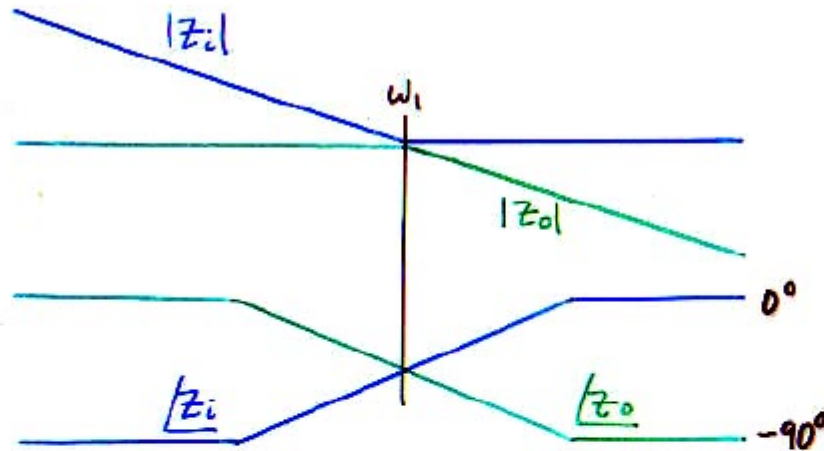



$$\begin{aligned} Z_i &= R + \frac{1}{sC} \\ &= R \left(1 + \frac{\omega_1}{s} \right) \quad \omega_1 = \frac{1}{CR} \end{aligned}$$

$$\begin{aligned} Z_o &= R \parallel \frac{1}{sC} \\ &= R \frac{1}{1 + \frac{s}{\omega_1}} \end{aligned}$$

Exercise 3.3 - Solution

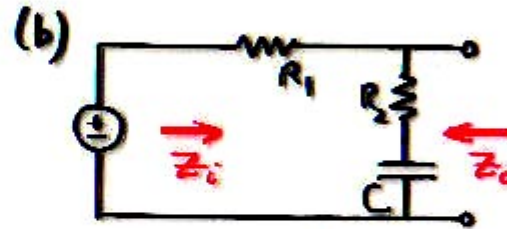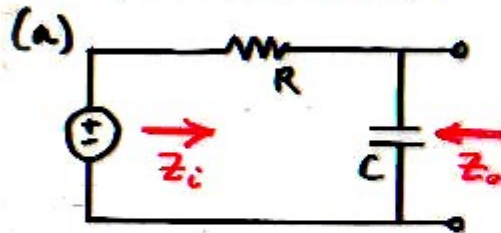Exercise


Find the input and output impedances Z_i and Z_o in factored pole-zero form, and sketch the magnitude and phase asymptotes, for each of the two networks:



$$Z_i = R_1 + R_2 + \frac{1}{sC}$$
$$= (R_1 + R_2) \left(1 + \frac{\omega_3}{s} \right)$$
$$\omega_3 = \frac{1}{C(R_1 + R_2)}$$

$$Z_o = R_1 \parallel \left(R_2 + \frac{1}{sC} \right)$$
$$= (R_1 \parallel R_2) \frac{1 + \frac{\omega_4}{s}}{1 + \frac{\omega_3}{s}}$$
$$\omega_4 = \frac{1}{CR_2}$$

Exercise 3.3 - Solution

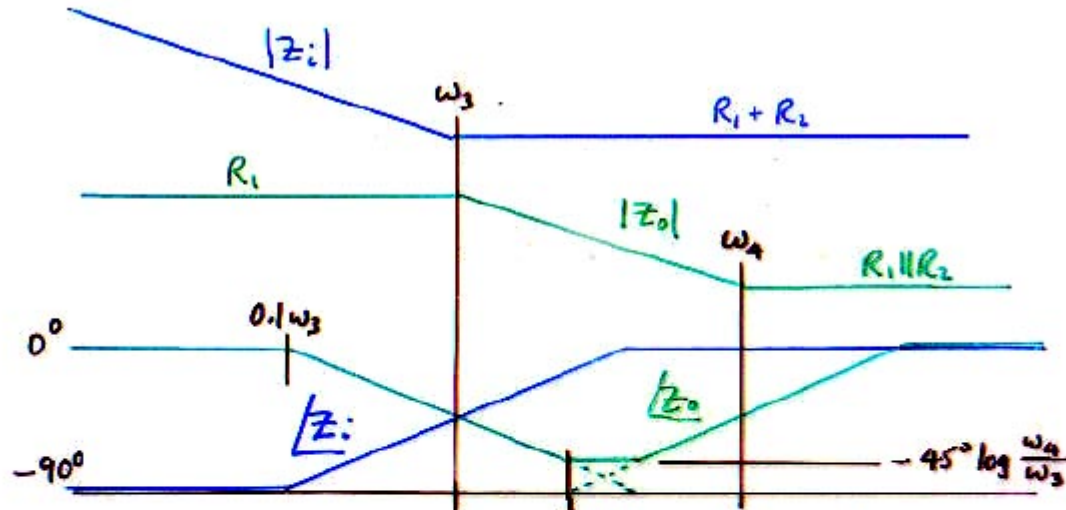

$$\begin{aligned} Z_i &= R_1 + R_2 + \frac{1}{sC} \\ &= (R_1 + R_2) \left(1 + \frac{\omega_3}{s} \right) \\ \omega_3 &= \frac{1}{C(R_1 + R_2)} \\ Z_o &= R_1 || \left(R_2 + \frac{1}{sC} \right) \\ &= (R_1 || R_2) \frac{1 + \frac{\omega_4}{s}}{1 + \frac{\omega_3}{s}} \\ \omega_4 &= \frac{1}{CR_2} \end{aligned}$$