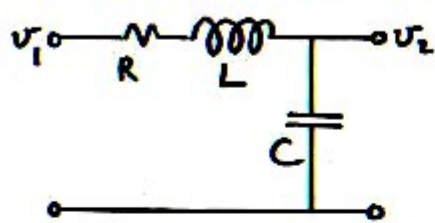


# 5. APPROXIMATIONS AND ASSUMPTIONS

How to build Low Entropy Expressions with minimum work

## Double-pole low-pass LC filter



$$\frac{v_2}{v_1} = \frac{1}{1 + sRC + s^2LC}$$

$$= \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

in which

$$\omega_0 \equiv \frac{1}{\sqrt{LC}} \quad \leftarrow \text{corner (resonant) frequency}$$

$$= \frac{1}{\left(1 + \frac{s}{\omega_1}\right) \left(1 + \frac{s}{\omega_2}\right)}$$

↑ roots ↑

$$Q \equiv \frac{\omega_0 L}{R} = \frac{1}{\omega_0 CR} = \frac{R_0}{R} \quad \text{where } R_0 \equiv \sqrt{\frac{L}{C}}$$

↑ characteristic resistance

$Q < 0.5$ : roots  $\omega_1$  and  $\omega_2$  are real

$Q > 0.5$ : roots  $\omega_1$  and  $\omega_2$  are complex

$$\frac{2}{s} = \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$


$$\left| \frac{2}{s} \right| \xrightarrow{\omega \rightarrow 0} 1 \Rightarrow 0 \text{ dB}$$

$$\xrightarrow{\omega \rightarrow \infty} \left(\frac{\omega_0}{\omega}\right)^2$$


Asymptotes intersect at  $\omega_0$


Asymptotes are independent of  $Q$ ;

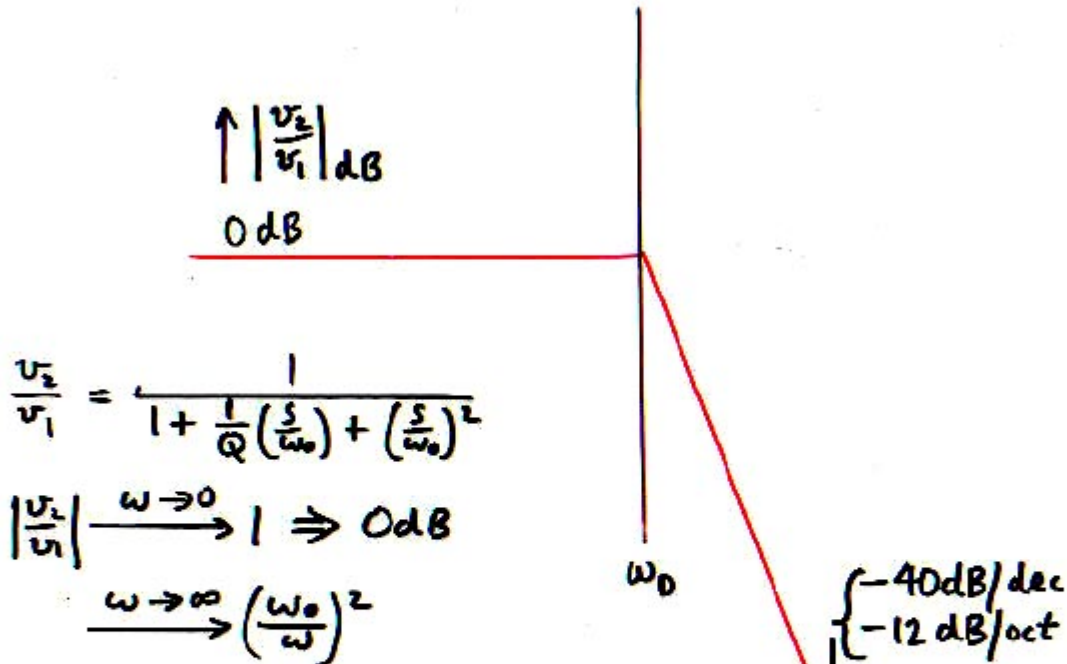
$Q$  affects shape only in neighborhood of  $\omega_0$




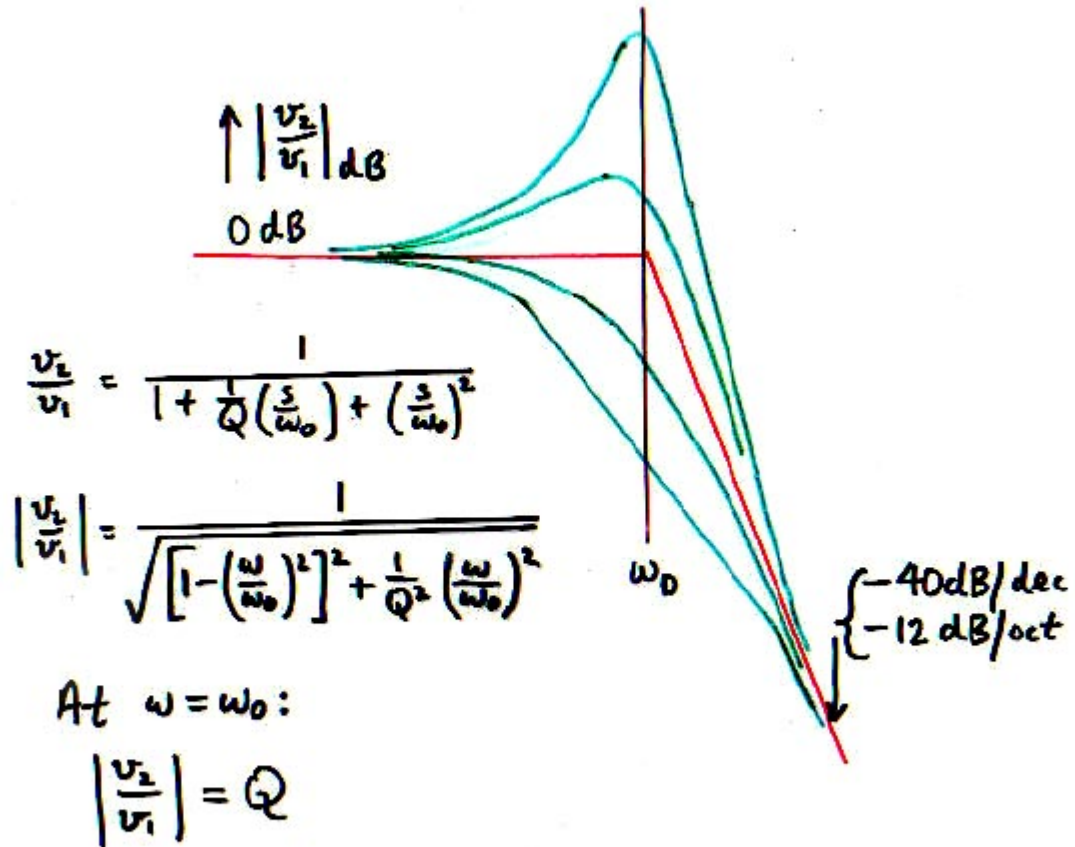Asymptotes intersect at  $\omega_0$   
 Asymptotes are independent of  $Q$ ;  
 $Q$  affects shape only in  
 neighborhood of  $\omega_0$




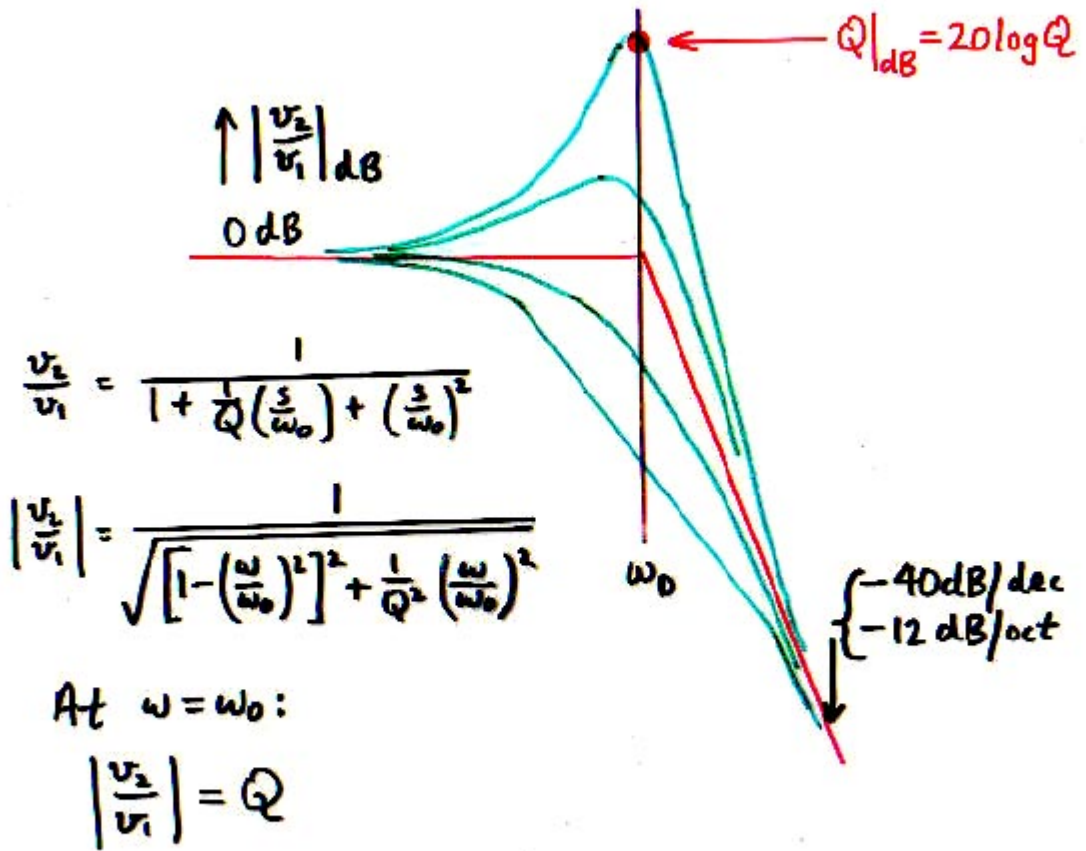

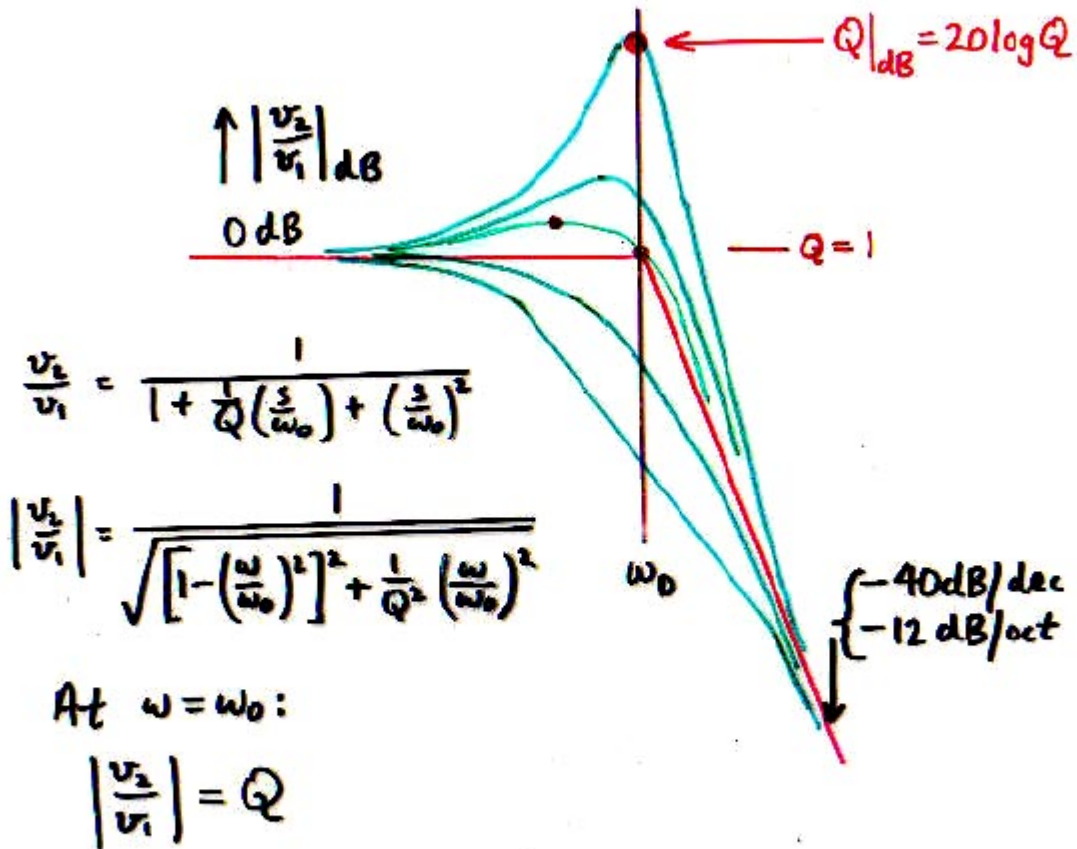

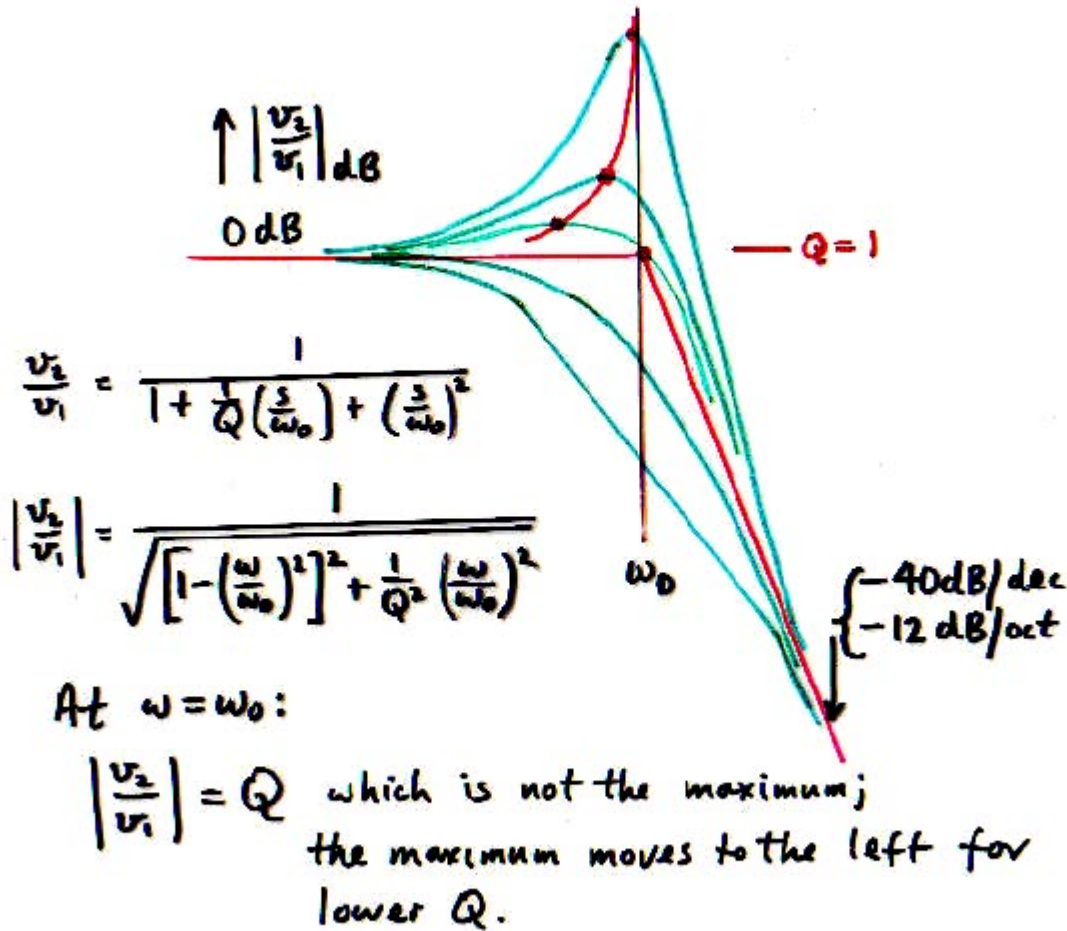



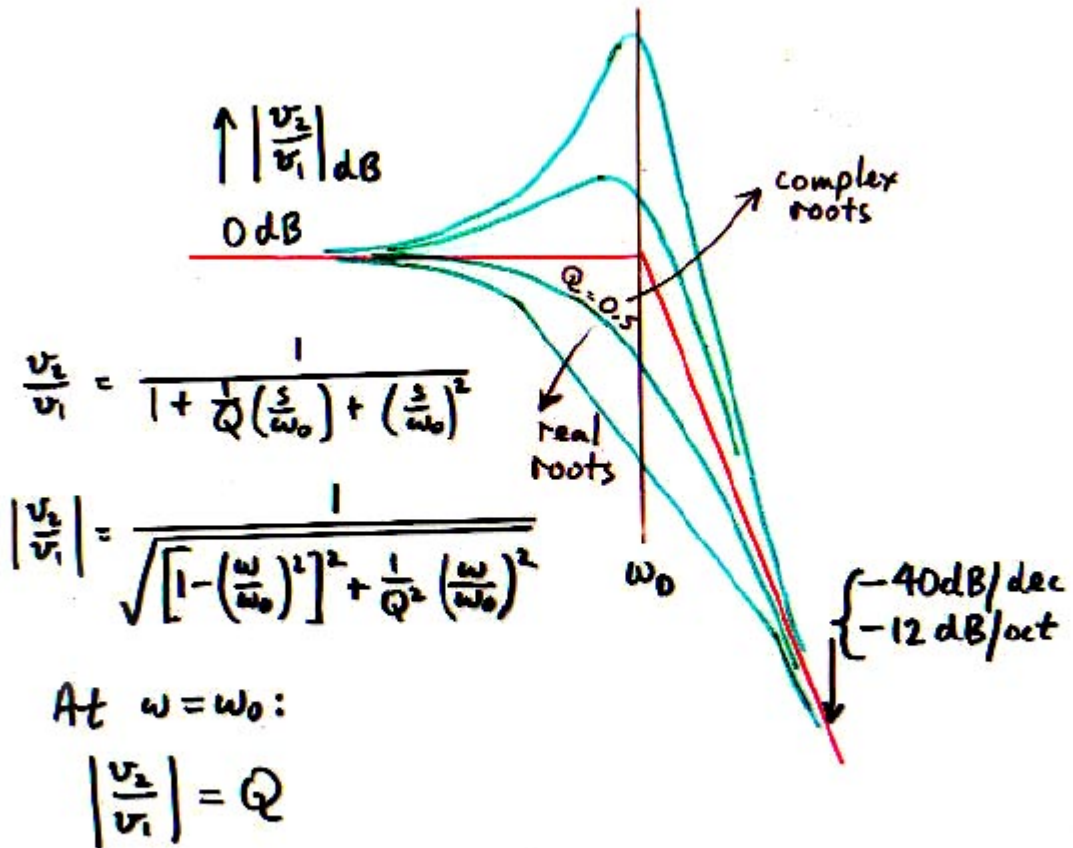


Phase shape:

$$\frac{v_2}{v_1} = - \tan^{-1} \left[ \frac{\frac{1}{Q} \left( \frac{\omega}{\omega_0} \right)}{1 - \left( \frac{\omega}{\omega_0} \right)^2} \right]$$

$$\begin{array}{l} \xrightarrow{\omega \rightarrow 0} 0^\circ \\ \xrightarrow{\omega = \omega_0} -90^\circ \\ \xrightarrow{\omega = \infty} -180^\circ \end{array} \left. \vphantom{\begin{array}{l} \xrightarrow{\omega \rightarrow 0} 0^\circ \\ \xrightarrow{\omega = \omega_0} -90^\circ \\ \xrightarrow{\omega = \infty} -180^\circ \end{array}} \right\}$$

independent  
of  $Q$

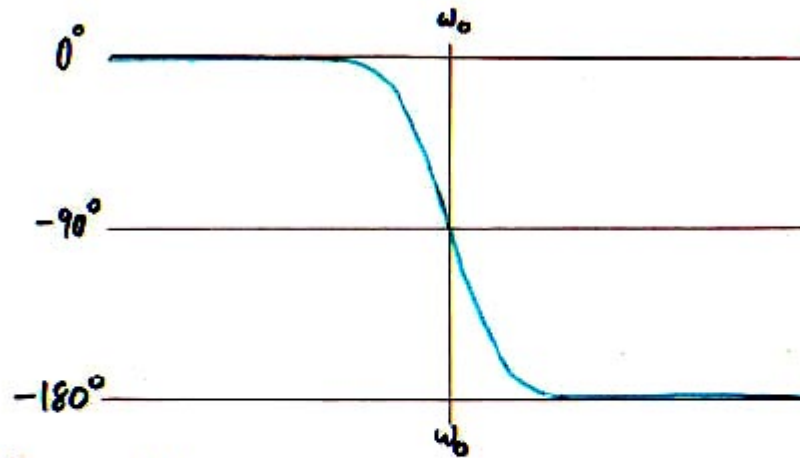


Phase shape:

$$\frac{v_2}{v_1} = -\tan^{-1} \left[ \frac{\frac{1}{Q} \left( \frac{\omega}{\omega_0} \right)}{1 - \left( \frac{\omega}{\omega_0} \right)^2} \right]$$


$$\left. \begin{array}{l} \omega \rightarrow 0 \rightarrow 0^\circ \\ \omega = \omega_0 \rightarrow -90^\circ \\ \omega \rightarrow \infty \rightarrow -180^\circ \end{array} \right\}$$

independent  
of Q

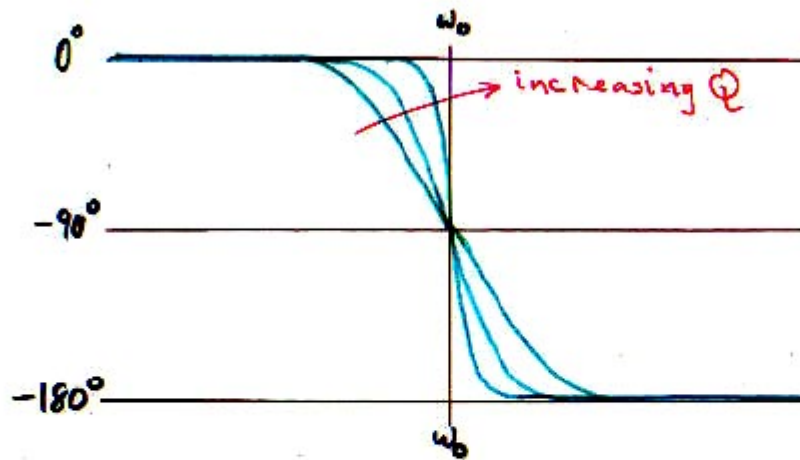


Increased  $Q$  causes sharper phase change between the  $0^\circ$  and  $-180^\circ$  asymptotes.

Need: a straight-line approximation.

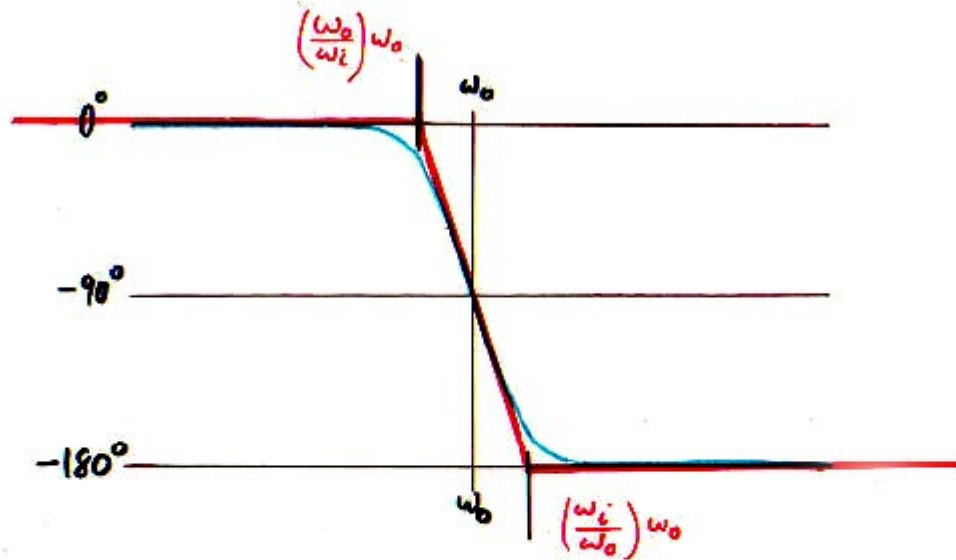

Choose same slope at  $\omega = \omega_0$ :
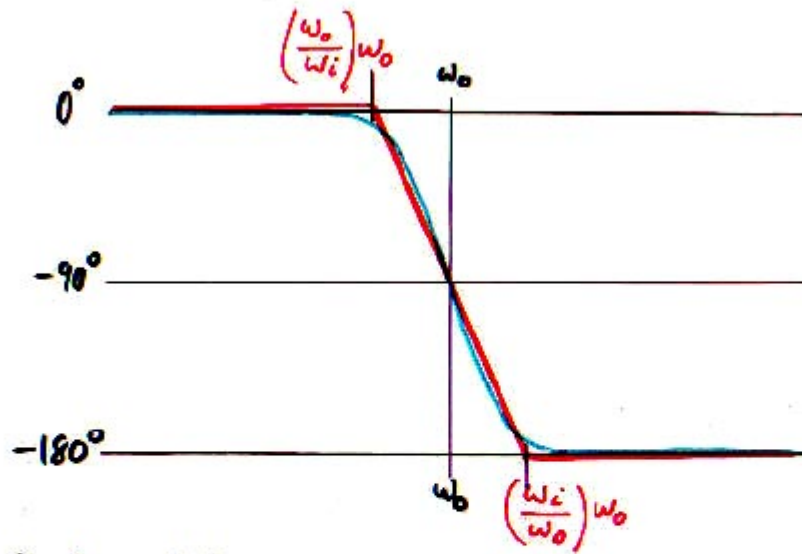
$$\frac{\omega_i}{\omega_0} = \left( e^{\frac{\pi}{2}} \right)^{\frac{1}{2Q}} = (4.81)^{\frac{1}{2Q}}$$



Better choice :

$$\frac{\omega_i}{\omega_0} \approx 5^{\frac{1}{2Q}}$$

**An even better choice is**

$$\frac{\omega_i}{\omega_o} = 10^{\frac{1}{2Q}}$$

**because for  $Q = 0.5$  (two equal real roots)**

$$\frac{\omega_i}{\omega_o} = 10$$

**and the slope is  $-90^\circ / \text{dec}$ , the same as twice the  $-45^\circ / \text{dec}$  slope for a single pole.**

Second-order response:

$$A = A_1 \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

$$A = A_1 \frac{1}{1 + a_1(x) + a_2(x)^2} = A_1 \frac{1}{1 + \frac{a_1}{\sqrt{a_2}} (\sqrt{a_2}x) + (\sqrt{a_2}x)^2}$$

$$x = \frac{s}{\omega_0}$$


$$a_2 = 1$$

$$a_1 = \frac{1}{Q}$$

$$x = s$$

$$a_2 = \frac{1}{\omega_0^2}$$

$$a_1 = \frac{1}{\omega_0 Q}$$

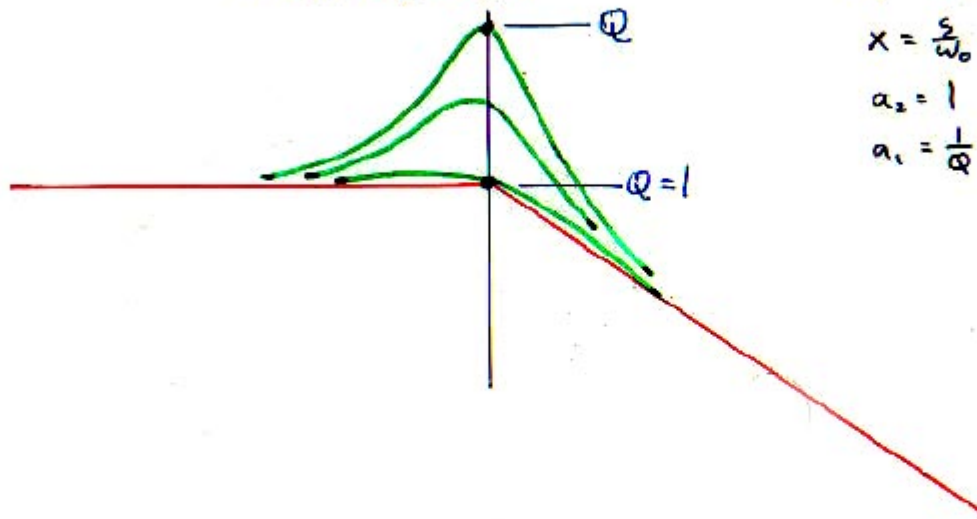




Second-order response:

$$A = A_1 \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$
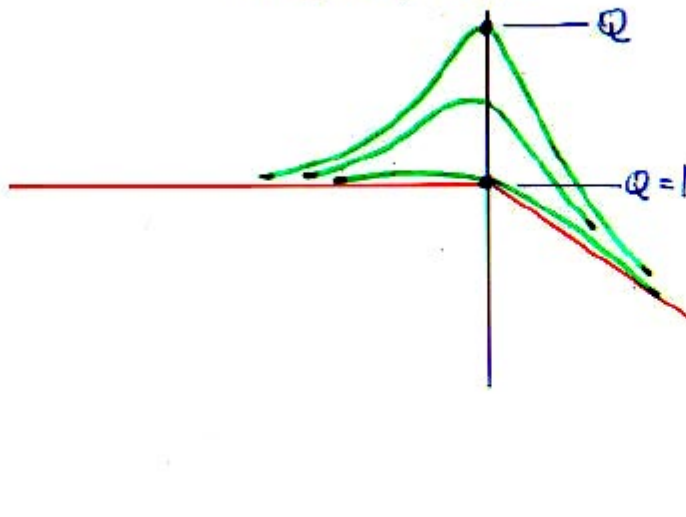
$$A = A_1 \frac{1}{1 + a_1(x) + a_2(x)^2} = A_1 \frac{1}{1 + \frac{a_1}{\sqrt{a_2}} (\sqrt{a_2}x) + (\sqrt{a_2}x)^2}$$



$$x = \frac{s}{\omega_0}$$

$$a_2 = 1$$

$$a_1 = \frac{1}{Q}$$

$$x = s$$

$$a_2 = \frac{1}{\omega_0^2}$$

$$a_1 = \frac{1}{\omega_0 Q}$$


$$F \equiv \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4a_2/a_1^2}$$

$$F \equiv \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2}$$

$$A = A_1 \frac{1}{(1 + a_1 F x)(1 + \frac{a_2}{a_1 F} x)}$$

Second-order response:
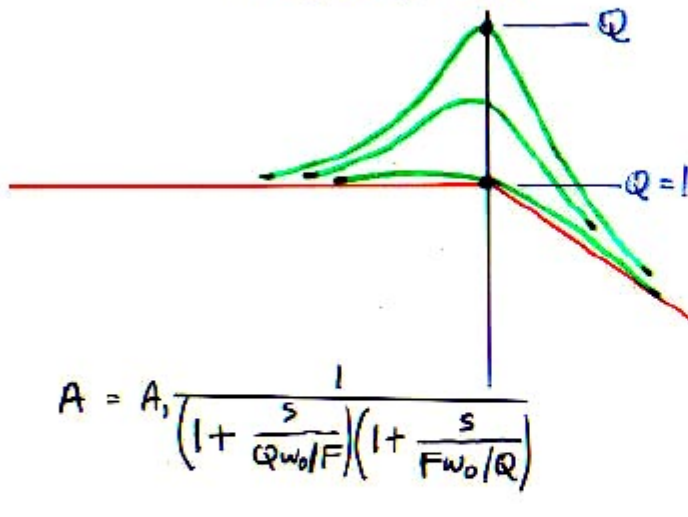
$$A = A_1 \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$



$$A = A_1 \frac{1}{\left(1 + \frac{s}{Q\omega_0/F}\right) \left(1 + \frac{s}{F\omega_0/Q}\right)}$$

$$A = A_1 \frac{1}{1 + a_1(x) + a_2(x)^2} = A_1 \frac{1}{1 + \frac{a_1}{\sqrt{a_2}} (\sqrt{a_2}x) + (\sqrt{a_2}x)^2}$$

$$x = \frac{s}{\omega_0}$$

$$a_2 = 1$$

$$a_1 = \frac{1}{Q}$$

$$x = s$$

$$a_2 = \frac{1}{\omega_0^2}$$

$$a_1 = \frac{1}{\omega_0 Q}$$

$$F = \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4a_2/a_1^2}$$


$$F = \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2}$$

$$A = A_1 \frac{1}{\left(1 + a_1 F x\right) \left(1 + \frac{a_2}{a_1 F} x\right)}$$

Second-order response:

$$A = A_1 \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$
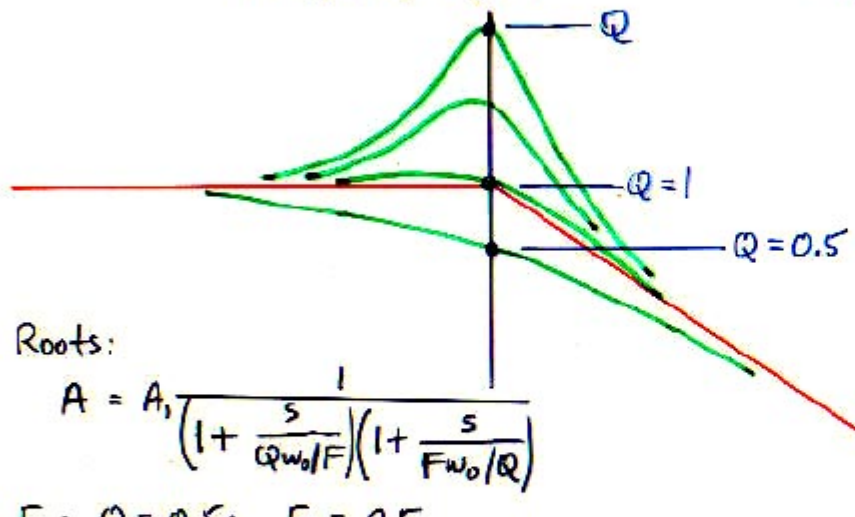
$$A = A_1 \frac{1}{1 + a_1(x) + a_2(x)^2} = A_1 \frac{1}{1 + \frac{a_1}{\sqrt{a_2}} (\sqrt{a_2}x) + (\sqrt{a_2}x)^2}$$



$$x = \frac{s}{\omega_0}$$

$$a_2 = 1$$

$$a_1 = \frac{1}{Q}$$

$$x = s$$

$$a_2 = \frac{1}{\omega_0^2}$$

$$a_1 = \frac{1}{\omega_0 Q}$$

$$F = \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4a_2/a_1^2}$$

$$F = \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2}$$

Roots:

$$A = A_1 \frac{1}{\left(1 + \frac{s}{Q\omega_0/F}\right) \left(1 + \frac{s}{F\omega_0/Q}\right)}$$

For  $Q = 0.5$ :  $F = 0.5$


$$A = A_1 \frac{1}{\left(1 + \frac{s}{\omega_0}\right)^2}$$

$$A = A_1 \frac{1}{\left(1 + a_1 F x\right) \left(1 + \frac{a_2}{a_1 F} x\right)}$$

Second-order response:

$$A = A_1 \frac{1}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$
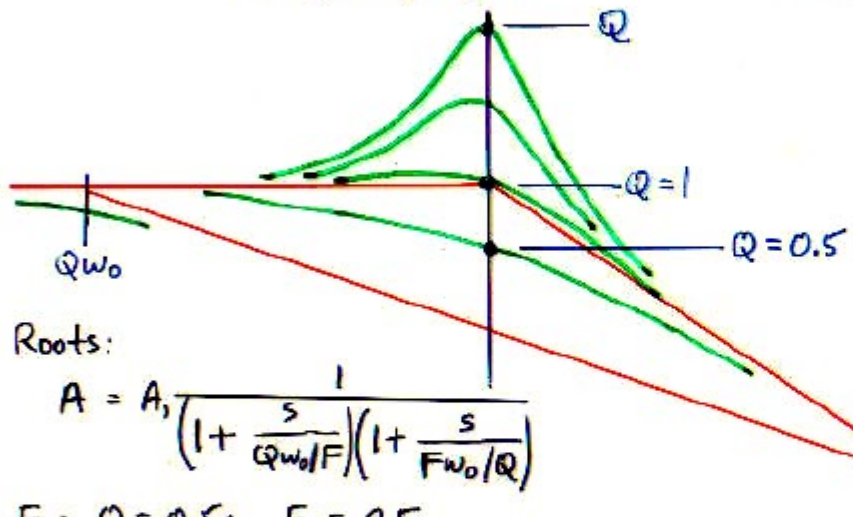
$$A = A_1 \frac{1}{1 + a_1(x) + a_2(x)^2} = A_1 \frac{1}{1 + \frac{a_1}{\sqrt{a_2}} (\sqrt{a_2}x) + (\sqrt{a_2}x)^2}$$



$$x = \frac{s}{\omega_0}$$

$$a_2 = 1$$

$$a_1 = \frac{1}{Q}$$

$$x = s$$

$$a_2 = \frac{1}{\omega_0^2}$$

$$a_1 = \frac{1}{\omega_0 Q}$$

$$F = \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4a_2/a_1^2}$$

$$F = \frac{1}{2} + \frac{1}{2} \sqrt{1 - 4Q^2}$$

Roots:

$$A = A_1 \frac{1}{\left(1 + \frac{s}{Q\omega_0 F}\right) \left(1 + \frac{s}{F\omega_0/Q}\right)}$$

For  $Q = 0.5$ :  $F = 0.5$

$$A = A_1 \frac{1}{\left(1 + \frac{s}{\omega_0}\right)^2}$$

For  $Q \ll 0.5$ :  $F \approx 1$


$$A = A_1 \frac{1}{\left(1 + \frac{s}{Q\omega_0}\right) \left(1 + \frac{s}{\omega_0/Q}\right)}$$


$$A = A_1 \frac{1}{\left(1 + a_1 F x\right) \left(1 + \frac{a_2}{a_1 F} x\right)}$$

$$\frac{\omega_0}{Q}$$

$$A = A_1 \frac{1}{\left(1 + a_1 x\right) \left(1 + \frac{a_2}{a_1} x\right)}$$


Low-pass 2-pole characteristic:

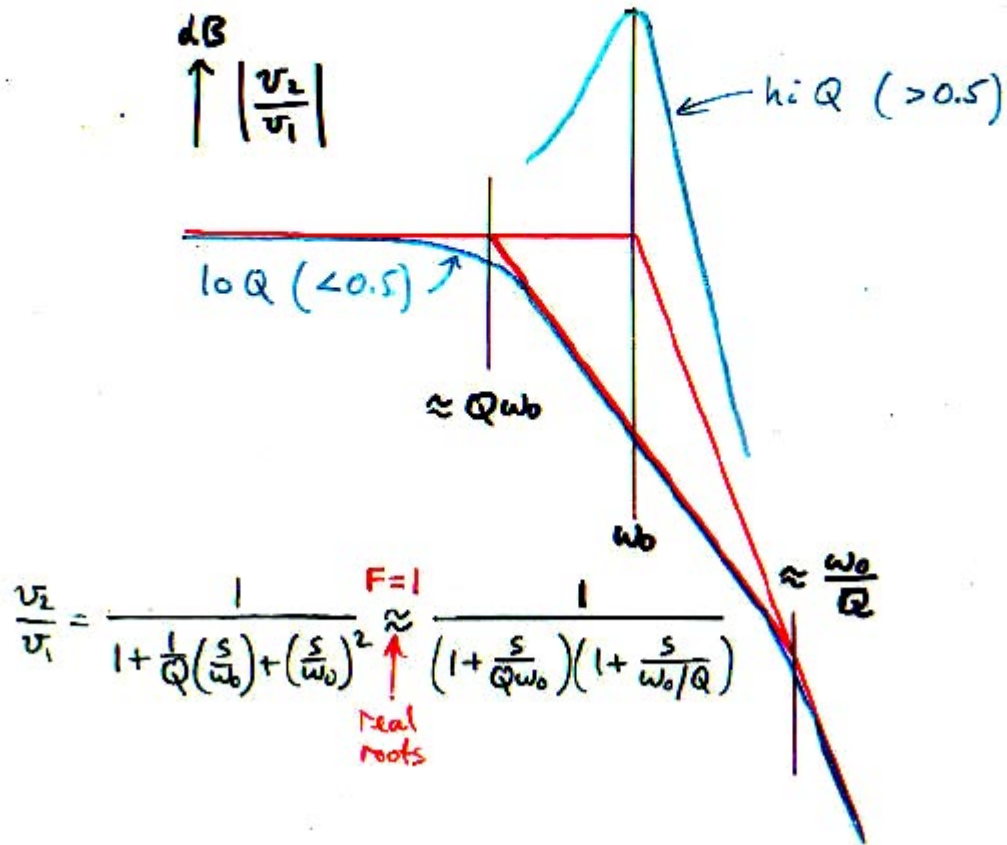







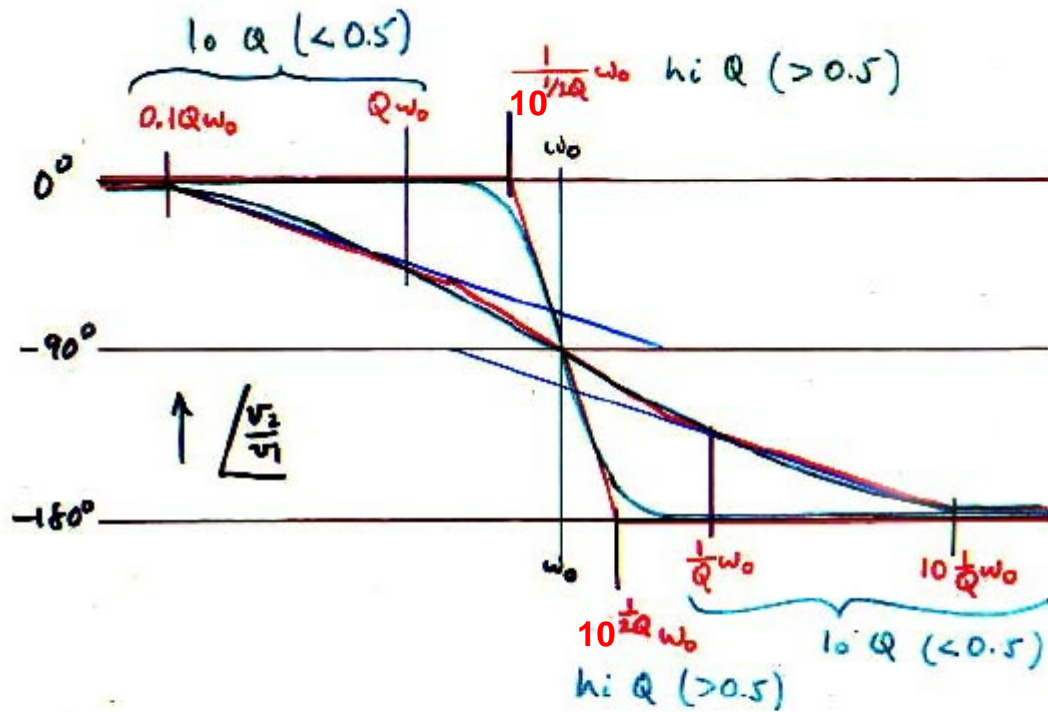





Normal and inverted poles and zeros:

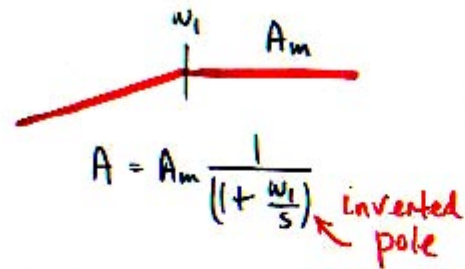

$|A|$  dB  
 $\uparrow$   
 $\omega$  (log)

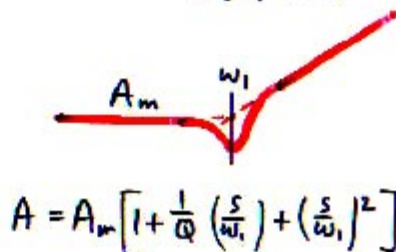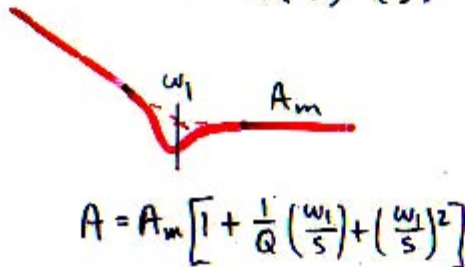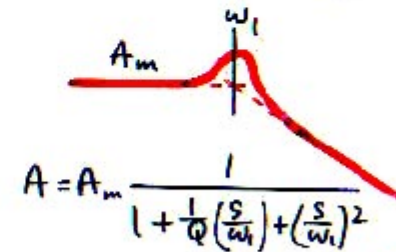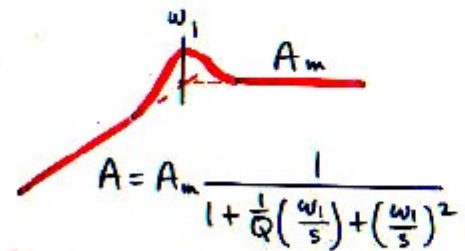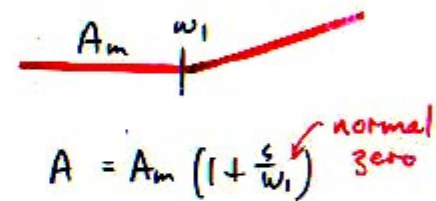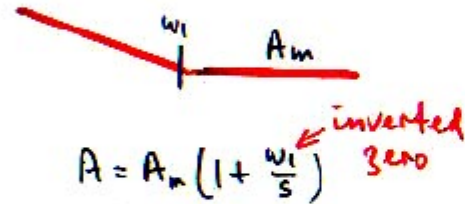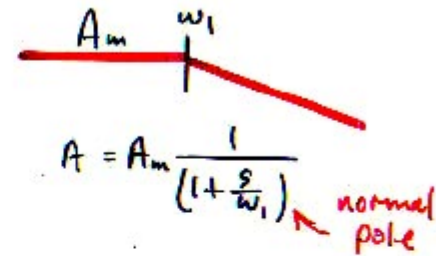
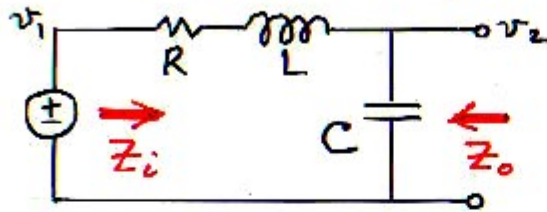
## Input and Output Impedances of low-pass filter



$$\omega_0 = \frac{1}{\sqrt{LC}} \quad Q = \frac{R_0}{R} = \frac{1}{\omega_0 CR} = \frac{\omega_0 L}{R}$$

$$R_0 = \sqrt{\frac{L}{C}}$$

$$Z_i = \frac{1}{sC} + R + sL$$

$$= \frac{1 + sCR + s^2LC}{sC}$$

$$Z_o = \frac{\frac{1}{sC}(R + sL)}{\frac{1}{sC} + R + sL}$$

$$= \frac{R + sL}{1 + sCR + s^2LC}$$

Express in terms of  $\omega_0$ ,  $Q$ ,  $R_0$ :

$$Z_i = \frac{1}{\omega_0 C} \frac{1 + \omega_0 CR \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right)}$$


$$= R_0 \frac{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right)}$$

$$Z_o = \omega_0 L \frac{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{R}{sL}\right)}{1 + \omega_0 CR \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

$$= R_0 \frac{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0/Q}{s}\right)}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$


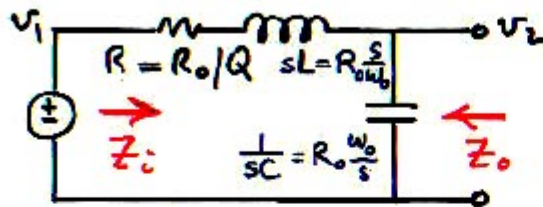
## Input and Output Impedances of low-pass filter



$$\omega_o \equiv \frac{1}{\sqrt{LC}} \quad Q = \frac{R_o}{R}$$

$$R_o \equiv \sqrt{\frac{L}{C}}$$

$$Z_i = \frac{R_o}{Q} + R_o \frac{s}{\omega_o} + R_o \frac{\omega_o}{s}$$


$$Z_o = \frac{\left(\frac{R_o}{Q} + R_o \frac{s}{\omega_o}\right) R_o \frac{\omega_o}{s}}{\frac{R_o}{Q} + R_o \frac{s}{\omega_o} + R_o \frac{\omega_o}{s}}$$

$$= R_o \frac{1 + \frac{1}{Q} \left(\frac{s}{\omega_o}\right) + \left(\frac{s}{\omega_o}\right)^2}{\left(\frac{s}{\omega_o}\right)}$$

$$= R_o \frac{\left(\frac{s}{\omega_o}\right) \left(1 + \frac{\omega_o/Q}{s}\right)}{1 + \frac{1}{Q} \left(\frac{s}{\omega_o}\right) + \left(\frac{s}{\omega_o}\right)^2}$$

Note how the algebra is shortened when the analysis starts with the normalized element values.
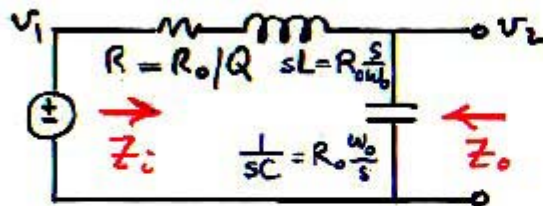
## Input and Output Impedances of low-pass filter



$$\omega_0 \equiv \frac{1}{\sqrt{LC}}$$

$$Q = \frac{R_0}{R}$$

$$R_0 \equiv \sqrt{\frac{L}{C}}$$

$$Z_i = \frac{R_0}{Q} + R_0 \frac{s}{\omega_0} + R_0 \frac{\omega_0}{s}$$


$$Z_o = \frac{\left(\frac{R_0}{Q} + R_0 \frac{s}{\omega_0}\right) R_0 \frac{\omega_0}{s}}{\frac{R_0}{Q} + R_0 \frac{s}{\omega_0} + R_0 \frac{\omega_0}{s}}$$

$$= R_0 \frac{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right)}$$

$$= R_0 \frac{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0/Q}{s}\right)}{1 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

Put the quantities you know you want in the answer into the statement of the problem as soon as possible, even into the circuit diagram.
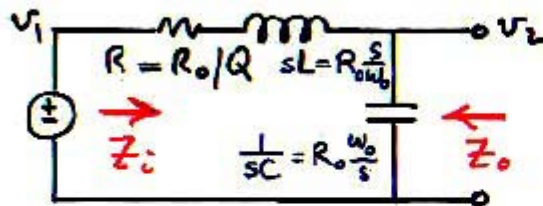
## Input and Output Impedances of low-pass filter



$$\omega_o \equiv \frac{1}{\sqrt{LC}} \quad Q = \frac{R_o}{R}$$

$$R_o \equiv \sqrt{\frac{L}{C}}$$

$$Z_i = \frac{R_o}{Q} + R_o \frac{s}{\omega_o} + R_o \frac{\omega_o}{s}$$

$$Z_o = \frac{\left(\frac{R_o}{Q} + R_o \frac{s}{\omega_o}\right) R_o \frac{\omega_o}{s}}{\frac{R_o}{Q} + R_o \frac{s}{\omega_o} + R_o \frac{\omega_o}{s}}$$

$$= R_o \frac{1 + \frac{1}{Q} \left(\frac{s}{\omega_o}\right) + \left(\frac{s}{\omega_o}\right)^2}{\left(\frac{s}{\omega_o}\right)}$$


$$= R_o \frac{\left(\frac{s}{\omega_o}\right) \left(1 + \frac{\omega_o/Q}{s}\right)}{1 + \frac{1}{Q} \left(\frac{s}{\omega_o}\right) + \left(\frac{s}{\omega_o}\right)^2}$$

Put the quantities you know you want in the answer into the statement of the problem as soon as possible, even into the circuit diagram.


$$Z_i = R_o \times \left[ 1 + \frac{1}{Q} \left( \frac{s}{\omega_o} \right) + \left( \frac{s}{\omega_o} \right)^2 \right] \times \left[ \frac{1}{\frac{s}{\omega_o}} \right]$$

ref. value
 $\frac{1}{H}$ 
single slope


$R_o$

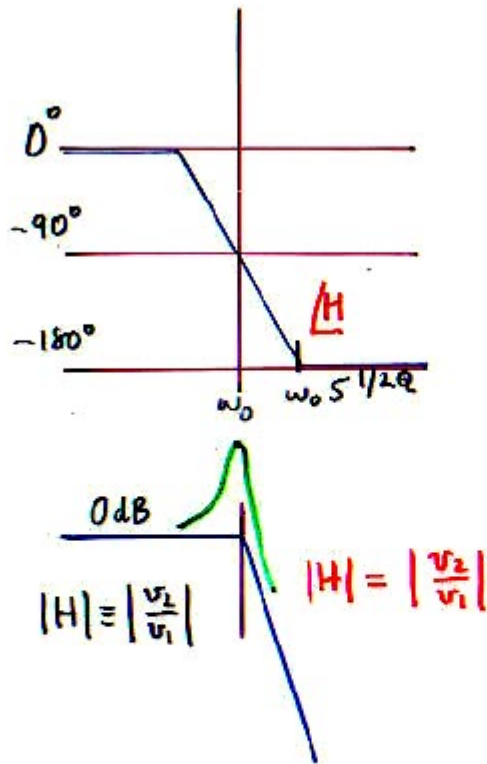


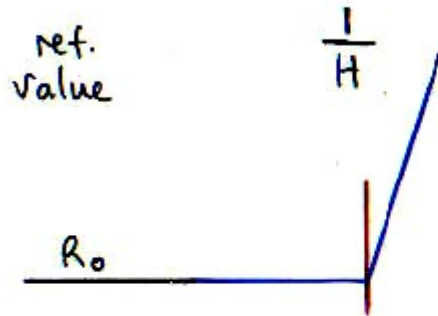
$$\bar{Z}_i = R_o \times \left[ 1 + \frac{1}{Q} \left( \frac{s}{\omega_o} \right) + \left( \frac{s}{\omega_o} \right)^2 \right] \times \left[ \frac{1}{\frac{s}{\omega_o}} \right]$$




single slope

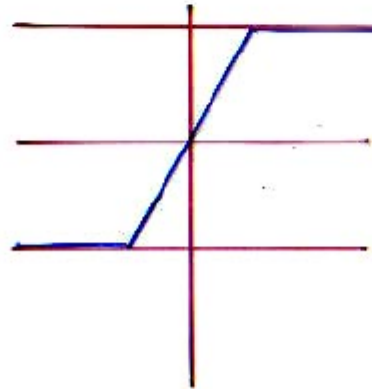
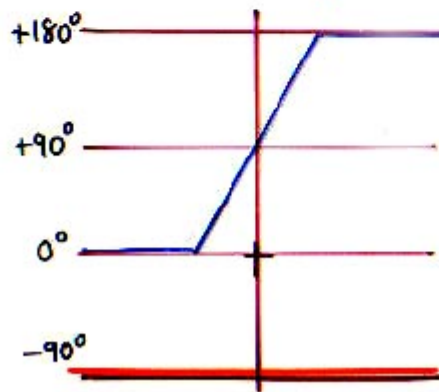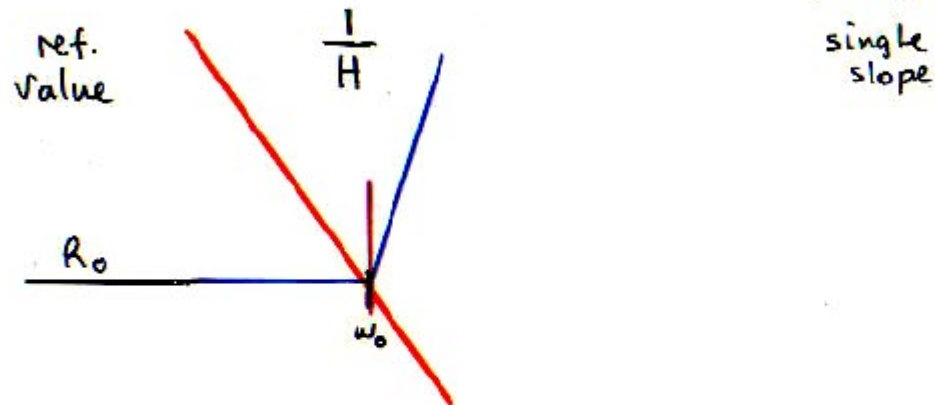
$$\bar{Z}_i = R_o \times \left[ 1 + \frac{1}{Q} \left( \frac{s}{\omega_o} \right) + \left( \frac{s}{\omega_o} \right)^2 \right] \times \left[ \frac{1}{\frac{s}{\omega_o}} \right]$$





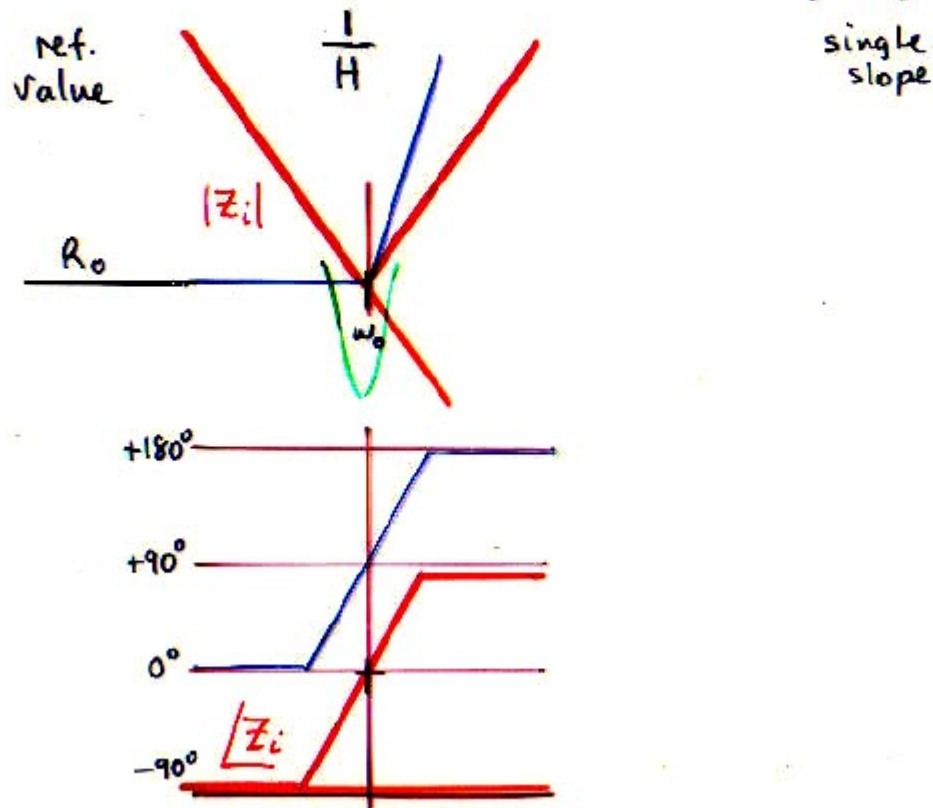
$$\bar{Z}_i = R_o \times \left[ 1 + \frac{1}{Q} \left( \frac{s}{\omega_o} \right) + \left( \frac{s}{\omega_o} \right)^2 \right] \times \left[ \frac{1}{\frac{s}{\omega_o}} \right]$$






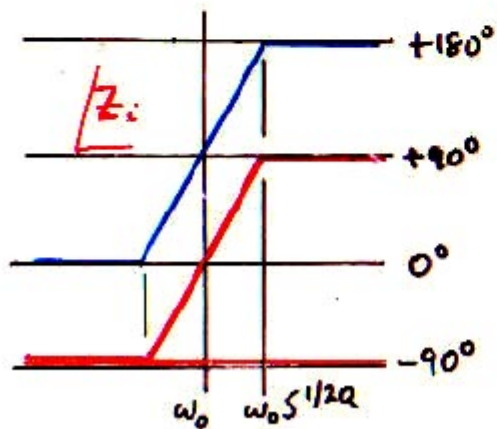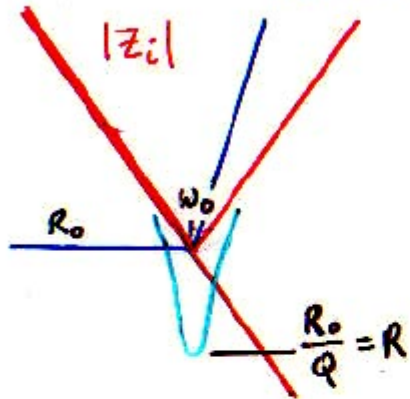Asymptote sketches for high  $Q$  ( $\gg 0.5$ )



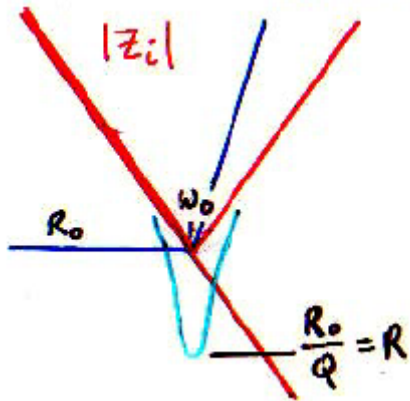
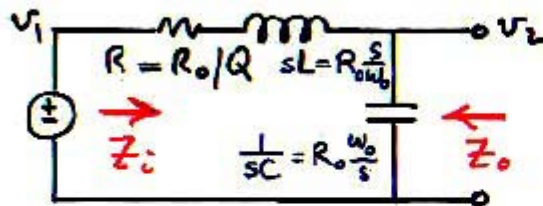
## Input and Output Impedances of low-pass filter



$$\omega_o \equiv \frac{1}{\sqrt{LC}} \quad Q = \frac{R_o}{R}$$

$$R_o \equiv \sqrt{\frac{L}{C}}$$

$$Z_i = \frac{R_o}{Q} + R_o \frac{s}{\omega_o} + R_o \frac{\omega_o}{s}$$

$$Z_o = \frac{\left(\frac{R_o}{Q} + R_o \frac{s}{\omega_o}\right) R_o \frac{\omega_o}{s}}{\frac{R_o}{Q} + R_o \frac{s}{\omega_o} + R_o \frac{\omega_o}{s}}$$

$$= R_o \frac{1 + \frac{1}{Q} \left(\frac{s}{\omega_o}\right) + \left(\frac{s}{\omega_o}\right)^2}{\left(\frac{s}{\omega_o}\right)}$$



$$= R_o \frac{\left(\frac{s}{\omega_o}\right) \left(1 + \frac{\omega_o/Q}{s}\right)}{1 + \frac{1}{Q} \left(\frac{s}{\omega_o}\right) + \left(\frac{s}{\omega_o}\right)^2}$$

Put the quantities you know you want in the answer into the statement of the problem as soon as possible, even into the circuit diagram.

$$Z_o = R_o \times \left[ \frac{\frac{s}{\omega_o}}{1 + \frac{1}{Q} \left( \frac{s}{\omega_o} \right) + \left( \frac{s}{\omega_o} \right)^2} \right] \times \left( 1 + \frac{\omega_o/Q}{s} \right)$$


ref. value
 $\frac{1}{Z_i}$ 
inverted zero

R<sub>o</sub>

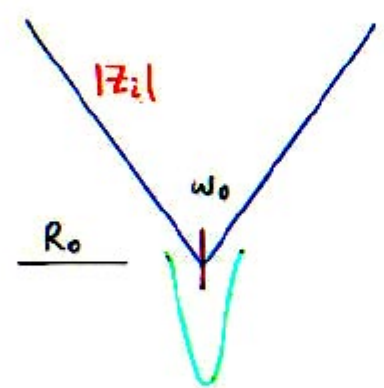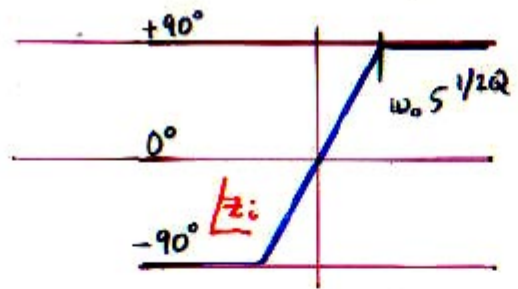

$$Z_o = R_o \times \left[ \frac{\frac{s}{\omega_o}}{1 + \frac{1}{Q} \left( \frac{s}{\omega_o} \right) + \left( \frac{s}{\omega_o} \right)^2} \right] \times \left( 1 + \frac{\omega_o/Q}{s} \right)$$

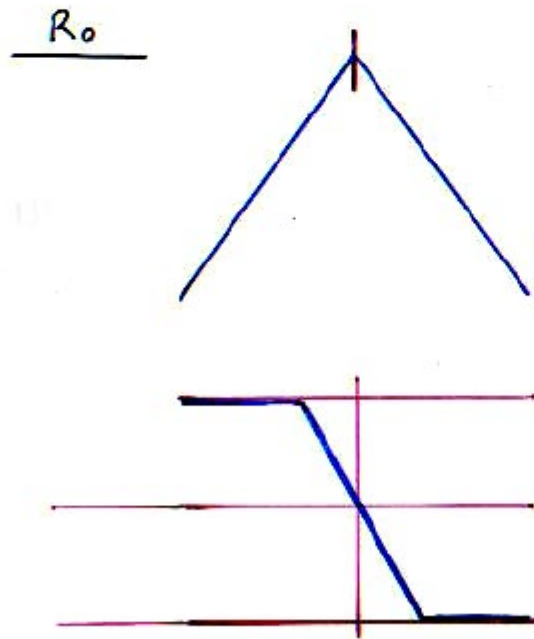ref. value
 $\frac{1}{Z_i}$ 
inverted zero





$$Z_o = R_o \times \left[ \frac{\frac{s}{\omega_o}}{1 + \frac{1}{Q} \left( \frac{s}{\omega_o} \right) + \left( \frac{s}{\omega_o} \right)^2} \right] \times \left( 1 + \frac{\omega_o/Q}{s} \right)$$

ref.  
value



$\frac{1}{Z_i}$

inverted  
zero

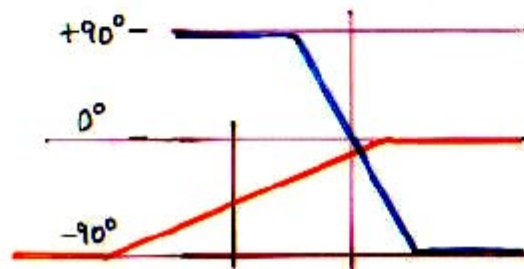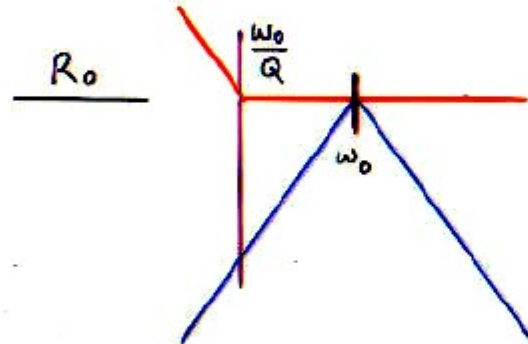


$$Z_o = R_o \times \left[ \frac{\frac{s}{\omega_o}}{1 + \frac{1}{Q} \left( \frac{s}{\omega_o} \right) + \left( \frac{s}{\omega_o} \right)^2} \right] \times \left( 1 + \frac{\omega_o/Q}{s} \right)$$

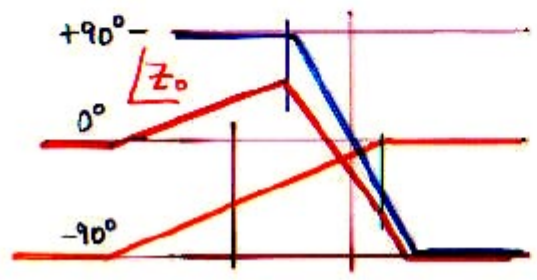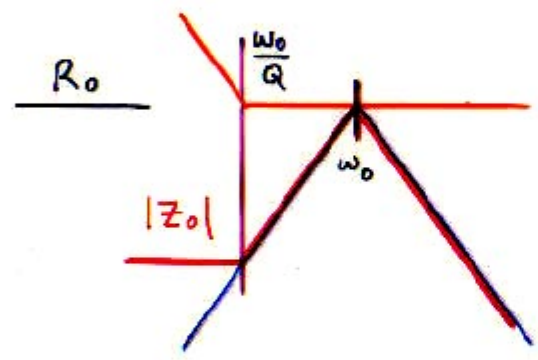ref. value
 $\frac{1}{Z_i}$ 
inverted zero





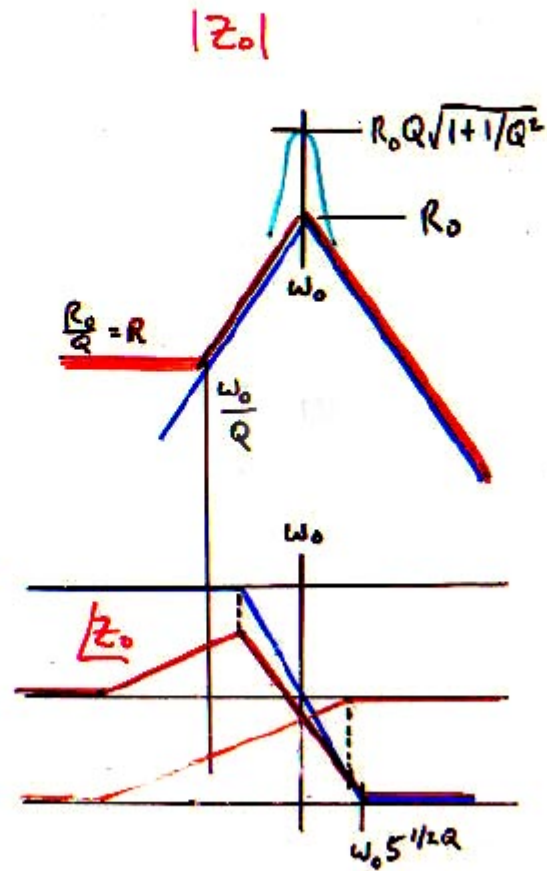

## Exercise 5.1

Sketch asymptotes for  $Z_i$  and  $Z_o$  for low  $Q$ .


Exercise

For the two-pole low-pass LC filter,  
sketch the magnitude and phase asymptotes  
of  $Z_i$  and  $Z_o$  for low  $Q$  ( $\ll 0.5$ ).

(But take  $Q > 0.1$ )

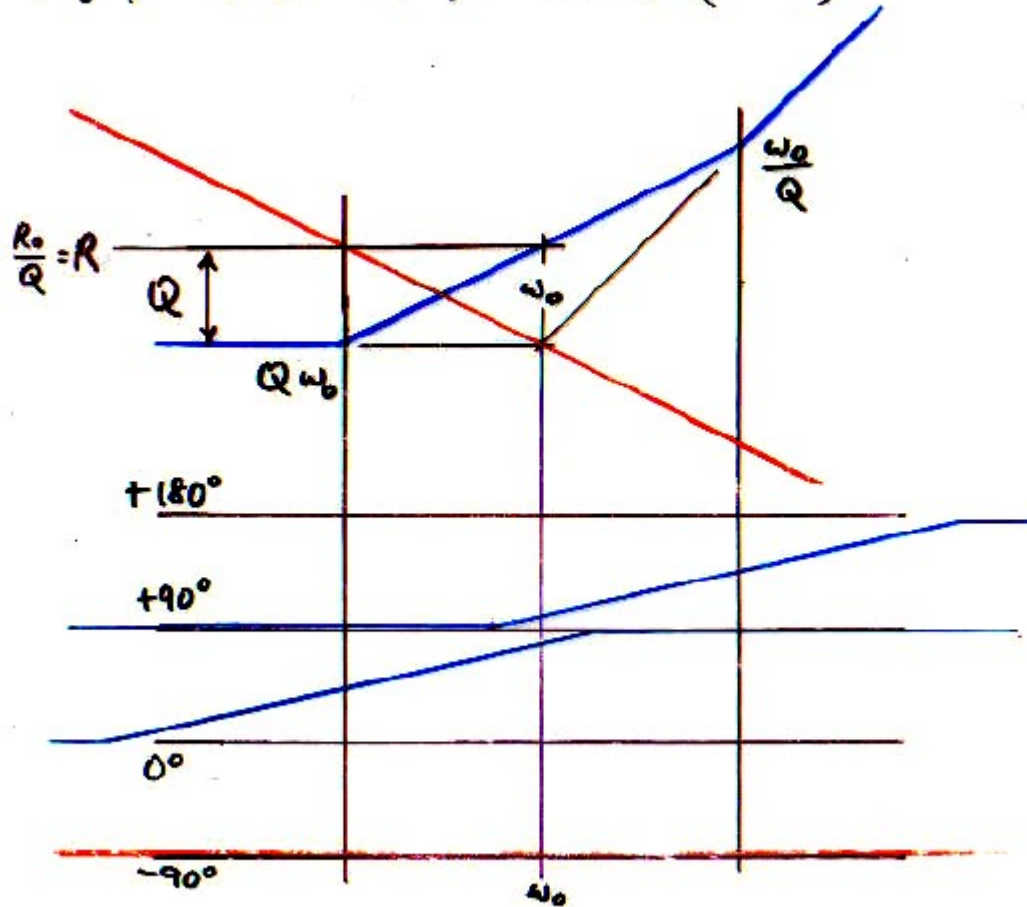
# Exercise 5.1 - Solution

Asymptotes for  $Z_i$  for low  $Q$  ( $\ll 0.5$ ):



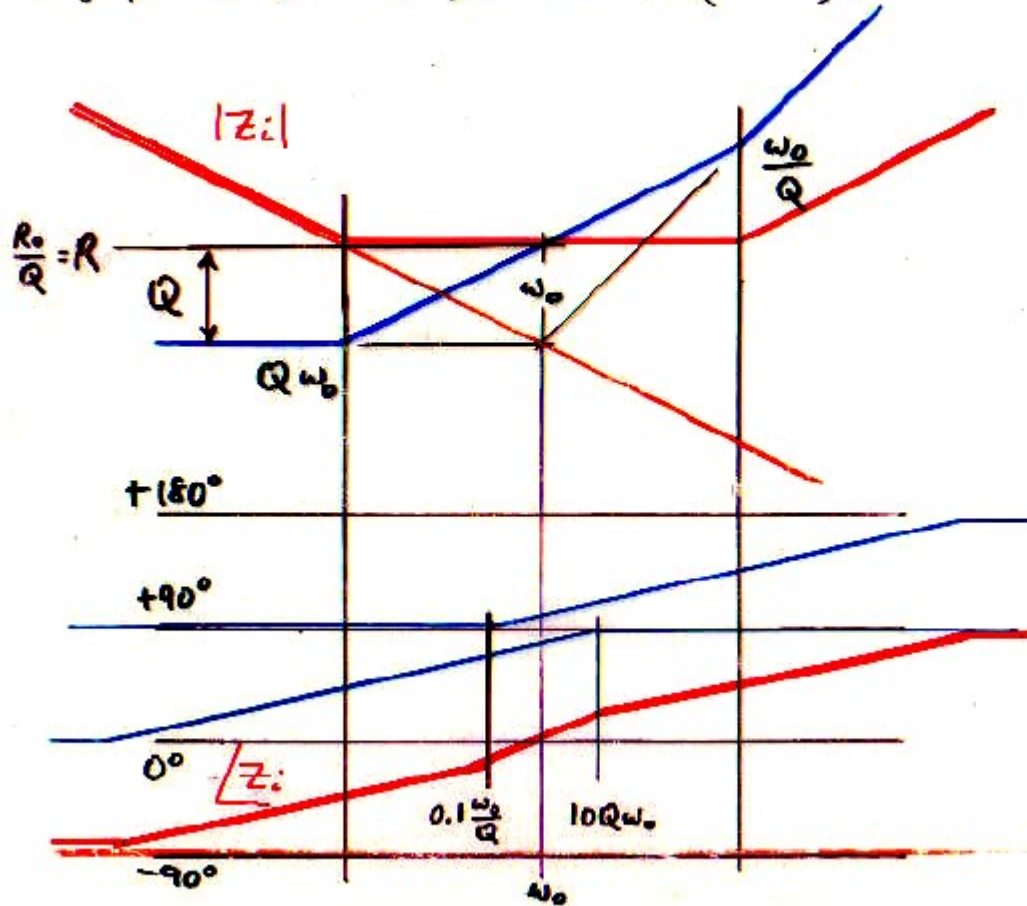
# Exercise 5.1 - Solution

Asymptotes for  $Z_i$  for low  $Q$  ( $\ll 0.5$ ):



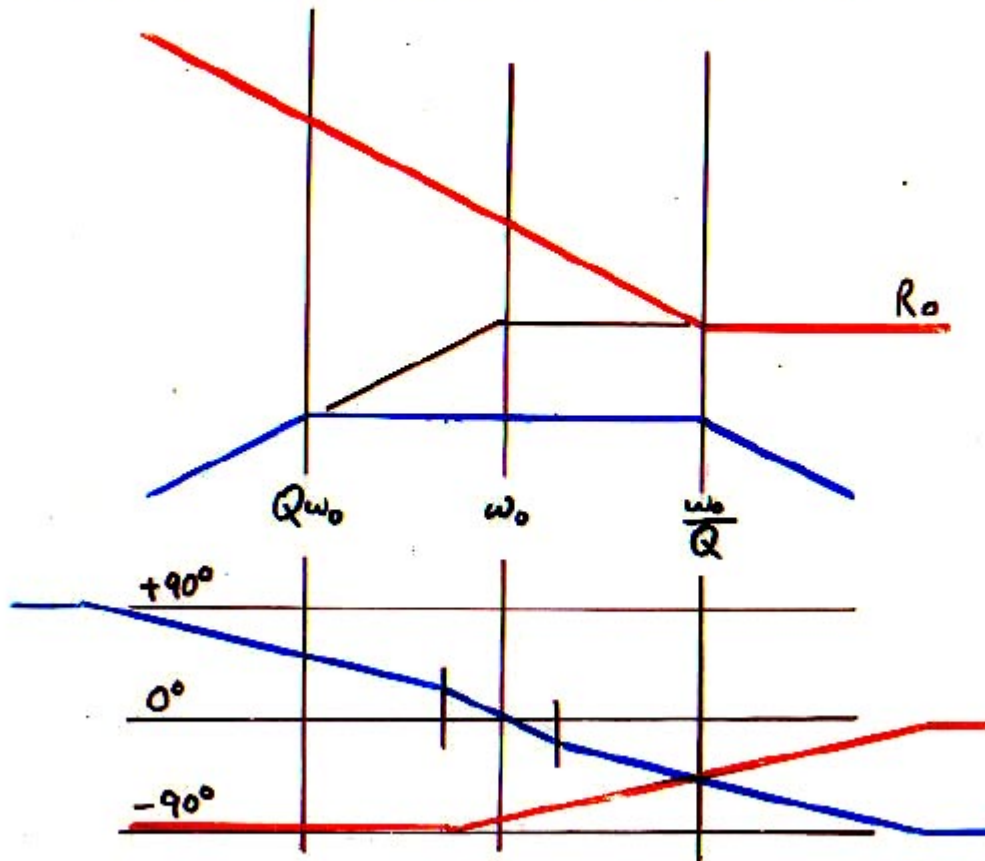
# Exercise 5.1 - Solution

Asymptotes for  $Z_o$  for low  $Q$  ( $\ll 0.5$ ):



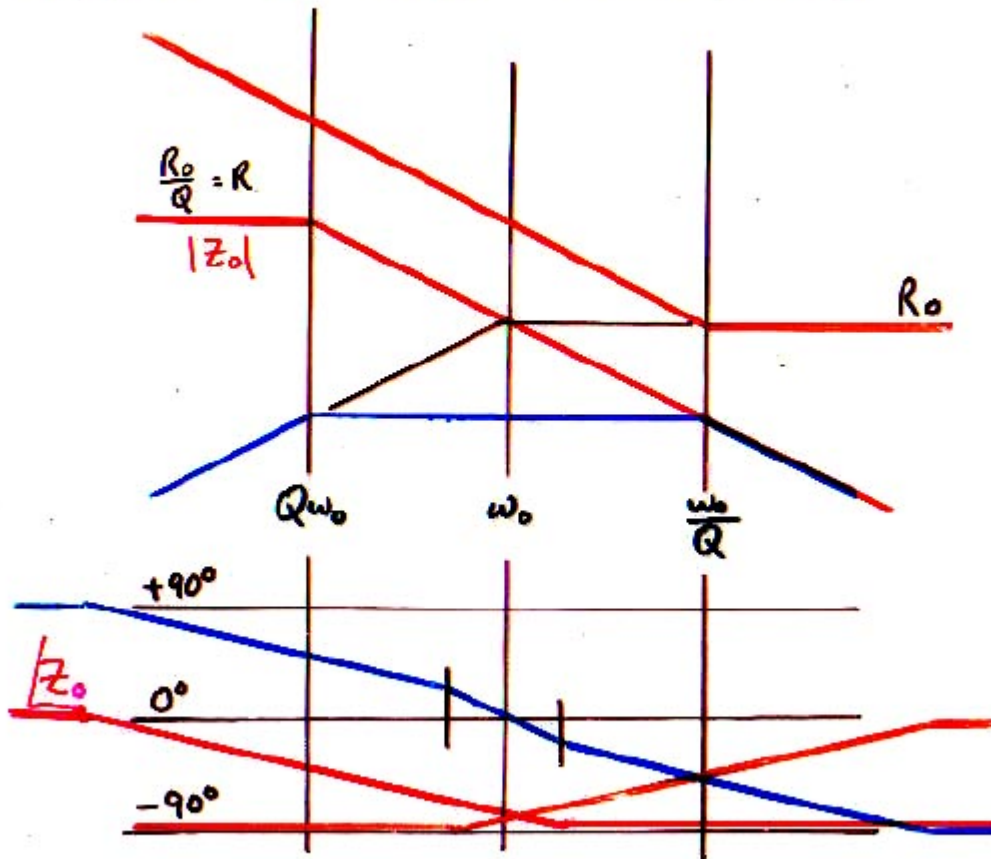
# Exercise 5.1 - Solution

Asymptotes for  $Z_o$  for low  $Q$  ( $\ll 0.5$ ):




Loaded low-pass LC filter

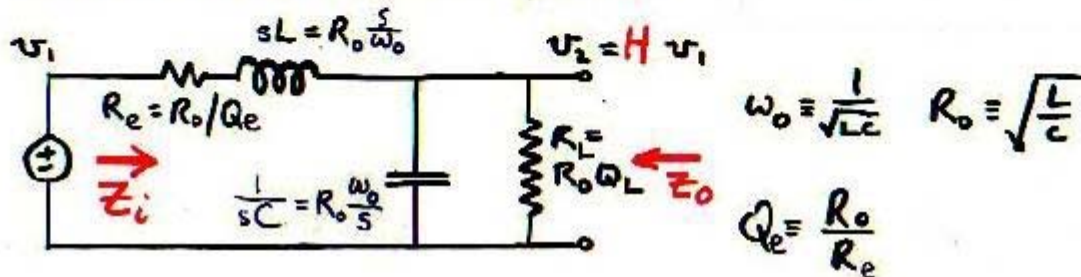

Since there are now two resistances, re-name  
 $R \rightarrow R_e, Q \rightarrow Q_e$

By analogy, define  $Q_L \equiv \frac{R_L}{R_o}$

### Loaded low-pass LC filter

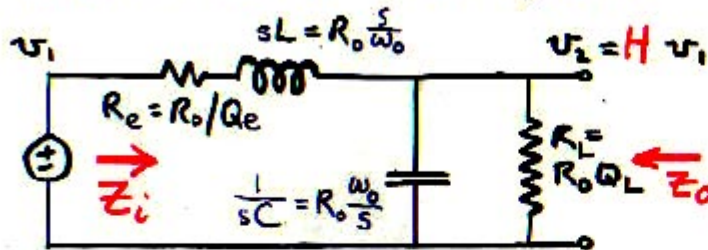

Note:  $R \rightarrow R_e$ ,  $Q \rightarrow Q_e$


$$\omega_o = \frac{1}{\sqrt{LC}} \quad R_o = \sqrt{\frac{L}{C}}$$

$$Q_e = \frac{R_o}{R_e} \quad Q_L = \frac{R_L}{R_o}$$

Why is  $Q_L$  defined "upside down" relative to  $Q_e$ ?



## Loaded low-pass LC filter

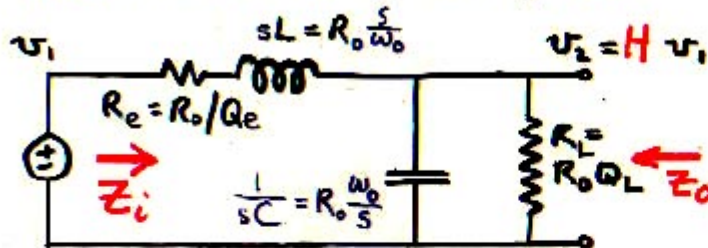

Note:  $R \rightarrow R_e$ ,  $Q \rightarrow Q_e$

$$\omega_o = \frac{1}{\sqrt{LC}} \quad R_o = \sqrt{\frac{L}{C}}$$


$$Q_e = \frac{R_o}{R_e} \quad Q_L = \frac{R_L}{R_o}$$

$$H = \frac{\frac{R_o Q_L}{1 + Q_L \frac{s}{\omega_o}}}{\frac{R_o Q_L}{1 + Q_L \frac{s}{\omega_o}} + \frac{R_o}{Q_e} + R_o \frac{s}{\omega_o}} = \frac{Q_L}{Q_L + \frac{1}{Q_e} + \left(\frac{Q_L}{Q_e} + 1\right)\left(\frac{s}{\omega_o}\right) + Q_L \left(\frac{s}{\omega_o}\right)^2}$$

$$= \frac{1}{1 + 1/Q_e Q_L} \frac{1}{1 + \frac{\left(\frac{1}{Q_e} + \frac{1}{Q_L}\right)}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_o}\right) + \frac{1}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_o}\right)^2}$$

## Conventional result:

Loaded low-pass LC filter

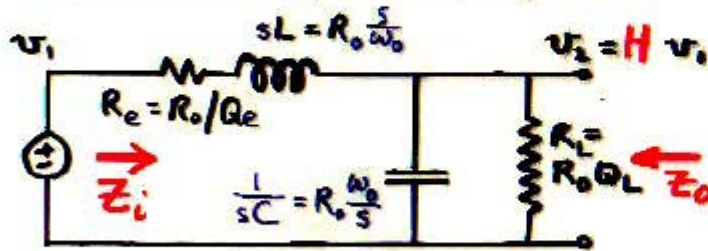

Note:  $R \rightarrow R_e$ ,  $Q \rightarrow Q_e$


$$\omega_0 = \frac{1}{\sqrt{LC}} \quad R_0 = \sqrt{\frac{L}{C}}$$

$$Q_e = \frac{R_0}{R_e} \quad Q_L = \frac{R_L}{R_0}$$

$$H = \frac{\frac{R_L}{1+sCR_L}}{\frac{R_L}{1+sCR_L} + R_e + sL} = \frac{R_L}{R_L + R_e + s(CR_L R_e + L) + s^2 LCR_L}$$

Reveals no insight

## Conventional result:

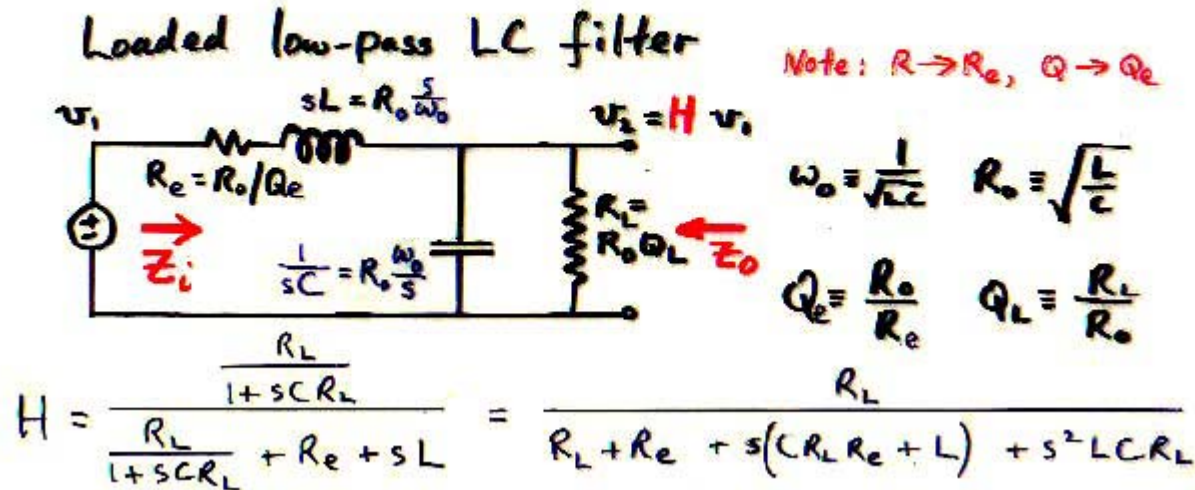


Reveals no insight

This high entropy result can be converted into the desired low entropy version by application of mental energy, but it takes quite an effort, and you have to know where you're going!

# Conventional result:

Loaded low-pass LC filter

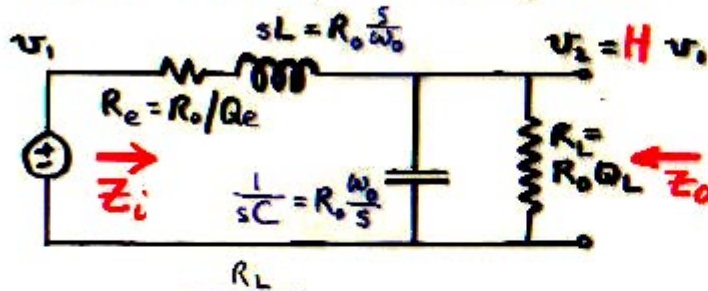

Note:  $R \rightarrow R_e$ ,  $Q \rightarrow Q_e$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad R_0 = \sqrt{\frac{L}{C}}$$

$$Q_e = \frac{R_0}{R_e} \quad Q_L = \frac{R_L}{R_0}$$

$$H = \frac{\frac{R_L}{1+sCR_L}}{\frac{R_L}{1+sCR_L} + R_e + sL} = \frac{R_L}{R_L + R_e + s(CR_L R_e + L) + s^2 LCR_L}$$

$$= \frac{R_L}{R_L + R_e} \frac{1}{1 + s\left(CR_e + \frac{L}{R_L}\right) \frac{R_L}{R_L + R_e} + s^2 LC \frac{R_L}{R_L + R_e}}$$

$$= \frac{R_L}{R_L + R_e} \frac{1}{1 + s\sqrt{LC} \left( R_e \sqrt{\frac{C}{L}} + \frac{1}{R_L} \sqrt{\frac{L}{C}} \right) \frac{R_L}{R_L + R_e} + s^2 LC \frac{R_L}{R_L + R_e}}$$

$$= \frac{1}{1 + 1/Q_e Q_L} \frac{1}{1 + \frac{\left(\frac{1}{Q_e} + \frac{1}{Q_L}\right)}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_0}\right) + \frac{1}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_0}\right)^2}$$

$$H = \frac{1}{1 + 1/Q_e Q_L} \frac{1}{1 + \frac{1/Q_e + 1/Q_L}{\sqrt{1 + 1/Q_e Q_L}} \left( \frac{s}{\omega_0 \sqrt{1 + 1/Q_e Q_L}} \right) + \left( \frac{s}{\omega_0 \sqrt{1 + 1/Q_e Q_L}} \right)^2}$$

Result, compared with unloaded case:

1. Low-freq. asymptote is  $\frac{1}{1 + 1/Q_e Q_L} = \frac{R_L}{R_L + R_e}$   
(resistive divider)
2. The corner frequency is changed to  $\sqrt{1 + 1/Q_e Q_L} \omega_0$
3. The damping coefficient is changed to  $\frac{1/Q_e + 1/Q_L}{\sqrt{1 + 1/Q_e Q_L}}$

This is a good example of how a low entropy format can allow one equation to disclose more than one useful piece of information.



$$H = \frac{1}{1 + 1/Q_e Q_L} \frac{1}{1 + \frac{1}{Q_e} + \frac{1}{Q_L} \left( \frac{s}{\omega_0 \sqrt{1 + 1/Q_e Q_L}} \right) + \left( \frac{s}{\omega_0 \sqrt{1 + 1/Q_e Q_L}} \right)^2}$$

Result, compared with unloaded case:

second  
order

- ⇒ 1. Low-freq. asymptote is  $\frac{1}{1 + 1/Q_e Q_L} = \frac{R_L}{R_L + R_e}$   
(resistive divider)

second  
order

- ⇒ 2. The corner frequency is changed to  
 $\sqrt{1 + 1/Q_e Q_L} \omega_0$

first  
order

- ⇒ 3. The damping coefficient is changed to  
 $\frac{\frac{1}{Q_e} + \frac{1}{Q_L}}{\sqrt{1 + 1/Q_e Q_L}}$

For the high-Q case,  $Q_e, Q_L \gg 0.5$ ,  $Q_e Q_L \gg 1$  and the first two effects are negligible, and the damping coefficient becomes



$$\frac{1}{Q_e} + \frac{1}{Q_L}$$

Hence, for the high-Q case,

$$H \approx \frac{1}{1 + \frac{1}{Q_t} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$


where  $Q_t$  is a "total" Q-factor given by the "parallel combination"
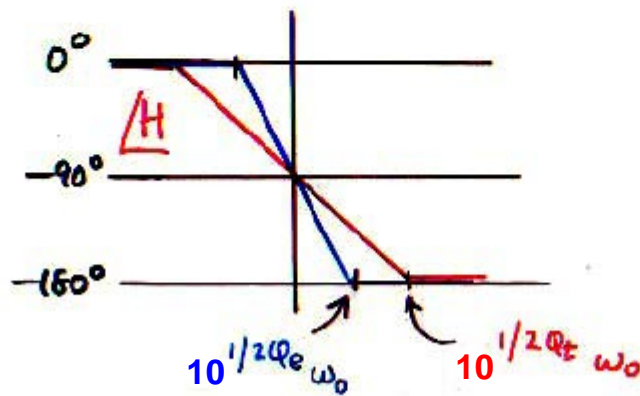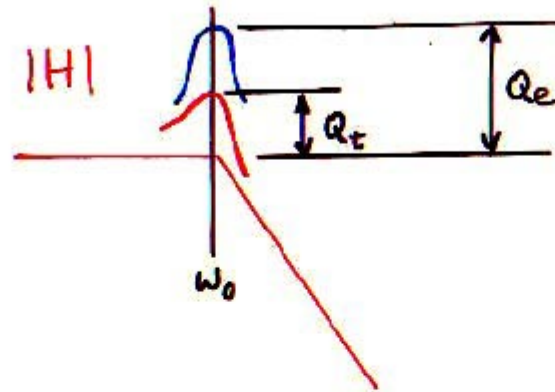
$$\frac{1}{Q_t} \equiv \frac{1}{Q_e} + \frac{1}{Q_L}$$





## Loaded low-pass LC filter

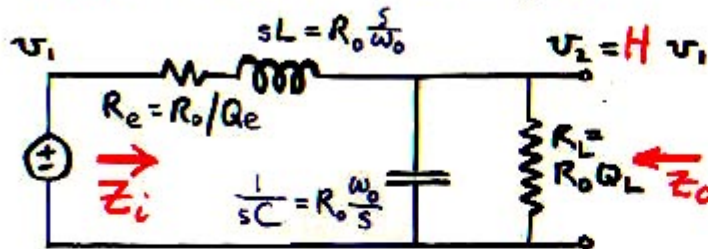

Note:  $R \rightarrow R_e$ ,  $Q \rightarrow Q_e$


$$\omega_0 \equiv \frac{1}{\sqrt{LC}} \quad R_0 \equiv \sqrt{\frac{L}{C}}$$

$$Q_e \equiv \frac{R_0}{R_e} \quad Q_L \equiv \frac{R_L}{R_0}$$

$$\begin{aligned} Z_i &= \frac{R_0 Q_L}{1 + Q_L \left(\frac{s}{\omega_0}\right)} + \frac{R_0}{Q_e} + R_0 \frac{s}{\omega_0} = R_0 \frac{Q_L + \frac{1}{Q_e} + \left(\frac{Q_L}{Q_e} + 1\right) \left(\frac{s}{\omega_0}\right) + Q_L \left(\frac{s}{\omega_0}\right)^2}{1 + Q_L \left(\frac{s}{\omega_0}\right)} \\ &= R_0 \left(1 + \frac{1}{Q_e Q_L}\right) \frac{1 + \frac{\frac{1}{Q_e} + \frac{1}{Q_L}}{1 + \frac{1}{Q_e Q_L}} \left(\frac{s}{\omega_0}\right) + \frac{1}{1 + \frac{1}{Q_e Q_L}} \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0 Q_L}{s}\right)} \end{aligned}$$

Same three effects as for  $H$ , but with addition of an inverted pole at  $\omega_0/Q_L$ .

## Loaded low-pass LC filter

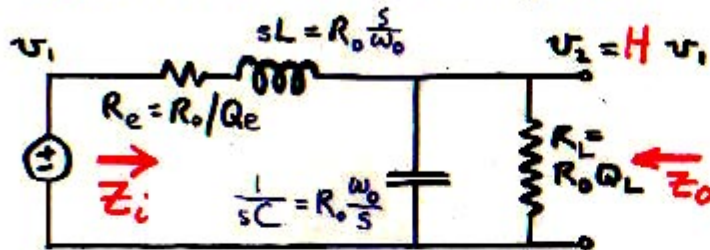

Note:  $R \rightarrow R_e$ ,  $Q \rightarrow Q_e$


$$\omega_o = \frac{1}{\sqrt{LC}} \quad R_o = \sqrt{\frac{L}{C}}$$


$$Q_e = \frac{R_o}{R_e} \quad Q_L = \frac{R_L}{R_o}$$

Hence, for the high- $Q$  case,

$$Z_i \approx R_o \frac{1 + \frac{1}{Q_e} \left(\frac{s}{\omega_o}\right) + \left(\frac{s}{\omega_o}\right)^2}{\left(\frac{s}{\omega_o}\right) \left(1 + \frac{\omega_o/Q_e}{s}\right)}$$

For high-Q case:

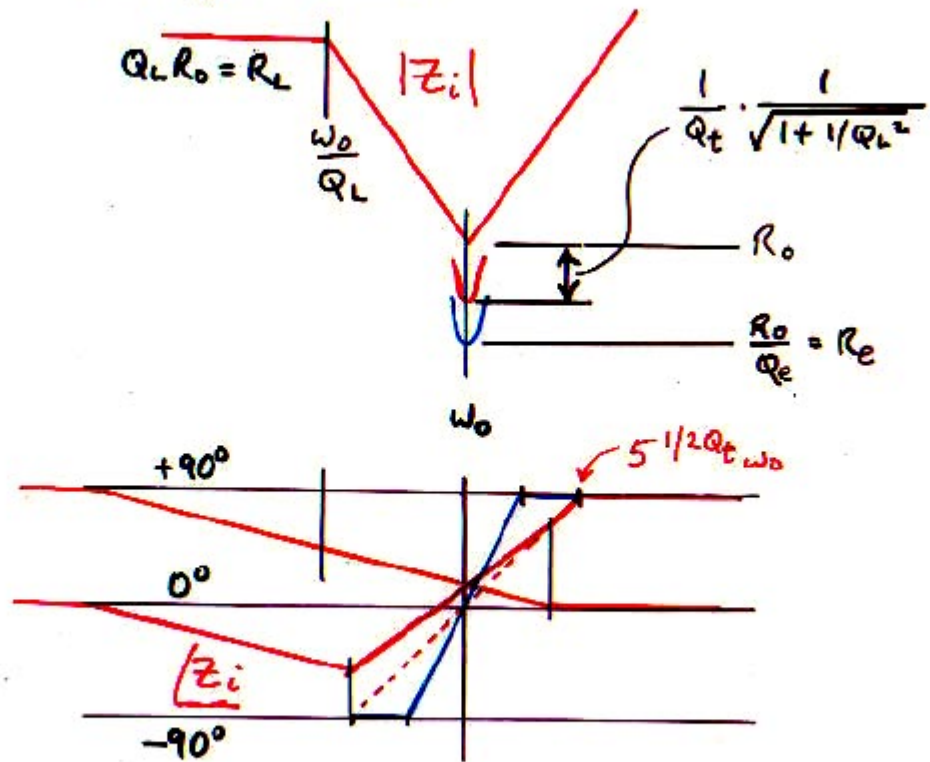


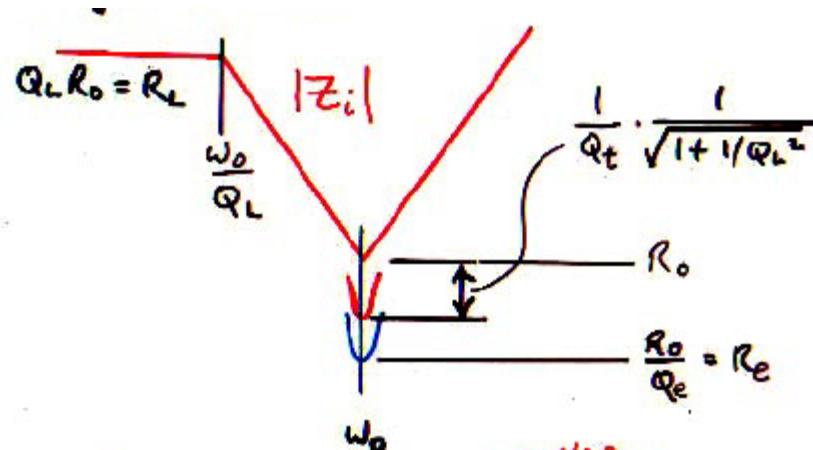

# Compare the $Z_i$ asymptotes with and without $R_L$ :


Without  $R_L$ :

$$(Q_L = \infty)$$

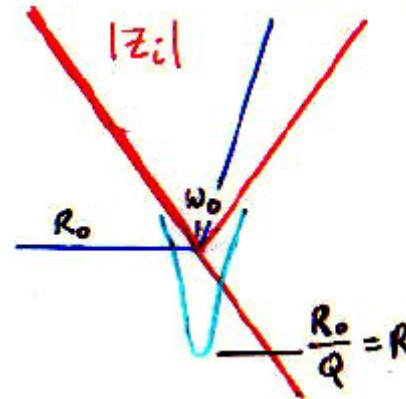


With  $R_L$ :

$$(Q_L \neq \infty)$$

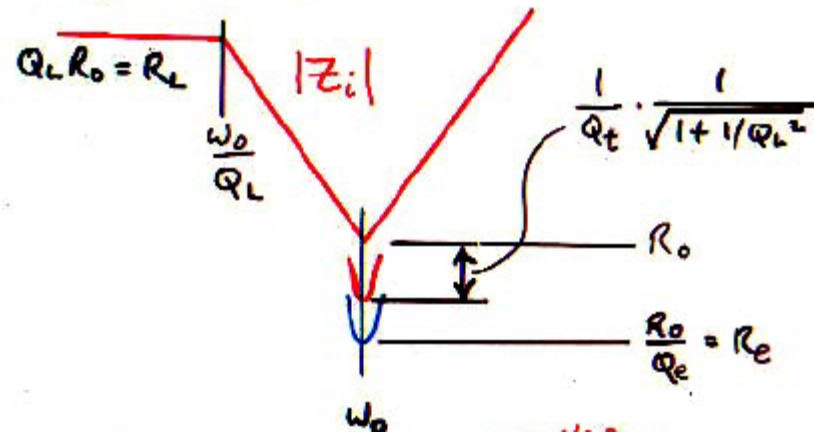

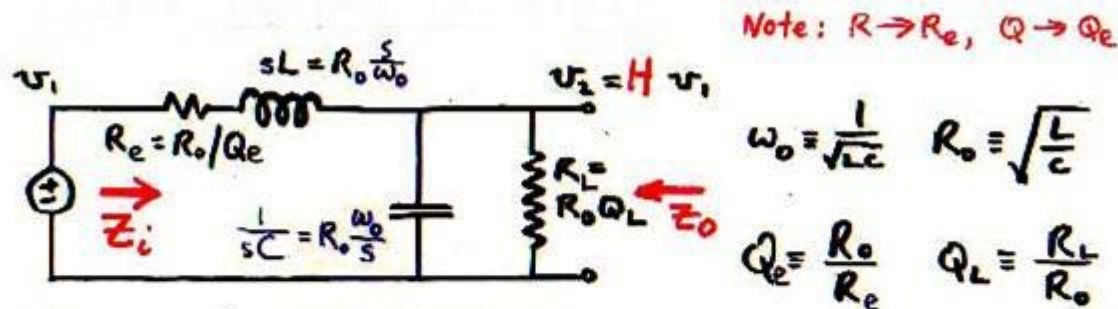The appearance of the new corner frequency  $\omega_0/Q_L$  can be confirmed by a mental frequency sweep:




Hence, for the high- $Q$  case,

$$Z_i \approx R_o \frac{1 + \frac{1}{Q_L} \left(\frac{s}{\omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{\omega_0/Q_L}{s}\right)}$$

Without  $R_L$ ,  $Z_i \rightarrow \infty$  as  $\omega \rightarrow 0$  because of the capacitive reactance.

With  $R_L$ ,  $Z_i$  flattens, so a concave downwards corner is introduced, which is an inverted pole.

### Loaded low-pass LC filter

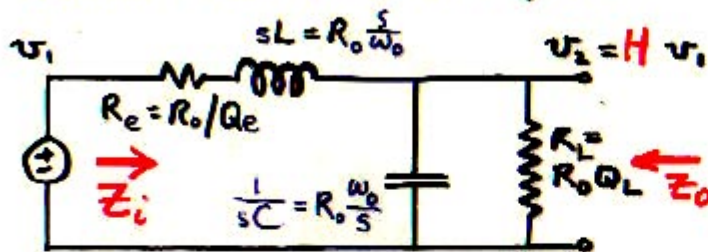

Note:  $R \rightarrow R_e, Q \rightarrow Q_e$

$$\omega_o = \frac{1}{\sqrt{LC}} \quad R_o = \sqrt{\frac{L}{C}}$$

$$Q_e = \frac{R_o}{R_e} \quad Q_L = \frac{R_L}{R_o}$$

$$Z_o = \frac{\frac{Q_L R_o}{1 + Q_L \left(\frac{s}{\omega_o}\right)} \left(\frac{R_o}{Q_e} + R_o \frac{s}{\omega_o}\right)}{\frac{Q_L R_o}{1 + Q_L \left(\frac{s}{\omega_o}\right)} + \frac{R_o}{Q_e} + R_o \frac{s}{\omega_o}} = R_o Q_L \frac{\frac{1}{Q_e} + \frac{s}{\omega_o}}{Q_L + \frac{1}{Q_e} + \left(\frac{Q_L}{Q_e} + 1\right) \left(\frac{s}{\omega_o}\right) + \left(\frac{s}{\omega_o}\right)^2}$$


$$= R_o \cdot \frac{1}{1 + 1/Q_e Q_L} \cdot \frac{\left(\frac{s}{\omega_o}\right) \left(1 + \frac{\omega_o / Q_e}{s}\right)}{1 + \frac{\left(\frac{1}{Q_e} + \frac{1}{Q_L}\right)}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_o}\right) + \frac{1}{1 + 1/Q_e Q_L} \left(\frac{s}{\omega_o}\right)^2}$$

Same three effects as for  $H$ , so for high- $Q$  case

$$Z_o \approx R_o \frac{\left(\frac{s}{\omega_o}\right) \left(1 + \frac{\omega_o / Q_e}{s}\right)}{1 + \frac{1}{Q_L} \left(\frac{s}{\omega_o}\right) + \left(\frac{s}{\omega_o}\right)^2}$$



For high-Q case:

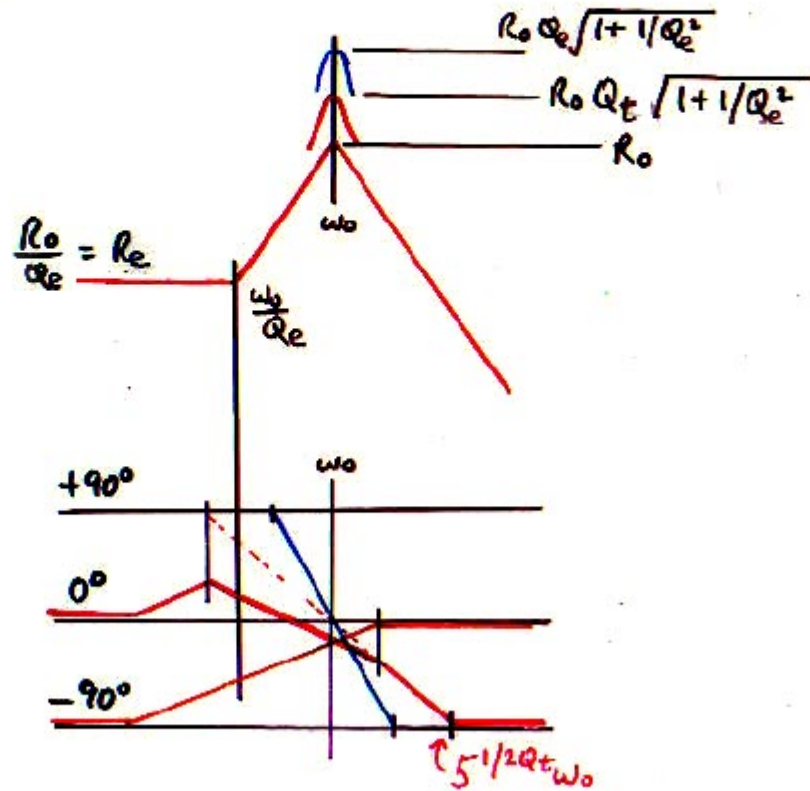



# When an LC filter is loaded, a 4th effect needs to be accounted for:

Result, compared with unloaded case:

second order

- ⇒ 1. Low-freq. asymptote is  $\frac{1}{1+1/Q_e Q_L} = \frac{R_L}{R_L + R_e}$   
(resistive divider)

second order

- ⇒ 2. The corner frequency is changed to  $\sqrt{1+1/Q_e Q_L} \omega_0$


first order

- ⇒ 3. The damping coefficient is changed to  $\frac{\frac{1}{Q_e} + \frac{1}{Q_L}}{\sqrt{1+1/Q_e Q_L}}$

first order

- ⇒ 4. New corner frequencies may appear in some transfer functions

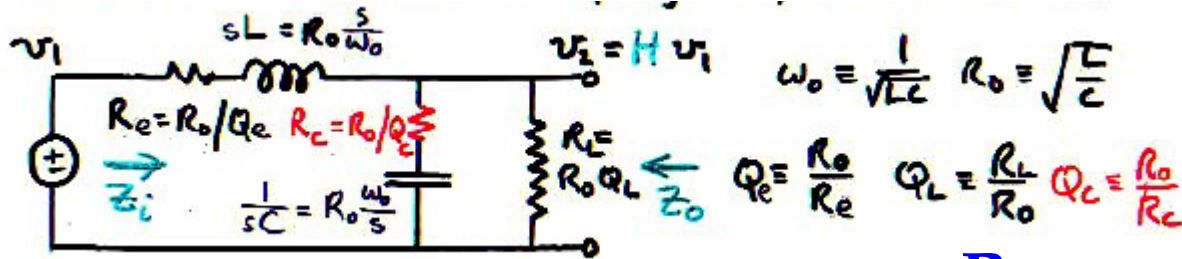A third damping resistance  $R_c$  may be present, representing the capacitor esr:




By analogy with  $Q_e$ , define  $Q_c \equiv \frac{R_0}{R_c}$

The analysis for  $H$ ,  $Z_i$ , and  $Z_o$  could be re-done in the same way.

Instead, let's *build* the result by applying what we already know about the two simpler cases.

The price we are willing to pay, in order to leap-frog directly to the result, is that the second-order effects will be omitted.

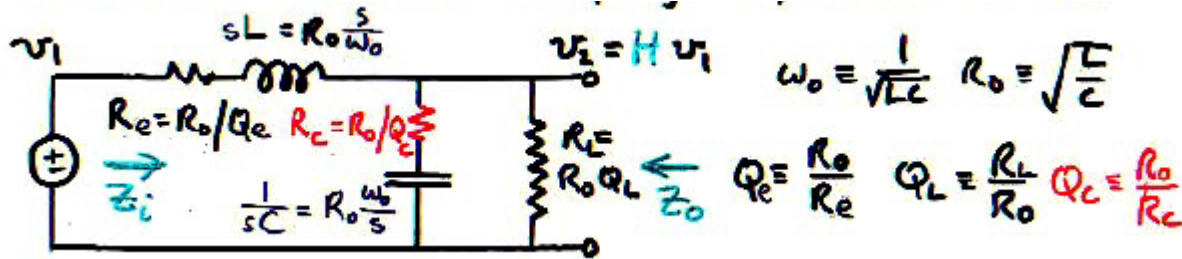
A third damping resistance  $R_c$  may be present, representing the capacitor esr:



One first-order effect of adding a second damping resistance was to lower the total  $Q_t$  to the parallel combination

$$\frac{1}{Q_t} = \frac{1}{Q_e} + \frac{1}{Q_L}$$

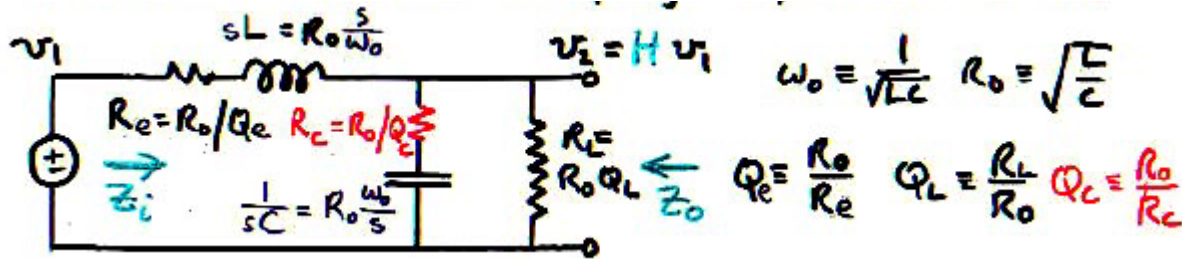A third damping resistance  $R_c$  may be present, representing the capacitor esr:



A good guess would be that adding a third damping resistance would lower the total  $Q_t$  to the triple parallel combination


$$\frac{1}{Q_t} = \frac{1}{Q_e} + \frac{1}{Q_L} + \frac{1}{Q_c}$$

**Another possible first-order effect of adding a third damping resistance is the appearance of additional corner frequencies.**

**A mental frequency sweep can be used to verify an analytical result, but it can also be used "in reverse" to expose new corner frequencies.**

**The strategy is to determine whether or not the addition of the third damping resistance changes the asymptote slope as frequency approaches either zero or infinity.**

For the voltage transfer function H:

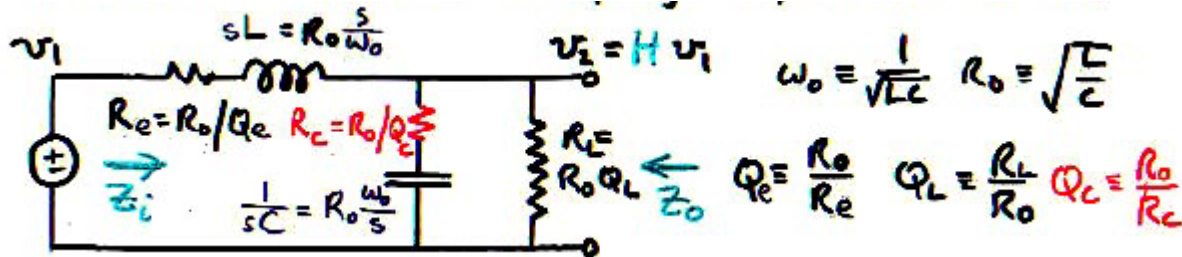


$\omega \rightarrow 0$ : no change of slope, so no new inverted pole or zero;

$\omega \rightarrow \infty$ : a concave upwards corner appears, so there is a new normal zero.

Further, the value of the corner is where  $1/\omega C = R_c$ , which is  $1/RC = Q_c \omega_o$ .
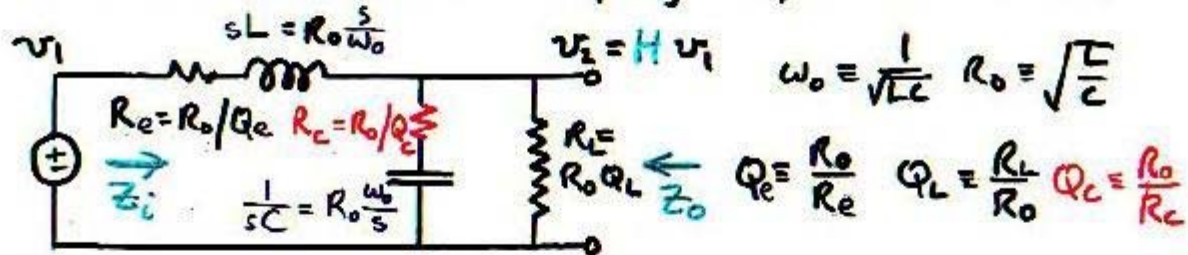
## Assembled results:

Consider additional damping: Capacitor est  $R_c$



For the high- $Q$  case, the previous results can be extended by inspection:

$$H = \frac{1 + \frac{1}{Q_c} \left( \frac{s}{\omega_0} \right)}{1 + \frac{1}{Q_t} \left( \frac{s}{\omega_0} \right) + \left( \frac{s}{\omega_0} \right)^2}$$


$\leftarrow 1 + sR_c C$

**triple parallel combination:**

$$\frac{1}{Q_t} = \frac{1}{Q_e} + \frac{1}{Q_L} + \frac{1}{Q_c}$$



## Assembled results:

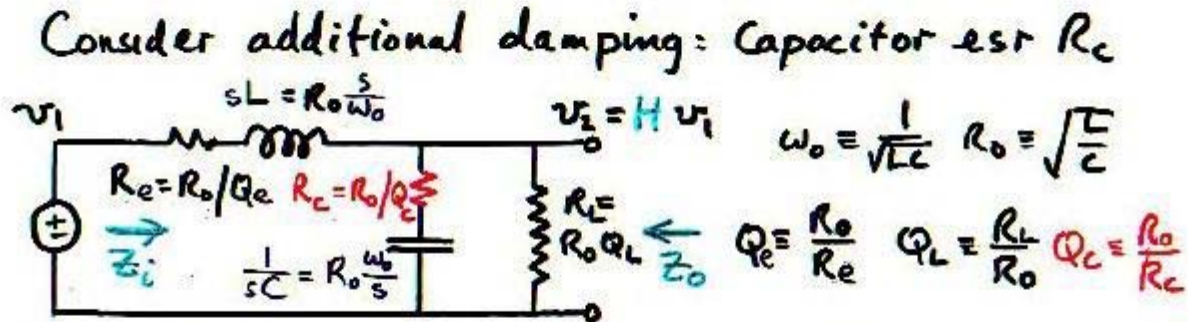

For the high- $Q$  case, the previous results can be extended by inspection:

$$H = \frac{1 + \frac{1}{Q_c} \left( \frac{s}{\omega_0} \right)}{1 + \frac{1}{Q_t} \left( \frac{s}{\omega_0} \right) + \left( \frac{s}{\omega_0} \right)^2}$$

$\leftarrow 1 + sR_cC$

**triple parallel combination:**



$$\frac{1}{Q_t} = \frac{1}{Q_e} + \frac{1}{Q_L} + \frac{1}{Q_c}$$

A similar process leads to the assembled result for  $Z_i$ :

$$Z_i = R_0 \frac{1 + \frac{1}{Q_t} \left( \frac{s}{\omega_0} \right) + \left( \frac{s}{\omega_0} \right)^2}{\left( \frac{s}{\omega_0} \right) \left( 1 + \frac{\omega_0 / Q_L}{s} \right)}$$

**(No new corners)**



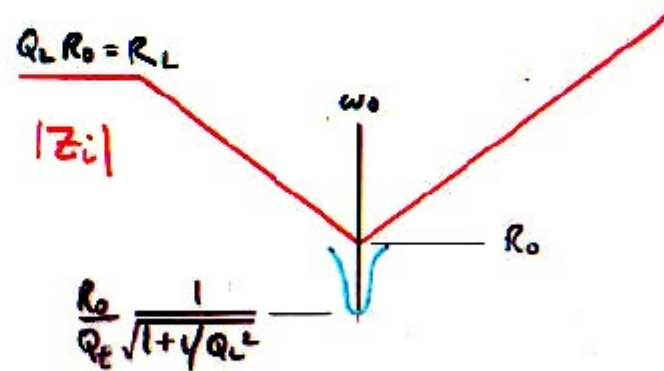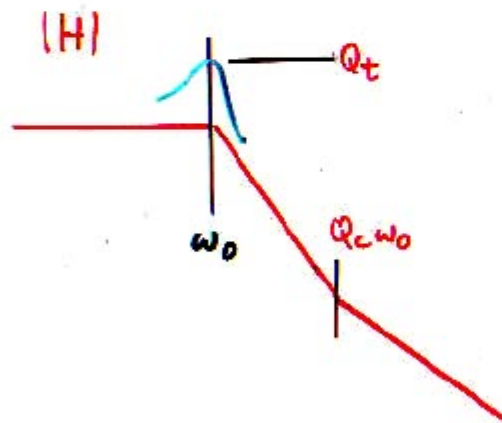

Principle for extension of results to a more complicated case:

1. Determine the new total  $Q_t$ .
2. Add any additional pole or zero factors  
(Is there any change in the  $\omega \rightarrow 0$   
or  $\omega \rightarrow \infty$  asymptotes?)

Exercise:


Obtain the corresponding results for  $Z_0$ .

Exercise solution:

$$Z_o = R_o \frac{\left(\frac{s}{\omega_o}\right) \left(1 + \frac{\omega_o/Q_c}{s}\right) \left(1 + \frac{1}{Q_c} \frac{s}{\omega_o}\right)}{1 + \frac{1}{Q_c} \left(\frac{s}{\omega_o}\right) + \left(\frac{s}{\omega_o}\right)^2}$$

Check high-frequency limit:
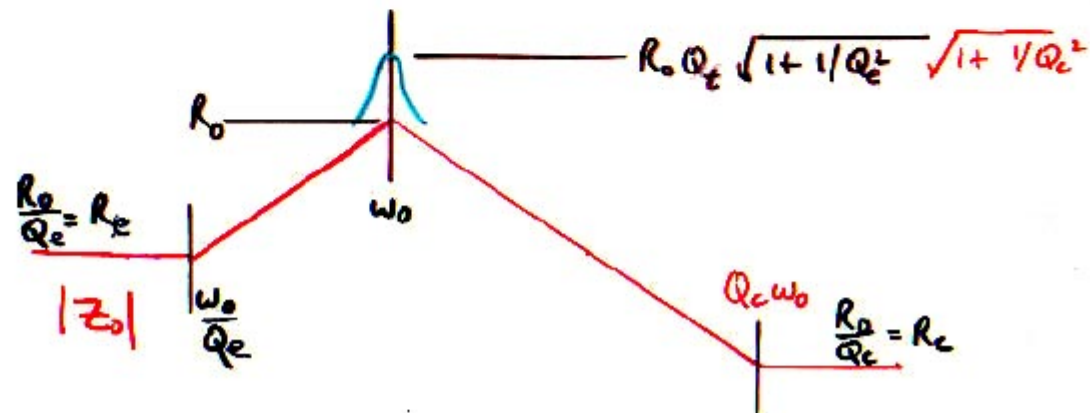
$$Z_o \xrightarrow{\omega \rightarrow \infty} \frac{R_o}{Q_c} = R_c$$



The key step is now to determine T12 and T22 from the small signal model for the condition  $\hat{v}_i = 0$ :

$$T_{12} = \left[ \frac{VO \times (RL - D^2 \times N^2 \times Z) \times (1 + sC \times RC)}{D \times N \times \Delta} \right] \quad [15]$$

$$T_{22} = \left[ \frac{VO \times (RL - D^2 \times N^2 \times Z) \times (1 + sC \times RL)}{D \times N \times RL \times \Delta} \right] \quad [16]$$

where  $(sL_1 + R_{L1})(sC_1 R_{C1} + 1)$

$$Z = \left[ \frac{(s^2 L_1 \times C_1 \times RC_1) + (sC_1 \times RC_1 \times RL_1) + sL_1 + RL_1}{(s^2 L_1 \times C_1) + sC_1 \times (RL_1 + RC_1) + 1} \right] \quad [17]$$

$$\Delta = [a_1 + (D^2 \times N^2 \times Z) \times (1 + sC \times RL)] \quad [18]$$

$$a_1 = \left[ (s^2 L \times C \times RL) + sC \times RL \times (RI + RC + \frac{L}{C \times RL}) + RL \right] \quad [19]$$

At the resonant frequency of the input filter, the impedance Z will attain a very high value, limited only by the series resistances RL1 and RC1. The peaking in the value of Z will affect both the numerators and denominators of the transfer functions T12 and T22, as shown in equations 15 and 16. The net effect will be a reduction in the loop gain  $G_T$  and a corresponding phase margin reduction.

