


EXAMPLE


16. A DESIGN SOLUTION TO DARLINGTON FOLLOWER INSTABILITY

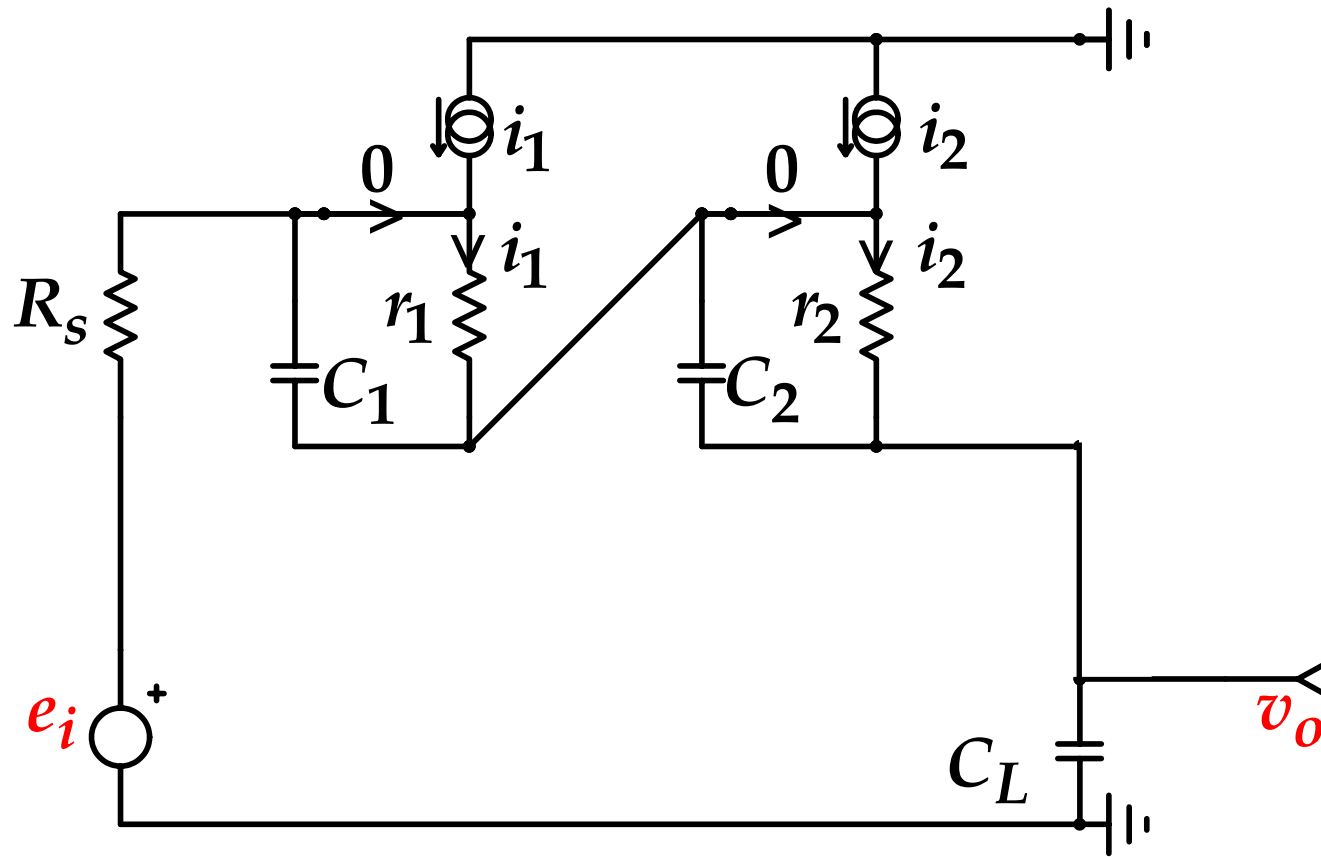
Example 3: Darlington Emitter/Source Follower

The Darlington Follower is known to be unstable for certain values of load capacitance.

The Design Problem is to select a damping resistance so that the Follower is not only stable, but has a maximum peaking , regardless of the load capacitance.




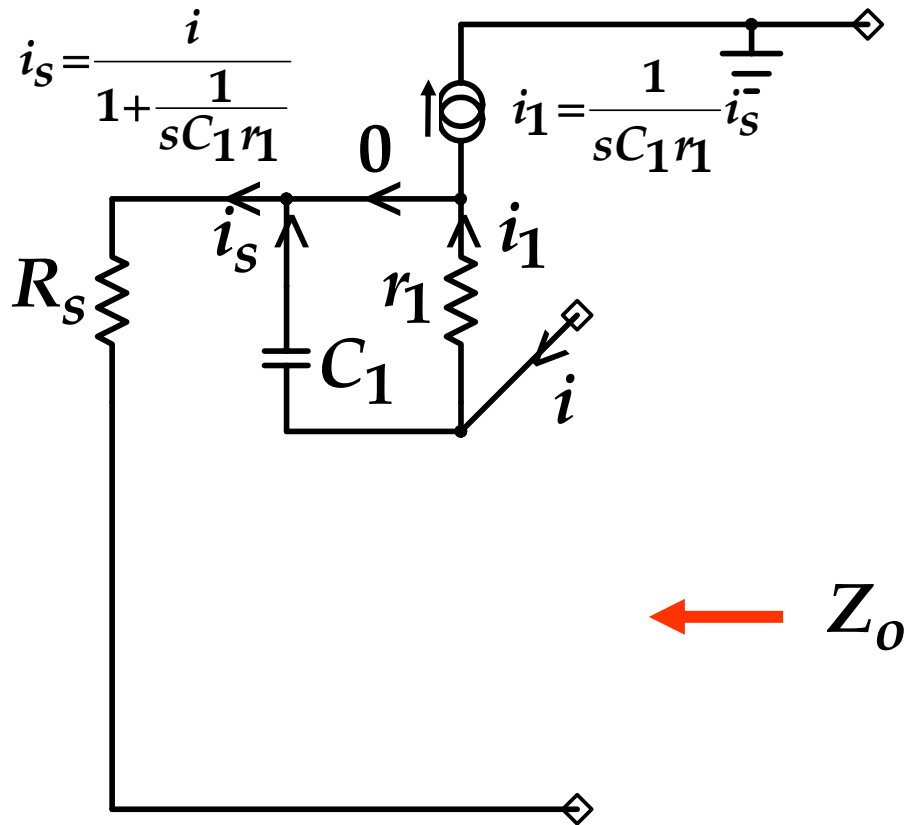

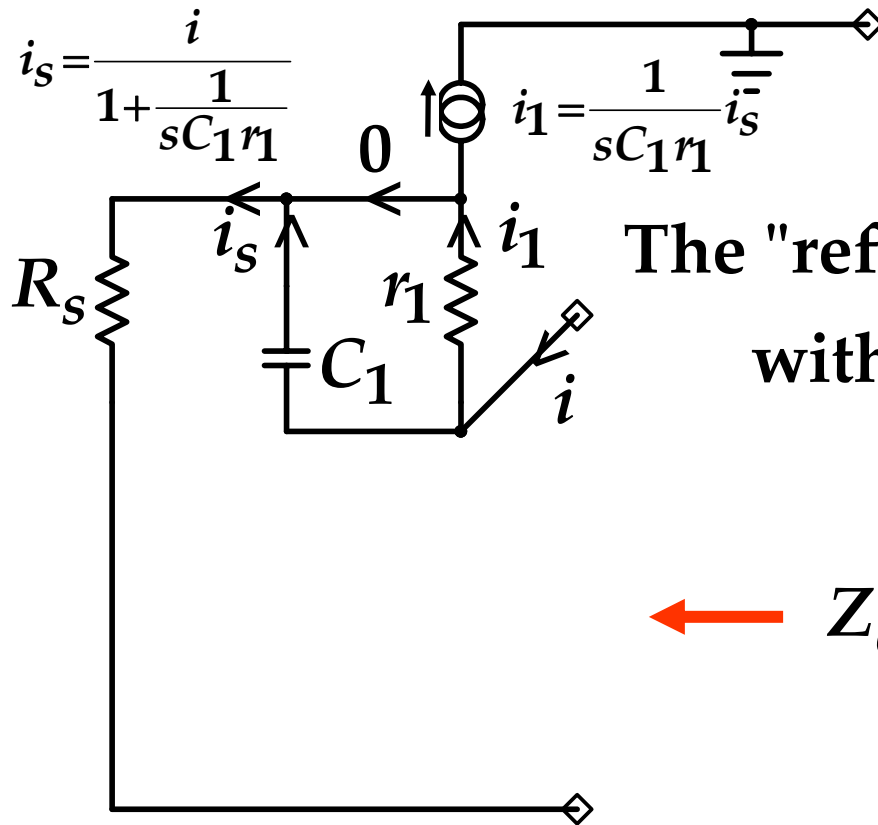

The "reflection" process works with effective $\beta_1 = \frac{1}{sC_1 r_1}$:
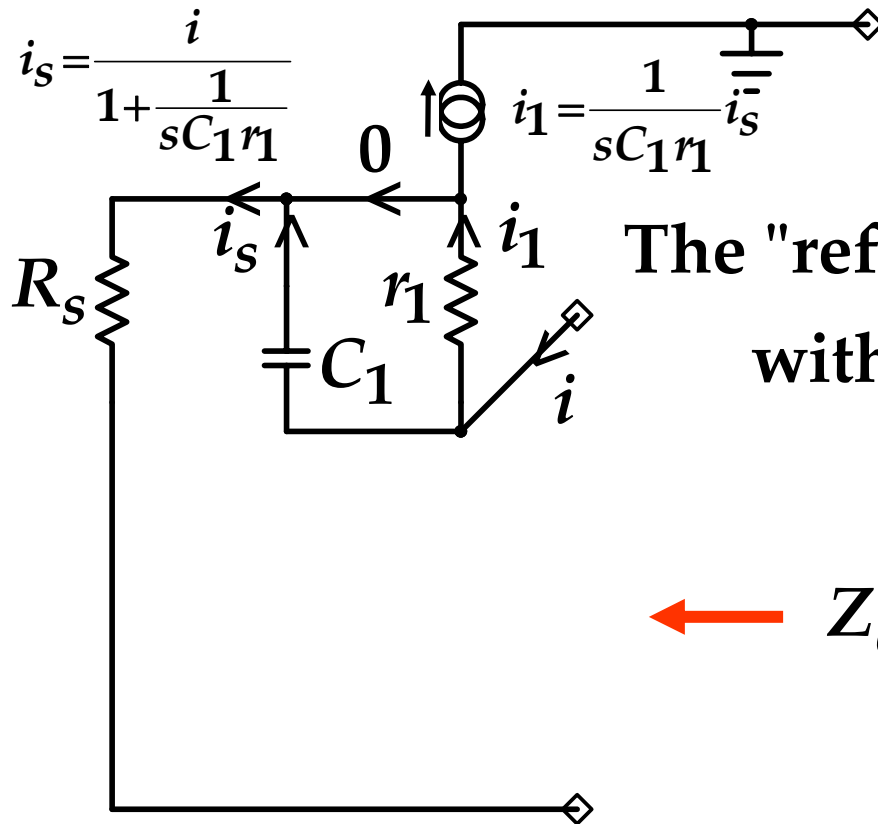
$$\leftarrow Z_o = \frac{R_s}{1 + \beta_1} + r_1 \parallel \frac{1}{sC_1}$$





The "reflection" process works with effective $\beta_1 = \frac{1}{sC_1 r_1}$:

$$\leftarrow Z_o = \frac{R_s}{1 + \beta_1} + r_1 \parallel \frac{1}{sC_1}$$

$$Z_o = \frac{R_s + \frac{1}{sC_1}}{1 + \frac{1}{sC_1 r_1}} = \frac{R_s (r_1 + sC_1 R_s r_1)}{R_s + sC_1 R_s r_1} = \frac{R_s (r_1 + sL)}{R_s + sL}$$

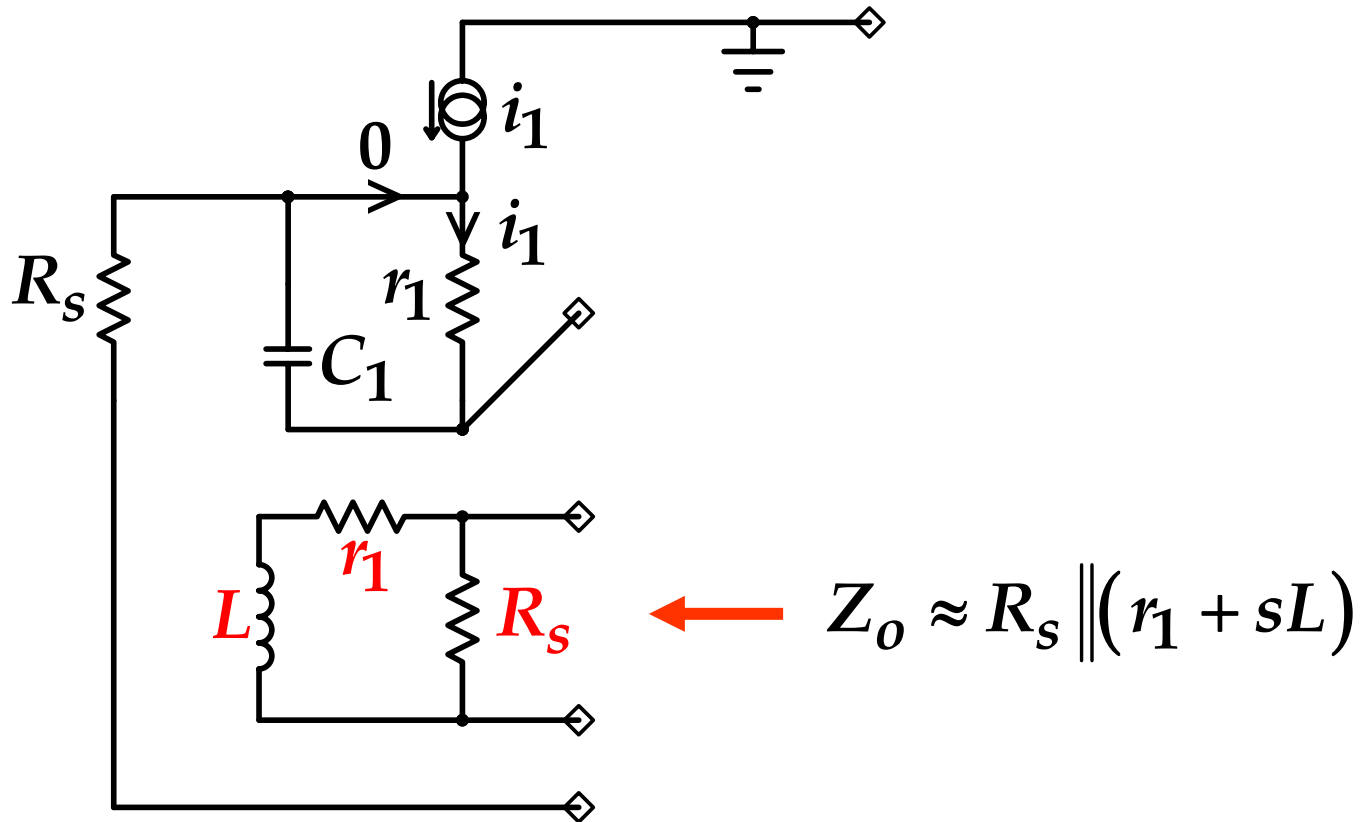where $L \equiv C_1 R_s r_1$. If $R_s \gg r_1$, $Z_o \approx R_s \parallel (r_1 + sL)$




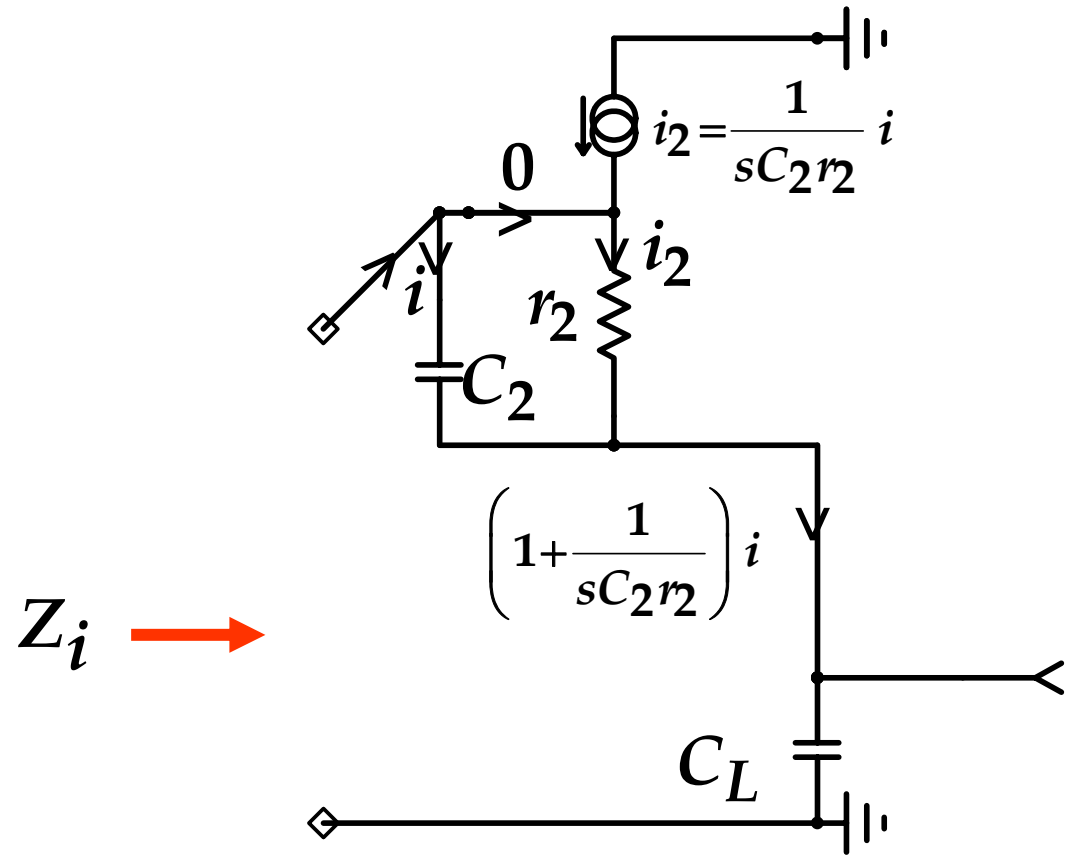

The "reflection" process works

with effective $\beta_2 = \frac{1}{sC_2 r_2}$:

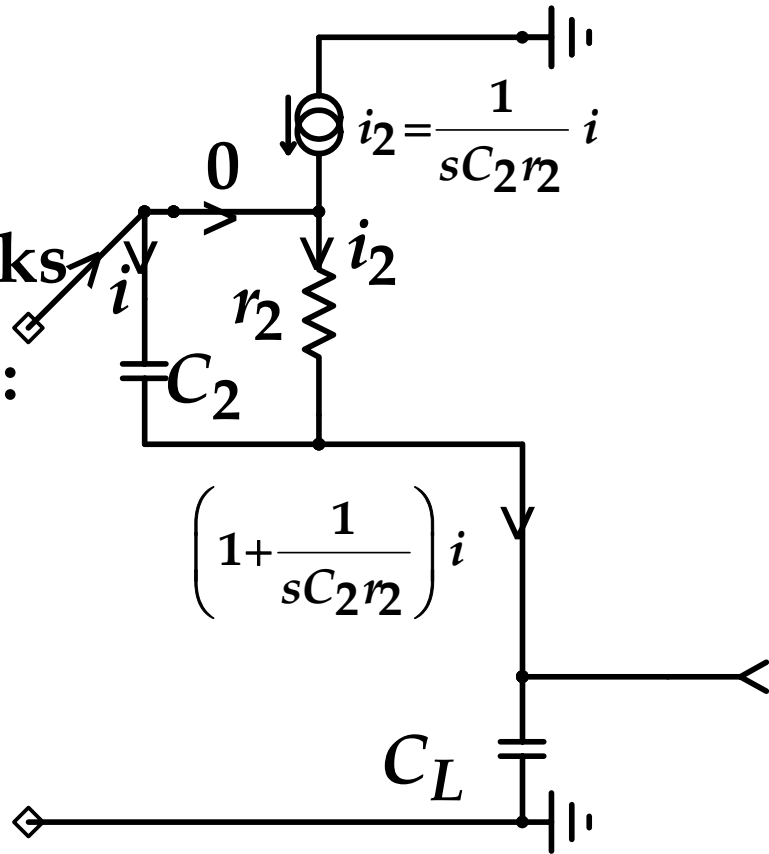
$$Z_i = \frac{1}{sC_2} + \frac{1 + \beta_2}{sC_L} \rightarrow$$



The "reflection" process works

with effective $\beta_2 = \frac{1}{sC_2 r_2}$:

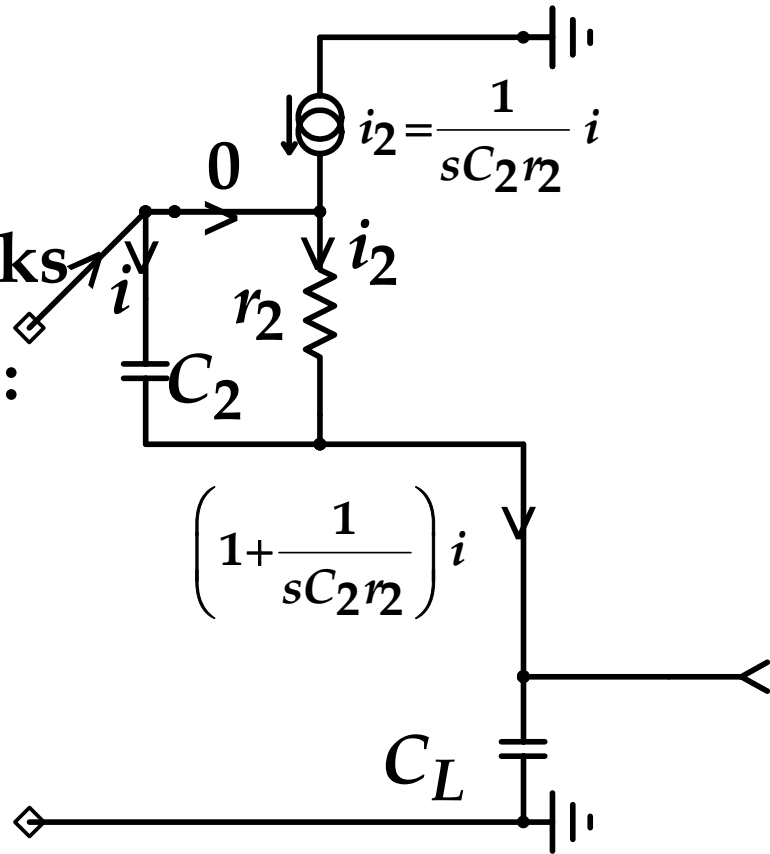
$$Z_i = \frac{1}{sC_2} + \frac{1 + \beta_2}{sC_L} \quad \rightarrow$$




$$Z_i = \frac{1}{sC_2} + \frac{1}{sC_L} \left(1 + \frac{1}{sC_2 r_2} \right) = \frac{1}{sC} - R_{neg}$$


where $\frac{1}{C} \equiv \frac{1}{C_2} + \frac{1}{C_L}$ and $R_{neg} \equiv \frac{1}{\omega^2 C_2 r_2 C_L}$

$$Z_i = \frac{1}{sC} - R_{neg}$$

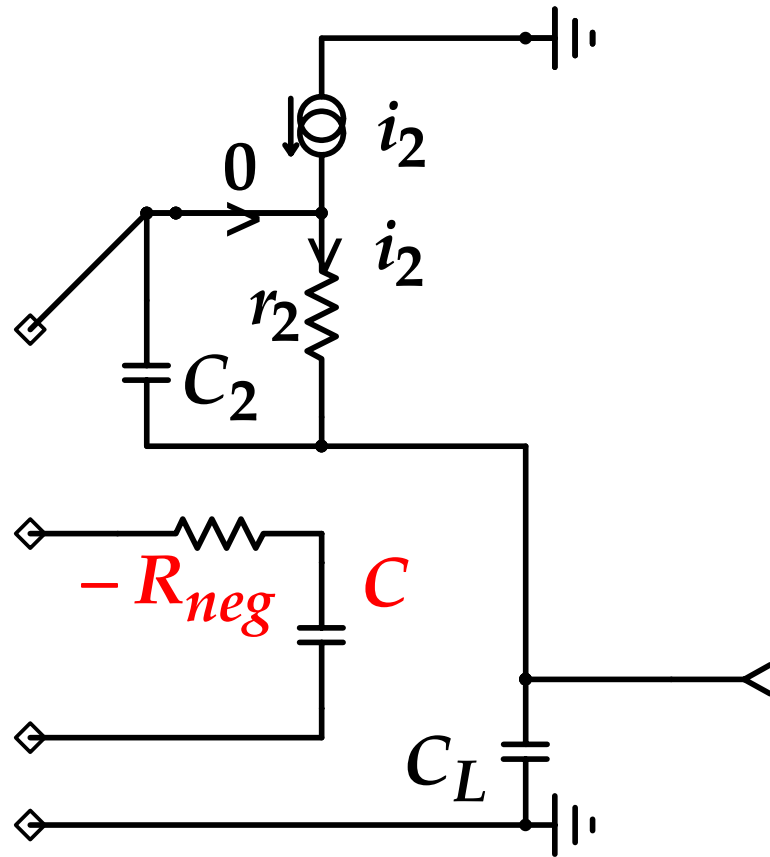

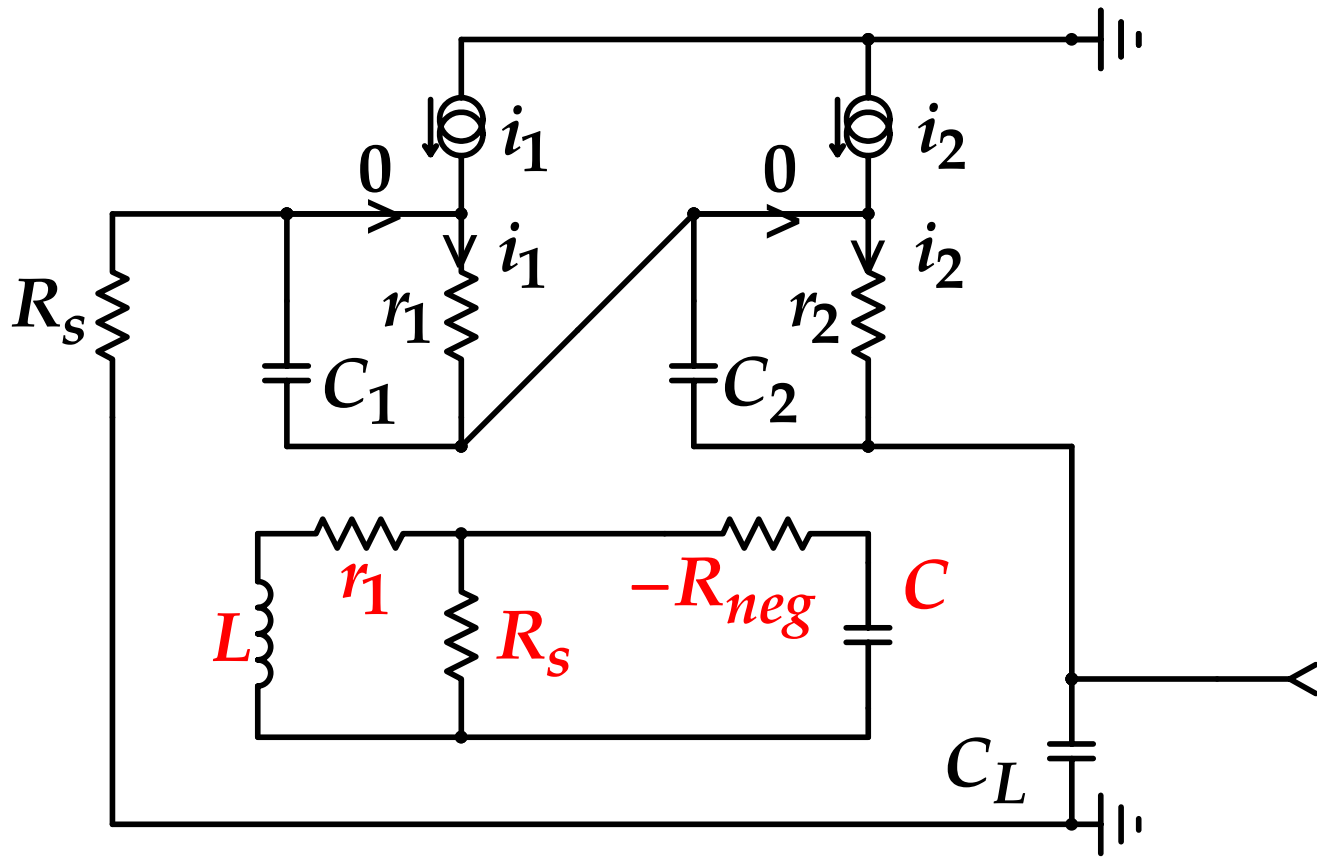

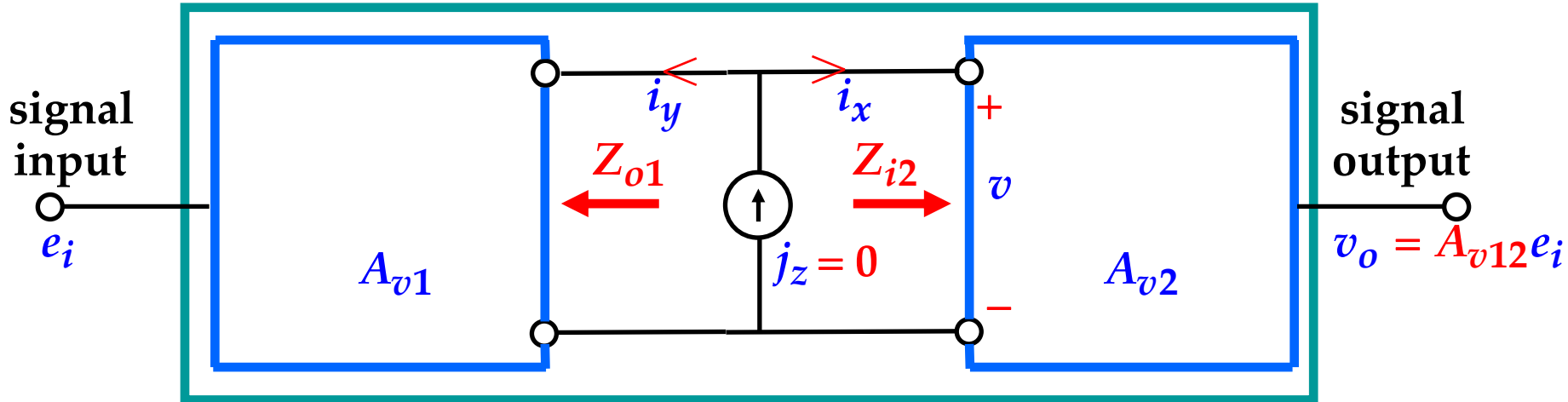A detailed analysis can be done with the DT/CT





The gain $A_{v12} \equiv \frac{v_o}{e_i}$ is given by the DT:

$$A_{v12} = A_{v12}^{i_y} \frac{1 + \frac{1}{T_{ni}}}{1 + \frac{1}{T_i}}$$

The null return ratio $T_{ni} \equiv i_y/i_x \Big|_{v_o=0}$ is an ndi calculation with the output v_o nulled. If v_o is nulled, so is i_x , so $T_{ni} = \infty$.

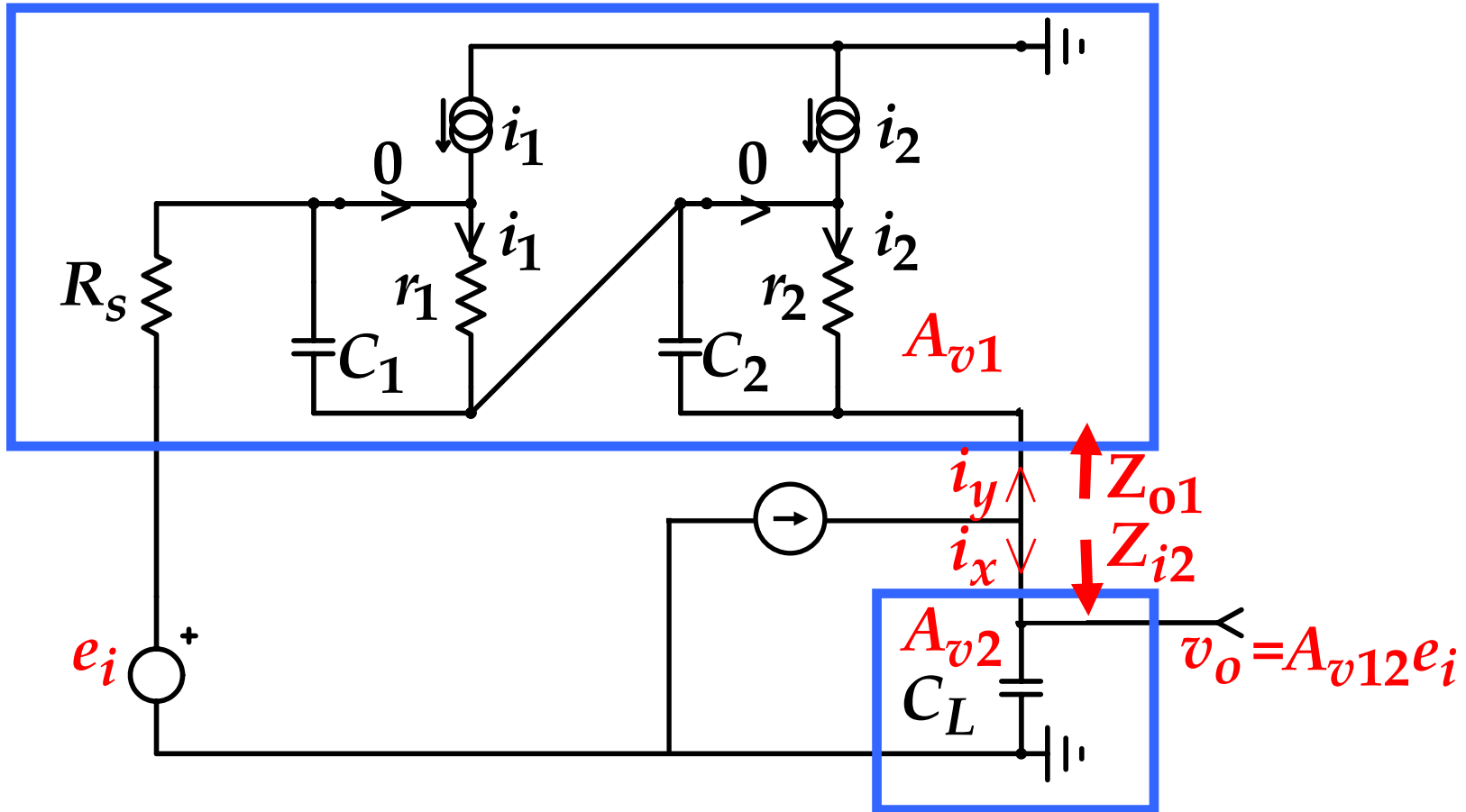This implies that T_{ni} is infinite unless the signal can bypass the injection point.



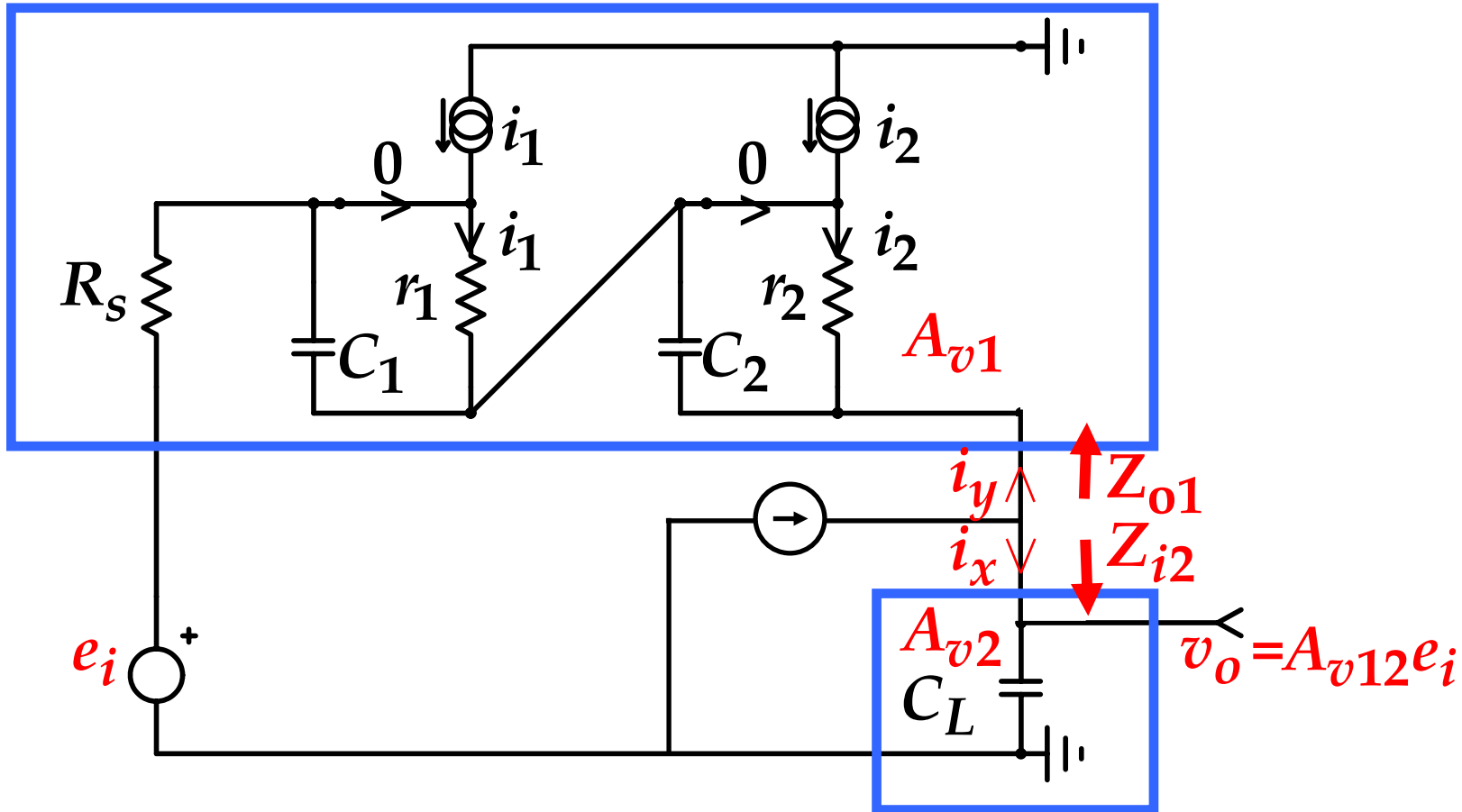


Nulled i_y means that the A_{v1} box is unloaded, so the input voltage to the A_{v2} box is the open-circuit (oc) output voltage of the A_{v1} box. Thus

$$A_{v12}^{i_y} = A_{v1}^{oc} A_{v2}$$

$$\text{Also, } T_i = Z_{i2} / Z_{o1},$$

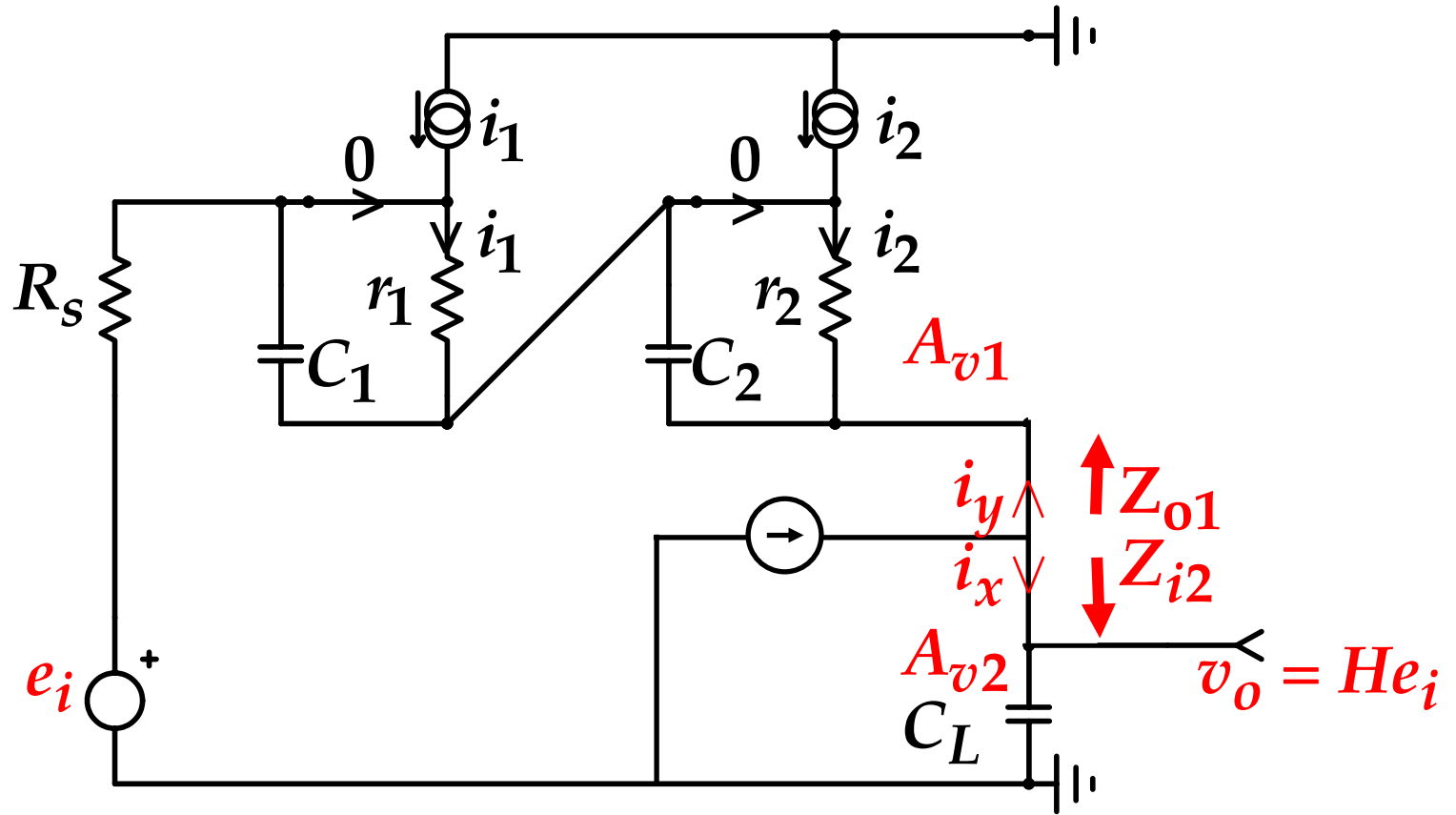v.0.1 3/07 so the DT becomes $A_{v12}^{i_y} = A_{v1}^{oc} A_{v2} \frac{1}{1 + \frac{Z_{o1}}{Z_{i2}}}$



$$A_{v1}^{OC} = 1, \quad A_{v2} = 1, \quad \text{so}$$

$$H = A_{v12} = \frac{1}{1 + \frac{1}{T}} = D \quad \text{where } T = T_i = \frac{Z_{i2}}{Z_{o1}}$$

We can figure out a lot about T before doing a simulation.

Z_{o1} has two poles, because it has two capacitances.


By "mental frequency sweep,"

$$Z_{o1}(0) = r_2, \quad Z_{o1}(\infty) = R_s$$

Since Z_{o1} is flat at zero and infinite frequency, Z_{o1} must have two zeros as well as two poles.

Also, $Z_{i2} = \frac{1}{sC_L}$

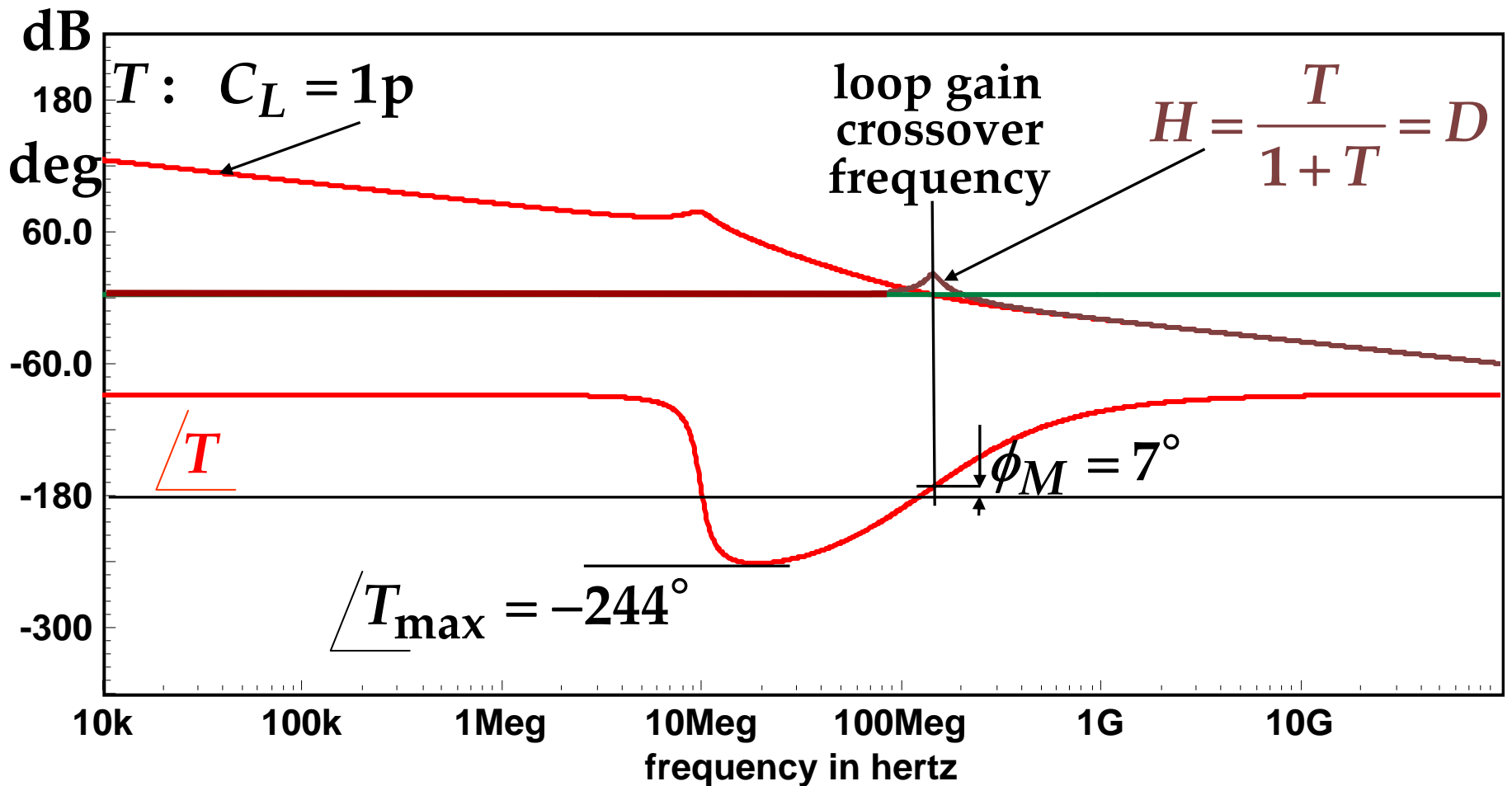Therefore, $T = \frac{Z_{i2}}{Z_{o1}}$ has three poles and two zeros.




The phase margin ϕ_M is positive, so the Follower is stable. However, ϕ_M is small, so H has a large peak.


For design, C_L is to be considered a variable.

Examine the effect of C_L upon $T = 1/sC_L Z_{o1}$.

Since C_L is not inside Z_{o1} , increasing C_L does not change the shape of either $|T|$ or $\angle T$; $|T|$ decreases in inverse proportion to C_L , but $\angle T$ does not change at all.


The decrease of $|T|$ results in lowered loop gain crossover frequency:

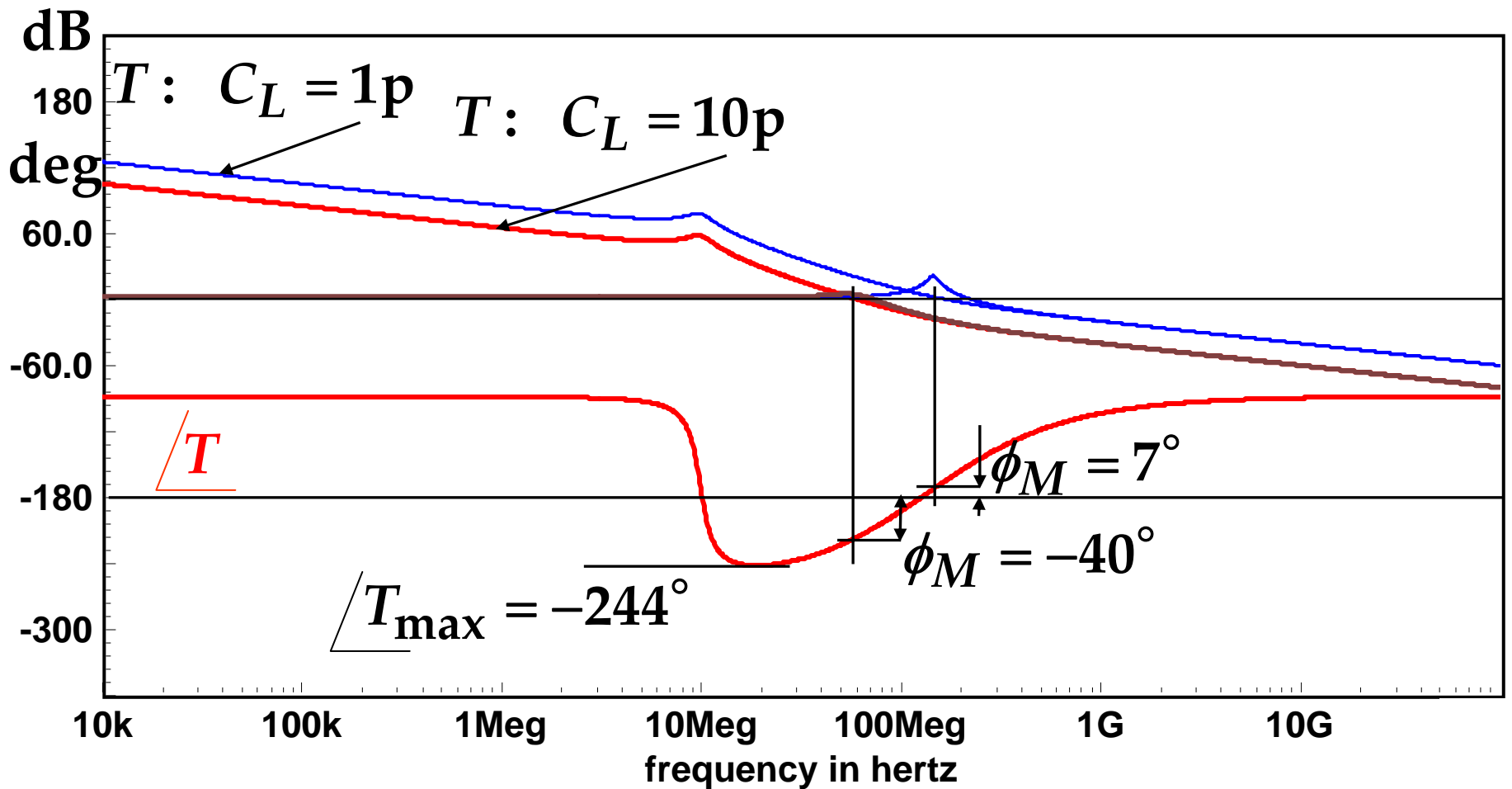

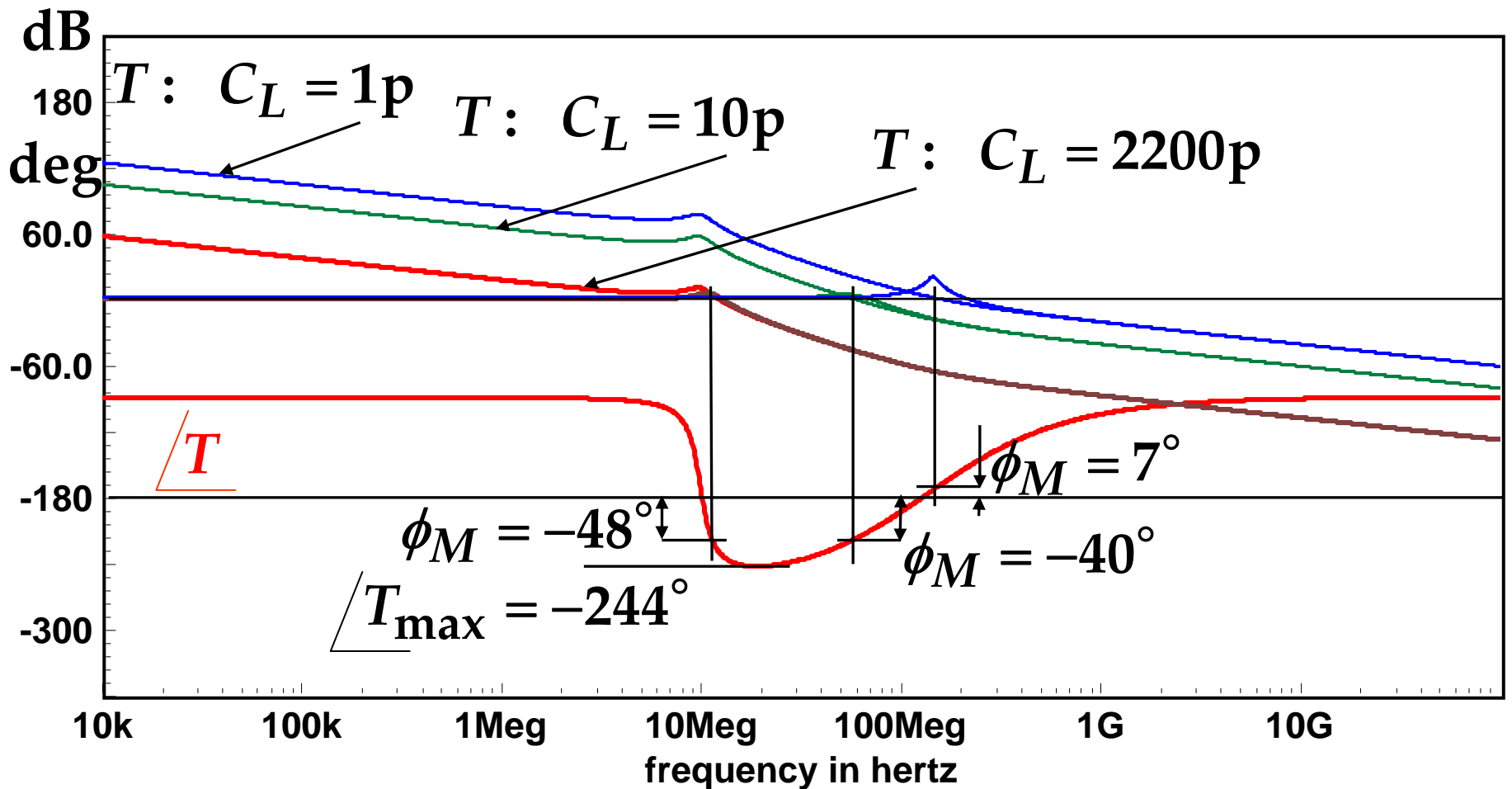


There is a range of C_L for which the phase margin ϕ_M is negative, and the Follower is unstable.

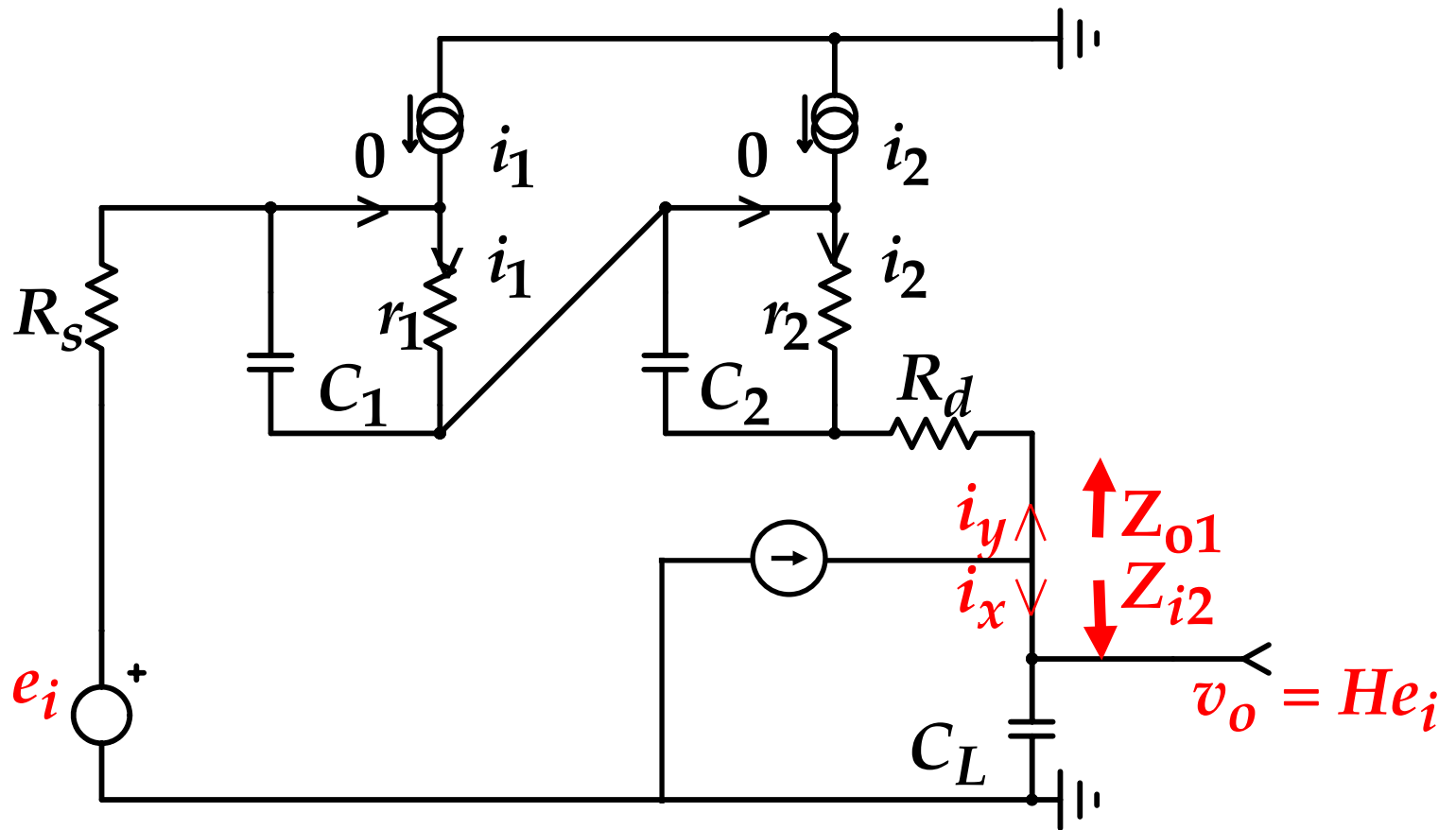
A design strategy is to add sufficient damping resistance R_d to Z_{o1} so that the maximum phase lag is less than 180° by some desired phase margin.




Damping resistance R_d added

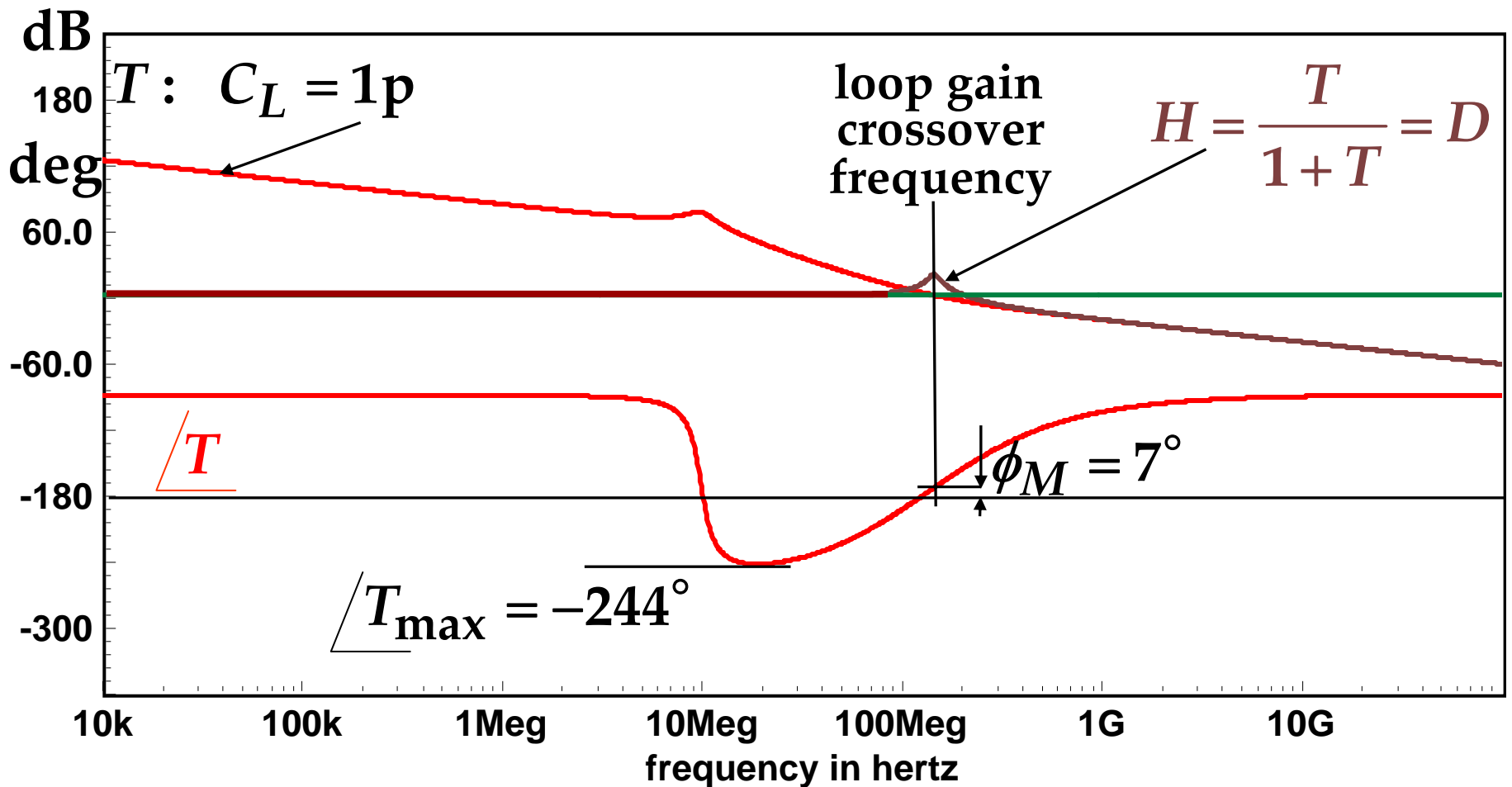

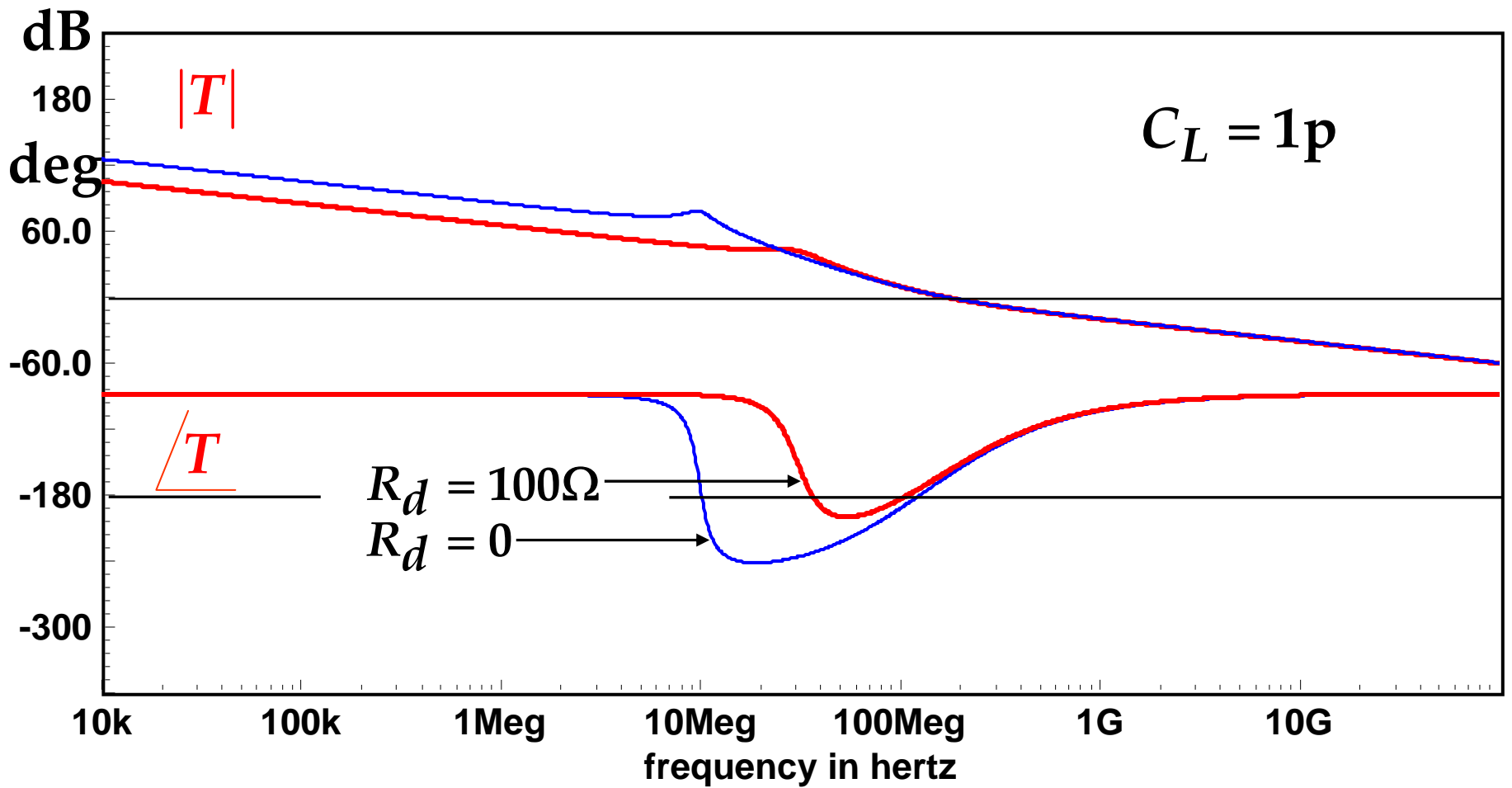
The phase margin ϕ_M is positive, so the Follower is stable. However, ϕ_M is small, so H has a large peak.



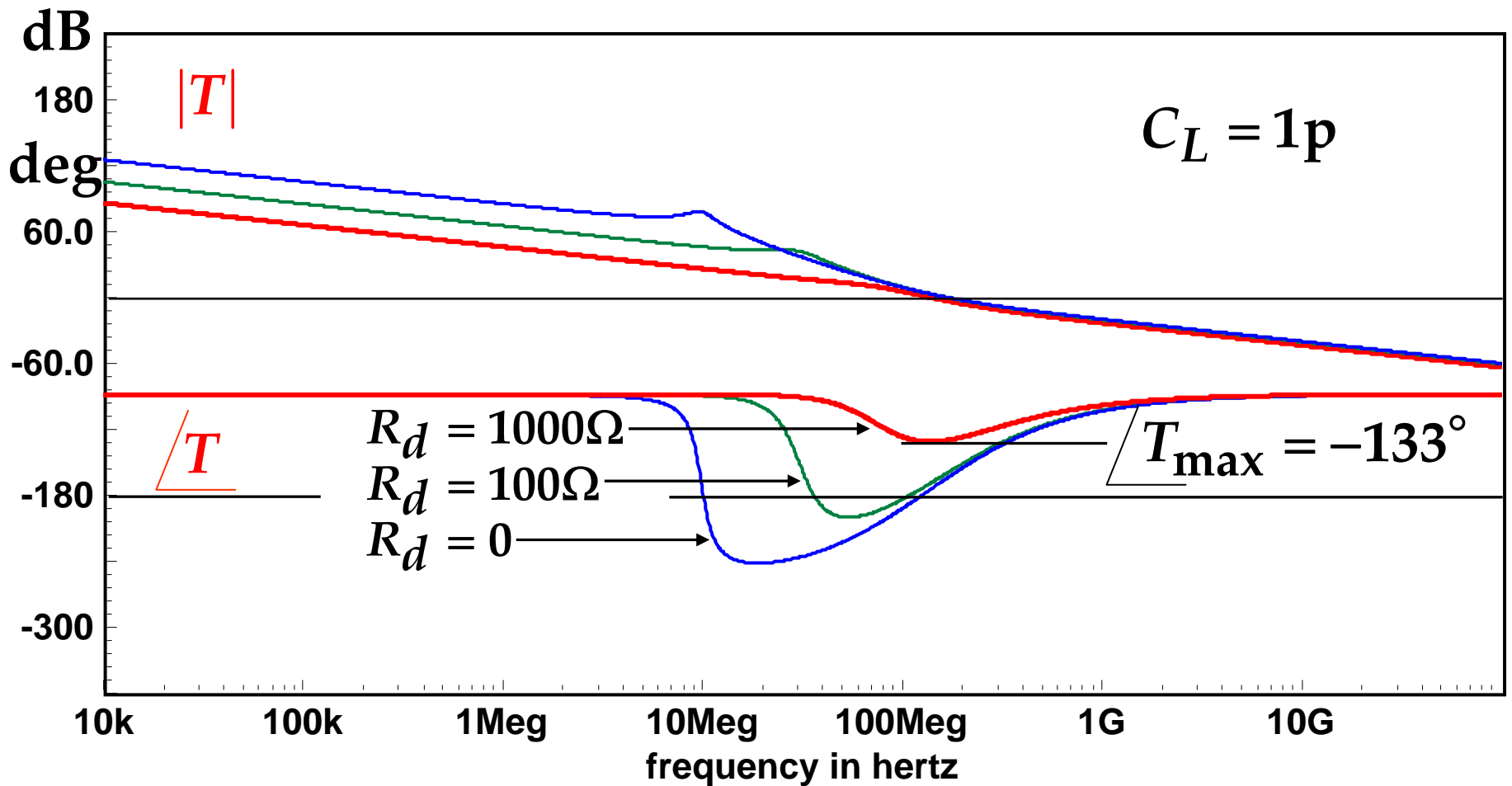

The worst-case phase margin thus occurs when C_L is such that the $|T|$ crossover frequency f_c is at the

frequency where $\angle T$ is maximum:

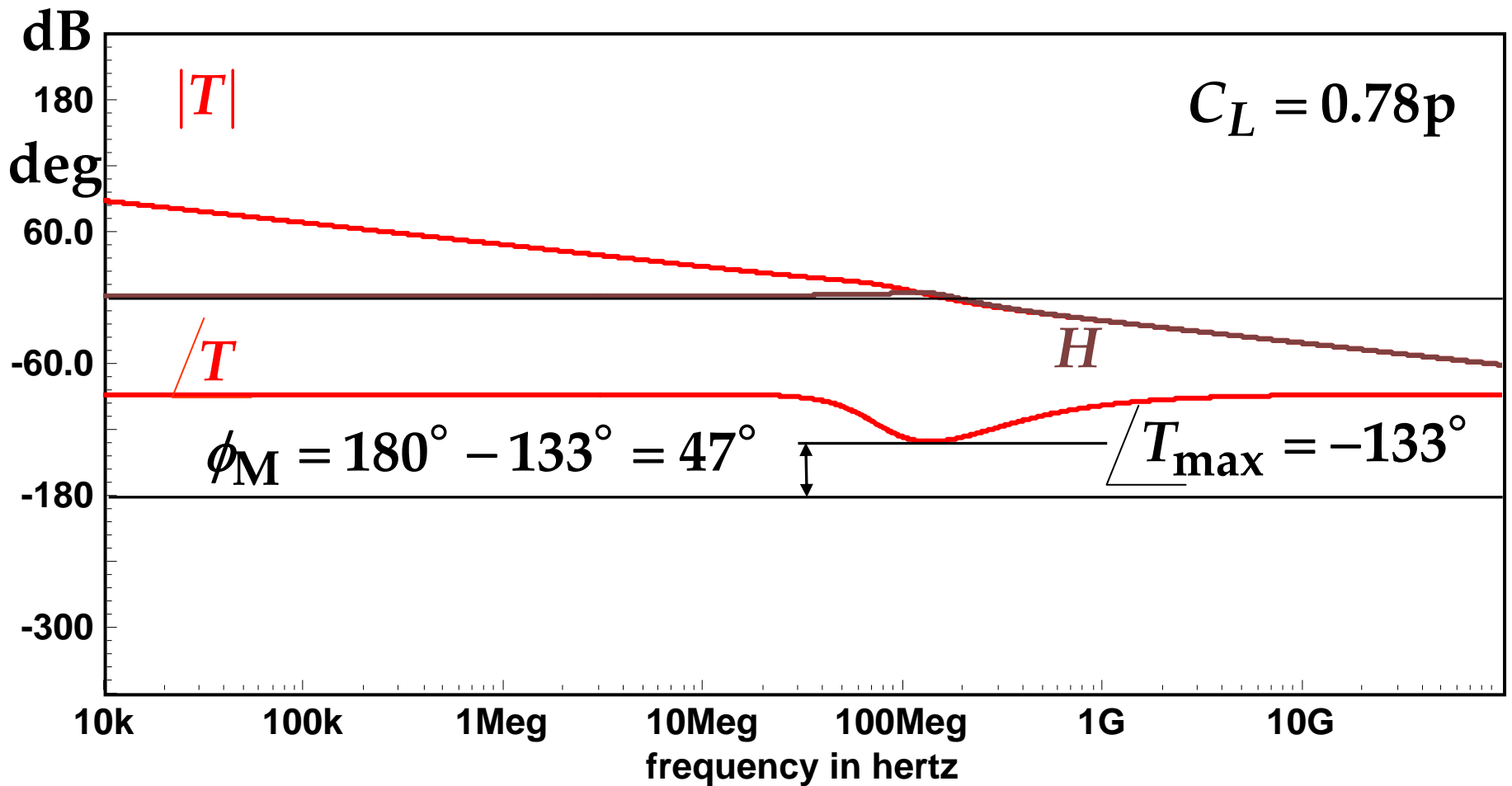

Worst-case $\phi_M = 47^\circ$, and consequent greatest peaking in H , occurs for $C_L = 0.78\text{p}$.

Expanded scale:

