

EXAMPLE

17. THE INPUT FILTER PROBLEM OF A SWITCHED-MODE REGULATOR

A different application of the EET is useful in design of the input filter for a switching regulator.

"The Input Filter Problem" was discussed in a 1976 paper:

R.D.Middlebrook, "Input Filter Considerations in Design and Application of Switching Regulators," IEEE Industry Applications Society Annual Meeting, 1976 Record, pp. 366 - 382.

Problem:

How to design an input filter for a switched-mode regulator without significantly disturbing its properties.

Conclusion:

The output impedance Z_s of the input filter should be much less than certain line input impedances of the regulator.


The design-oriented inequalities can easily be established by use of the Extra Element Theorem.

Objective

To find conditions on the input filter so that properties of the regulator are unaffected.

Approach

Use the Extra Element Theorem (EET)

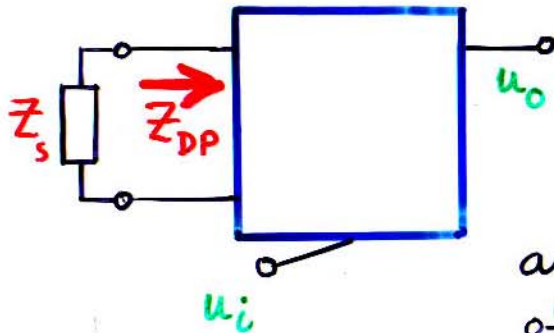

$$\frac{u_o}{u_i} = \frac{u_o}{u_i} \Big|_{z_s=0} \cdot \frac{1 + \frac{z_s}{z_n}}{1 + \frac{z_s}{z_d}}$$

any transfer function of a linear system, e.g. gain, loop gain, output impedance

same transfer function with $z_s = 0$.


z_n, z_d are dpi's (driving point impedances) seen by a test signal u_t applied in place of z_s :

Objective

To find conditions on the input filter so that properties of the regulator are unaffected.

Approach

Use the Extra Element Theorem (EET)

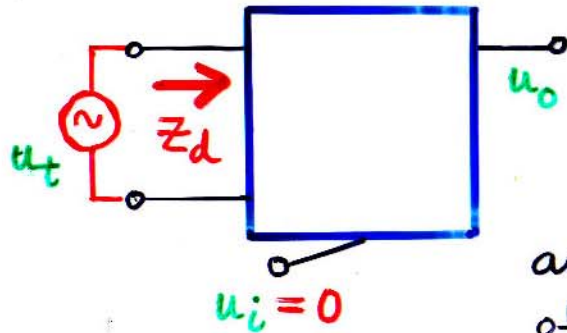

any transfer function of a linear system, e.g. gain, loop gain, output impedance

$$\frac{u_o}{u_i} = \frac{u_o}{u_i} \Big|_{z_s=0} \cdot \frac{1 + \frac{z_s}{z_n}}{1 + \frac{z_s}{z_d}}$$

same transfer function with $z_s = 0$.


$Z_d = Z_{DP}$ seen by u_t with $u_i = 0$ (single injection)

Objective

To find conditions on the input filter so that properties of the regulator are unaffected.

Approach

Use the Extra Element Theorem (EET)

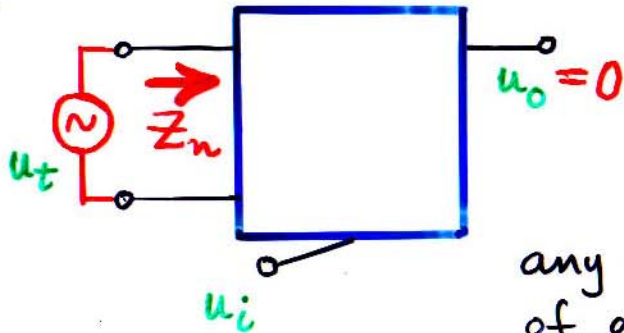

$$\frac{u_o}{u_i} = \frac{u_o}{u_i} \Big|_{z_s=0} \cdot \frac{1 + \frac{z_s}{z_n}}{1 + \frac{z_s}{z_d}}$$

any transfer function of a linear system, e.g. gain, loop gain, output impedance

same transfer function with $z_s = 0$.


$Z_n = Z_{DP}$ seen by u_t in presence of u_i adjusted to make $u_o = 0$
(null double injection)

Objective

To find conditions on the input filter so that properties of the regulator are unaffected.

Approach

Use the Extra Element Theorem (EET)

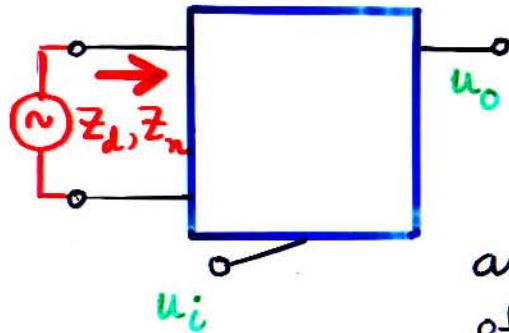

$$\frac{u_o}{u_i} = \frac{u_o}{u_i} \Big|_{z_s=0} \cdot \frac{1 + \frac{z_s}{z_n}}{1 + \frac{z_s}{z_d}}$$

any transfer function of a linear system, e.g. gain, loop gain, output impedance

same transfer function with $z_s = 0$.


Note that, even for a given element z_s , z_n but not z_d are different for different transfer functions of the same system (different u_i 's and u_o 's).

Objective

To find conditions on the input filter so that properties of the regulator are unaffected.

Approach

Use the Extra Element Theorem (EET)

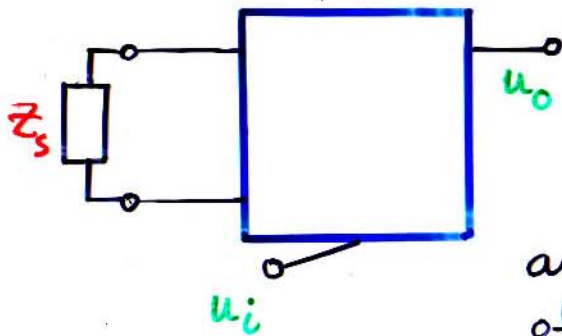

$$\frac{u_o}{u_i} = \frac{u_o}{u_i} \Big|_{z_s=0} \cdot \frac{1 + \frac{z_s}{z_n}}{1 + \frac{z_s}{z_d}}$$

any transfer function of a linear system, e.g. gain, loop gain, output impedance

same transfer function with $z_s = 0$.

Application of the EET to a regulator with input filter:

I identify z_s as the output impedance of the input filter
Hence, the design criteria are:

$z_s \ll z_d, z_n$ corresponding to each property (transfer function) of interest.

The EET for one extra element Z_s is

$$\frac{u_o}{u_i} = \frac{u_o}{u_i} \bigg|_{Z_s=0} \frac{1 + \frac{Z_s}{Z_n}}{1 + \frac{Z_s}{Z_d}}$$

This is the same as the GFT for one injected test signal:


$$H = H_\infty \frac{1 + \frac{1}{T_n}}{1 + \frac{1}{T}} = H_\infty DD_n$$

where $H = \text{loopgain}[\text{with } Z_s]$ and $H_\infty = \text{loopgain}[Z_s = 0]$.

Z_d and Z_n can be found from T and T_n by test voltage

e_z injection at a source resistance $Z_s = R_s = 1\Omega$. Then,


$$Z_d = T \text{ and } Z_n = T_n$$

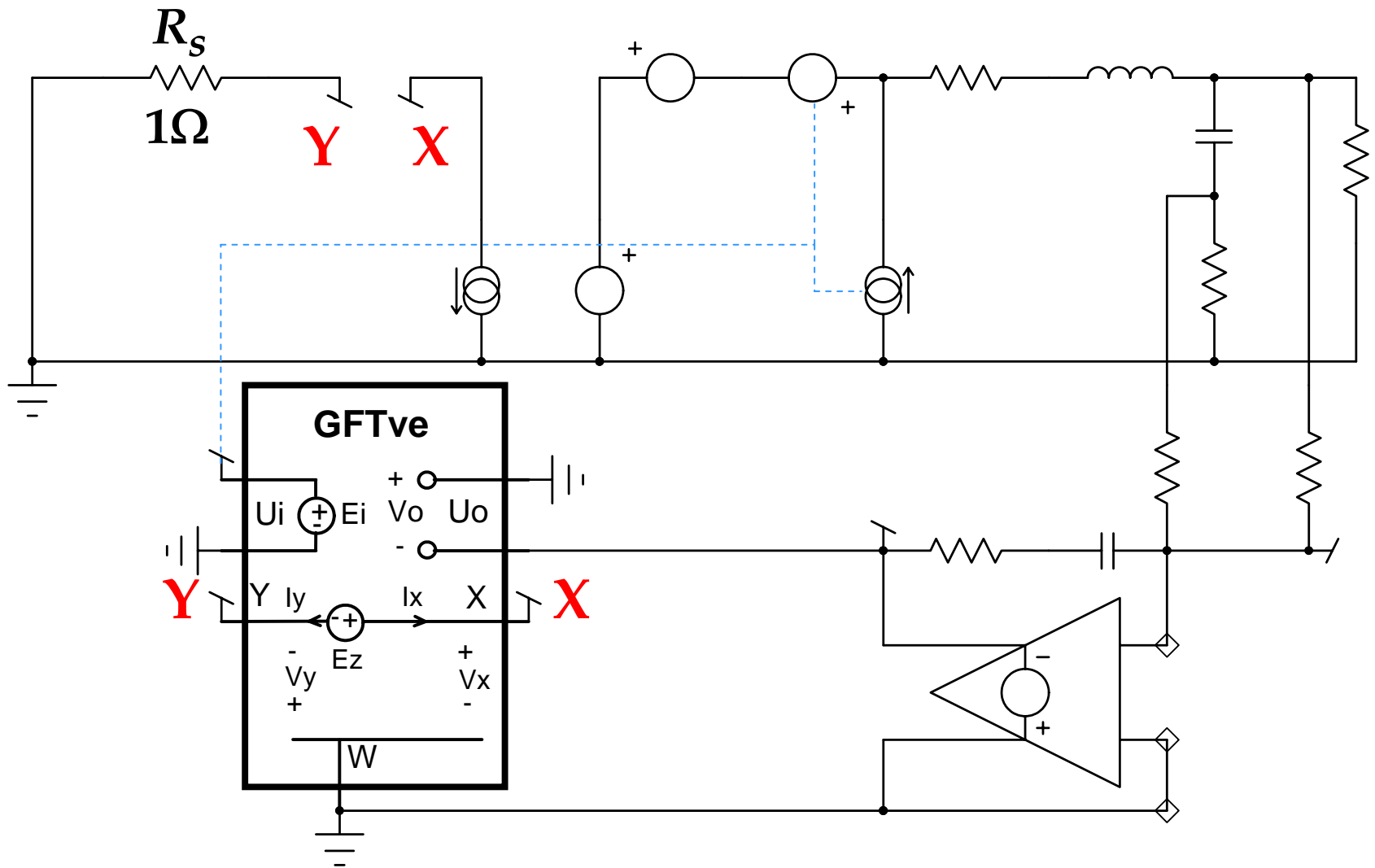


Values as in 1976 Paper Fig. 13

v.0.1 3/07
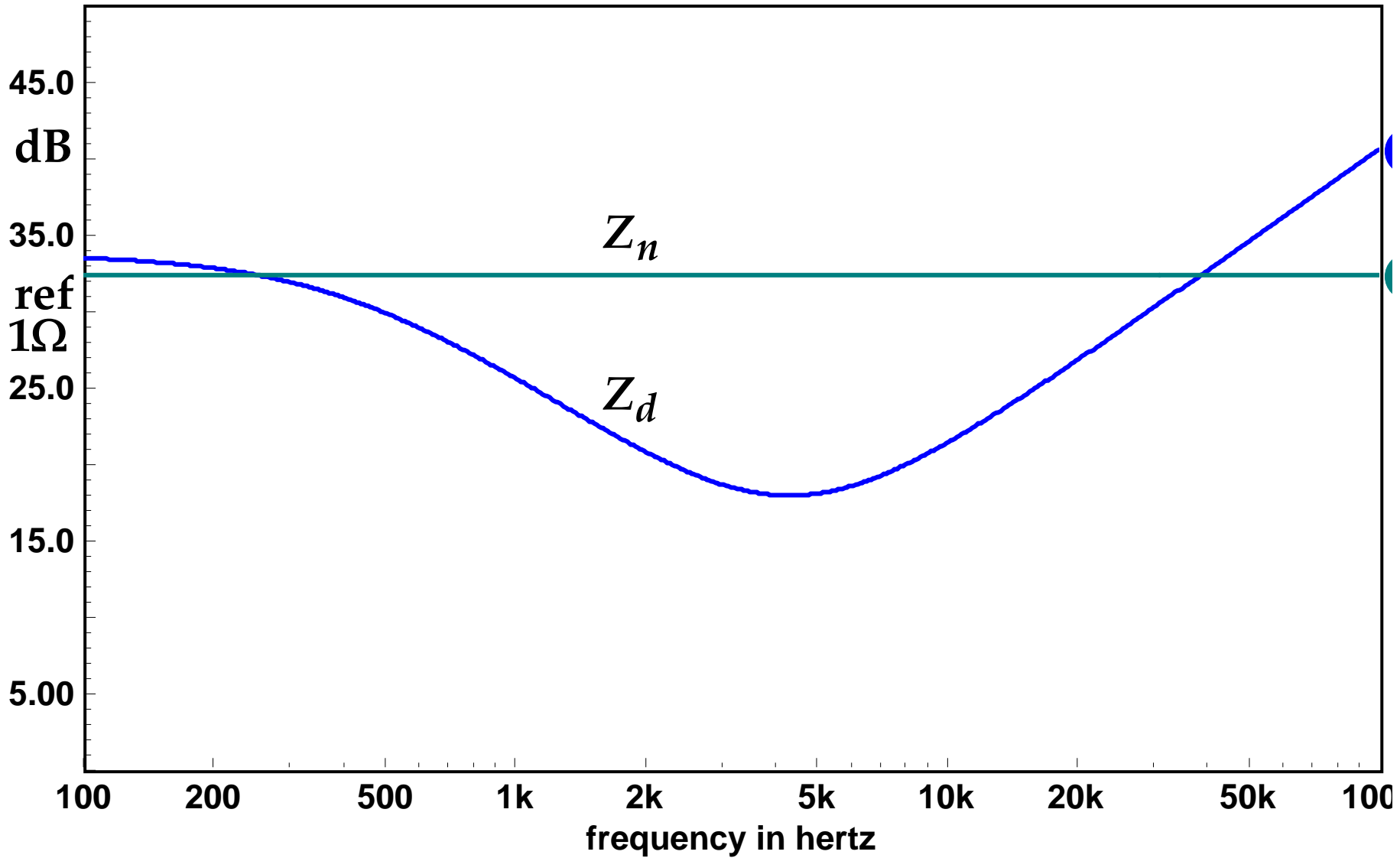
<http://www.RDMiddlebrook.com>
17.Switcher Input Filter Problem



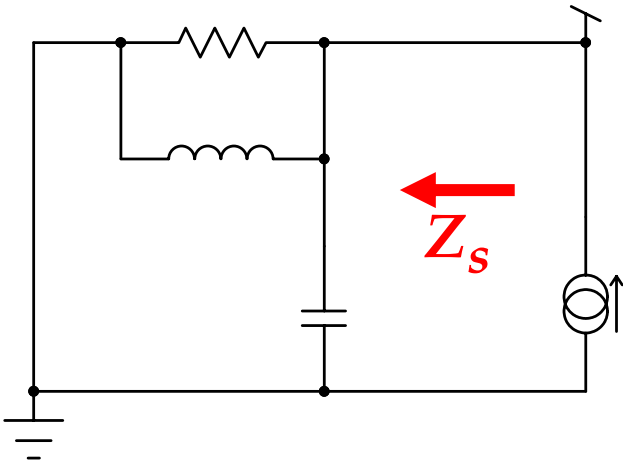

Values as in 1976 Paper Fig. 17, Filter B

v.0.1 3/07

<http://www.RDMiddlebrook.com>
17.Switcher Input Filter Problem

