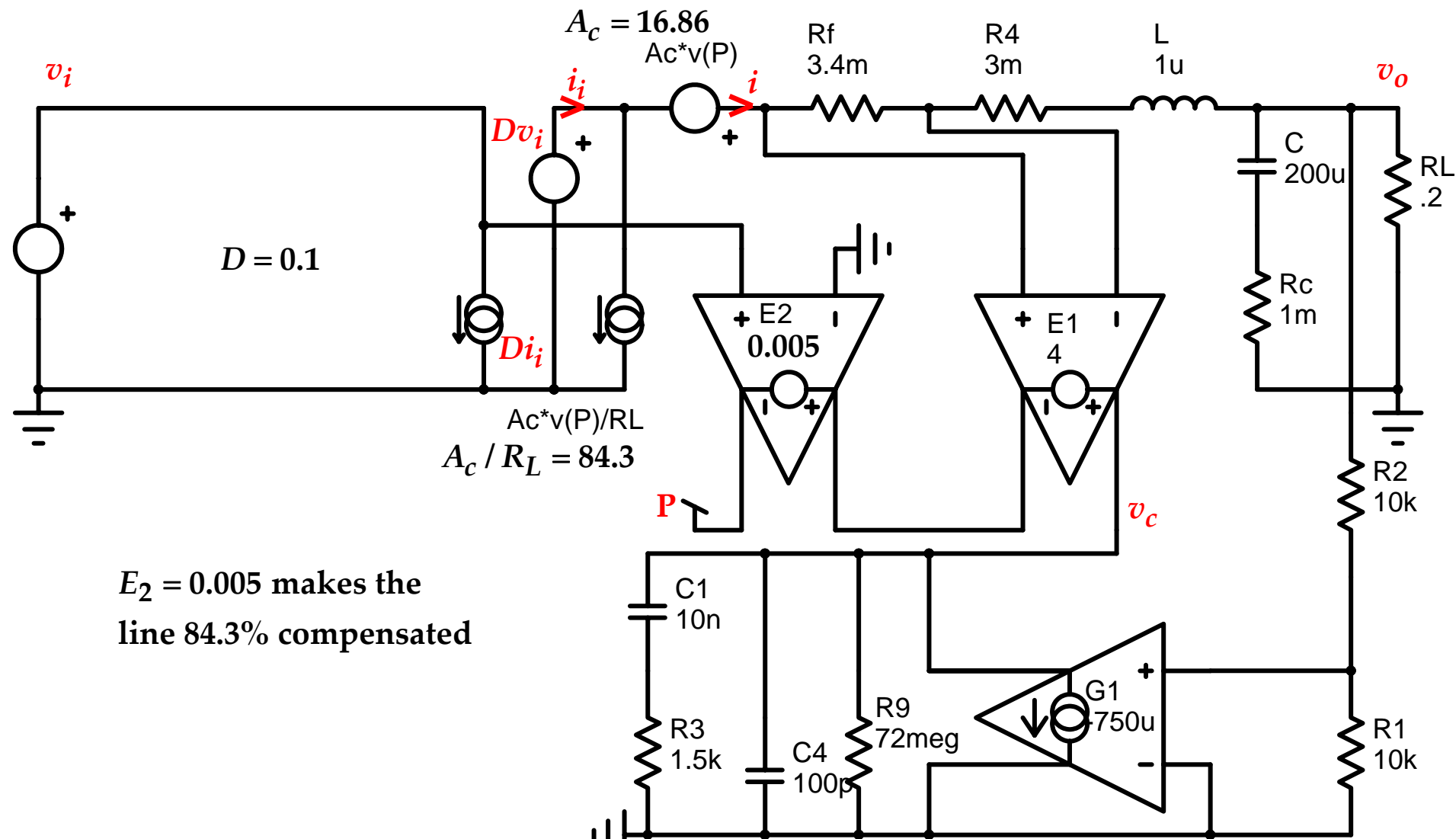


EXAMPLE

18. CURRENT-PROGRAMMED SWITCHED-MODE REGULATOR




$E_2 = 0.005$ makes the line 84.3% compensated

The power stage has an internal current loop and a voltage feedforward loop.

STEP 1

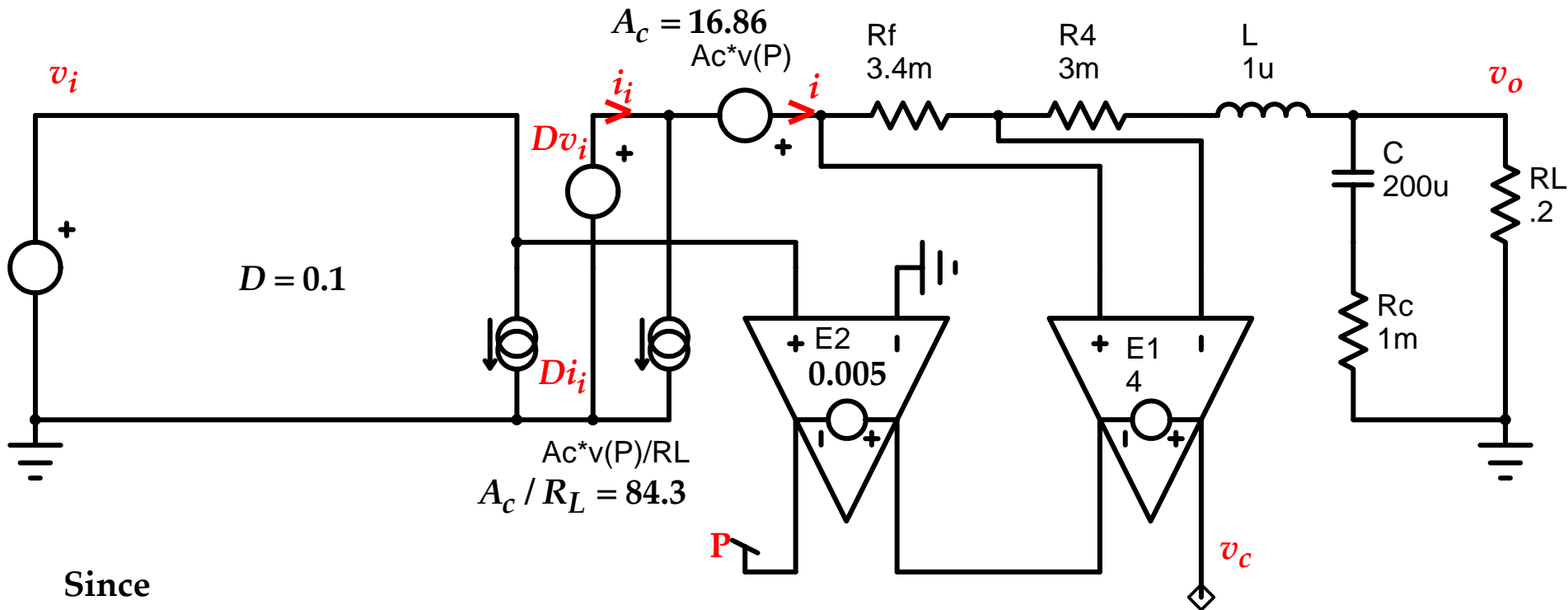Strategy: absorb both loops into an equivalent power stage model, by Doing Some Algebra on the Circuit Diagram (Ch.2)




Since

$$v(P) = -E_2 v_i + v_c - E_1 R_f i$$


split the voltage and current modulation generators into three:

v.0.1 3/07


<http://www.RDMMiddlebrook.com>

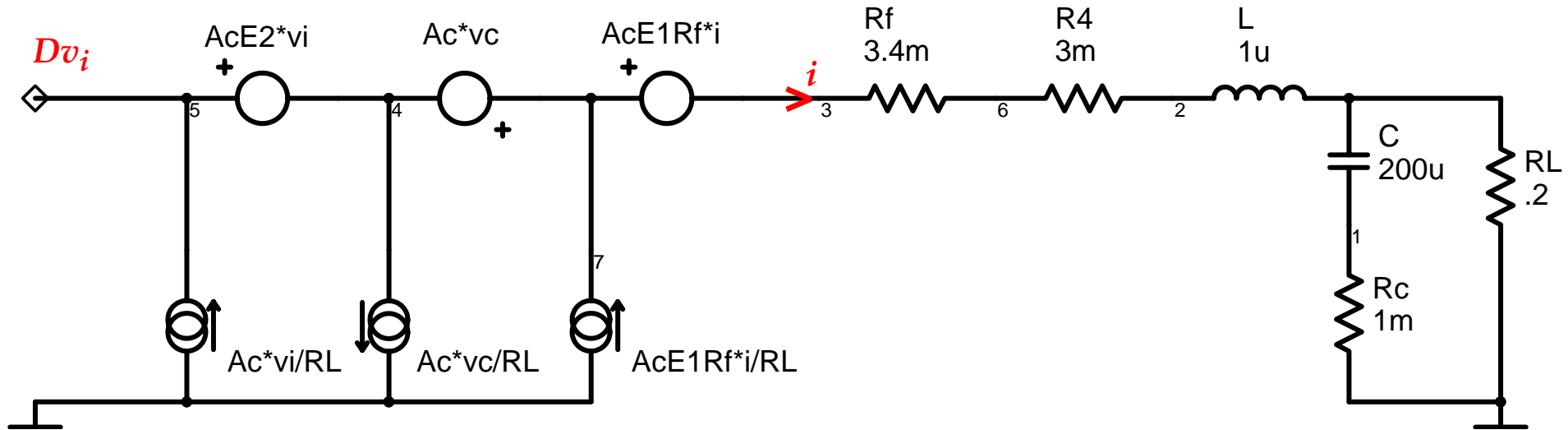

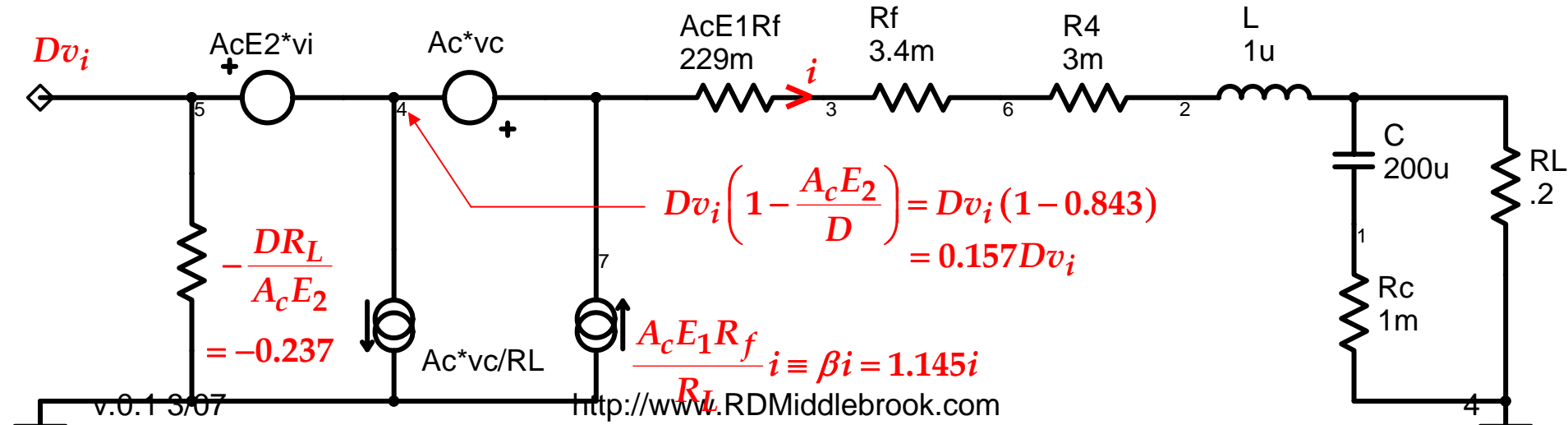Since the voltage generator $A_c E_1 R_f i$ is proportional to the current through it, it can be replaced by a resistance $A_c E_1 R_f$. Also, since the current generator $A_c E_2 v_i / R_L$ is proportional to the voltage Dv_i across it, it can be replaced by a (negative) resistance $-DR_L / A_c E_2$.



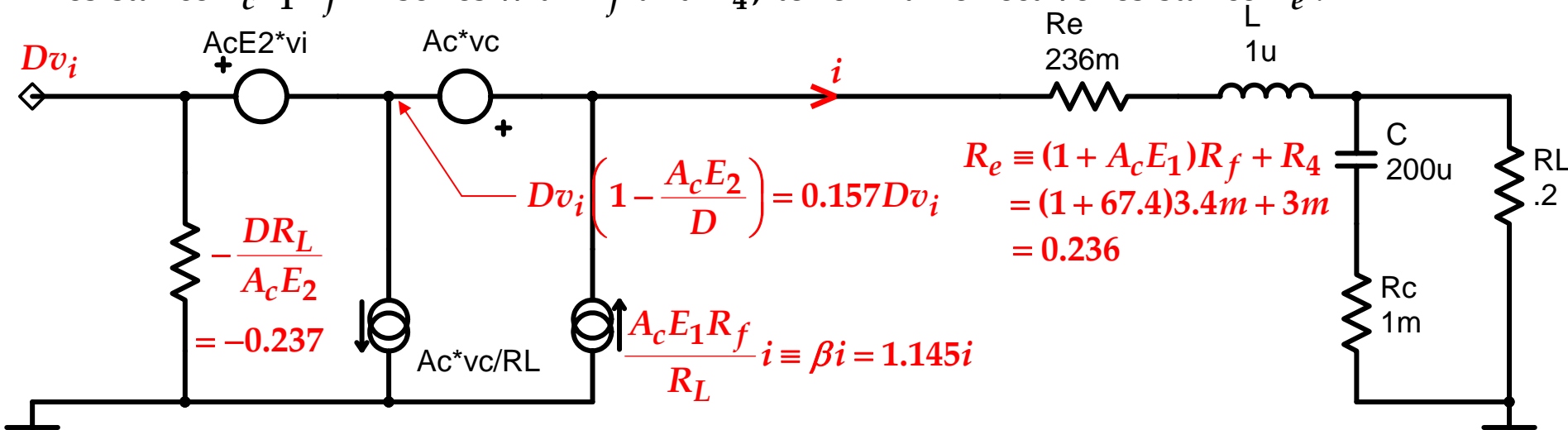The consequence of the current loop is that it introduces a (lossless) damping resistance $A_c E_1 R_f$ in series with R_f and R_4 , to form an effective resistance R_e :



STEP 2

Normalize the element values in the filter (Ch. 5):

$$\omega_o \equiv \frac{1}{\sqrt{LC}}$$

$$f_o = 11.2 \text{ kHz}$$


$$R_o \equiv \sqrt{\frac{L}{C}} = 70.7 \text{ m}$$

$$Q_e \equiv \frac{R_o}{R_e} = 0.300$$

$$Q_c \equiv \frac{R_o}{R_c} = 70.7$$

$$Q_L \equiv \frac{R_L}{R_o} = 2.83$$

v.0.1 3/07

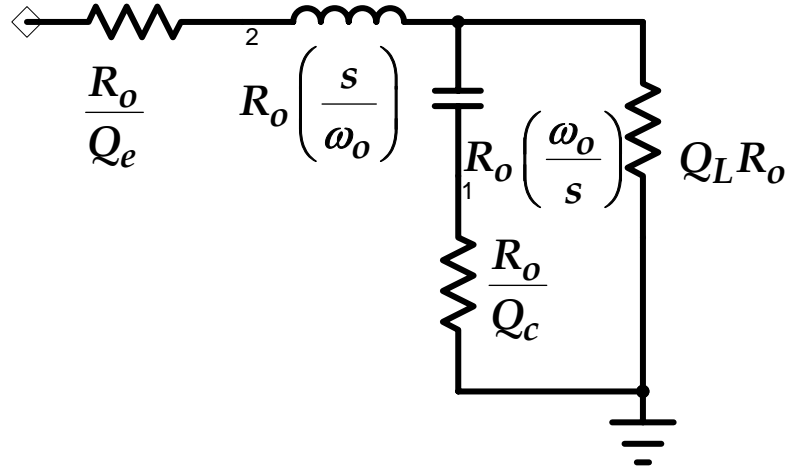

The voltage transfer function H for this triple-damped RLC filter was obtained in Ch. 12:

$$H = \frac{1}{1 + \frac{1}{Q_e Q_L}} \frac{1 + \frac{1}{Q_c} \left(\frac{s}{\omega_0} \right)}{1 + \left(\frac{1}{Q_L \left(1 + \frac{1}{Q_e Q_L} \right)} + \frac{1}{Q_c} + \frac{1}{Q_e \left(1 + \frac{1}{Q_e Q_L} \right)} \right) \left(\frac{s}{\omega_0} \right) + \frac{1 + \frac{1}{Q_e Q_L}}{1 + \frac{1}{Q_e Q_L}} \left(\frac{s}{\omega_0} \right)^2}$$

$$= \frac{1}{1 + \frac{1}{Q_e Q_L}} \frac{1 + \frac{1}{Q_c} \left(\frac{s}{\omega_0} \right)}{1 + \frac{\frac{1}{Q_e} + \frac{1}{Q_L} + \frac{1 + 1/Q_e Q_L}{Q_c}}{1 + \frac{1}{Q_e Q_L}} \left(\frac{s}{\omega_0} \right) + \frac{1 + \frac{1}{Q_e Q_L}}{1 + \frac{1}{Q_e Q_L}} \left(\frac{s}{\omega_0} \right)^2}$$

For $Q_e Q_c \gg 1$, $Q_e Q_L \gg 1$, the result reduces to that previously obtained by extrapolation of the result for $Q_c = \infty$:

$$H \approx \frac{1 + \frac{1}{Q_c} \left(\frac{s}{\omega_0} \right)}{1 + \left(\frac{1}{Q_e} + \frac{1}{Q_c} + \frac{1}{Q_L} \right) \left(\frac{s}{\omega_0} \right) + \left(\frac{s}{\omega_0} \right)^2}$$

For the LM3495, however, the inequality $Q_c Q_L = 70.7 * 2.83 = 200 \gg 1$ still holds, but the inequality $Q_e Q_L = 0.300 * 2.83 = 0.848 \gg 1$ does not.

The result therefore becomes

$$H = \frac{1}{1 + \frac{1}{Q_e Q_L}} \frac{1 + \frac{1}{Q_c} \left(\frac{s}{\omega_o} \right)}{\left(1 + \frac{1}{Q_e} + \frac{1}{Q_L} + \frac{1}{Q_c} \right) \left(\frac{s}{\omega_o} \right) + \frac{1 + \frac{1}{Q_e Q_L}}{1 + \frac{1}{Q_e Q_L}} \left(\frac{s}{\omega_o} \right)^2}$$

$\frac{1}{Q_c Q_L}$

$$H = \frac{1}{1 + \frac{1}{Q_e Q_L}} \frac{1 + \frac{1}{Q_c} \left(\frac{s}{\omega_o} \right)}{1 + \frac{1}{Q_e Q_L} \left(\frac{s}{\omega_o} \right) + \frac{1}{1 + \frac{1}{Q_e Q_L}} \left(\frac{s}{\omega_o} \right)^2}$$

where $Q_e \parallel Q_L = 0.300 \parallel 2.83 = 0.271$ and $\frac{1}{1 + \frac{1}{Q_e Q_L}} = \frac{1}{2.18} = 0.459$

The Q_t of the denominator quadratic is (Ch. 4)

$$Q_t \equiv \frac{\sqrt{ac}}{b} = \sqrt{\left(1 + \frac{1}{Q_e Q_L} \right)} (Q_e \parallel Q_L) = 0.400, \quad Q_t = -7.96dB$$


$$\omega_o \Rightarrow \sqrt{\left(1 + \frac{1}{Q_e Q_L} \right)} \omega_o,$$

$f_o = \frac{1}{2\pi} \sqrt{2.18} * 11.2kHz = 16.5kHz$
<http://www.RDModelBook.com>
 18. Current-Programmed Switcher

The power stage control-to-output voltage gain is $v_o/v_c|_{v_i=0} = A_c H$ where $A_c = 16.86$.


Insertion of numbers gives
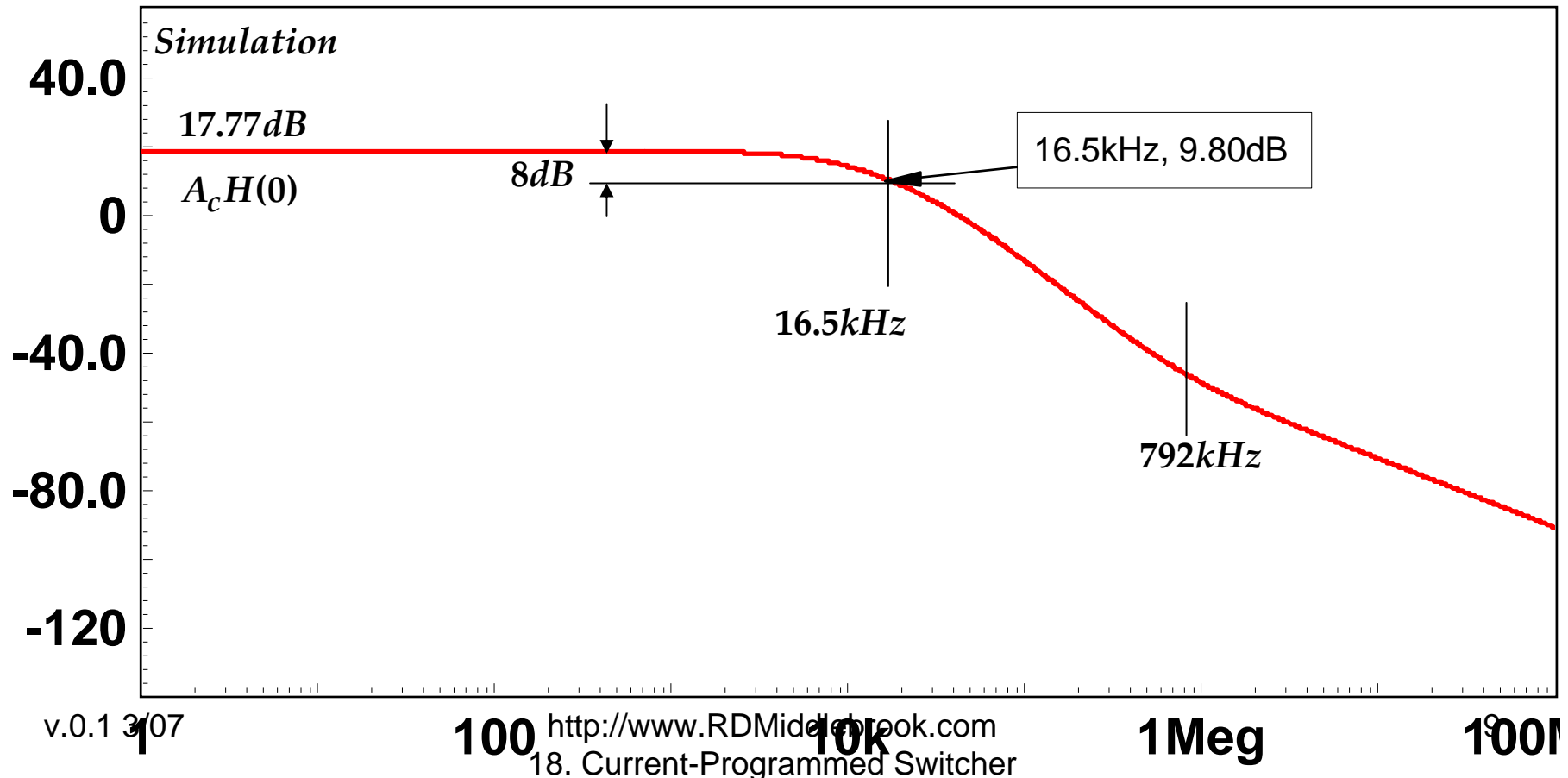
$$A_c H = 17.77 \text{ dB} \frac{1 + \frac{s/2\pi}{792 \text{ kHz}}}{1 + \frac{1}{0.400} \left(\frac{s/2\pi}{16.5 \text{ kHz}} \right) + \left(\frac{s/2\pi}{16.5 \text{ kHz}} \right)^2}$$



STEP 3

Error Amplifier

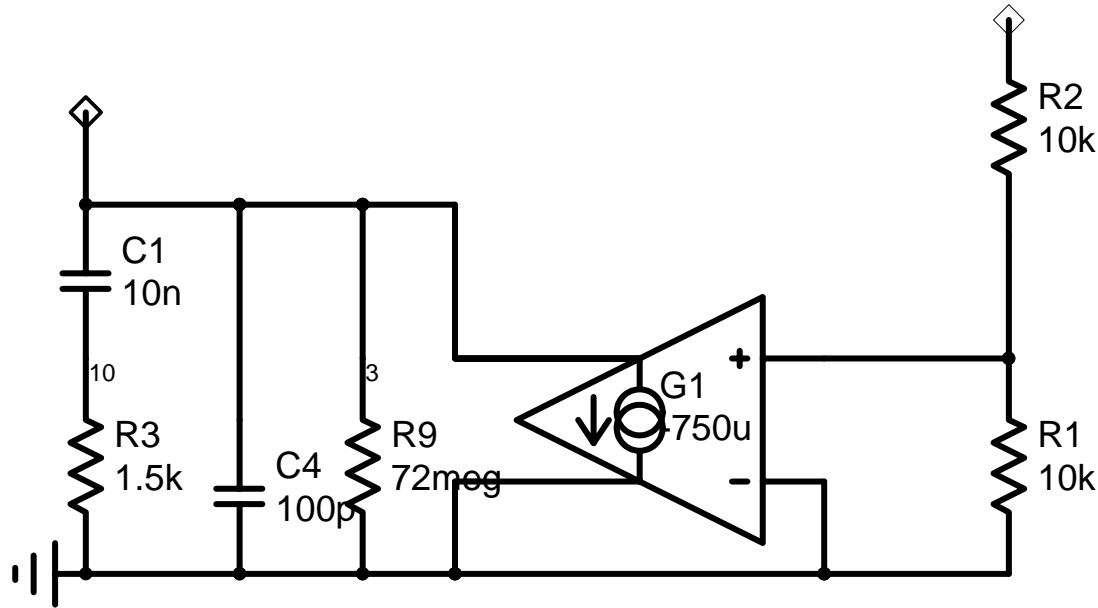

The flat gain that sets the loop gain crossover occurs when C_1 is short, and C_4 open, so take this gain as reference (Ch. 3). The two poles are obviously well separated, so the gain can be written by inspection as


$$A = A_{em} \frac{1}{\left(\frac{1}{sC_1R_3} + 1\right)(1 + sC_4R_3)}$$

where

$$A_{em} = \frac{R_1}{R_1 + R_2} G1R_3 = 0.563 \Rightarrow -5.0dB$$

With substitution of numbers,

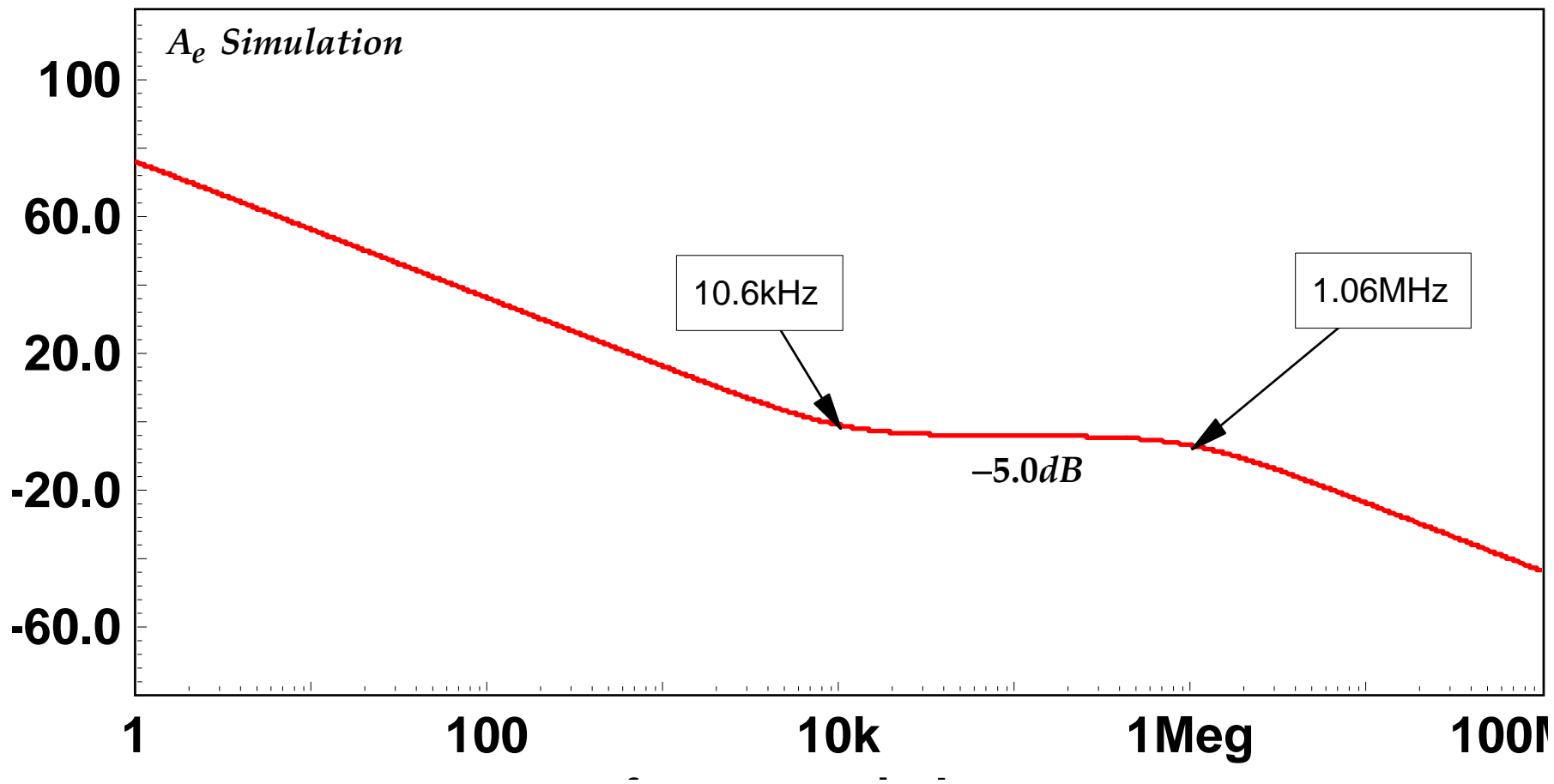
$$A_{em} = -5dB \frac{1}{\left(\frac{10.6kHz}{s/2\pi} + 1\right)\left(1 + \frac{s/2\pi}{1.068MHz}\right)}$$



STEP 4

The loop gain T is:
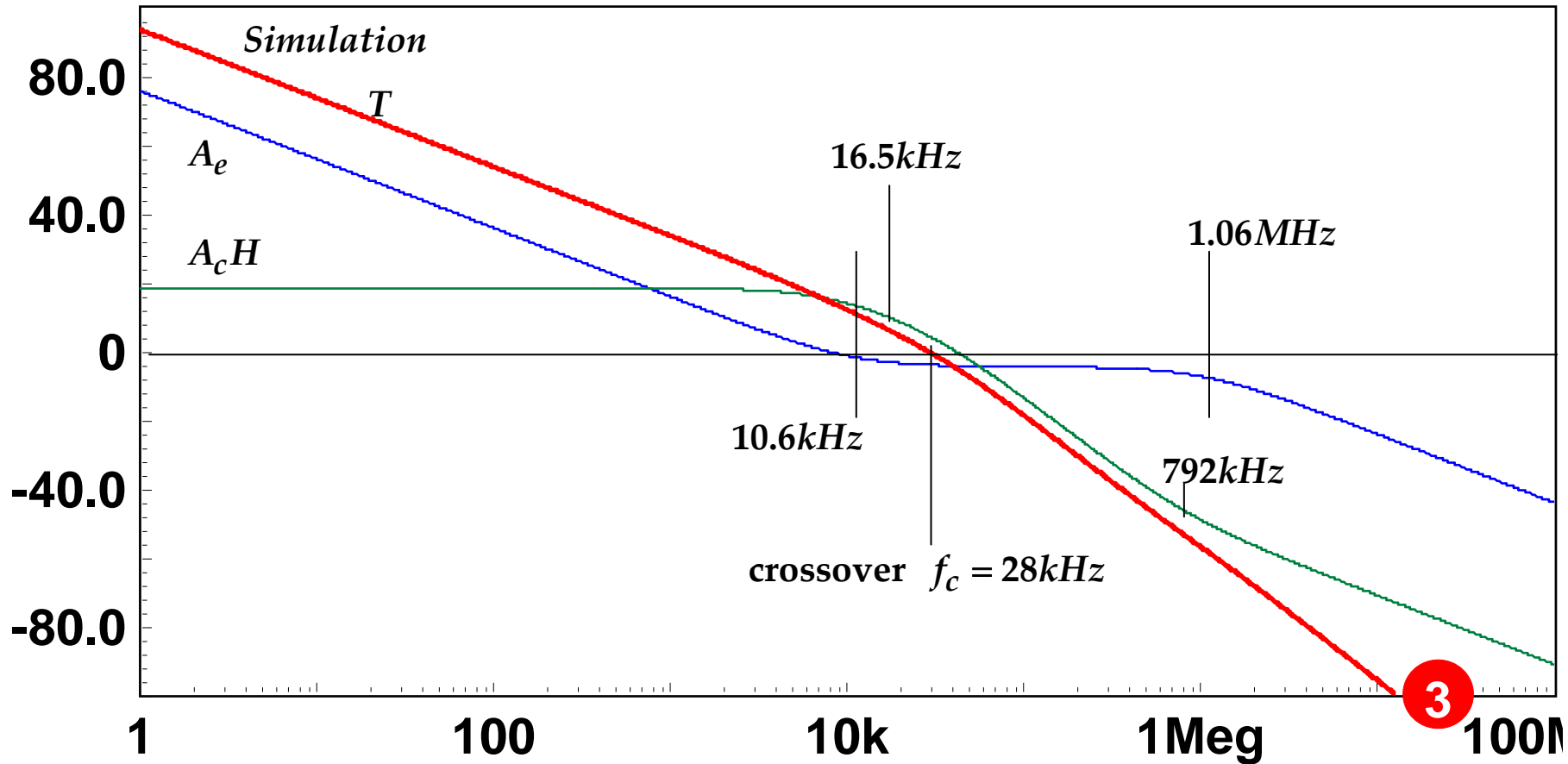
$$T = A_e A_c H = 12.77 \text{ dB} \frac{1 + \frac{s/2\pi}{792 \text{ kHz}}}{\left(\frac{10.6 \text{ kHz}}{s/2\pi} + 1\right) \left[1 + \frac{1}{0.400} \left(\frac{s/2\pi}{16.5 \text{ kHz}}\right) + \left(\frac{s/2\pi}{16.5 \text{ kHz}}\right)^2\right] \left(1 + \frac{s/2\pi}{1.06 \text{ MHz}}\right)}$$




Since three poles close together determine the crossover frequency f_c , there is no point in trying to predict its value. Instead, the simulation shows it to be $f_c = 28\text{kHz}$.

From the predicted corner frequencies of T , $\underline{\angle T}$ can then be calculated as:

$$\begin{aligned}\underline{\angle T} &= -90^\circ + \tan^{-1} \frac{28}{10.6} - \left(180^\circ + \tan^{-1} \frac{\frac{1}{0.4} \frac{28}{16.5}}{1 - \left(\frac{28}{16.5}\right)^2} \right) + \tan^{-1} \frac{28}{792} - \tan^{-1} \frac{28}{1060} \\ &= -90^\circ + 70^\circ - (180^\circ - 66^\circ) + 2^\circ - 2^\circ \\ &= -134^\circ\end{aligned}$$

This agrees with the simulation:

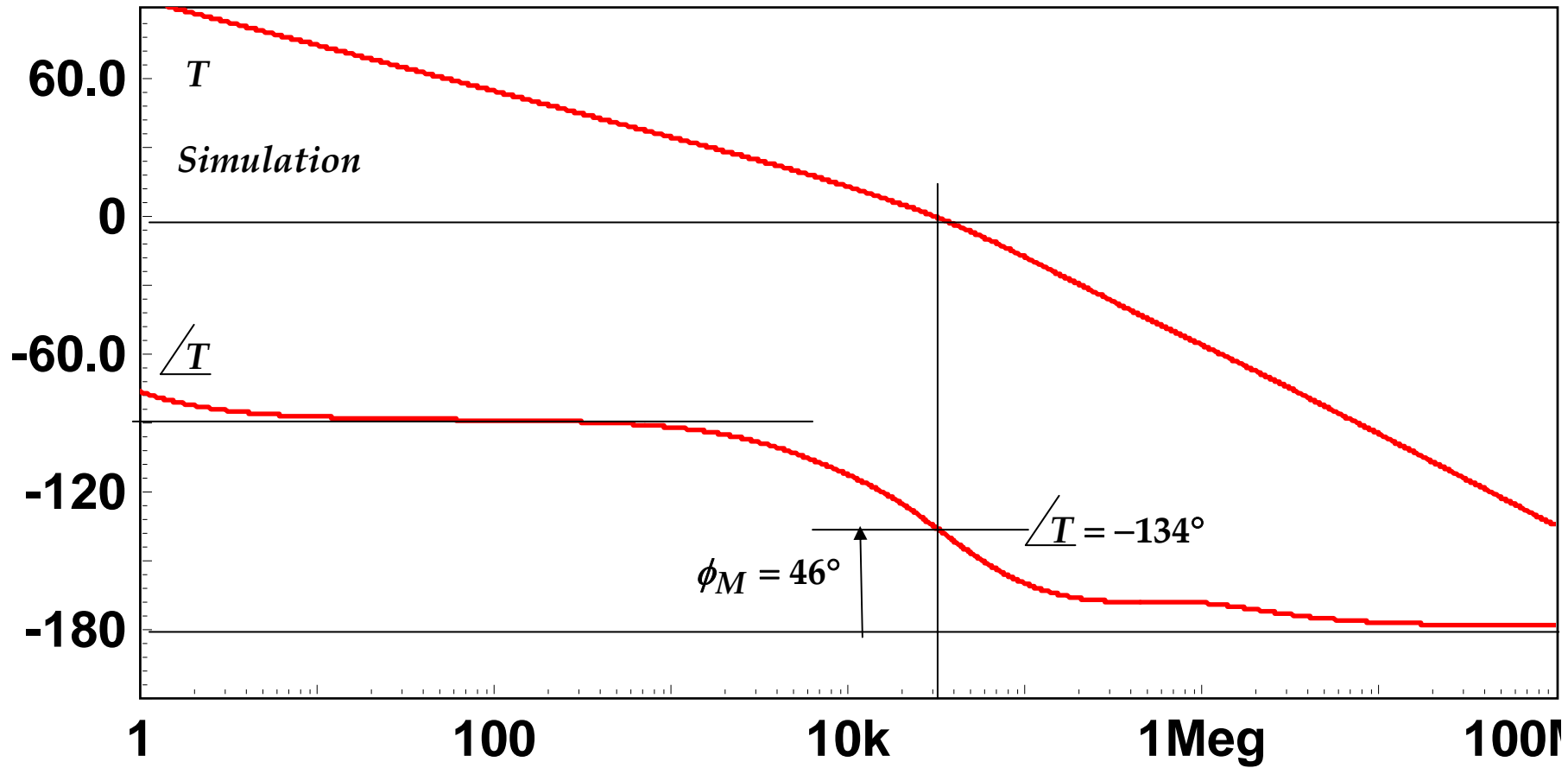

STEP 5: Closed-loop gain G

The closed-loop gain $G = G_\infty D$ where $G_\infty = \frac{R_1 + R_2}{R_1} = 2 = 6.02dB$ is the ideal closed-loop

gain, and $D = \frac{T}{1+T}$ is the discrepancy factor (Ch. 10).

Since D is a unique function of T , D can be evaluated at the loop gain crossover frequency in terms of the phase margin φ_M .

In polar form,


$$T = |T|e^{j\angle T}, \quad |D| = \left| \frac{T}{1+T} \right| = \left| \frac{1}{1+\frac{1}{T}} \right| = \left| \frac{1}{1+\frac{1}{|T|}e^{-j\angle T}} \right|$$

If the phase margin is φ_M , then $-\angle T = (\pi - \varphi_M)$ at the crossover frequency where $|T| = 1$. Substitute in $|D|$:

$$\begin{aligned} |D|_{f_c} &= \left| \frac{1}{1+e^{j(\pi-\varphi_M)}} \right| = \left| \frac{1}{1+e^{-j\varphi_M}} \right| = \left| \frac{1}{1-(\cos\varphi_M - j\sin\varphi_M)} \right| = \frac{1}{\sqrt{(1-\cos\varphi_M)^2 + \sin^2\varphi_M}} \\ &= \frac{1}{\sqrt{2(1-\cos\varphi_M)}} = \frac{1}{2\sin\frac{\varphi_M}{2}} \end{aligned}$$


In the LM3495, $G_\infty = 2 = 6.02dB$ and $\varphi_M = 46^\circ$ at the crossover frequency $f_c = 28kHz$. Hence,

$|D|_{28kHz} = 1.28 \Rightarrow 2.10dB$. These results are in agreement with the simulation using the

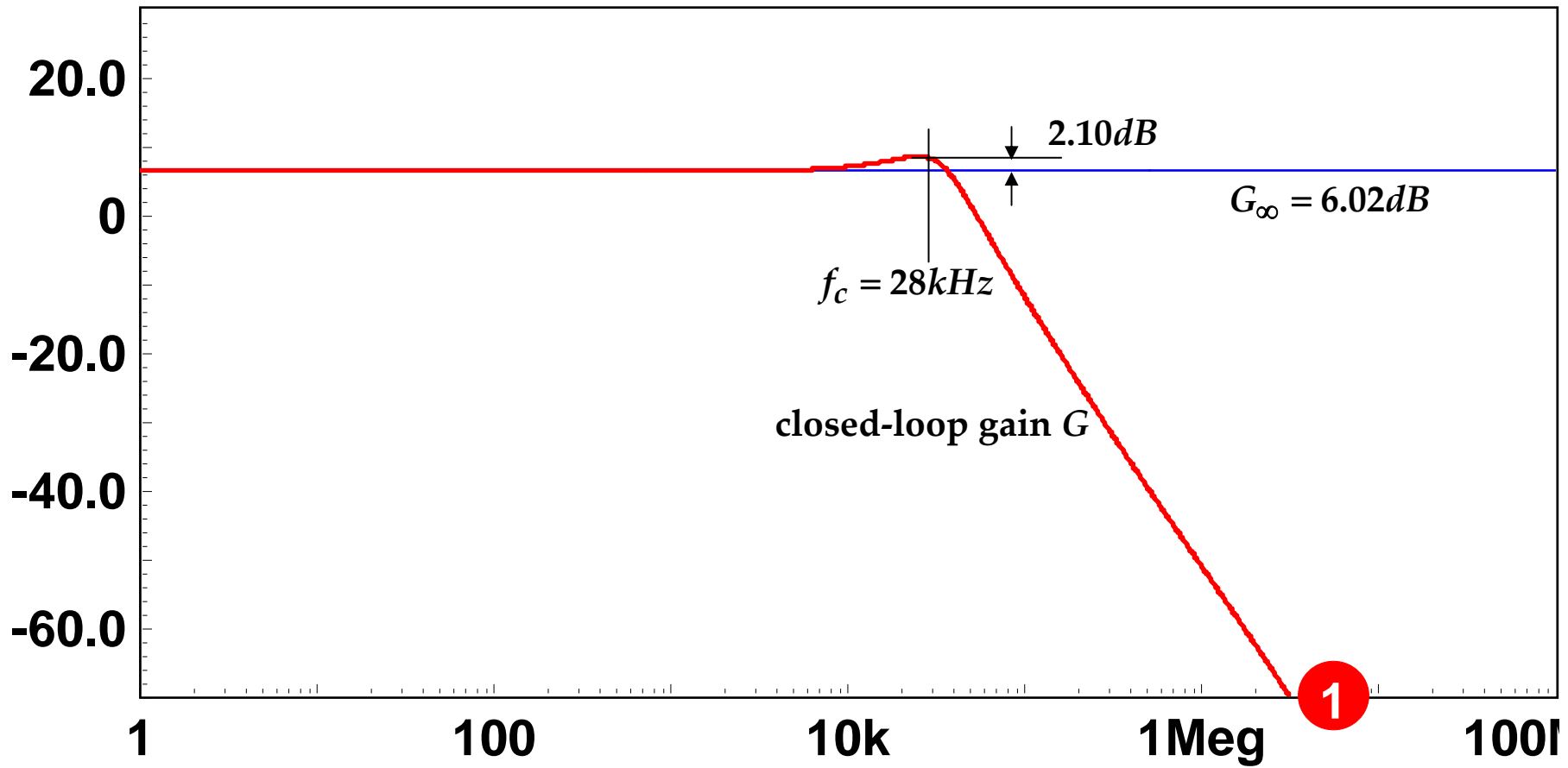


Model for simulation using the Intusoft ICAP/4 GFT Template.

(No input filter)

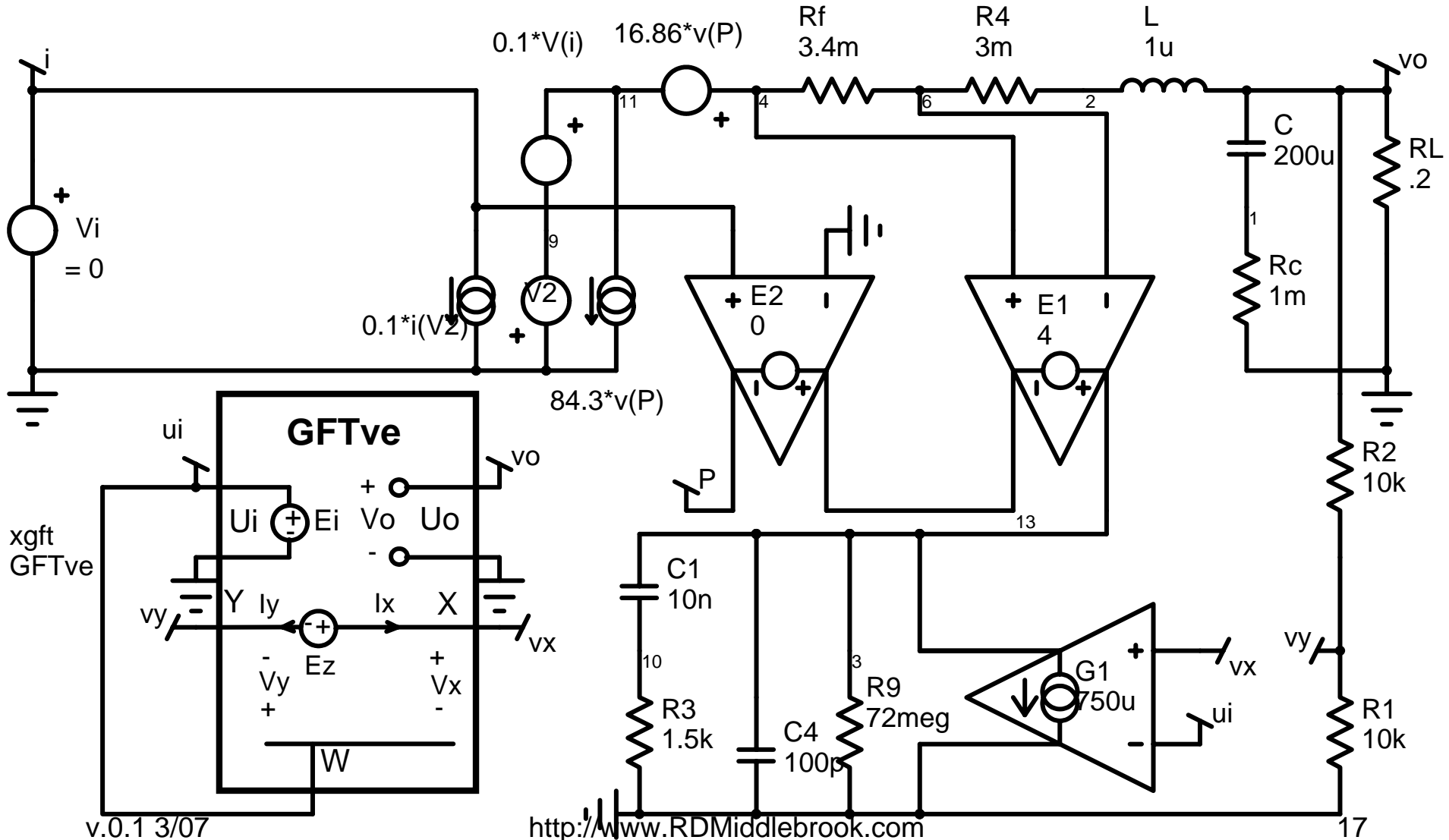


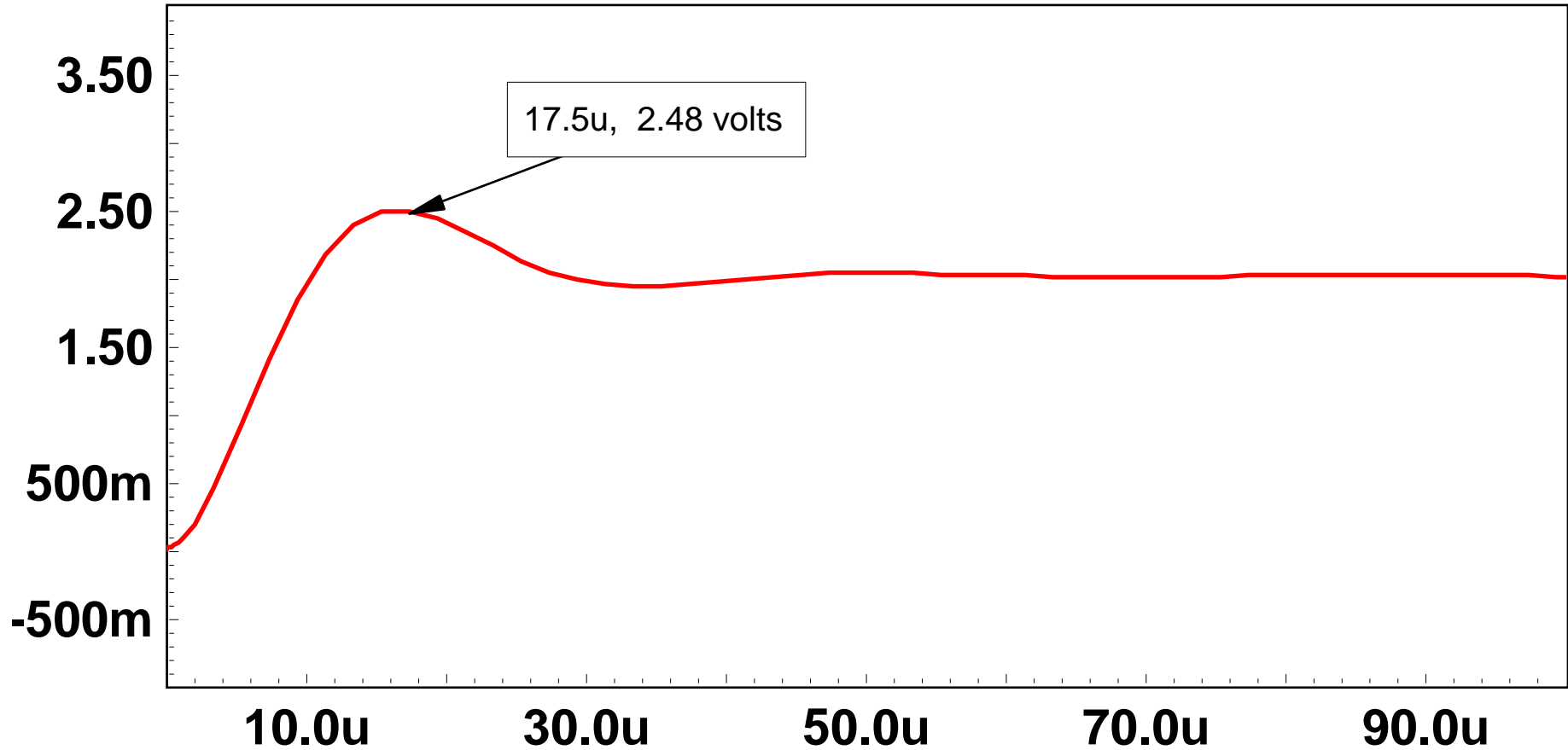Output voltage response to a 1v step in reference voltage



STEP 6: Check for nonidealities

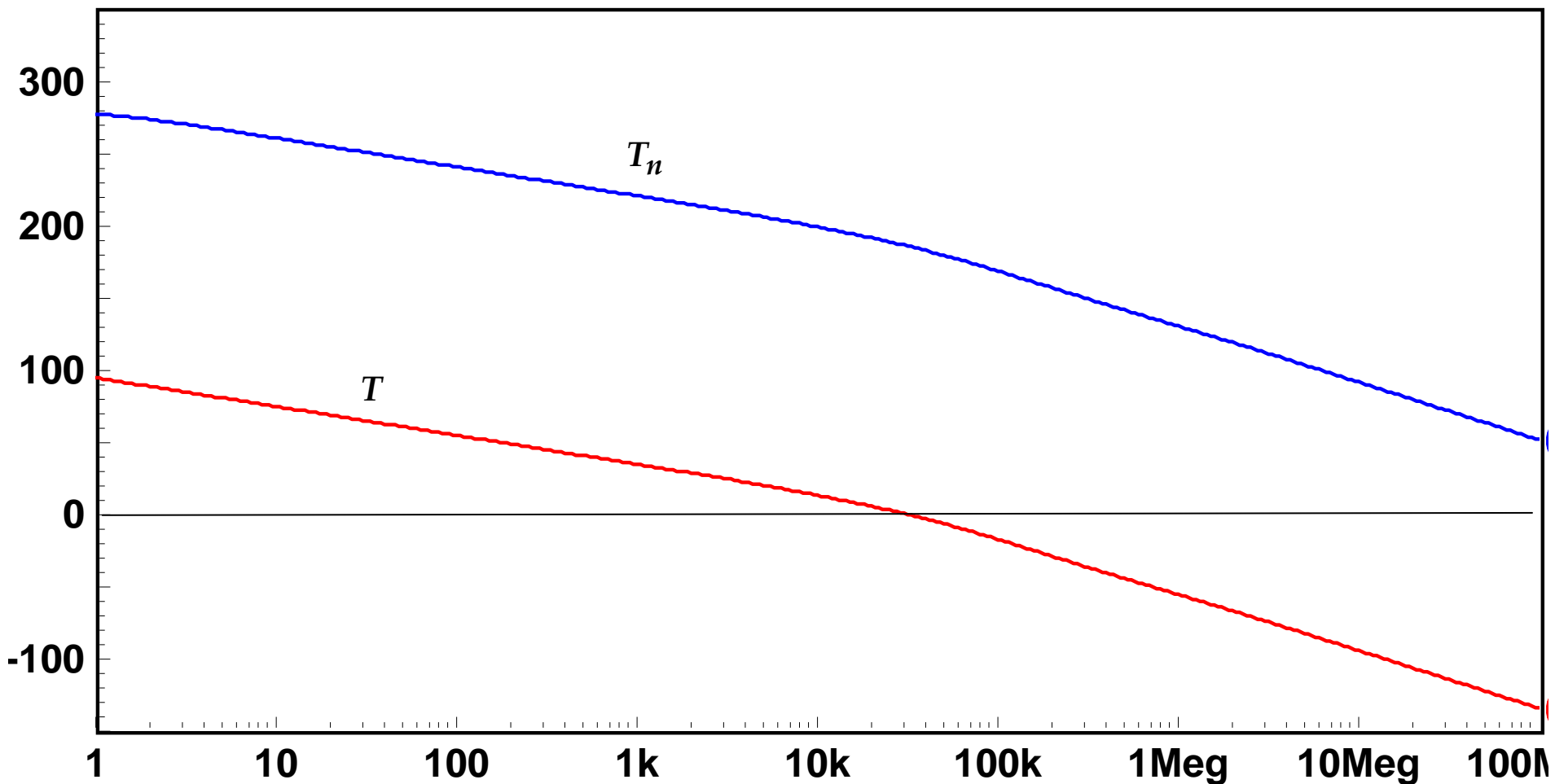
The ICAP/4 simulation also delivers the null loop gain T_n :



Since $T_n \gg 1$ at all frequencies of interest, the nonidealities are negligible.

STEP 7: Output Impedance

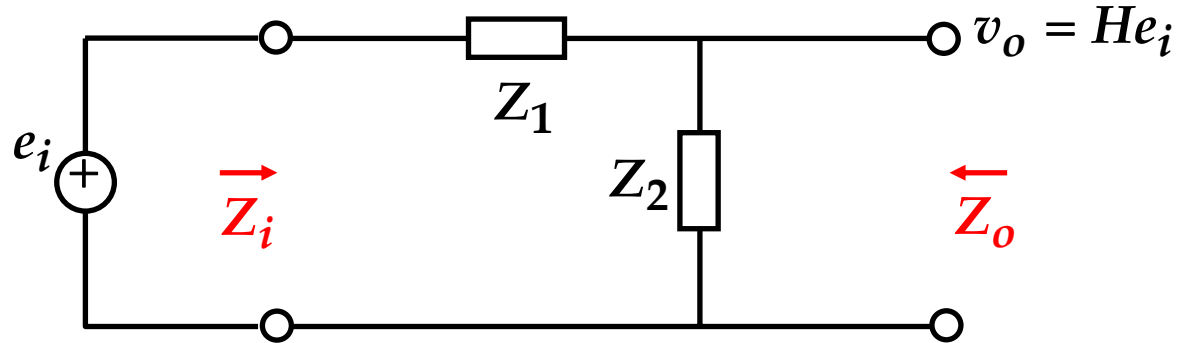
As seen in Ch. 7, for a ladder network such as



the output impedance is

$$Z_o = Z_1 H$$


Here,

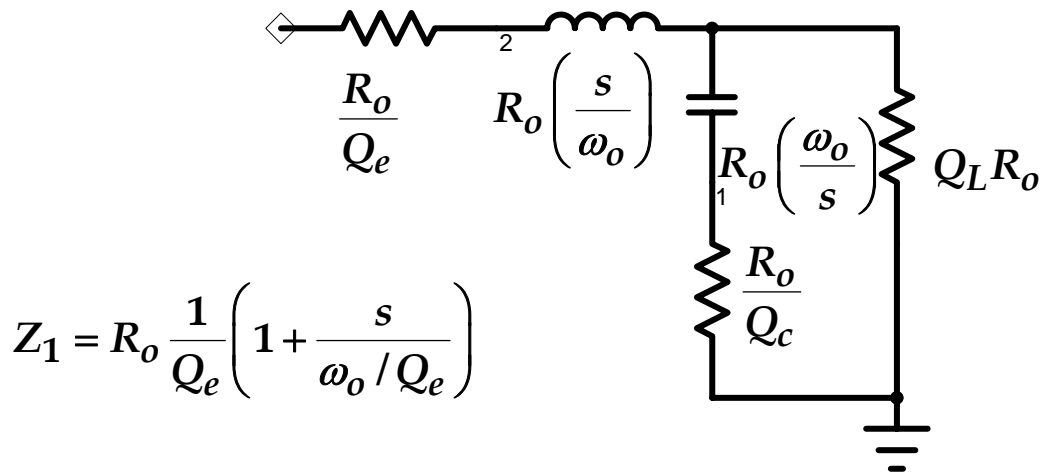

$$Z_1 = R_o \frac{1}{Q_e} \left(1 + \frac{s}{\omega_o / Q_e} \right)$$

and H is already known, so

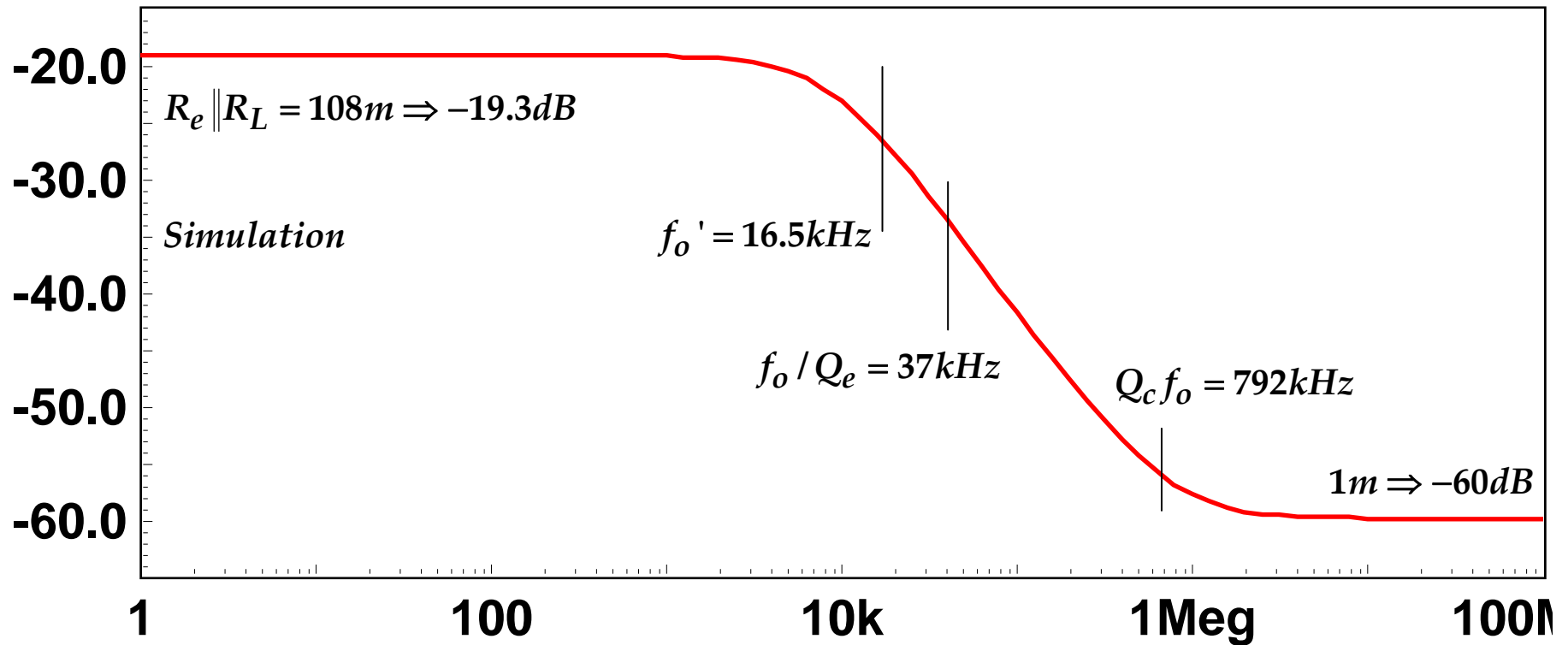
$$Z_o = (R_e \parallel R_L) \frac{\left(1 + \frac{s}{\omega_o / Q_e}\right) \left(1 + \frac{s}{Q_c \omega_o}\right)}{1 + \frac{1}{1 + \frac{1}{Q_e Q_L}} \frac{1}{Q_e \parallel Q_L} \left(\frac{s}{\omega_o}\right) + \frac{1}{1 + \frac{1}{Q_e Q_L}} \left(\frac{s}{\omega_o}\right)^2}$$





Closed loop output impedance Z_{of}

$$Z_{of} = \frac{Z_o}{1+T}$$

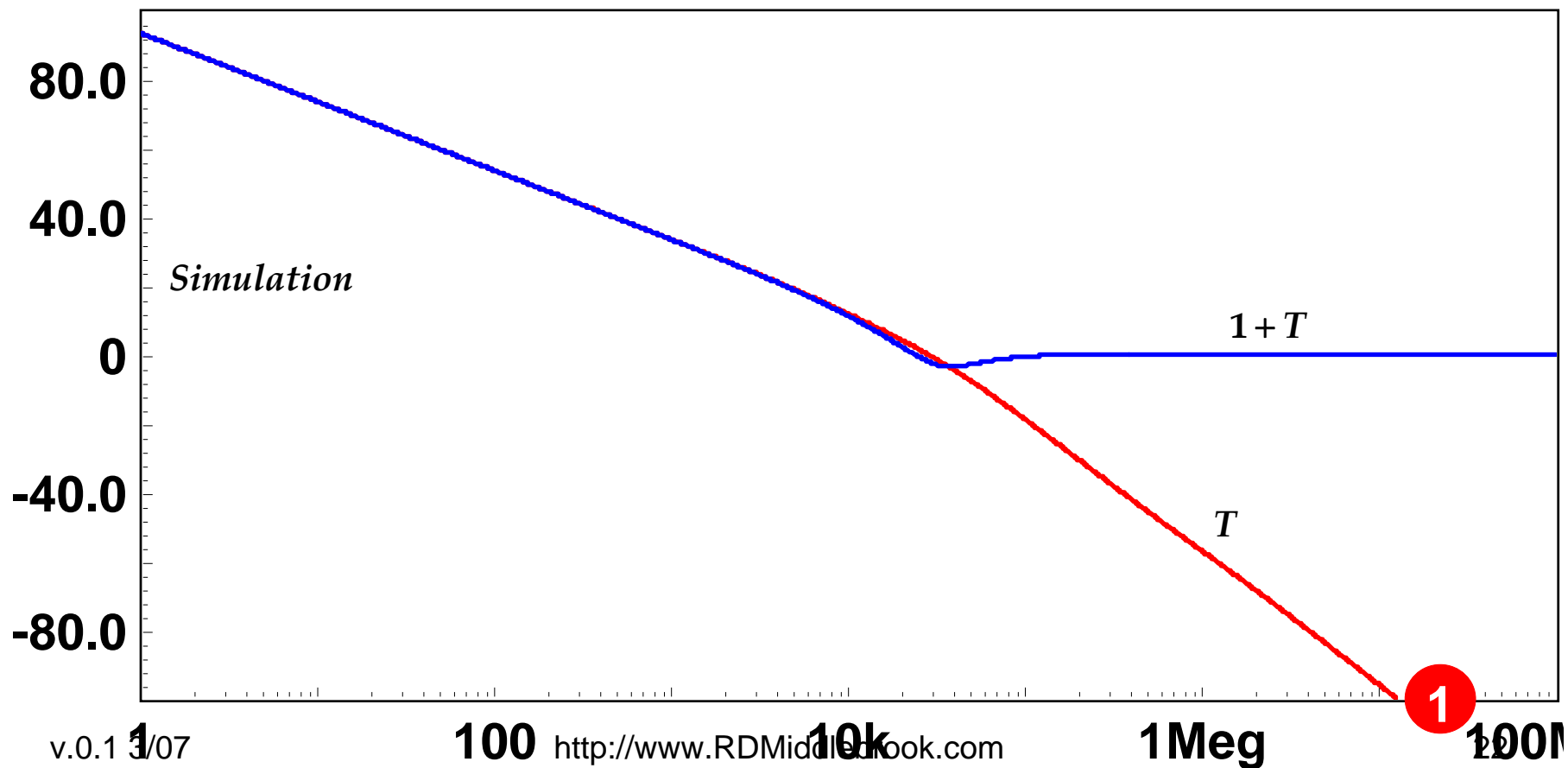Since T is already known, $1+T$ and $\frac{1}{1+T}$ can be found by the methods of Ch. 6.



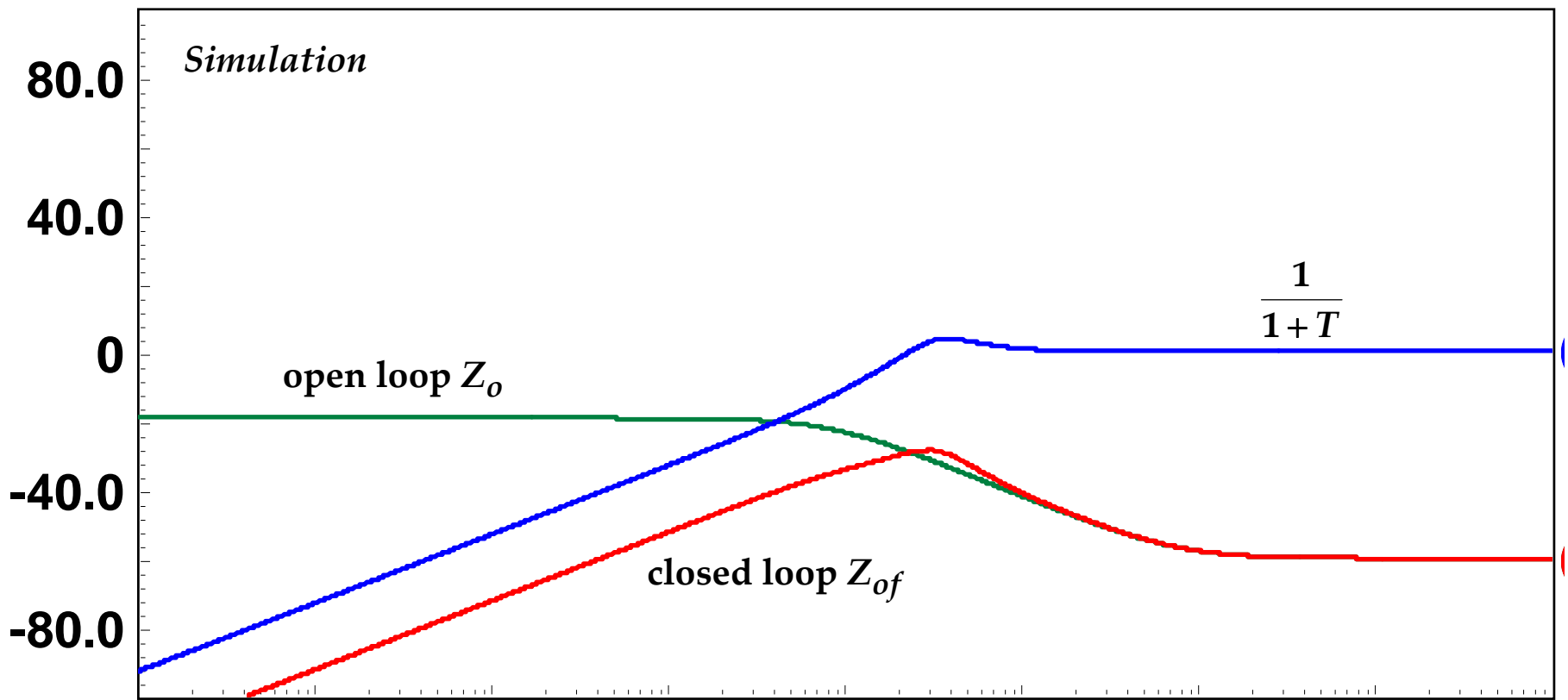


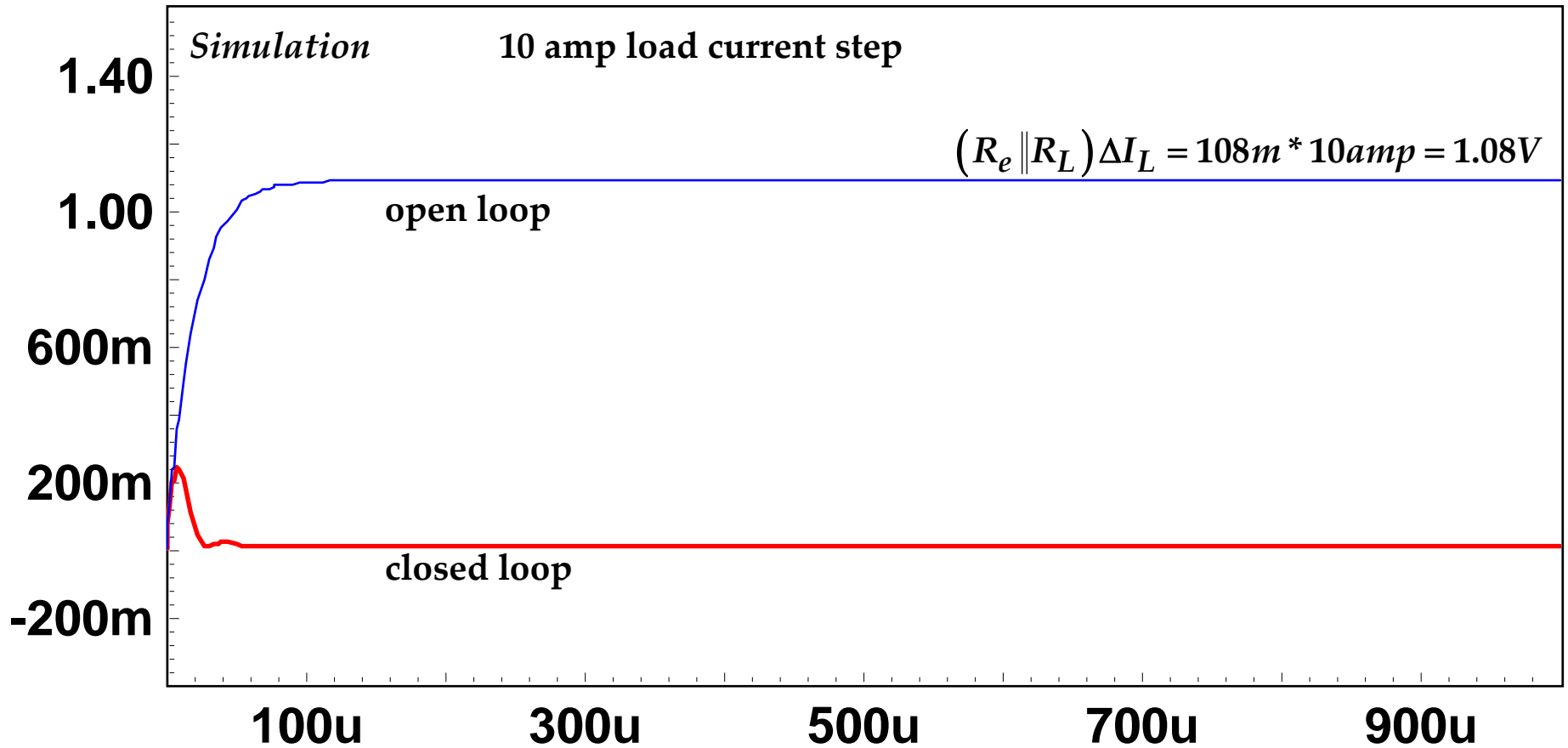

The power stage line-to-output voltage gain is $v_o/v_i|_{v_c=0} = Dv_i \left(1 - \frac{A_c E_2}{D}\right) H = 0.157DHv_i$


Insertion of numbers gives

$$v_o/v_i|_{v_c=0} = -42.85dB \frac{1 + \frac{s/2\pi}{792kHz}}{1 + \frac{1}{0.400} \left(\frac{s/2\pi}{16.5kHz}\right) + \left(\frac{s/2\pi}{16.5kHz}\right)^2}$$

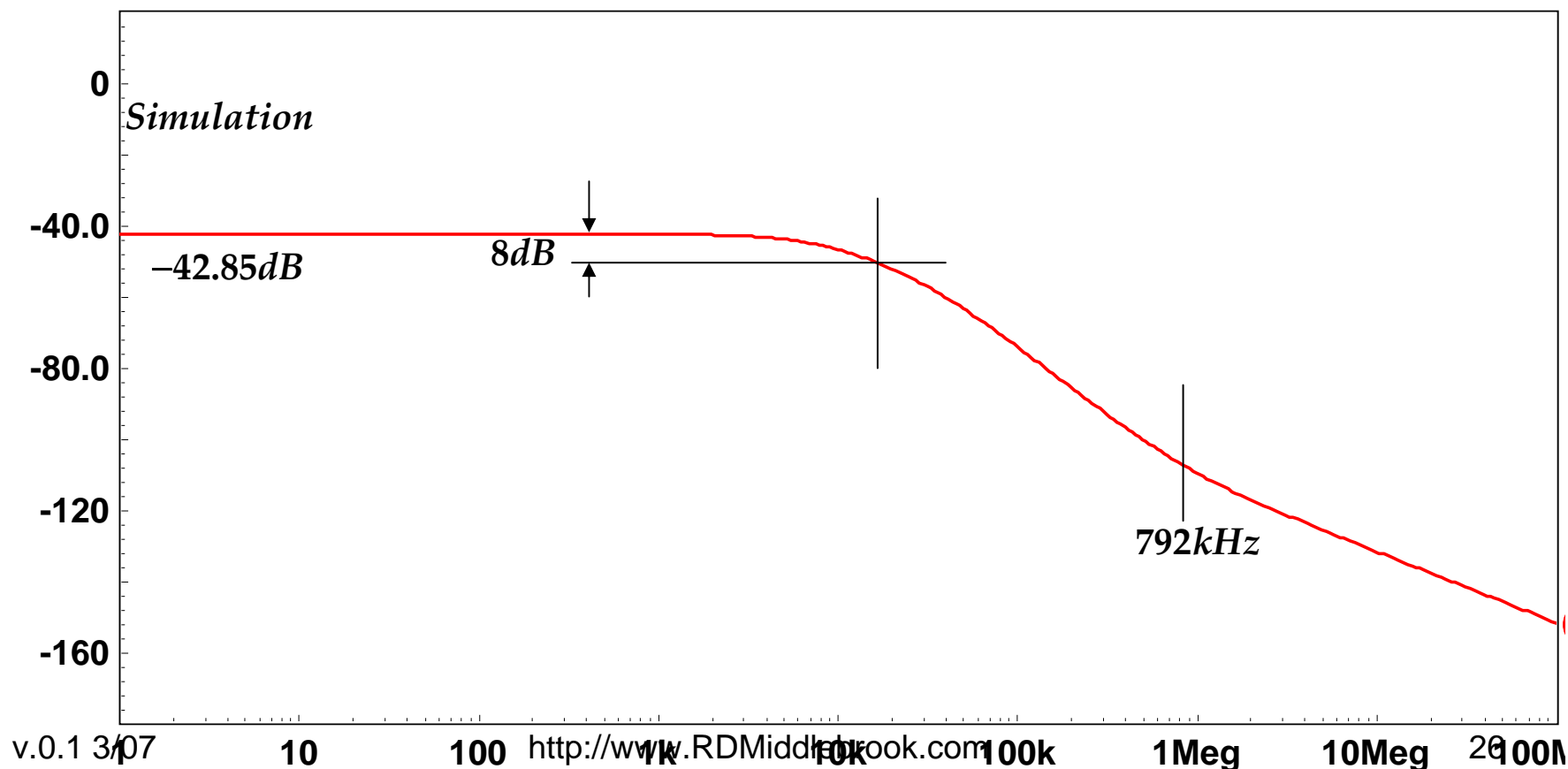

STEP 9: Line input impedance TF Z_i

Same model as for the line-to-output TF:

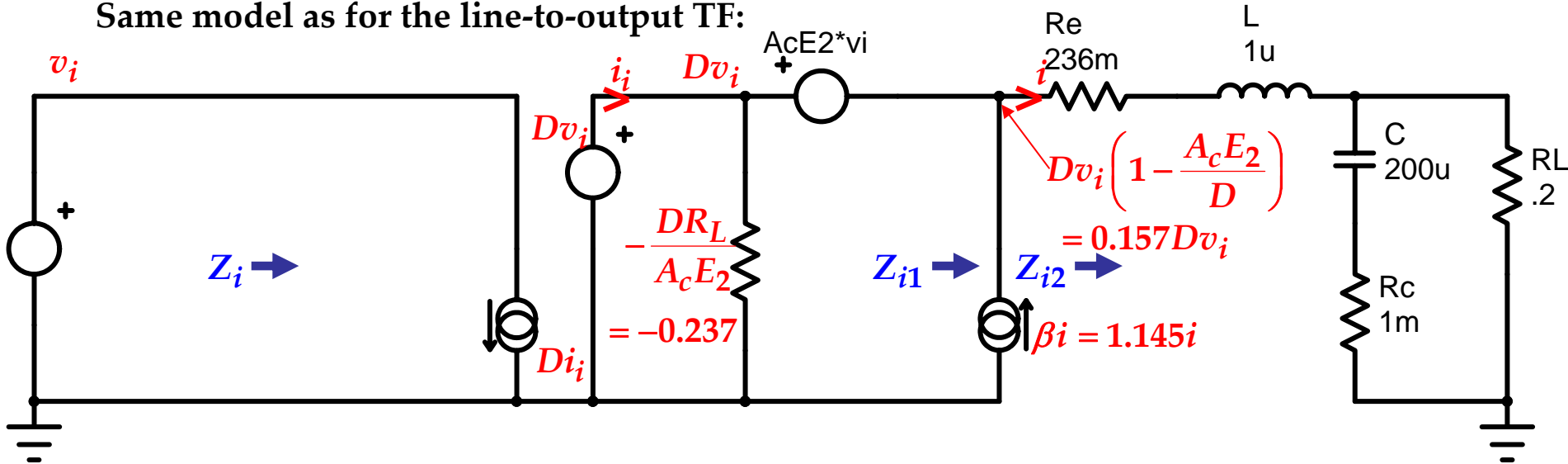

$$Z_i = \frac{1}{D^2} \left[-\frac{DR_L}{A_cE_2} \parallel \frac{Z_{i1}}{1 - \frac{A_cE_2}{D}} \right] \quad \text{where} \quad Z_{i1} = \frac{1}{1 - \beta} Z_{i2} \quad \text{in which}$$


Z_{i2} = input impedance of the filter, which is already known.

Since $\beta > 1$, the result can be written

$$Z_i = -\frac{1}{D^2} \left[\frac{DR_L}{A_cE_2} \parallel \frac{Z_{i2}}{(\beta - 1) \left(1 - \frac{A_cE_2}{D} \right)} \right]$$

STEP 9: Line input impedance TF Z_i

Same model as for the line-to-output TF:

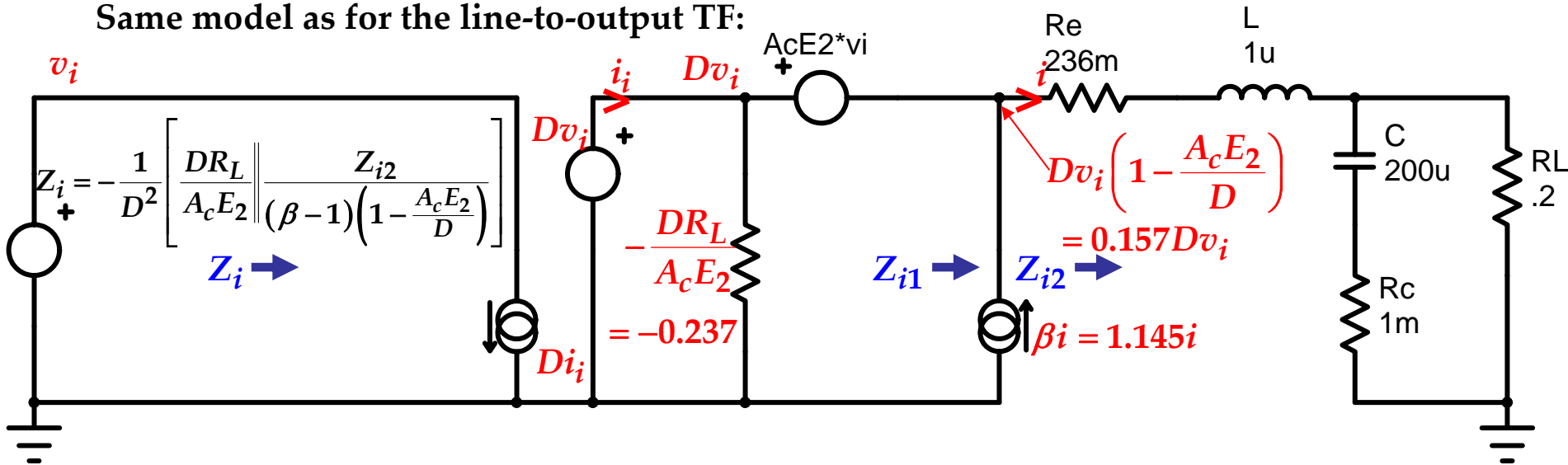

Since $Z_{i2}(0) = R_e + R_L = 0.236 + 0.2 = 0.436$,


$$Z_i(0) = -\frac{1}{0.1^2} \left[0.237 \parallel \frac{0.436}{(1.146 - 1)0.157} \right] = -100 [0.237 \parallel 19] = -100 [0.234] = -23.4 \Rightarrow 27.38\text{dB}$$


Since $Z_{i2}(\infty) = \infty$,

$$Z_i(\infty) = -\frac{1}{0.1^2} [0.237 \parallel \infty] = -100 [0.237] = -23.7 \Rightarrow 27.49\text{dB}$$

Conclusion: the current-programming loop makes the filter input impedance look high, and the (negative) line input impedance is dominated by the term due to the line feedforward.

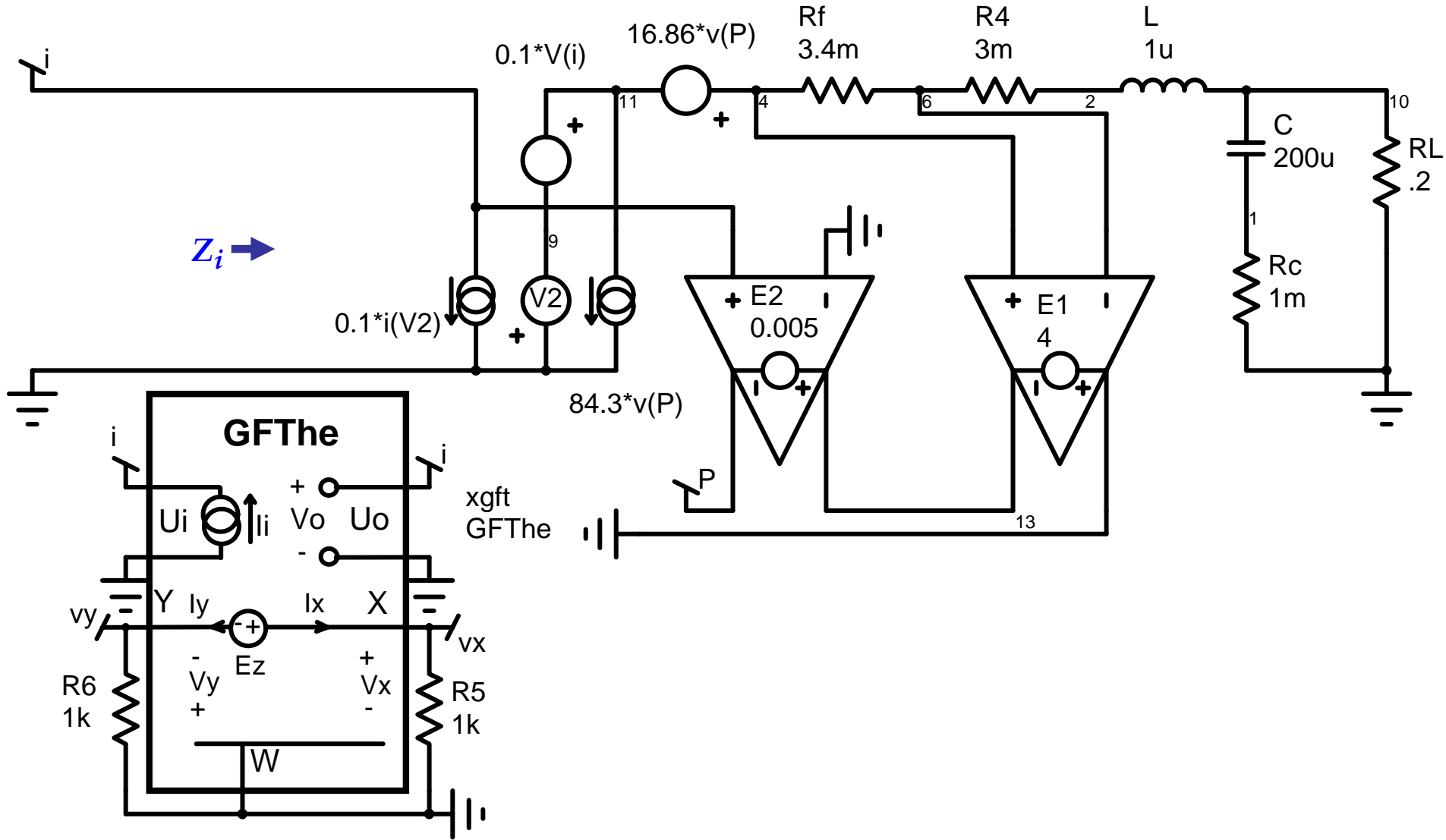Input impedance Z_i by the ICAP/4 GFT Template:



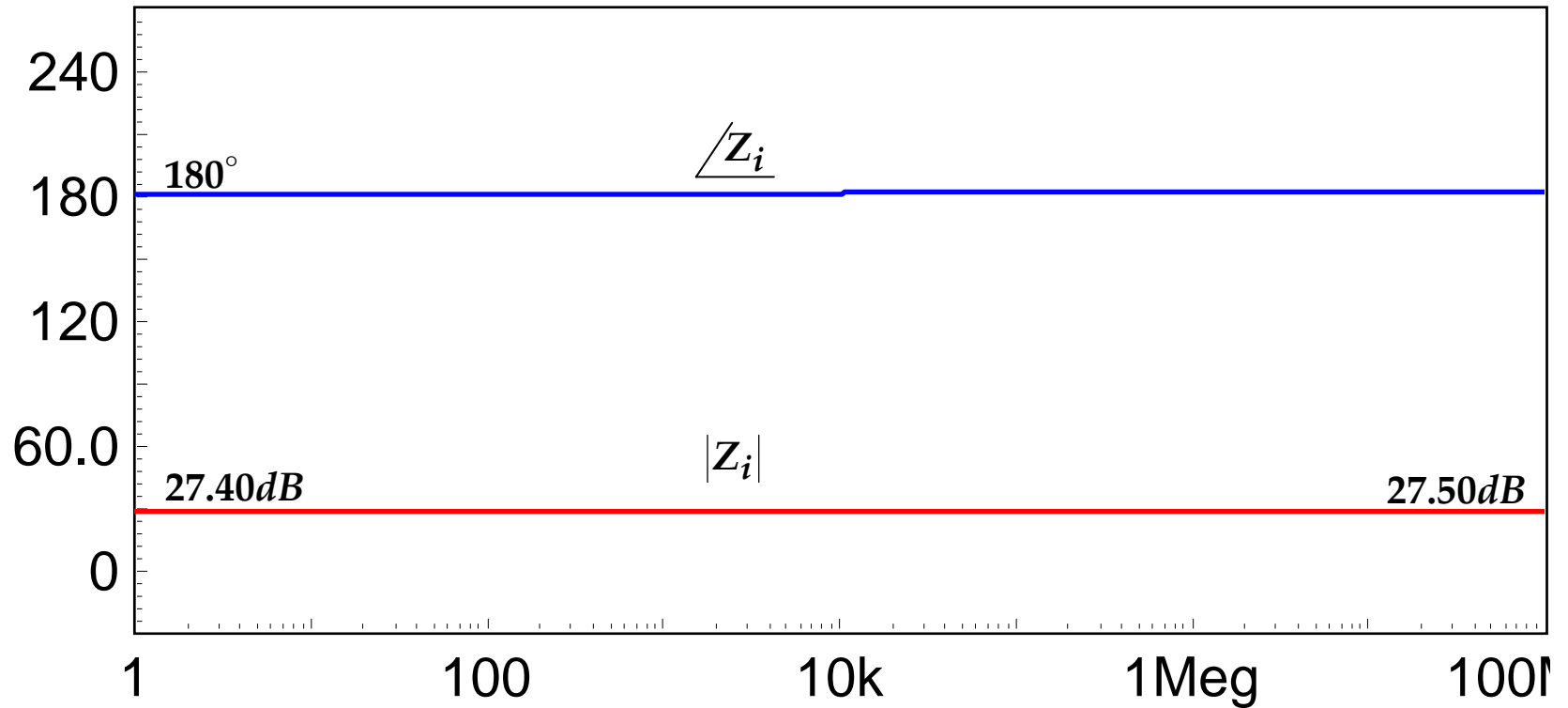

The result is in agreement with that predicted by the modified model.