

Middlebrook's

DESIGN-ORIENTED ANALYSIS

RULES AND TOOLS

Copyright 2007 by R.D.Middlebrook

CONTENTS

1. MOTIVATION AND BACKGROUND

The Design-Oriented Analysis (D-OA) Paradigm

1A. FETs AND BJTs ARE CCDs

Field-Effect Transistors and Bipolar Junction Transistors are Charge-Controlled Devices

Both can be represented by the same small-signal equivalent circuit model

2. LOW ENTROPY EXPRESSIONS

The Key to D-OA

3. NORMAL AND INVERTED POLES AND ZEROS

How to choose the gain at any frequency as the Reference Gain

4. AN IMPROVED FORMULA FOR QUADRATIC ROOTS

The Conventional Formula suffers from two congenital defects

5. APPROXIMATIONS AND ASSUMPTIONS

How to build Low Entropy Expressions with minimum work

6. PRODUCTS AND SUMS OF FACTORED POLE-ZERO EXPRESSIONS

Doing the Algebra on the Graph

7. THE I/O IT:

The Input/Output Impedance Theorem

How to find them directly from the Gain, thereby saving almost two-thirds of the work

8. NDI AND THE EET:

Null Double Injection and the Extra Element Theorem

How to find the contribution of a particular element to the transfer function

9. THE DT AND THE CT:

The Dissection Theorem and the Chain Theorem

How to find the gain of a multistage amplifier as the product of separately calculated low entropy factors

10. BASIC FEEDBACK

An Improved Formula expresses the closed-loop gain G in terms of only two quantities, the Specification G_∞ and the Loop Gain T

11. NDI AND THE GFT:

Null Double Injection and the General Feedback Theorem

How to identify and include nonidealities in a third quantity,

the Null Loop Gain T <http://www.RDMiddlebrook.com>

12. DNTI AND THE 2EET:

Double Null Triple Injection and the Two Extra Element Theorem

A short and easy way to find the poles and zeros of a circuit containing two reactances

13. DNTI AND THE 2GFT:

Double Null Triple Injection and the Two General Feedback Theorem

Why two injected test signals are needed in the general case

EXAMPLES

14. A 2CE/S FEEDBACK AMPLIFIER

A 2-stage Common-Emitter/-Source Amplifier

15. A REALISTIC IC FEEDBACK AMPLIFIER

16. A DESIGN SOLUTION TO DARLINGTON FOLLOWER INSTABILITY

17. THE INPUT FILTER PROBLEM OF A SWITCHED-MODE REGULATOR

18. CURRENT-PROGRAMMED SWITCHED-MODE REGULATOR