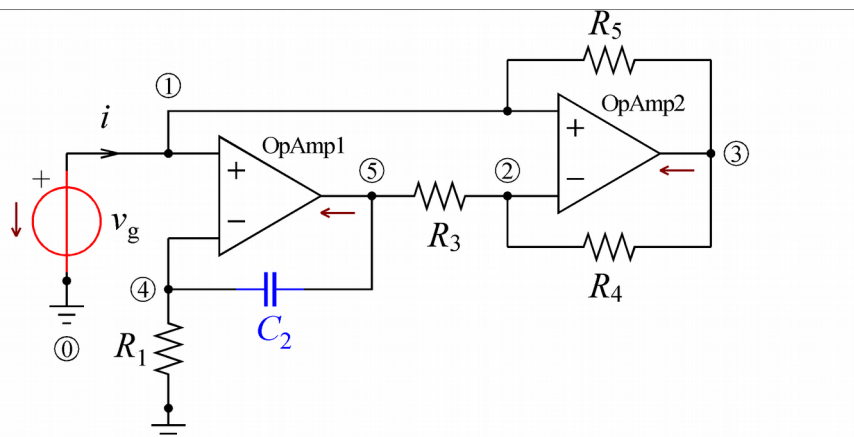


Symbolic analysis of linear electric circuits with Maxima CAS

Dejan V. Tošić, Milka M. Potrebić
 University of Belgrade – School of Electrical
 Engineering, Belgrade, Serbia
 tosic@etf.rs, milka_potrebic@etf.rs

Application of Free Software and Open Hardware, PSSOH 2019, International Conference, University of Belgrade – School of Electrical Engineering, Belgrade, Serbia, Oct. 26, 2019. <http://pssoh.etf.bg.ac.rs/>



```
(%i3) Riordan_response: SALECx(Riordan_shema);
(Riordan_response) [ V1 = Vg, V2 = Vg, V3 = -\frac{R4 Vg - C2 R1 R3 Vg s}{C2 R1 R3 s}, V4 = Vg, V5 = \frac{C2 R1 Vg s + Vg}{C2 R1 s}
, I_{OpAmp2} = \frac{R5 Vg + R4 Vg}{C2 R1 R3 R5 s}, I_{OpAmp1} = -\frac{C2 R3 Vg s + Vg}{C2 R1 R3 s}, I_{Vg} = -\frac{R4 Vg}{C2 R1 R3 R5 s} ]

(%i4) Zin: Vg/(-I["Vg"]), Riordan_response;
(Zin) \frac{C2 R1 R3 R5 s}{R4}

(%i5) Lsynthetic: Zin/s;
(Lsynthetic) \frac{C2 R1 R3 R5}{R4}
```

What is symbolic simulation

- **Symbolic simulation or analysis** is a formal technique to calculate the behavior or a characteristic of a system (e.g. digital system, electronic circuit, or continuous-time system) with an independent variable (sample index, time, or frequency), the dependent variables (sample values, signals, voltages, and currents), and (some or all) the element values represented by **symbols**.
- A **symbolic simulator** is a computer program that receives the system description as input and can automatically carry out the symbolic analysis and thus generate the **symbolic** expression for the desired system characteristic.
- P. Lin, **Symbolic Network Analysis**. Amsterdam, The Netherlands: Elsevier, 1991.
- G. Gielen and W. Sansen, **Symbolic Analysis for Automated Design of Analog Integrated Circuits**. Norwell, MA: Kluwer, 1991.
- L. Huelsman and G. Gielen (Eds.), **Symbolic Analysis of Analog Circuits: Techniques and Applications**. Norwell, MA: Kluwer, 1993.
- G. Gielen, P. Wambacq, and W. Sansen, “**Symbolic Analysis Methods and Applications for Analog Circuits: A Tutorial Overview**,” *Proceedings of the IEEE*, vol. 82, no. 2, pp. 286–304, Feb. 1994.
- F. Fernández, A. Rodríguez-Vázquez, J. Huertas, and G. Gielen, **Symbolic analysis techniques: Applications to analog design automation**. New York, NY: Wiley-IEEE Press, 1997.
- G. Shi, S. X.-D. Tan, E. T. Cuautle, **Advanced Symbolic Analysis for VLSI Systems**. New York, NY: Springer, 2014.

What is SALEC_x

- **SALEC_x** is a symbolic simulator for symbolic analysis of linear time-invariant finite circuits.
- SALEC_x is an acronym for **S**ymbolic **A**nalysis of **L**inear **E**lectric **C**ircuits with **M**axima.
- SALEC_x is distributed as **free/libre open-source** software under the Creative Commons license.
- SALEC_x is developed and maintained by Dr. *Dejan Tošić*, Full Professor, University of Belgrade – School of Electrical Engineering.

What is Maxima?

- **Computer Algebra System (CAS)** is software designed primarily for symbolic manipulation. CAS performs symbolic calculation one might do “by hand”, i.e. works with closed-form, analytic, expressions and manipulates them.
- **Maxima** is a free/libre open-source CAS for technical and mathematical computing.
- **wxMaxima** is a free/libre open-source user interface for the computer algebra system Maxima.

Seifedine Kadry, Pauly Awad, *Mathematics for Engineers and Science Labs Using Maxima*, Apple Academic Press, 2019.

Zachary Hannan, *wxMaxima for Calculus I and II*. Fairfield, CA: Solano Community College, 2015.

Why is it important?

- SALEC_x can be included in **Electric Circuit Theory** teaching and learning, at initial learning stages, to motivate and encourage students
- (1) to **solve** their homework and numerous circuit problems by automated computer-aided symbolic analysis, and
- (2) to **verify** their designs and confirm circuit analyses obtained traditionally by hand, i.e. by paper and pencil.
- SALEC_x free open-source code reveals the underlining algorithm in full detail, promotes a **better understanding** of the corresponding circuit analysis method, and might prompt some students to edit the code and **add** their own extensions and contributions.

From passive to active learner

- SALEC_x can help students to solve much **more** real-life circuit example problems compared to the relatively smaller number of problems they are willing to solve by hand.
- The example-problem-based learning paradigm can be supported.
- Allows novice students to grasp concepts and phenomena from circuit theory with **higher learning performance** and lower mental effort, until they reach expert levels.
- The role of a student might change from passive to **active learner** under the new learning paradigm.

Overcome the difficult barriers of mathematics

- Mastering circuit analysis requires some degree of practice and one must be adept in algebraic manipulation.
- The burden of algebraic manipulation causes the student to lose sight of the wood from the trees.
- In the classic method of study a student must overcome the difficult barriers of mathematics, which makes the subject very unattractive.


Ernst Mach, 1883

- When doing mathematics, instead of burdening the brain with the repetitive job of redoing numerical operations which have already been done before, it's possible to save that brainpower for more important situations by using symbols, instead, to represent those numerical calculations.
- Today, with computer algebra systems, such as Maxima/Macsyma, it is possible to calculate in minutes or hours the results that would (and did) years to accomplish by paper and pencil.
- SALECx can help students acquire a “functional understanding” of Electric Circuit Theory and foster mastery of the MNA (Modified Nodal Analysis) equation formulation.

Better insight

- Symbolic circuit response generated by SALEC_x, i.e. closed-form **analytic** expressions for circuit voltages and currents, can provide **better insight** than numerical solutions, e.g. obtained by SPICE.
- By inspection of the symbolic response, it might be immediately clear **how** a parameter (or an element value) **contributes** to the performance and **behavior** of the electric circuit.

In Medias Res

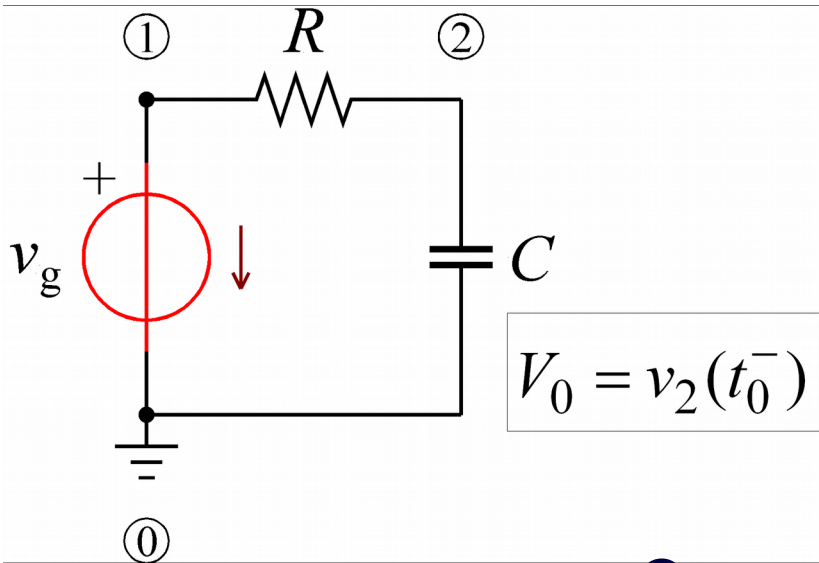

Let us solve a simple capacitor circuit.

Assume that SALEC_x has been installed in the directory "C:\SALEC_x\\" as the **mac** file "SALEC_x.mac".


Open a **wxMaxima** notebook and load SALEC_x.

wxMaxima 16.04.2 [Capacitor Simple Circuit.wmx]

File Edit View Cell Maxima Equations Algebra Calculus Simplify Plot Numeric Help

```
(%i1) load("C:\\SALECx\\SALECx.mac");  
(%o1) C:\\SALECx\\SALECx.mac
```

Create the Circuit Netlist

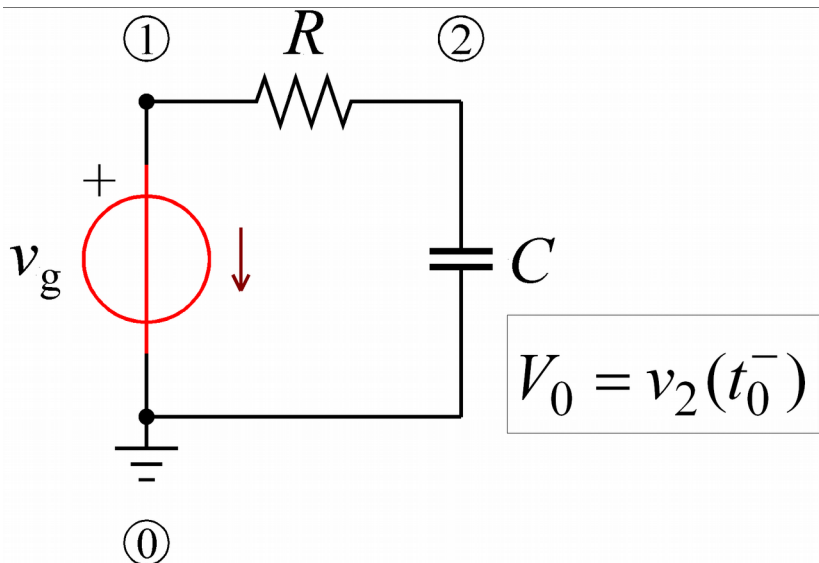

The circuit is textually specified as a list, **netlist**, of element specifications. Nodes are numbered by consecutive integers starting from zero, 0.

Each one-port circuit element is specified as a list of the form




```
[type, label, a, b, p]  
[type, label, a, b, p, IC]
```

type – string that specifies the element type: "R" for resistors, "C" for capacitors, "V" for voltage sources (independent voltage generators). **label** – string that uniquely identifies circuit element. **a** – positive terminal, integer, **b** – negative terminal, integer. **p** – parameter, element value, resistance, capacitance, excitation. **IC** – initial condition, initial voltage V_0 for capacitors $v_C(t_0^-)$.

```
(%i2) VgRCVo_Schema: [  
    ["V", "Vg", 1, 0, Vg],  
    ["R", "R", 1, 2, R],  
    ["C", "C", 2, 0, C, Vo]];  
(VgRCVo_Schema) [[V, Vg, 1, 0, Vg], [R, R, 1, 2, R], [C, C, 2, 0, C, Vo]]
```



If the circuit graph is not connected then ...

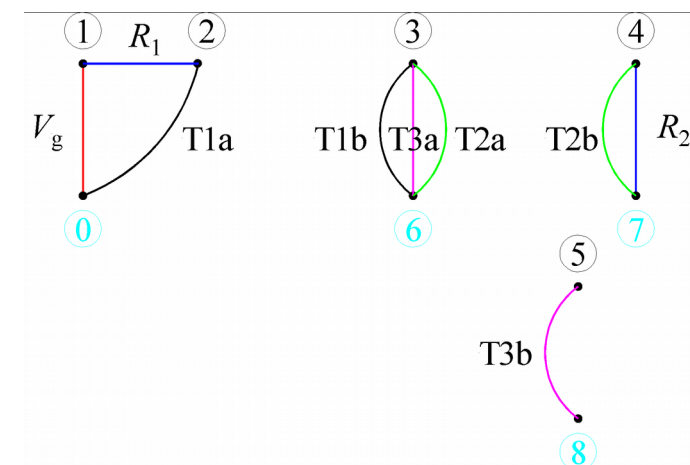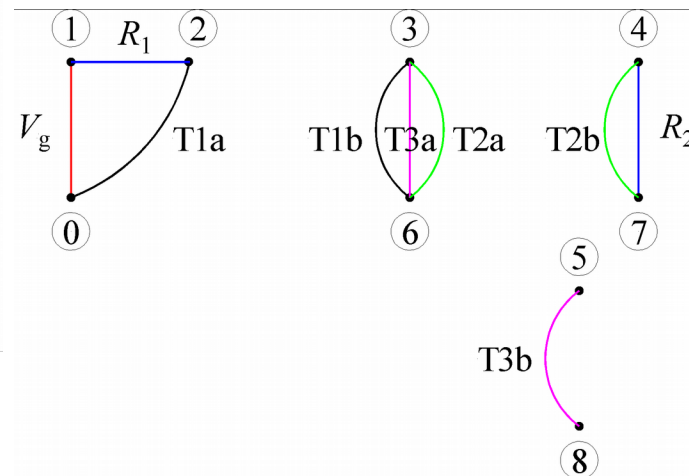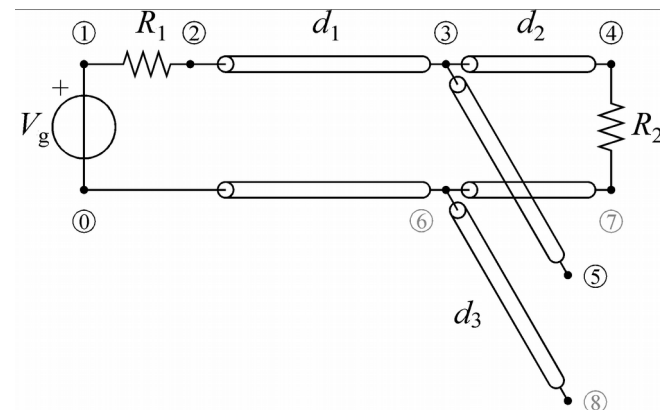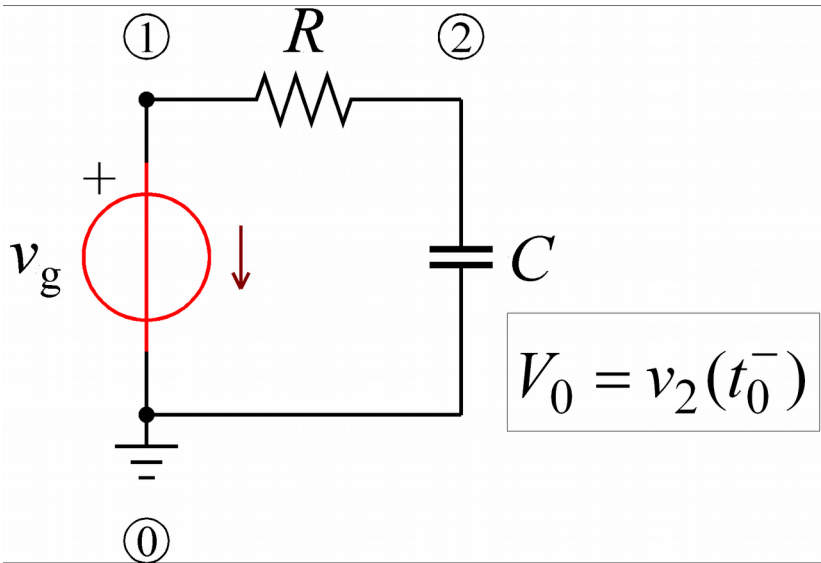- Identify the disconnected components.
- Choose one node in each component.
- Connect the chosen nodes, join together, to make the graph connected.



Node 6, Node 7, Node 8
are connected to **Node 0**.

SALECx Solve. Phasor Transform



SALECx can compute complex node voltages and some complex currents in the domain of the *Phasor Transform*. The initial conditions are ignored and the complex response corresponds to the sinusoidal steady-state response for a given angular frequency ω [rad/s]. I_{Vg} is the voltage source current directed from Node 1 to Node 0.

```
(%i3) VgRCVo_Response_PT: SALECx(VgRCVo_Schema, omega);
```

Phasor Transform at angular frequency ω


(VgRCVo_Response_PT)
$$\left[V_1 = Vg, V_2 = \frac{Vg}{\%i C R \omega + 1}, I_{Vg} = -\frac{\%i C Vg \omega}{\%i C R \omega + 1} \right]$$

```
(%i4) V2PT: V[2], VgRCVo_Response_PT;
```

(V2PT)
$$\frac{Vg}{\%i C R \omega + 1}$$

V2PT is the capacitor complex voltage.

SALEC_x Solve. Laplace Transform

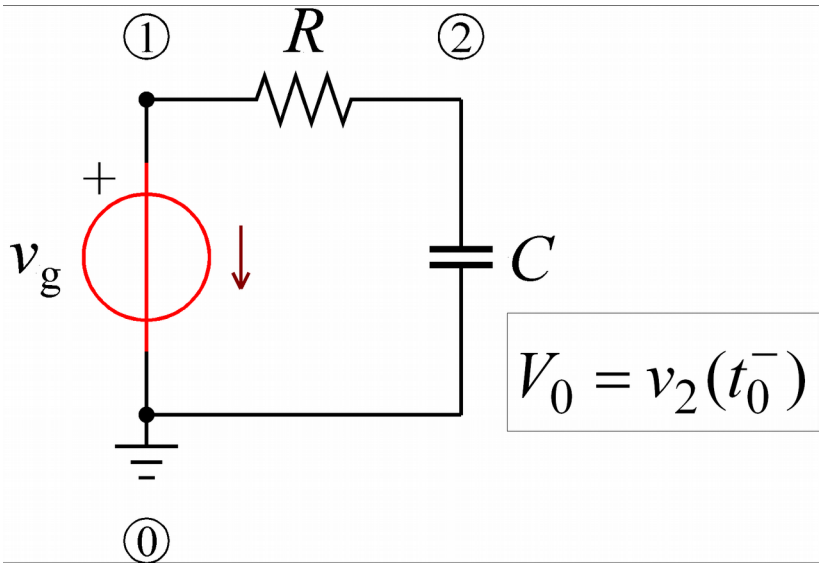

SALEC_x can compute complex node voltages and some complex currents in the domain of the *Unilateral Laplace Transform*. The initial conditions are taken into account and the *Laplace variable* is the complex angular frequency \mathbf{s} [rad/s], which is a SALEC_x reserved symbol.

```
(%i5) VgRCVo_Response: SALECx(VgRCVo_Schema),  
      SALECxPrint: true;
```

The option "**SALEC_xPrint: true**" instructs SALEC_x to print some analysis details. Use this option if you want to display the equations formulated by SALEC_x.

SALECx Solution

*Symbolic Analysis of Linear Electric Circuits with Maxima
SALECx version 1.0, Prof. Dr. Dejan Tošić, tosic@etf.rs*

Number of nodes excluding 0 node: 2

Electric circuit specification: $[[V, Vg, 1, 0, Vg], [R, R, 1, 2, R], [C, C, 2, 0, C, Vo]]$

Supported element: $[true, true, true]$

Element values: $[Vg, R, C]$

Initial conditions: $[false, false, Vo]$


MNA equations: $[\frac{V_1 - V_2}{R} + I_{Vg} = 0, V_2 C s - C Vo + \frac{V_2 - V_1}{R} = 0, V_1 = Vg]$

MNA variables: $[V_1, V_2, I_{Vg}]$

(VgRCVo_Response) $[V_1 = Vg, V_2 = \frac{C R Vo + Vg}{C R s + 1}, I_{Vg} = -\frac{C Vg s - C Vo}{C R s + 1}]$

SALECx formulates the **Modified Nodal Analysis (MNA)** equations to symbolically solve a circuit.

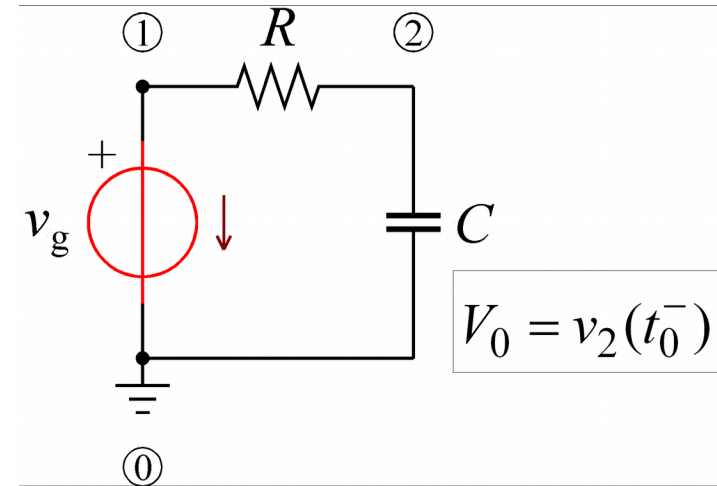Complex node voltages and some complex currents are returned as the complex response in terms of parameters, element values, initial conditions and the Laplace variable, complex frequency, **s**.




Postprocessing SALEC_x Solution

```
(%i6) V2s: V[2], VgRCVo_Response, Vg=Vstep/s;
```

```
(V2s) 
$$\frac{\frac{Vstep}{s} + C R V_0}{C R s + 1}$$

```

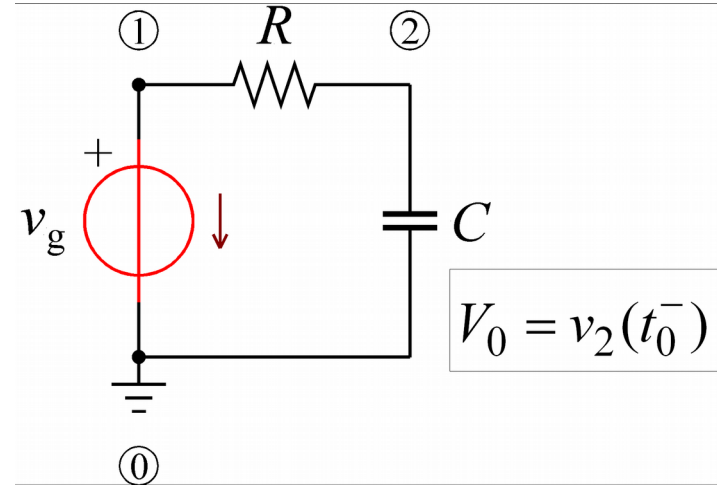

The excitation is assumed to be a step function. The time-domain transient response is computed by the *Inverse Unilateral Laplace Transform*, the Maxima `ilt` function.

```
(%i7) v2ilt: ilt(V2s,s,t), expand;
```

```
(v2ilt) 
$$-Vstep \%e^{-\frac{t}{C R}} + V_0 \%e^{-\frac{t}{C R}} + Vstep$$

```

```
(%i8) v2t: factorout(v2ilt,Vstep,V_0);
```


```
(v2t) 
$$(V_0 - Vstep) \%e^{-\frac{t}{C R}} + Vstep$$

```

What does SALEC_x return?

- SALEC_x returns the complex response as a list of equations of the form $V[\text{node}] = \text{expression}$ or $I[\text{"id"}] = \text{expression}$, or $I[\text{"id"}, \text{node}] = \text{expression}$.
- Complex node voltages are $V[1]$, $V[2]$, $V[3]$, ...
- Complex currents are the currents of the ports which **cannot** be expressed in terms of node voltages.
- The symbol **s** is a SALEC_x reserved symbol.
- The symbols **V** and **I** are Maxima arrays.

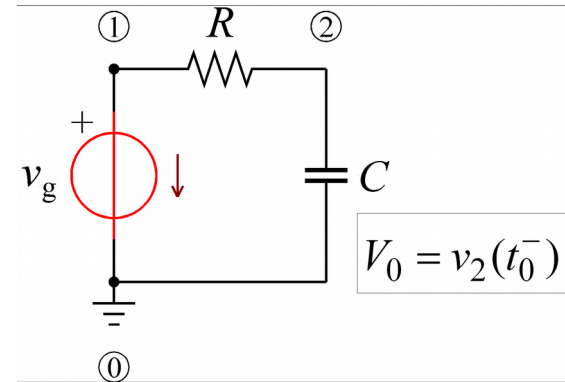
$$\left[V_1 = V_g, V_2 = \frac{C R V_0 + V_g}{C R s + 1}, I_{V_g} = - \frac{C V_g s - C V_0}{C R s + 1} \right]$$




How does wxMaxima prints $V[n]$?

- wxMaxima prints $V[1]$, $V[2]$, $V[3]$, ... as subscripted italic symbols V_1 , V_2 , V_3 , ...
- If the voltage source is specified as `["V", "Vg", 1, 0, Vg]` then ...
- ... the corresponding voltage source current is `I["Vg"]` and wxMaxima prints that designation as subscripted italic symbol I_{Vg} omitting the quotes "".
- The current is directed from Node 1 to Node 0. It is referred to as a current into pin 1.
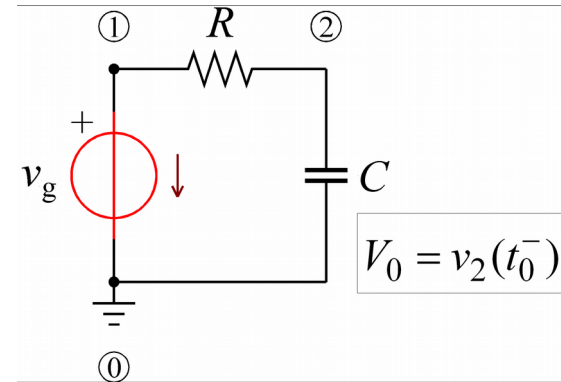
$$\left[V_1 = Vg, V_2 = \frac{C R V_0 + Vg}{C R s + 1}, I_{Vg} = - \frac{C Vg s - C V_0}{C R s + 1} \right]$$



Proof-of-concept symbolic analysis

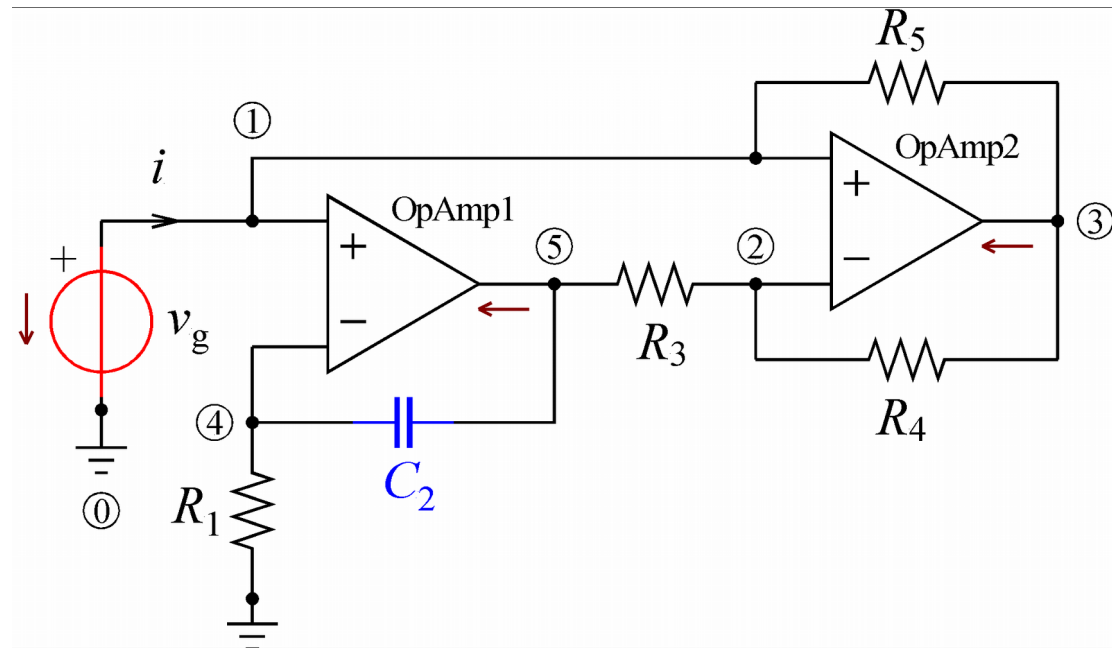

Synthetic inductor, which is realized with the Riordan gyrator network, can serve as a theoretical basis for implementation of **coilless** inductors. The circuit is **inductorless** but, theoretically, the impedance seen by the source is purely inductive.

```

wxMaxima 16.04.2 [ Riordan Gyrator Synthetic Inductor.wmx ]
File Edit View Cell Maxima Equations Algebra Calculus Simplify Plot Numeric Help

(%i1) load("C:\\SALECX\\SALECX.mac");
(%o1) C:\\SALECX\\SALECX.mac

(%i2) Riordan_shema: [
["V", "Vg", 1, 0, Vg],
["OpAmp", "OpAmp1", [1,4], 5],
["R", "R1", 4, 0, R1],
["C", "C2", 4, 5, C2],
["R", "R3", 5, 2, R3],
["OpAmp", "OpAmp2", [1,2], 3],
["R", "R4", 2, 3, R4],
["R", "R5", 1, 3, R5]
] $


(%i3) Riordan_response: SALECX(Riordan_shema);
(Riordan_response) [ V1=Vg, V2=Vg, V3=-\frac{R4 Vg - C2 R1 R3 Vg s}{C2 R1 R3 s},
V4=Vg, V5=\frac{C2 R1 Vg s + Vg}{C2 R1 s}, I_{OpAmp2}=\frac{R5 Vg + R4 Vg}{C2 R1 R3 R5 s},
I_{OpAmp1}=-\frac{C2 R3 Vg s + Vg}{C2 R1 R3 s}, I_{Vg}=-\frac{R4 Vg}{C2 R1 R3 R5 s} ]

(%i4) Zin: Vg/(-I["Vg"]), Riordan_response;
(Zin) \frac{C2 R1 R3 R5 s}{R4}

(%i5) Lsynthetic: Zin/s;
(Lsynthetic) \frac{C2 R1 R3 R5}{R4}

Welcome to wxMaxima Saving successful.
    
```

OTA-C lowpass and highpass filter

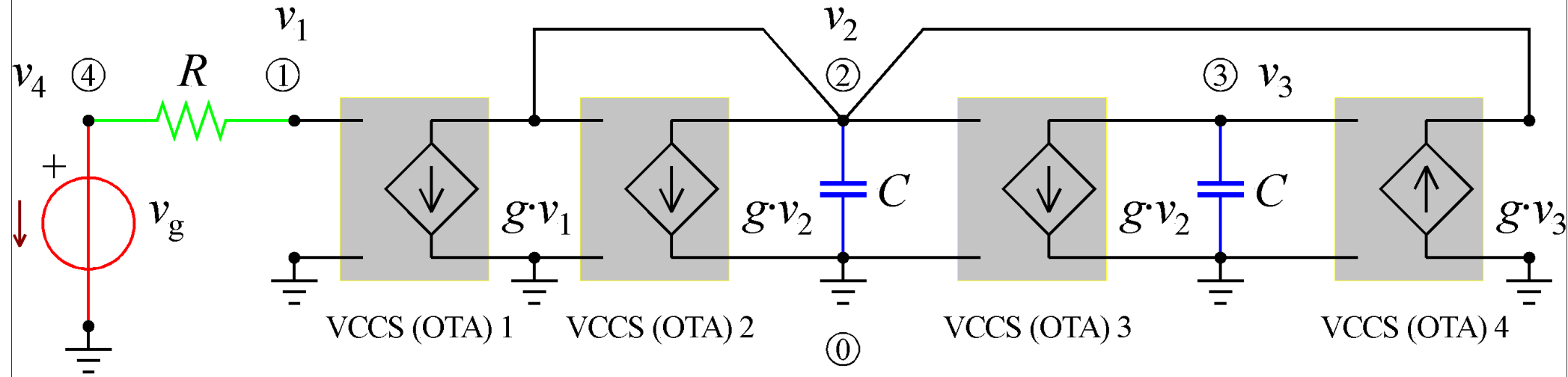

```
(%i2) OTA_C_shema: [
  ["V", "Vg", 4, 0, Vg],
  ["R", "R", 4, 1, R],
  ["VCCS", "OTA1", [1,0], [2,0], g],
  ["VCCS", "OTA2", [2,0], [2,0], g],
  ["VCCS", "OTA3", [2,0], [3,0], g],
  ["VCCS", "OTA4", [3,0], [0,2], g],
  ["C", "C1", 2, 0, C],
  ["C", "C2", 3, 0, C]
]$
```


```
(%i4) Hs2bandpass: V[2]/Vg, OTA_C_response;
(Hs2bandpass) - \frac{C g s}{C^2 s^2 + C g s + g^2}
```

```
(%i5) Hs3lowpass: V[3]/Vg, OTA_C_response;
(Hs3lowpass) \frac{g^2}{C^2 s^2 + C g s + g^2}
```

```
(%i3) OTA_C_response: SALECx(OTA_C_shema);
```

```
(OTA_C_response) [ V1 = Vg, V2 = - \frac{C Vg g s}{C^2 s^2 + C g s + g^2}, V3 = \frac{Vg g^2}{C^2 s^2 + C g s + g^2}, V4 = Vg, I_Vg = 0 ]
```

Wilkinson power divider

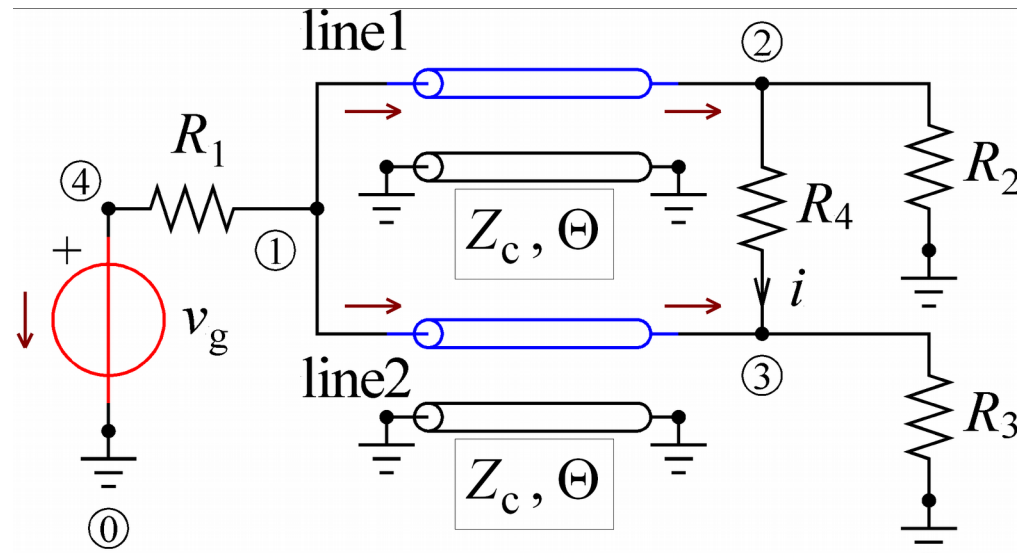

Wilkinson power divider is realized with ideal lossless transmission line sections. The corresponding symbolic analysis with SALECx, performed in the Phasor Transform domain, verifies that the circuit equally splits (divides) input power to the loads.

The reference directions for the output transmission line currents are OUT OF pin 2 and OUT OF pin 3.

```
wxMaxima 16.04.2 [ Wilkinson Power Divider.wmx ]
File Edit View Cell Maxima Equations Algebra Calculus Simplify Plot Numeric Help

(%i1) load("C:\\SALECx\\SALECx.mac");
(%o1) C:\\SALECx\\SALECx.mac

(%i2) Wilkinson_shema: [
["V", "Vg", 4, 0, Vg],
["R", "R1", 1, 4, R],
["R", "R2", 2, 0, R],
["R", "R3", 3, 0, R],
["R", "R4", 2, 3, 2*R],
["T", "T1", [1,0], [2,0], [sqrt(2)*R, pi/2]],
["T", "T2", [1,0], [3,0], [sqrt(2)*R, pi/2]]
] $


(%i3) Wilkinson_response:
SALECx(Wilkinson_shema, omega),
ratsimp;
Phasor Transform at angular frequency  $\omega$ 
(Wilkinson_response) [  $V_1 = \frac{Vg}{2}$ ,  $V_2 = -\frac{\%i Vg}{2^{3/2}}$ ,  $V_3 = -\frac{\%i Vg}{2^{3/2}}$ ,  $V_4 = Vg$ 
,  $I_{T2,3} = -\frac{\%i Vg}{2^{3/2} R}$ ,  $I_{T2,1} = \frac{Vg}{4 R}$ ,  $I_{T1,2} = -\frac{\%i Vg}{2^{3/2} R}$ ,
 $I_{T1,1} = \frac{Vg}{4 R}$ ,  $I_{Vg} = -\frac{Vg}{2 R}$  ]

(%i4) is(
ev(V[2]=V[3], Wilkinson_response)
);
(%o4) true

Welcome to wxMaxima Saving successful.
```

Ideal Transmission Line Section

Laplace Transform

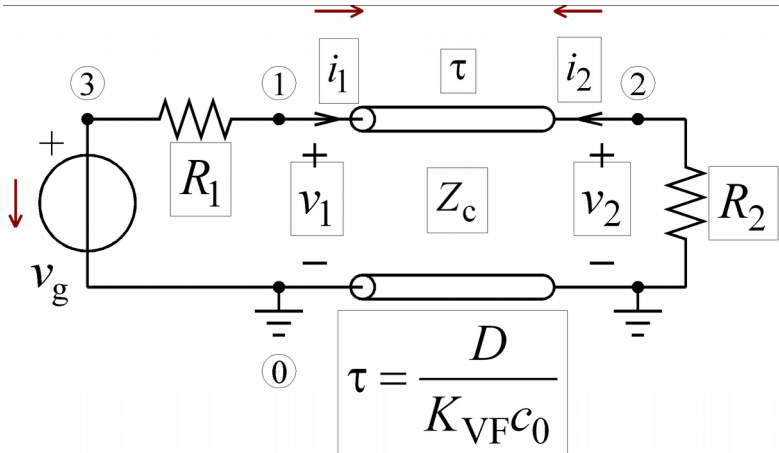

Doubly terminated lossless transmission line section. The corresponding symbolic analysis with SALECx, performed in the Unilateral Laplace Transform domain, verifies that the circuit acts as a delay line.

The reference directions for the transmission line currents are into the corresponding pins 1 and 2.

```
wxMaxima 16.04.2 [ Transmission Line.wxmx ]
File Edit View Cell Maxima Equations Algebra Calculus Simplify Plot Numeric Help

(%i1) load("C:\\SALECx\\SALECx.mac");
(%o1) C:\\SALECx\\SALECx.mac


(%i2) TLine_shema: [
["V", "Vg", 3, 0, Vg],
["R", "R1", 3, 1, Zc],
["T", "TL", [1,0], [2,0], [Zc,tau]],
["R", "R2", 2, 0, Zc]
]$,

(%i3) TLine_response: SALECx(TLine_shema);
(TLine_response) [ V_1 = \frac{Vg}{2}, V_2 = \frac{Vg \% e^{-s \tau}}{2}, V_3 = Vg, I_{TL,2} =
-\frac{Vg \% e^{-s \tau}}{2 Zc}, I_{TL,1} = \frac{Vg}{2 Zc}, I_{Vg} = -\frac{Vg}{2 Zc} ]

(%i4) Vout: V[2], TLine_response;
(Vout) \frac{Vg \% e^{-s \tau}}{2}

Welcome to wxMaxima Saving successful.
```


Three-phase Circuit: netlist

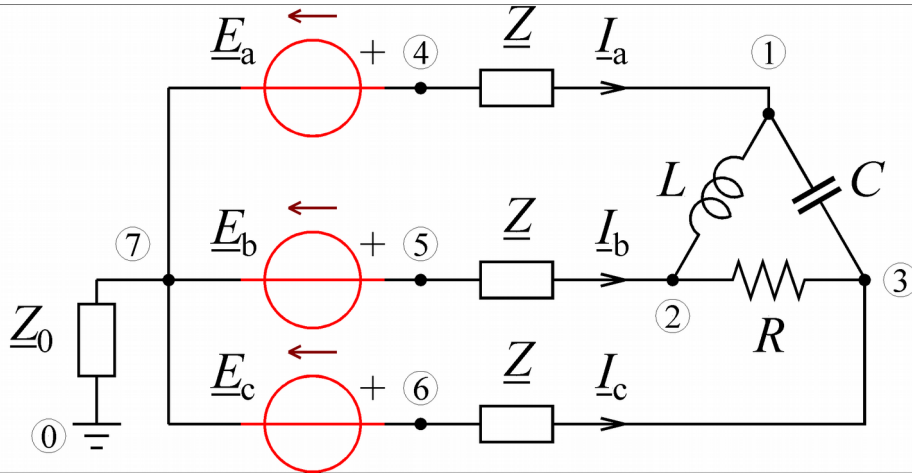


```

wxMaxima 16.04.2 [ Three-Phase Circuit.wxmx ]
File Edit View Cell Maxima Equations Algebra Calculus Simplify Plot Numeric Help

[ (%i1) load("C:\\SALECx\\SALECx.mac");
[ (%o1) C:\\SALECx\\SALECx.mac
[ (%i2) domain: complex$
[ (%i3) declare([Ea, Eb, Ec, Z, Z0],
[ complex)$
[ (%i4) declare([C, L, R, omega],
[ real)$
[ (%i5) assume(C > 0, L > 0, R > 0, omega > 0)$
[ (%i6) alias(j, %i)$
[ (%i7) ThreePhase_shema: [
[ ["Z", "Z0", 7, 0, Z0],
[ ["V", "Ea", 4, 7, Ea],
[ ["V", "Eb", 5, 7, Eb],
[ ["V", "Ec", 6, 7, Ec],
[ ["Z", "Zv1", 1, 4, Z],
[ ["Z", "Zv2", 2, 5, Z],
[ ["Z", "Zv3", 3, 6, Z],
[ ["L", "L", 1, 2, L],
[ ["R", "R", 2, 3, R],
[ ["C", "C", 3, 1, C]
] ]$

Welcome to wxMaxima Saving successful.
    
```


Three-phase Circuit: response

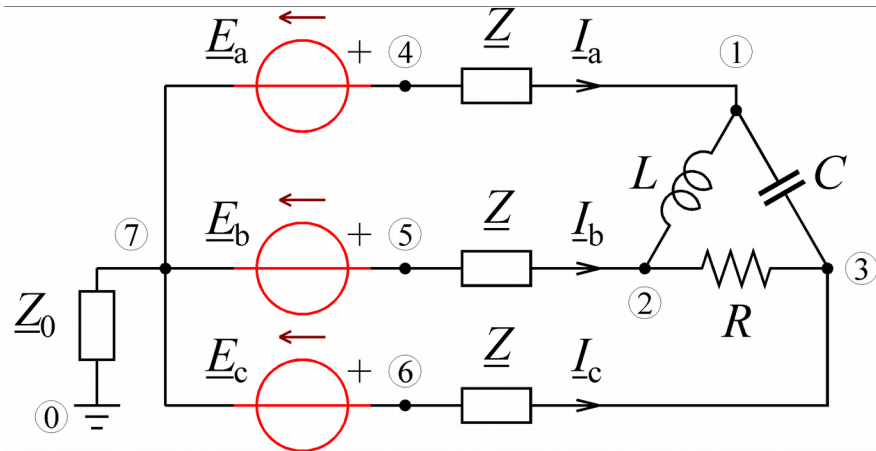

```

wxMaxima 16.04.2 [ Three-Phase Circuit.wmx ]
File Edit View Cell Maxima Equations Algebra Calculus Simplify Plot Numeric Help

(%i8) ThreePhase_response:
      SALECx(ThreePhase_shema, omega)$
Phasor Transform at angular frequency  $\omega$ 


(%i9) ThreePhase_response_CL:
      ThreePhase_response,
      C = 1/(sqrt(3)*R*omega),
      L = sqrt(3)*R/omega$

(%i10) ThreePhase_response_E:
      ThreePhase_response_CL,
      Eb=Ea*exp(-j*2*pi/3),
      Ec=Ea*exp(-j*4*pi/3),
      ratsimp;

(ThreePhase_response_E) [  $V_1 = \frac{Ea R}{Z+R}$ ,  $V_2 = -\frac{(3i + \sqrt{3}) Ea R}{2\sqrt{3}Z + 2\sqrt{3}R}$ ,  $V_3 =$ 
 $\frac{(3i - \sqrt{3}) Ea R}{2\sqrt{3}Z + 2\sqrt{3}R}$ ,  $V_4 = Ea$ ,  $V_5 = -\frac{(\sqrt{3}i + 1) Ea}{2}$ ,
 $V_6 = \frac{(\sqrt{3}i - 1) Ea}{2}$ ,  $V_7 = 0$ ,  $I_{Ec} = -\frac{(\sqrt{3}i - 1) Ea}{2Z + 2R}$ ,
 $I_{Eb} = \frac{(\sqrt{3}i + 1) Ea}{2Z + 2R}$ ,  $I_{Ea} = -\frac{Ea}{Z+R}$  ]

Welcome to wxMaxima Saving successful.
    
```

Three-phase Circuit: currents

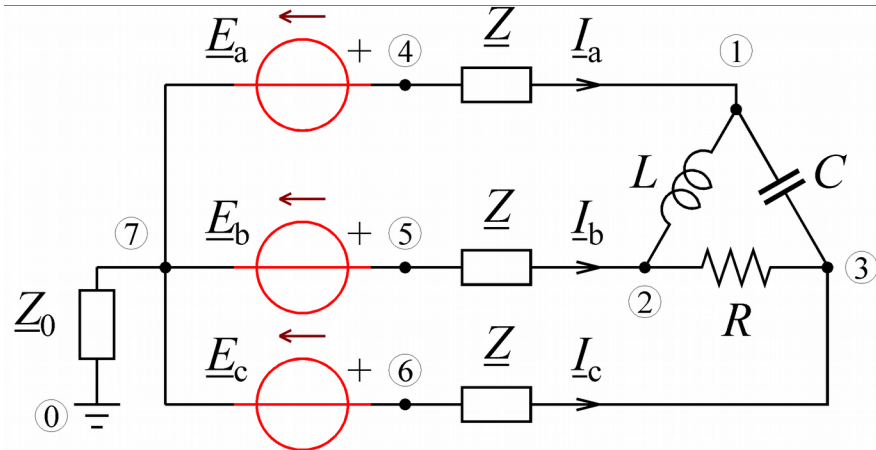

```

wxMaxima 16.04.2 [ Three-Phase Circuit.wmx ]
File Edit View Cell Maxima Equations Algebra Calculus Simplify Plot Numeric Help

(%i11) I12: (V[1]-V[2])/(j*L*omega),
ThreePhase_response_E,
L=sqrt(3)*R/omega, ratsimp;
(I12) - (sqrt(3) %i - 1) Ea
      2 Z + 2 R

(%i12) I23: (V[2]-V[3])/R,
ThreePhase_response_E, ratsimp;
(I23) - sqrt(3) %i Ea
      Z + R

(%i13) I31: (V[3]-V[1])*(j*C*omega),
ThreePhase_response_E,
C=1/(sqrt(3)*R*omega), ratsimp;
(I31) - (sqrt(3) %i + 1) Ea
      2 Z + 2 R

Welcome to wxMaxima Saving successful.
    
```

Three-phase Circuit: Symmetrical Components


wxMaxima 16.04.2 [Three-Phase Circuit.wmx]

File Edit View Cell Maxima Equations Algebra Calculus Simplify Plot Numeric Help

```
(%i14) IsymmetricalComponents:
invert(matrix(
[1, 1, 1],
[1, (exp(j*2*%pi/3))^2, exp(j*2*%pi/3)],
[1, exp(j*2*%pi/3), (exp(j*2*%pi/3))^2]
)
)
. matrix([I12], [I23], [I31]),
ratsimp, factor;
```

(IsymmetricalComponents)
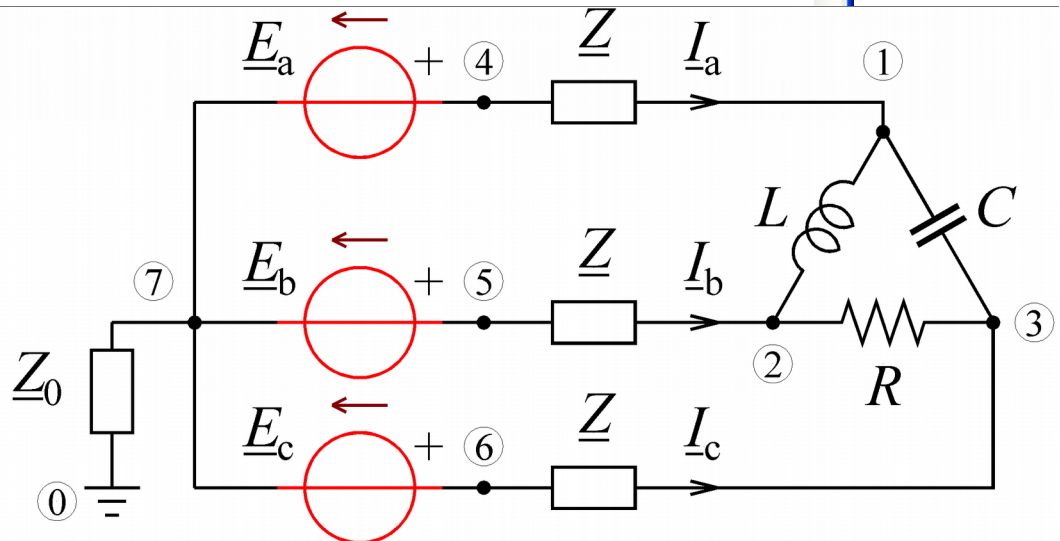
$$\begin{bmatrix} -\frac{2\%i E_a}{\sqrt{3}(Z+R)} \\ -\frac{\%i(\sqrt{3}\%i-1)E_a}{2\sqrt{3}(Z+R)} \\ 0 \end{bmatrix}$$



Conclusion

- Automated computer-aided symbolic analysis of linear time-invariant finite electric circuits, implemented in software **SALECx**, has been presented.
- Symbolic simulator SALECx, written in Maxima CAS, receives a textual circuit description in the form of a **netlist** and generates closed-form analytical expressions for the circuit response.
- The analysis is performed in the **complex domain** of the Unilateral Laplace Transform or the Phasor transform.
- Engineers, educators and students can **benefit** from SALECx when exploring design alternatives, verifying the circuit performance, or carrying out the proof-of-concept analyses.
- The **future directives** might be an integration of SALECx with a schematic capture editor so the user can specify circuits pictorially.

References: Classics

- C. A. Desoer, E. S. Kuh, *Basic Circuit Theory*. New York, NY: McGraw-Hill, 1969.
- L. O. Chua, C. A. Desoer, and E. S. Kuh, *Linear and Nonlinear Circuits*. New York, NY: McGraw-Hill, 1987.
- Hendrik Wade Bode, *Network Analysis and Feedback Amplifier Design*. New York, NY: D. Van Nostrand, 1945. (Reprinted 1953.)

References: Contemporary

- C. K. Alexander, M. N. O. Sadiku, *Fundamentals of Electric Circuits*, 6/e. New York, NY: McGraw-Hill, 2017.
- J. W. Nilsson, S. A. Riedel, *Electric Circuits*, 10/e. Upper Saddle River, NJ: Prentice Hall, 2015.
- J. D. Irwin, R. M. Nelms, *Basic Engineering Circuit Analysis*, 11/e. Hoboken, NJ: Wiley, 2015.
- J. A. Svoboda, R. C. Dorf, *Introduction to Electric Circuits*, 9/e. Hoboken, NJ: Wiley, 2014.
- W. H. Hayt, Jr., J. E. Kemmerly, S. M. Durbin, *Engineering circuit analysis*, 8/e. New York, NY: McGraw-Hill, 2012.


References: Special

- F. N. Najm, *Circuit Simulation*. Hoboken, New Jersey: John Wiley & Sons, 2010.
- O. Wing, *Classical Circuit Theory*. New York, NY: Springer Science+Business Media, LLC, 2008.
- W.-K. Chen (Ed.), *Circuit Analysis and Feedback Amplifier Theory*. Boca Raton, FL: CRC Press, Taylor & Francis Group, 2006.
- A. L. Shenkman, *Transient Analysis of Electric Power Circuits Handbook*. Dordrecht, The Netherlands: Springer, 2005.
- A. L. Shenkman, *Circuit Analysis for Power Engineering Handbook*. Dordrecht, The Netherlands: Springer, 1998.
- P. R. Clayton, *Analysis of Multiconductor Transmission Lines*, 2/e. Hoboken, NJ: Wiley IEEE Press, 2008.


Acknowledgments

- We thank Dr. **Predrag Pejović**, Full Professor, University of Belgrade – School of Electrical Engineering, for permanent encouragement and valuable discussions related to the SALECx project.
- This work was supported by the **Ministry of Education, Science, and Technological Development** of the Republic of Serbia.

SALEC_x with MaximaOnAndroid

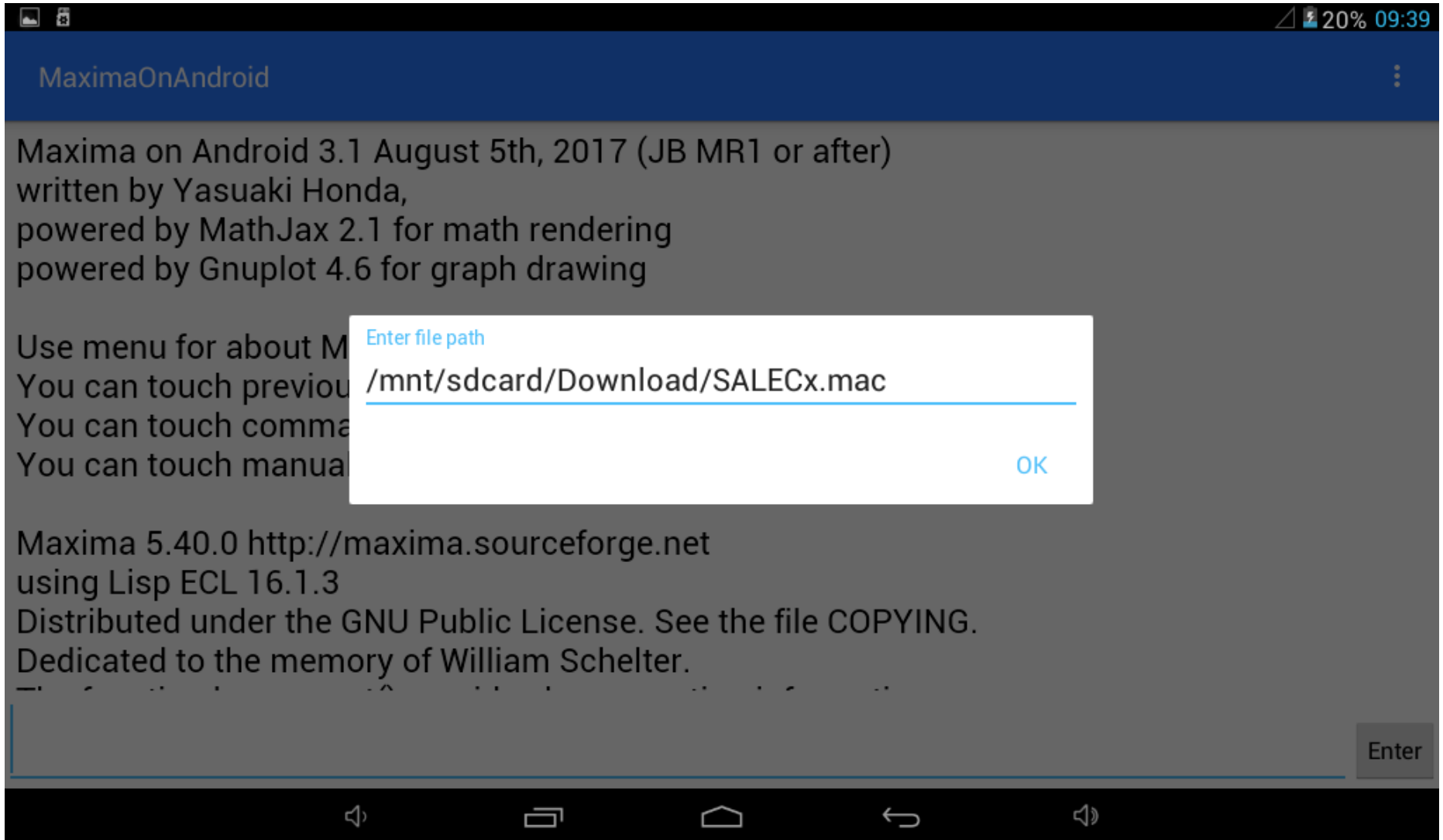

Netlist Script

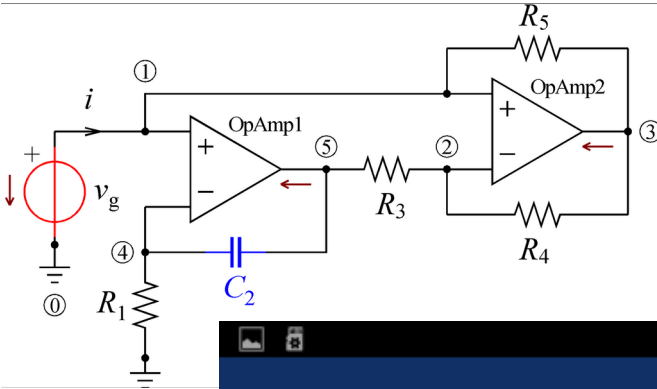


```
MaximaOnAndroid
then (print("Symbolic Analysis of Linear Electric Circuits with Maxima"),
print("SALECx version 1.0, Prof. Dr. Dejan Tomic, tosic@etf.rs"),
print("Number of nodes excluding 0 node: ",n_),
print("Electric circuit specification:",circuit_),
print("Supported element: ",m_),
print("Element values: ",e_),
print("Initial conditions: ",ic_),
print("MNA equations: ",eq_),
print("MNA variables: ",var_),
(%i4) SALECxPrint: false

/data/data/jp.yhonda/cache/userscript1493403953.mac

(%i5)
batch("/data/data/jp.yhonda/cache/userscript1493403953. Enter
```

Enter file path
/mnt/sdcard/Download/Riordan.mac
OK

Behavior

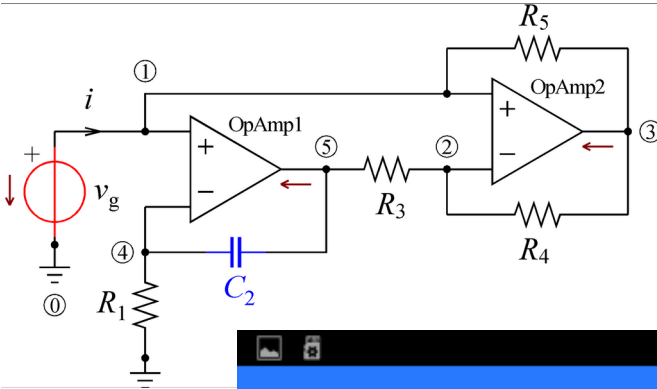

```
(%i9) ev(Zin:Vg/(-I["Vg"]),Riordan_response)
```

$$\frac{C_2 R_1 R_3 R_5 s}{R_4}$$

```
(%i10) Lsynthetic:Zin/s
```

$$\frac{C_2 R_1 R_3 R_5}{R_4}$$


```
/data/data/jp.yhonda/cache/userscript189093561.mac
```

```
(%i11)
```

```
batch("/data/data/jp.yhonda/cache/userscript189093561.n 
```



Response

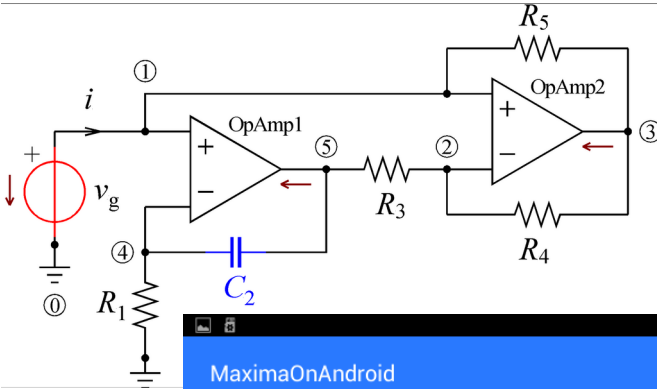

```
MaximaOnAndroid
```

```
read and interpret file: /data/data/jp.yhonda/cache/userscript189093561.mac
(%i6) Riordan_schema:[["V","Vg",1,0,Vg],["OpAmp","OpAmp1",[1,4],5],
["R","R1",4,0,R1],["C","C2",4,5,C2],["R","R3",5,2,R3],
["OpAmp","OpAmp2",[1,2],3],["R","R4",2,3,R4],
["R","R5",1,3,R5]]
(%i7) Riordan_response:SALECx(Riordan_schema)
ARRSTORE: use_fast_arrays=false; allocate a new property hash table for |$j|
ARRSTORE: use_fast_arrays=false; allocate a new property hash table for |$v|
```

$$\left[V_1 = V_g, V_2 = V_g, V_3 = -\frac{R_4 V_g - C_2 R_1 R_3 V_g s}{C_2 R_1 R_3 s}, V_4 = V_g, V_5 = \frac{C_2 R_1 V_g s + V_g}{C_2 R_1 s}, I_{OpAmp2} = \right.$$

```
MaximaOnAndroid
```

$$\left. \frac{+ V_g}{C_2 R_1 R_3 R_5 s}, I_{OpAmp2} = \frac{R_5 V_g + R_4 V_g}{C_2 R_1 R_3 R_5 s}, I_{OpAmp1} = -\frac{C_2 R_3 V_g s + V_g}{C_2 R_1 R_3 s}, I_{Vg} = -\frac{R_4 V_g}{C_2 R_1 R_3 R_5 s} \right] 3561.n \text{ Enter}$$

```
MaximaOnAndroid
```

```
(%i7) Riordan_response:SALECx(Riordan_schema)
ARRSTORE: use_fast_arrays=false; allocate a new property hash table for |$j|
ARRSTORE: use_fast_arrays=false; allocate a new property hash table for |$v|
```

$$\left[V_1 = V_g, V_2 = V_g, V_3 = -\frac{R_4 V_g - C_2 R_1 R_3 V_g s}{C_2 R_1 R_3 s}, V_4 = \right.$$

(%i8) transpose(Riordan_response)





$$\begin{pmatrix} V_1 = V_g \\ V_2 = V_g \\ V_3 = -\frac{R_4 V_g - C_2 R_1 R_3 V_g s}{C_2 R_1 R_3 s} \\ V_4 = V_g \\ V_5 = \frac{C_2 R_1 V_g s + V_g}{C_2 R_1 s} \\ I_{OpAmp2} = \frac{R_5 V_g + R_4 V_g}{C_2 R_1 R_3 R_5 s} \\ I_{OpAmp1} = -\frac{C_2 R_3 V_g s + V_g}{C_2 R_1 R_3 s} \\ I_{Vg} = -\frac{R_4 V_g}{C_2 R_1 R_3 R_5 s} \end{pmatrix}$$

(%i9) ev(Zin:Vg/(-I["Vg"]),Riordan_response)

```
batch("/data/data/jp.yhonda/cac Enter
```

```
batch("/data/data/jp.yhonda/cache/userscript189093561.n Enter
```

About

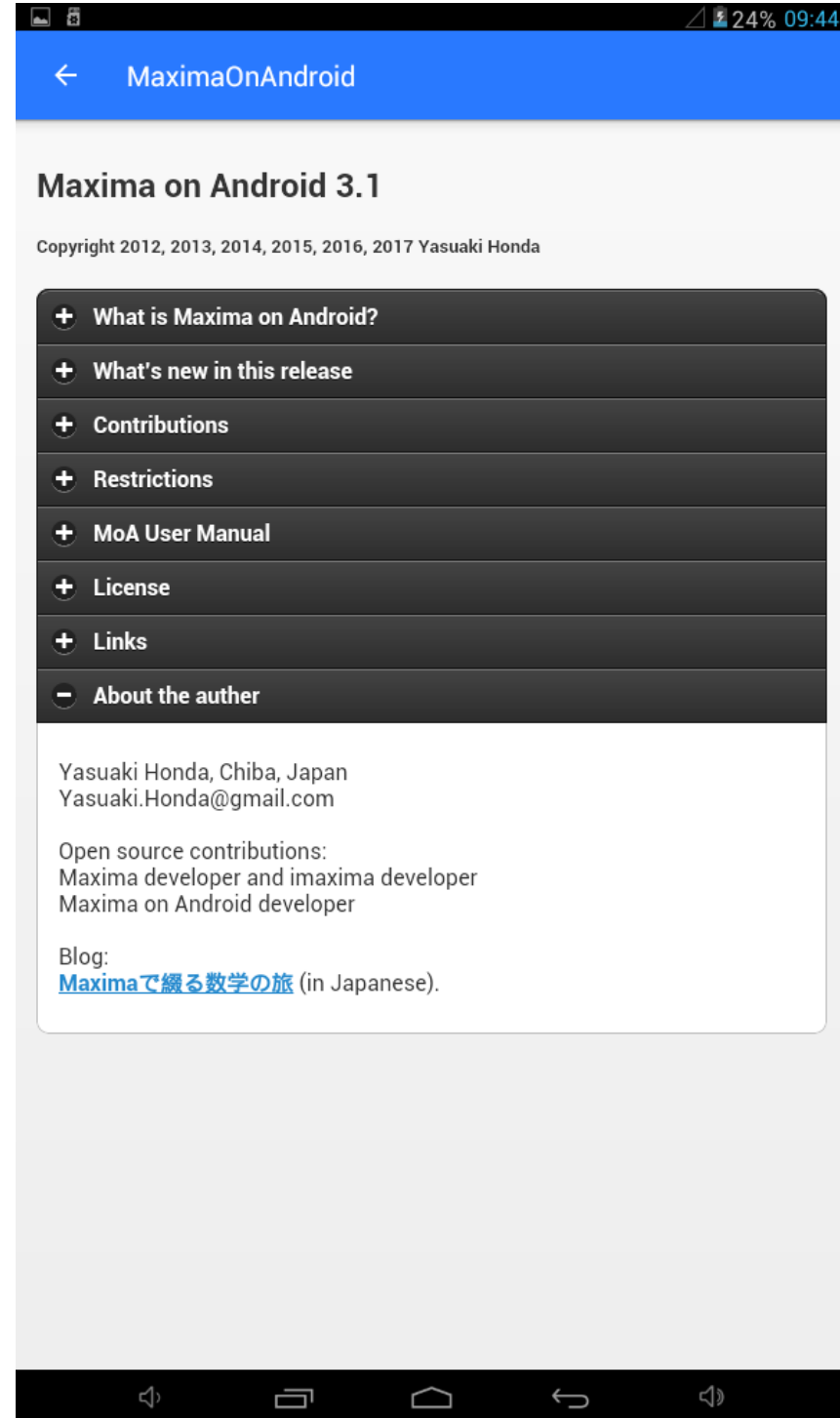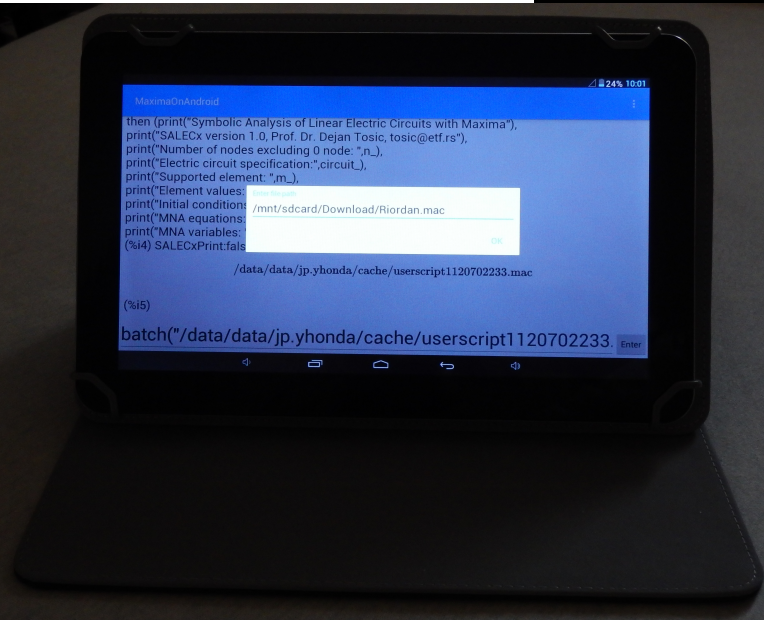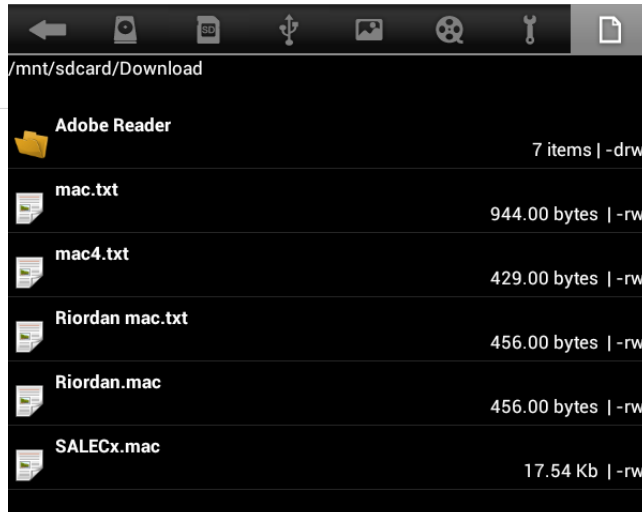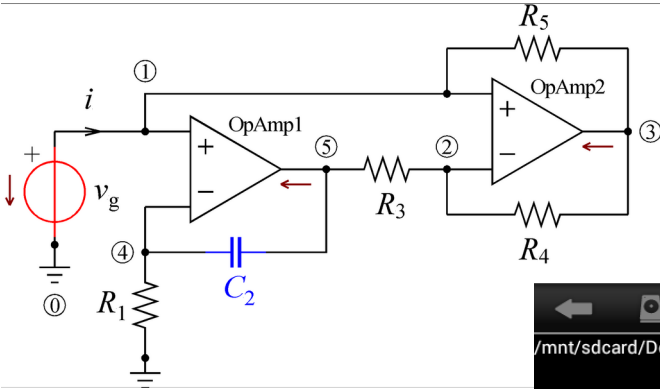

MaximaOnAndroid

Maxima on Android 3.1

Copyright 2012, 2013, 2014, 2015, 2016, 2017 Yasuaki Honda

- + What is Maxima on Android?
- + What's new in this release
- + Contributions
- + Restrictions
- + MoA User Manual
- + License
- + Links
- About the author

Yasuaki Honda, Chiba, Japan
Yasuaki.Honda@gmail.com

Open source contributions:
Maxima developer and imaxima developer
Maxima on Android developer

Blog:
[Maximaで繰る数学の旅](#) (in Japanese).