

Focal Plane Array Concept for ALMA 2030

ALMA-FED 2021
September 30, 2021

Doug Henke
NRC Herzberg

Chris Groppi
ASU



National Research
Council Canada

Conseil national de
recherches Canada

Canada

Overview (1)



Desires for Focal Plane Array (FPA) used within ALMA:

- Modularity vs. Integration trade-off:
 - Which parts are likely repeatable and can be integrated?
 - Which parts are variable, prone to failure, or require tweaking?
 - Trade-off: ‘N’ pieces \Leftrightarrow full integration
- Same performance as single-pixel receivers:
 - Dual-linear, 2SB
 - Ideally, share same components with single-pixel receiver (e.g., mixer block)
- Use components with isolation to reduce pixel-to-pixel leakage
- Size
- Split-block used for mixer block so that conventional chip mounting can be used
 - Serviceable (chip replacement)
 - Mixer block de-coupled within array (mixer block replacement)

Lessons Learned: Cycle 4 Study

Evaluated OMT-integrated, platelet-type architectures for future array implementation

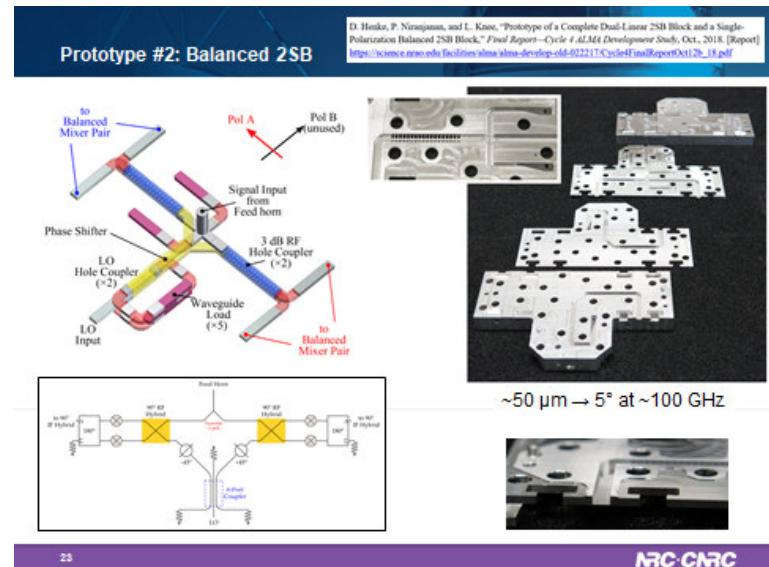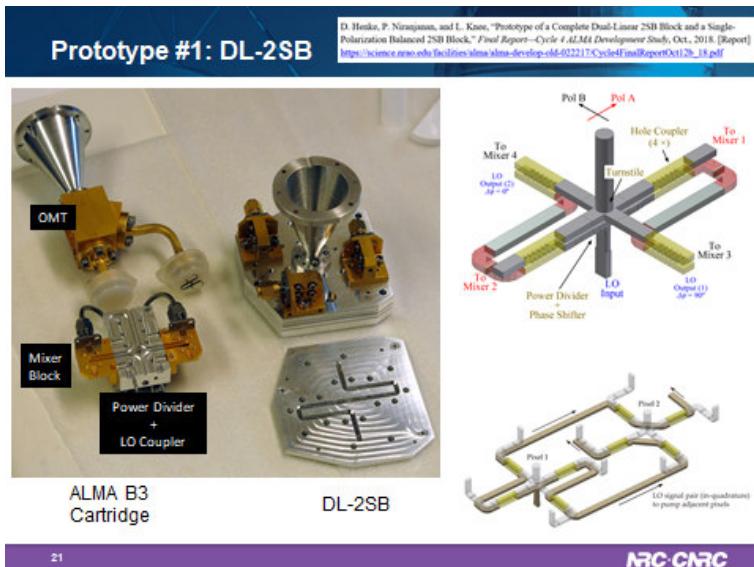- ✗ Using the turnstile as a power divider for 2SB didn't work – need isolation!
- ✓ Platelet implementation, integrating OMT
- ✓ Hole coupler for LO coupling and LO re-use worked
- ✓ Relative machining precision to give phase and amplitude balance




D. Henke, P. Niranjan, and L. Knee, "Prototype of a Complete Dual-Linear 2SB Block and a Single-Polarization Balanced 2SB Block," Final Report—Cycle 4 ALMA Development Study, Oct., 2018. [Report] https://science.nrao.edu/facilities/alma/alma-develop-old-022217/Cycle4FinalReportOct12b_18.pdf





Design Concept

- DL2SB “unit cell”

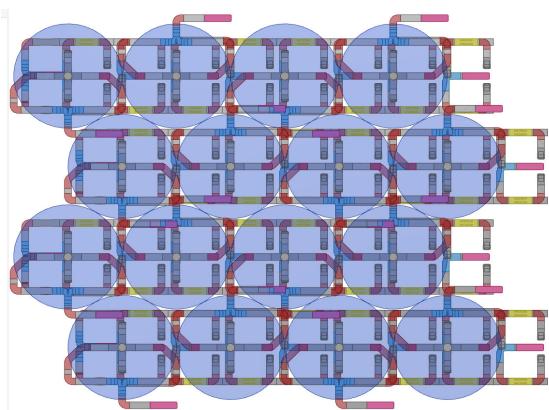- Integrate OMT, power dividers, and LO coupling
- Mixer blocks are separate
- Platelet assembly
- LO distributed along the array line




Example:
4 x 4 pixel array

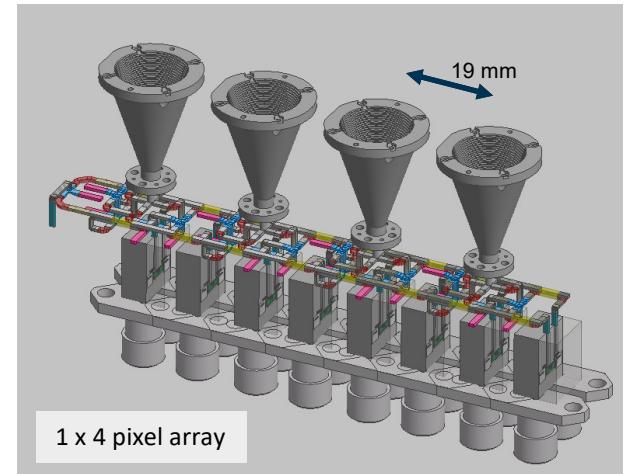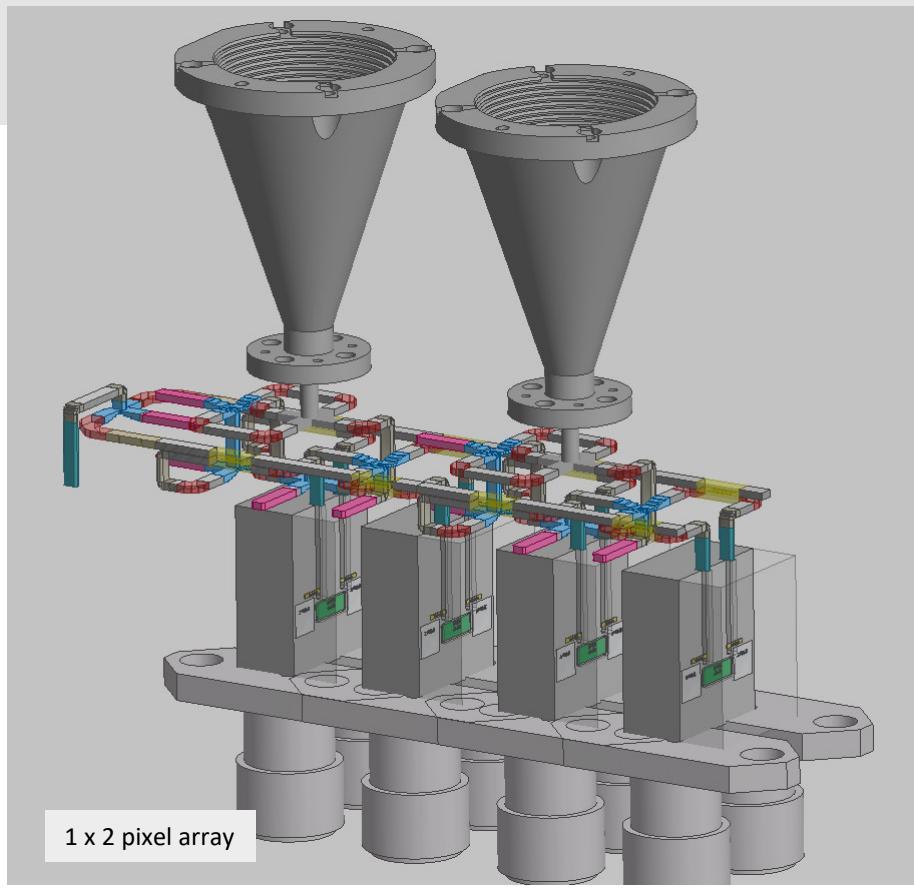


“Unit Cell” OMT + 2SB

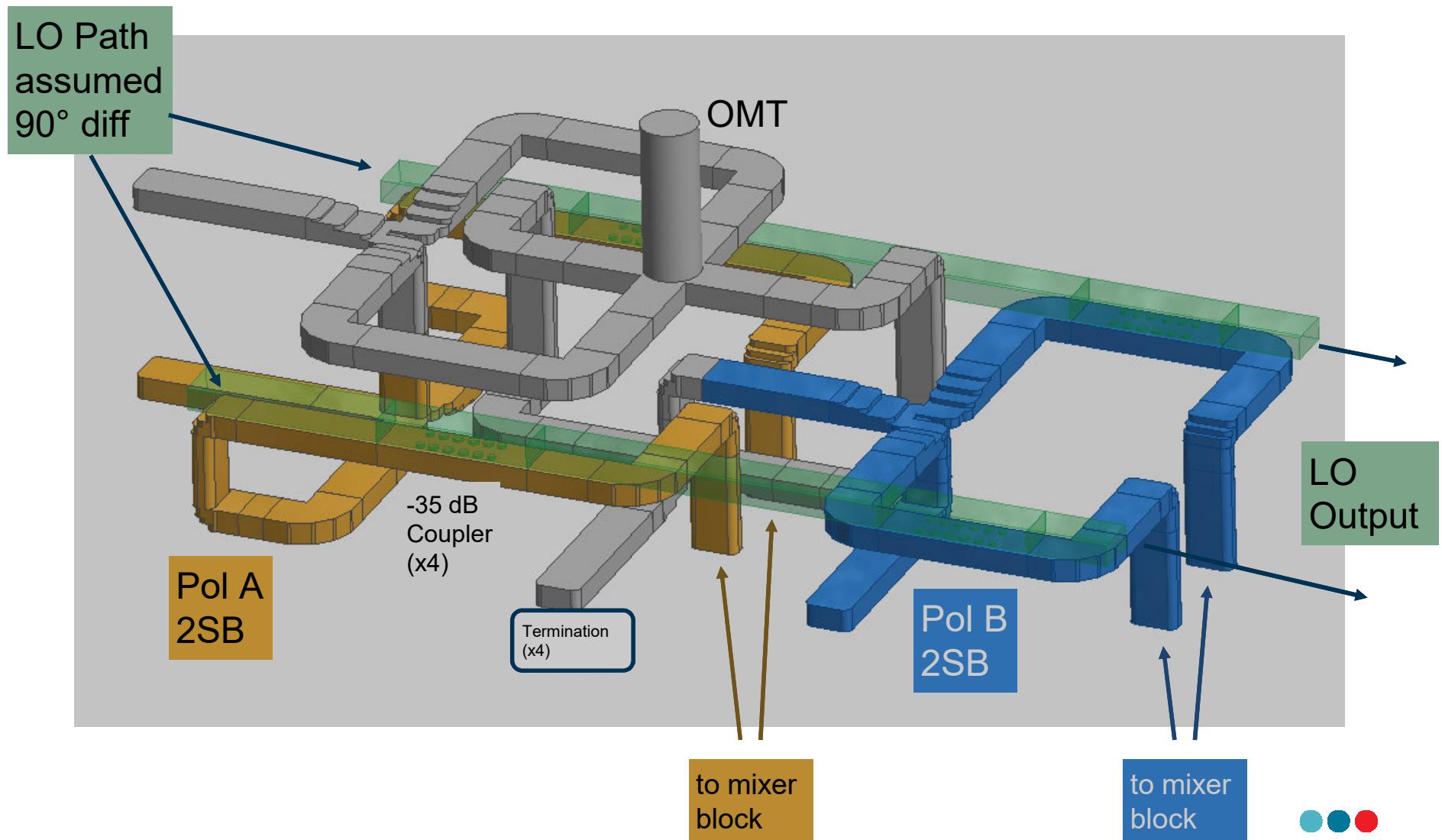Comprising: (1) OMT, (2) power dividers, and (3) LO path





“Unit Cell”: OMT Section

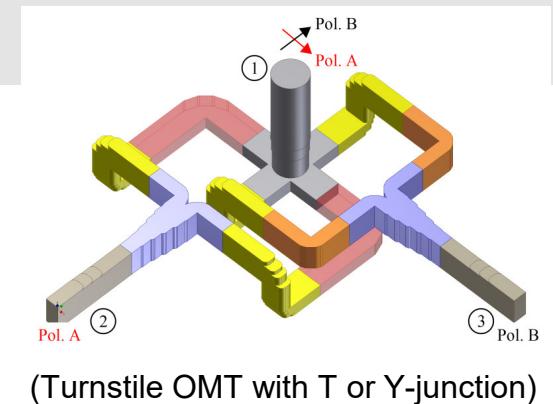- Turnstile
- Branch combiners are hybrid-Ts (replacing simple T-junction)
 - Absorber used to terminate 4th port
- Hybrid-T helps with layer misalignment
- Symmetric branches






(Turnstile OMT with T or Y-junction)

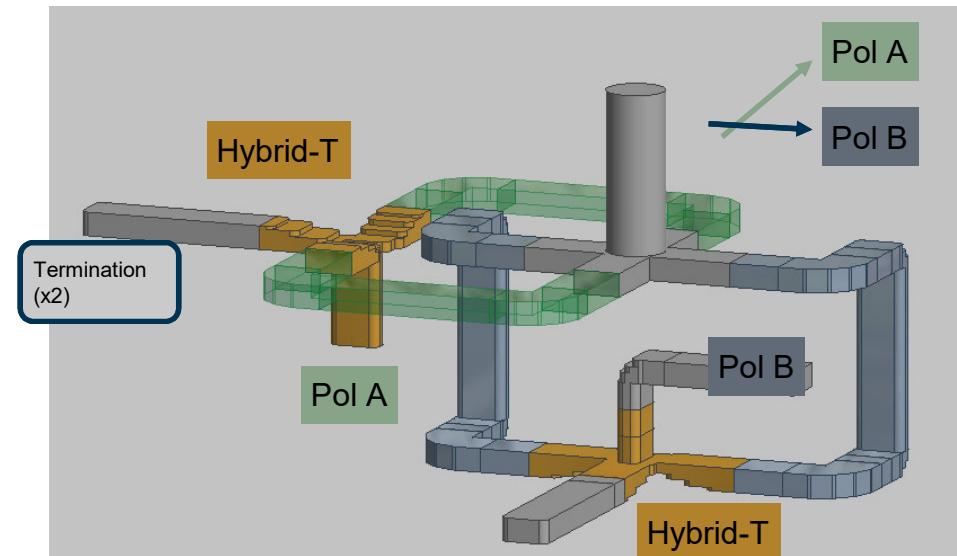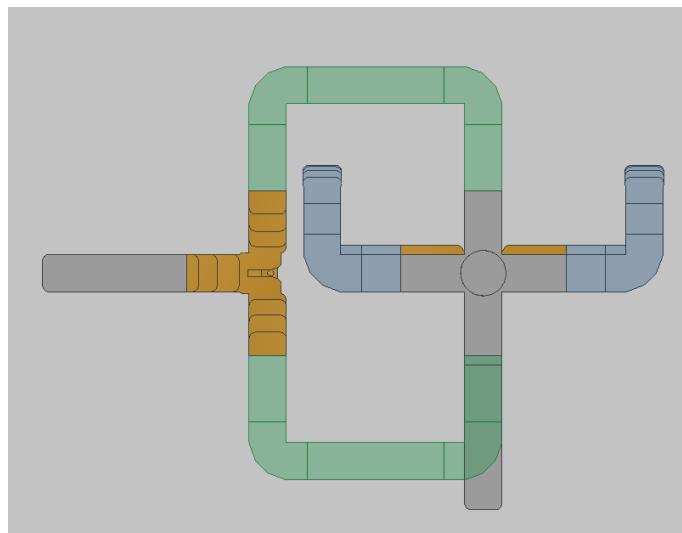

“Unit Cell”: Power Dividers for 2SB

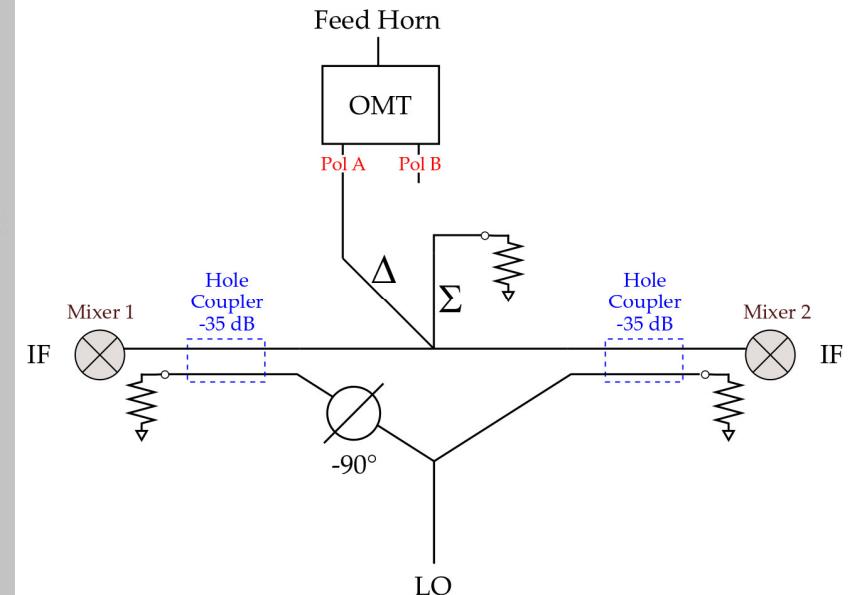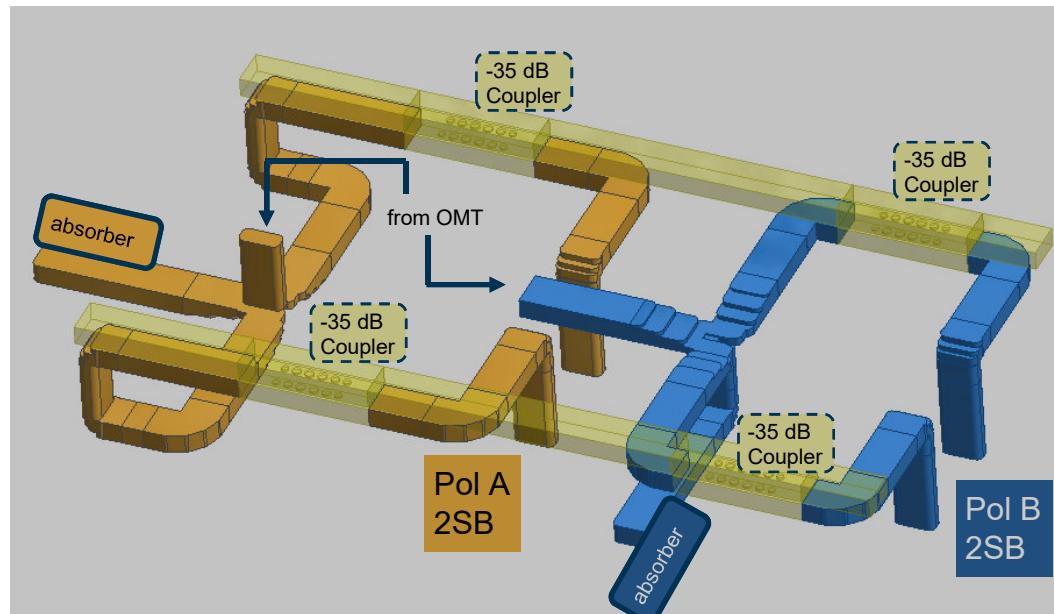
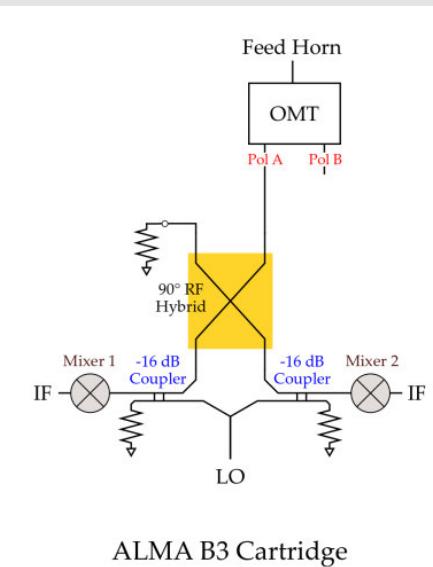
- Hybrid-Ts for power division to give isolation
- Mixers have high reflection, need to use 4-port hybrid as in current cartridge designs. Branchline couplers suitable for split-block, hybrid-T suitable for platelet.
- Pol A splits through diff port
- Pol B splits through sum port
- LO added in-quadrature, RF 0° or 180°



“Unit Cell”: LO Path

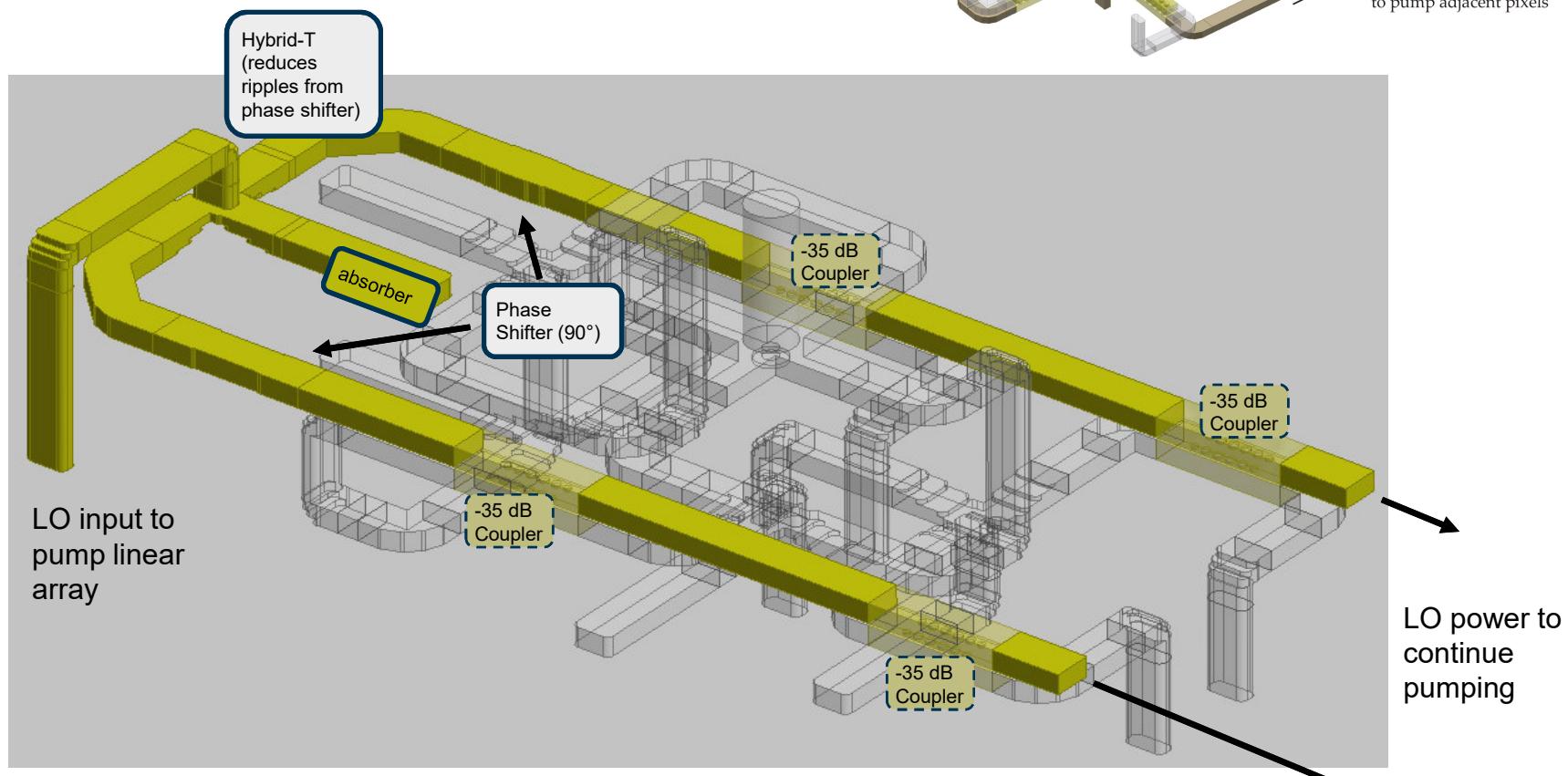
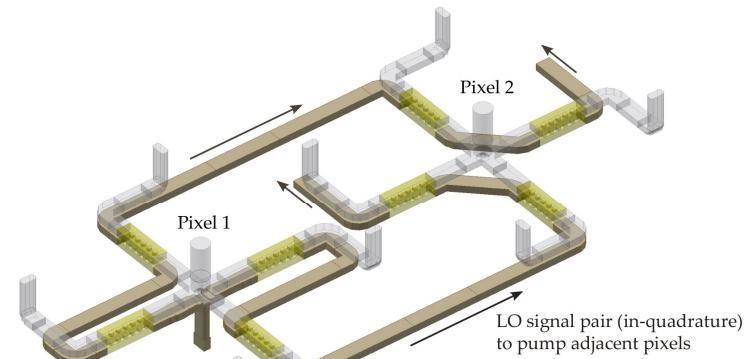
D. Henke, P. Niranjanan, and L. Knee, “Prototype of a Complete Dual-Linear 2SB Block and a Single-Polarization Balanced 2SB Block,” *Final Report—Cycle 4 ALMA Development Study*, Oct., 2018. [Report] https://science.nrao.edu/facilities/alma/alma-develop-old-022217/Cycle4FinalReportOct12b_18.pdf

- LO added in-quadrature, RF 0° or 180°
- Hole couplers were used to pump 4 mixers in Cycle 4 study prototype.





Mixer Blocks with IF Coupler

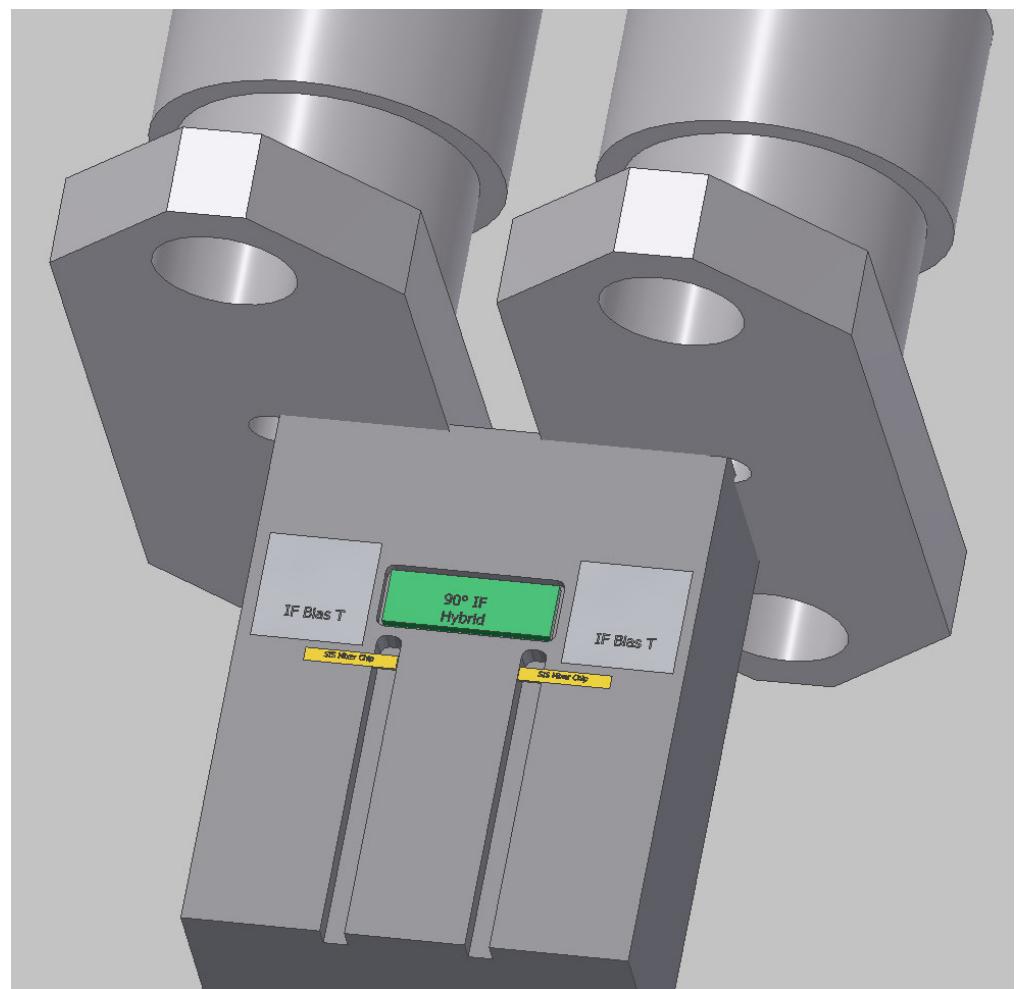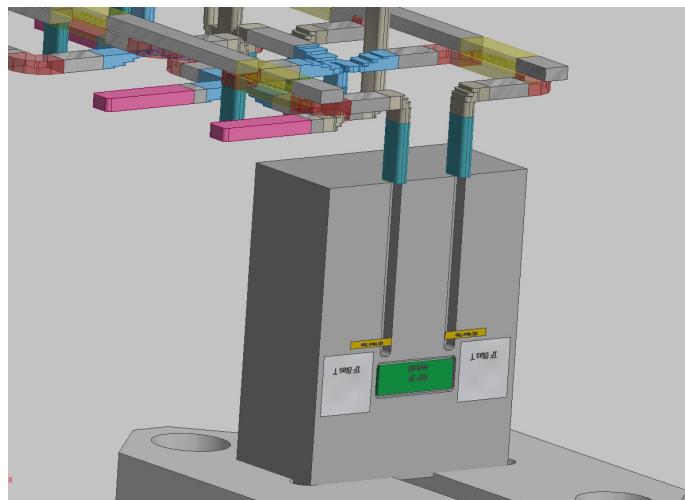- Mixer blocks are split-block to facilitate chip mounting
- No integrated RF couplers (facilitates “simple” measurement of DSB mixers during qualification)
- Machining complexity is shifted away from mixer block
- Integrated IF hybrid and bias T
- Smaller SMP coax needed, but SMA shown for scale
(shown here with respect to Band 6)





Implementation of DL2SB “Unit Cell” Block

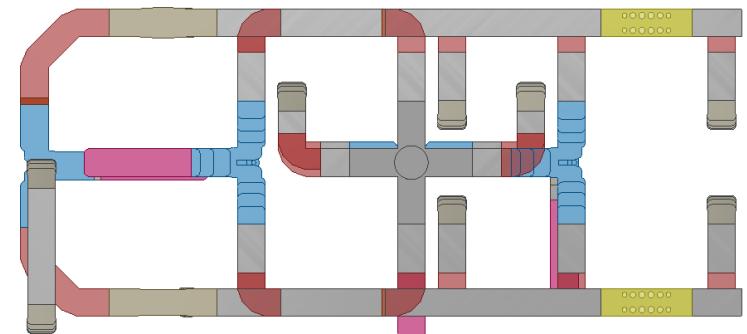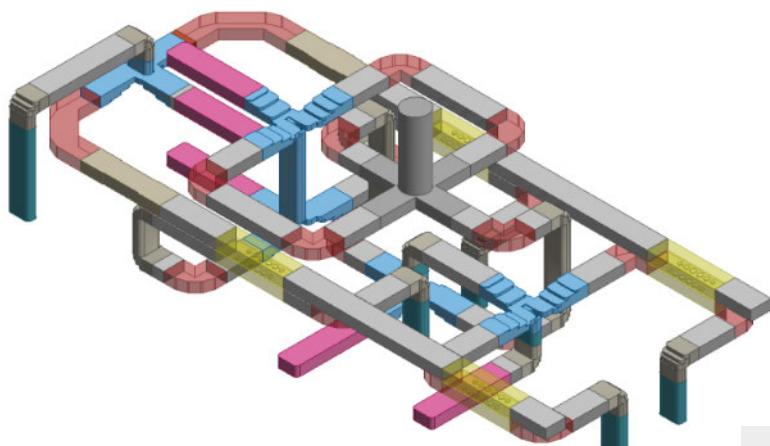- Platelet designs are naturally suited for arrays



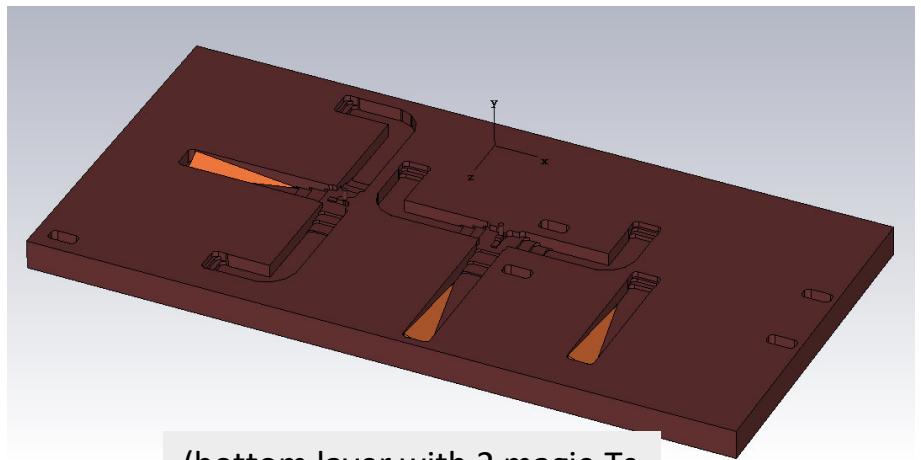
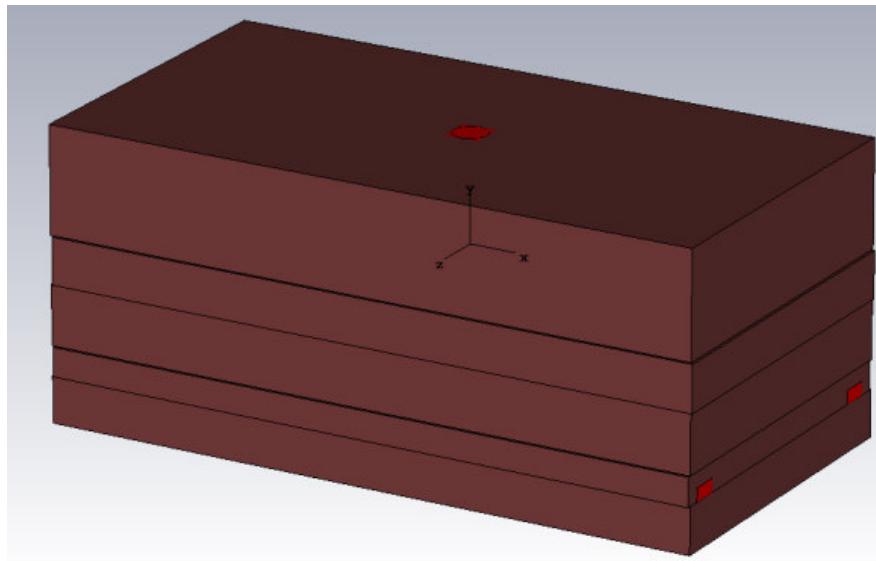
5-layer platelet design for a single-pixel



(bottom layer with 2 magic-Ts
and 3 wedge absorbers)





“Unit Cell”: Simulations

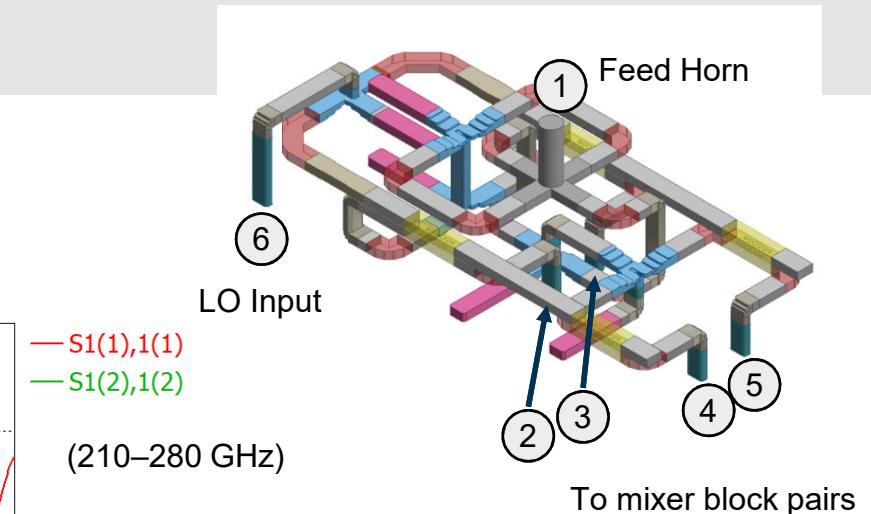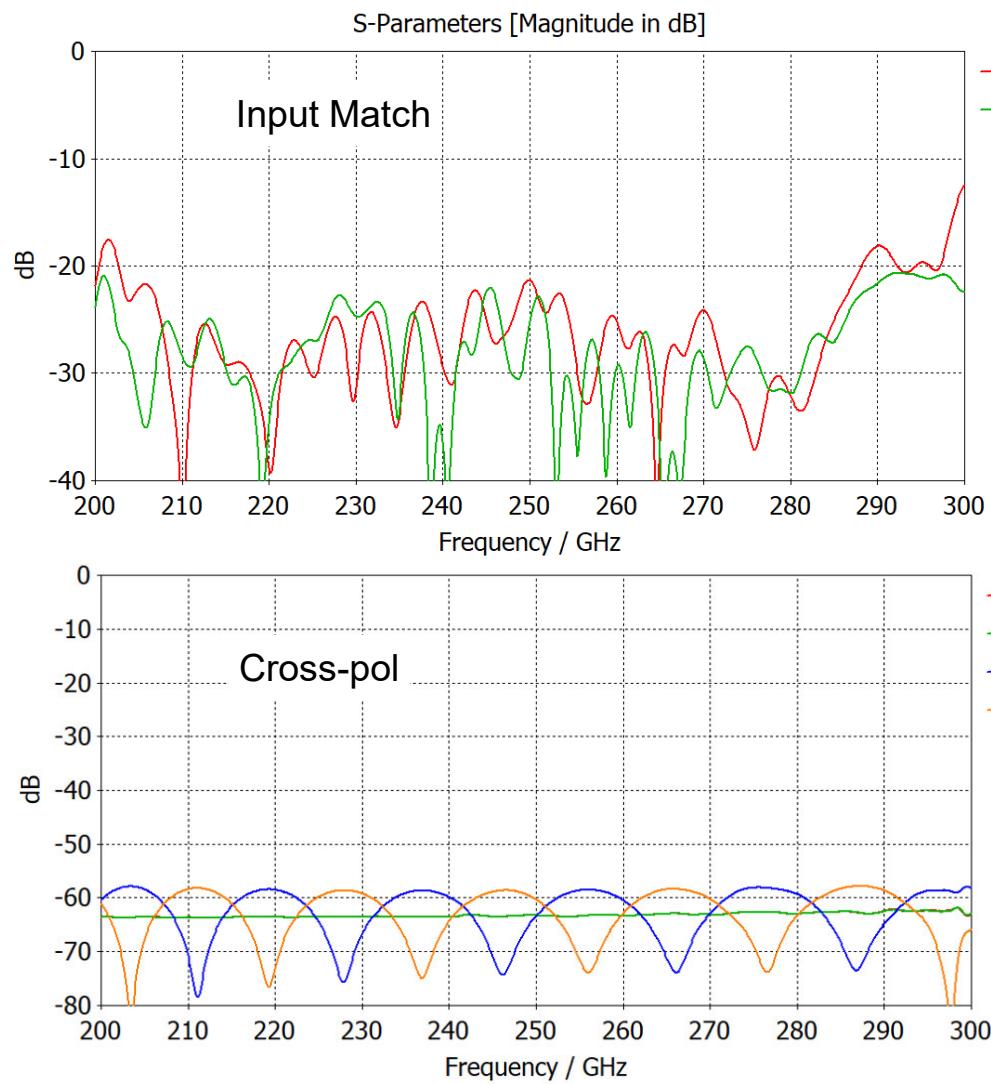

- S-parameter simulations from CST
- Metal conductivity is $5e7$ S/m
- Complete response of entire network: OMT+2SB dividers




“Unit Cell”: Simulations

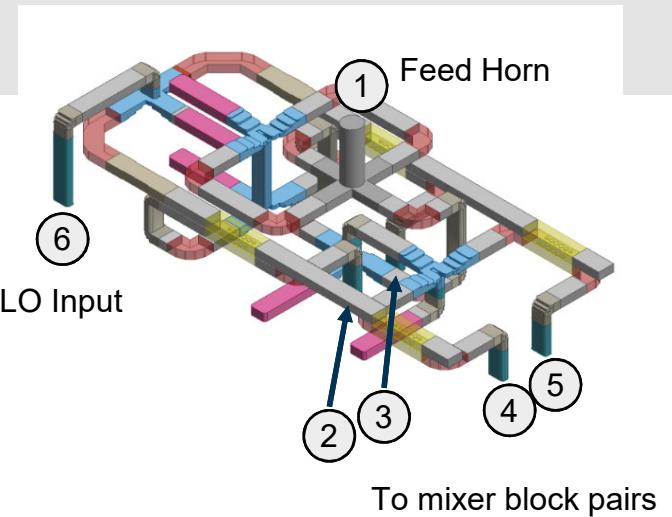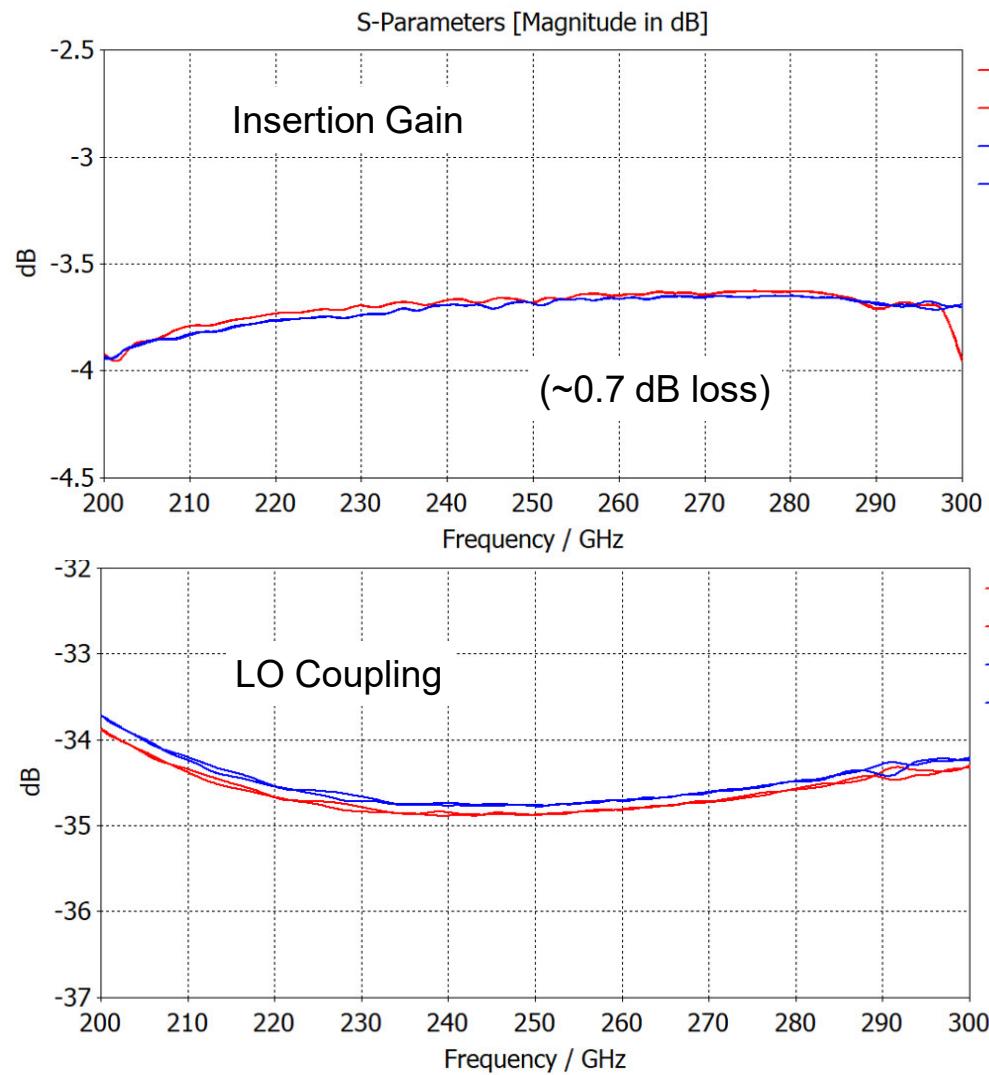


- S-parameter simulations from CST
- Metal conductivity is $5e7$ S/m
- Complete response of entire network: OMT+2SB dividers






“Unit Cell”: Simulations

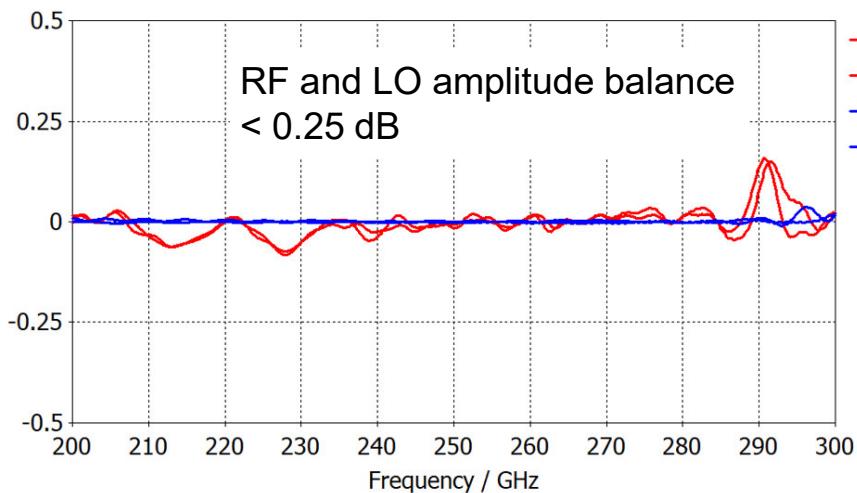

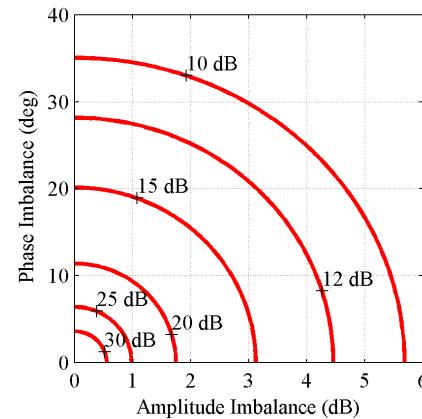LOampDiff_pol1
LOampDiff_pol2
RFampDiff_pol1
RFampDiff_pol2



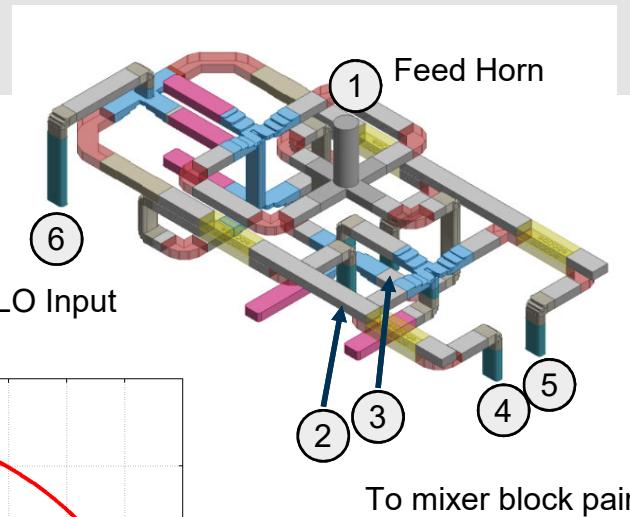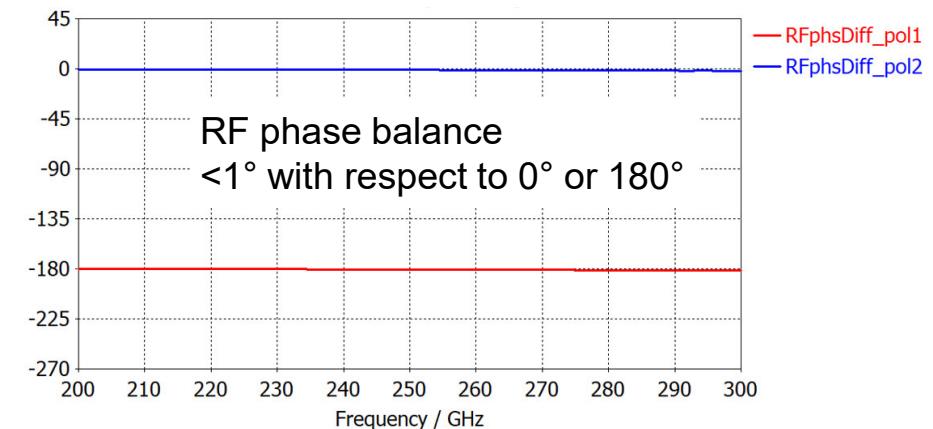
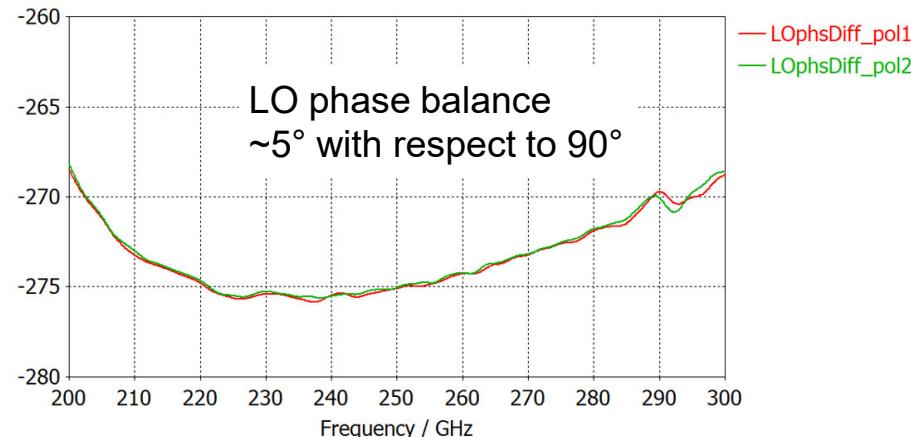
A. R. Kerr and S.-K. Pan, “Design of planar image-separating and balanced SIS mixers,” in Proc. 7th Int. Symp. Space Terahertz Technol., Mar. 12–14, 1996, pp. 207–219.



Misalignment in Platelet Stack-up

A common problem is block misalignment:

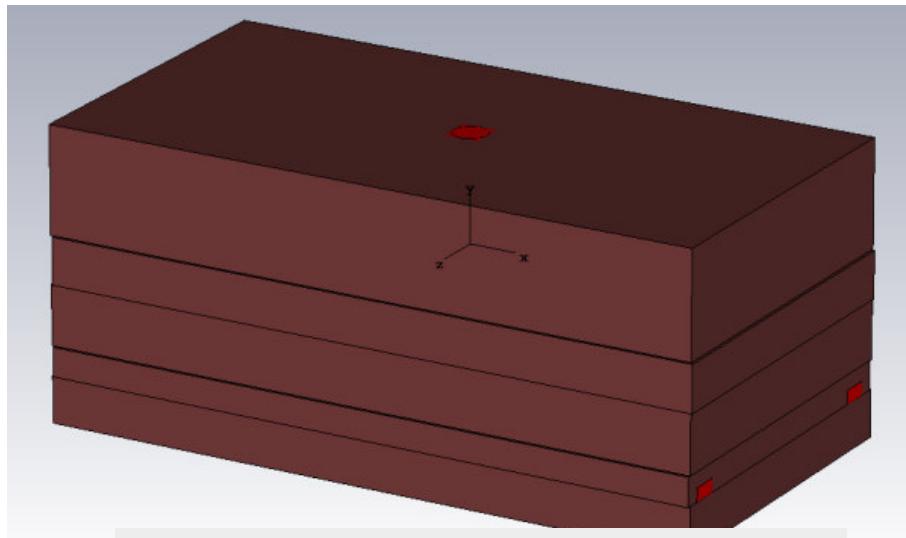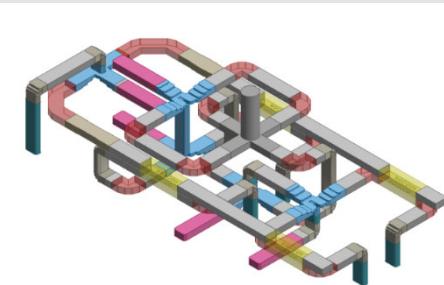
- Especially where multiple modes can propagate (e.g., circular or square waveguides...turnstile)
- Degrades balance
- Trapped energy/resonances
- Pixel-to-pixel leakage








5-layer platelet design for a single-pixel block

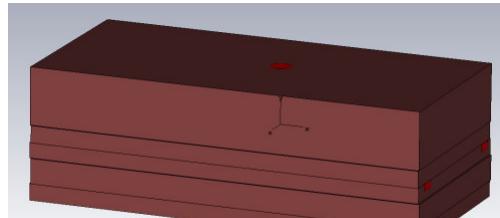In CST, shifted 2nd and 4th pieces in both X and Y







Effect of misaligning all layers

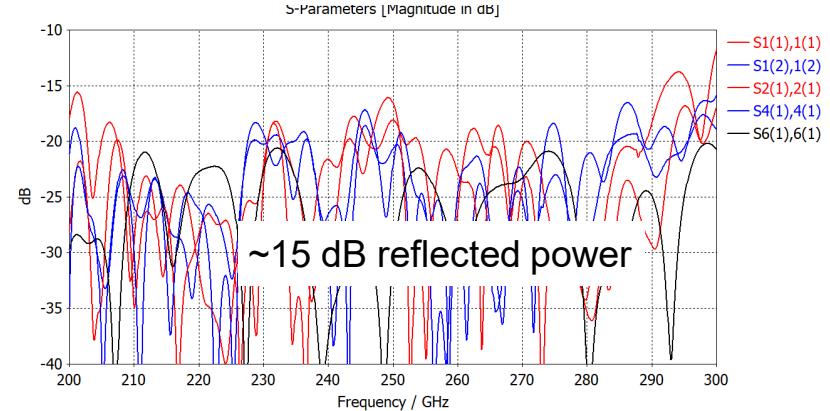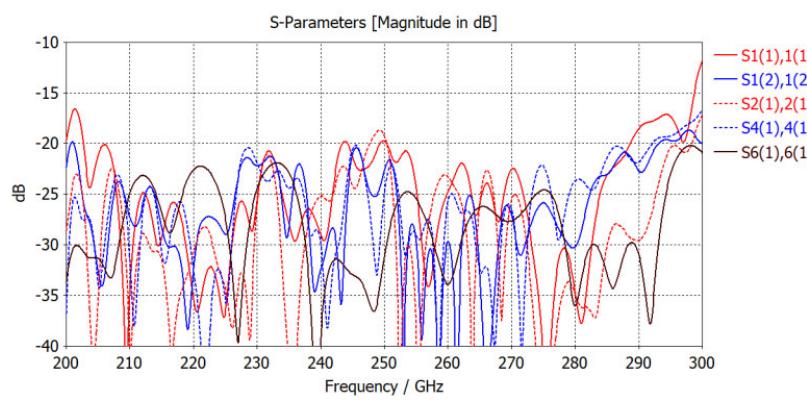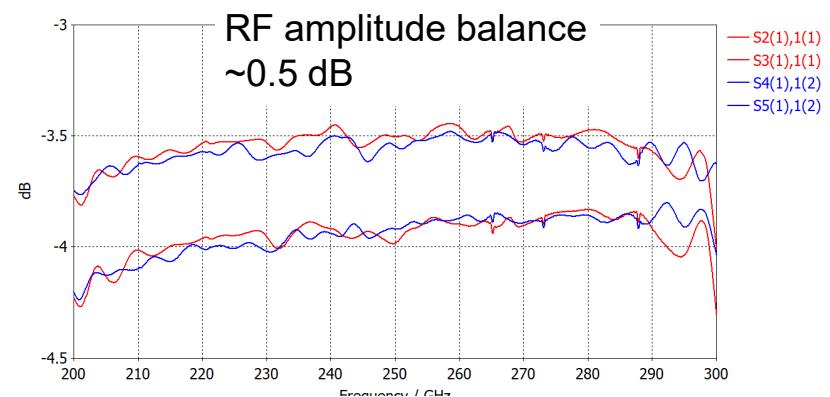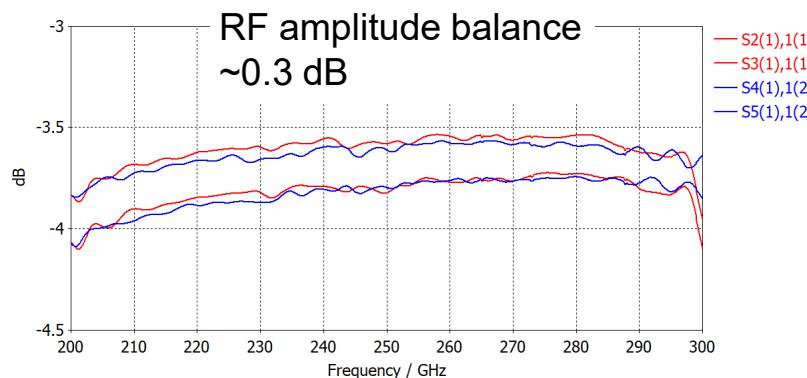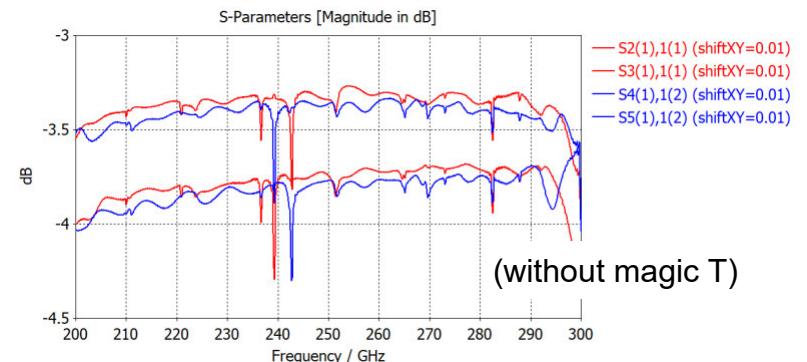


Integrated magic-Ts reduce spikes + trapped modes
Design should tolerate 5–10 μm of misalignment



2-Pixel Array

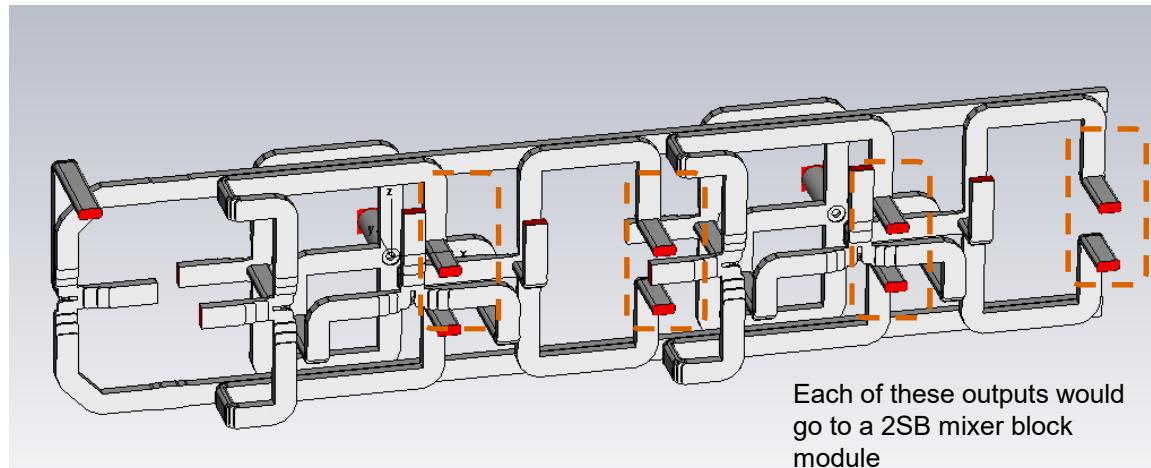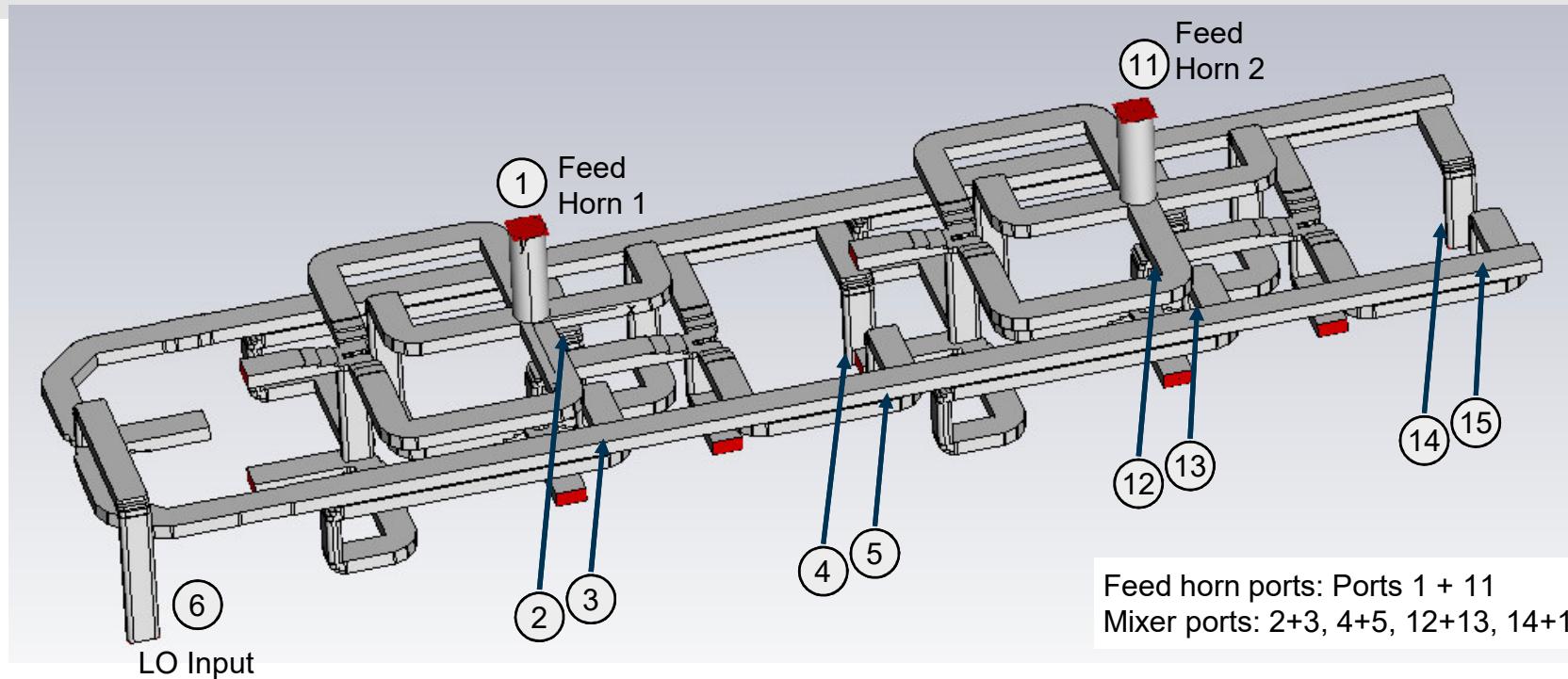


2-Pixel Array, Pixel-to-Pixel Leakage

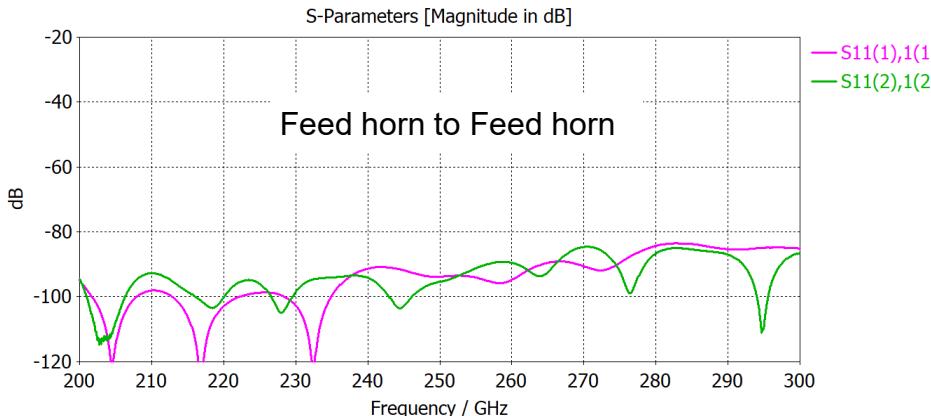

(perfect alignment, lossless)

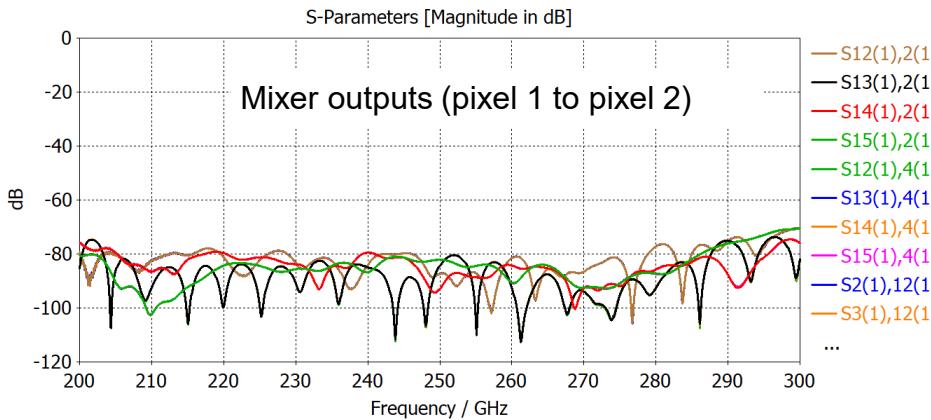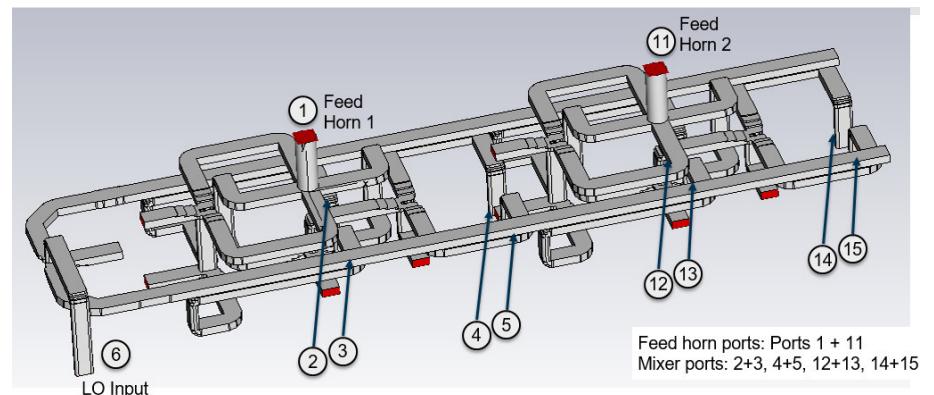

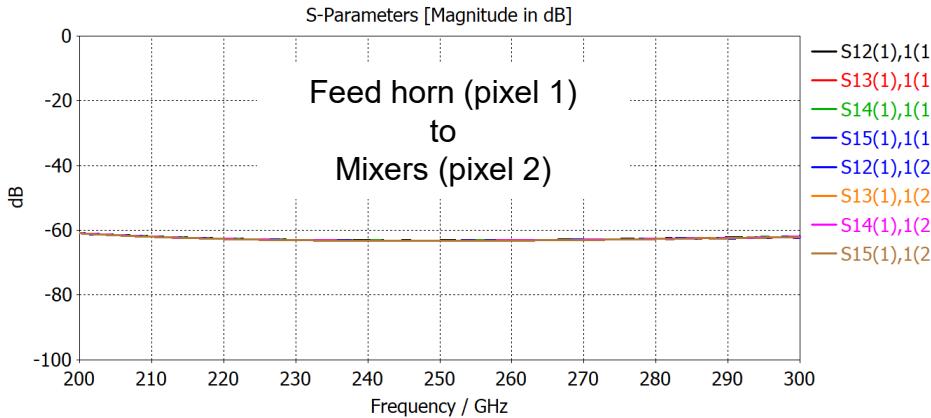Feed horn ports: Ports 1 + 11
Mixer ports: 2+3, 4+5, 12+13, 14+15




(leakage through LO coupling path)

Hybrid-T: Key Component!

Proceedings of the 43rd European Microwave Conference

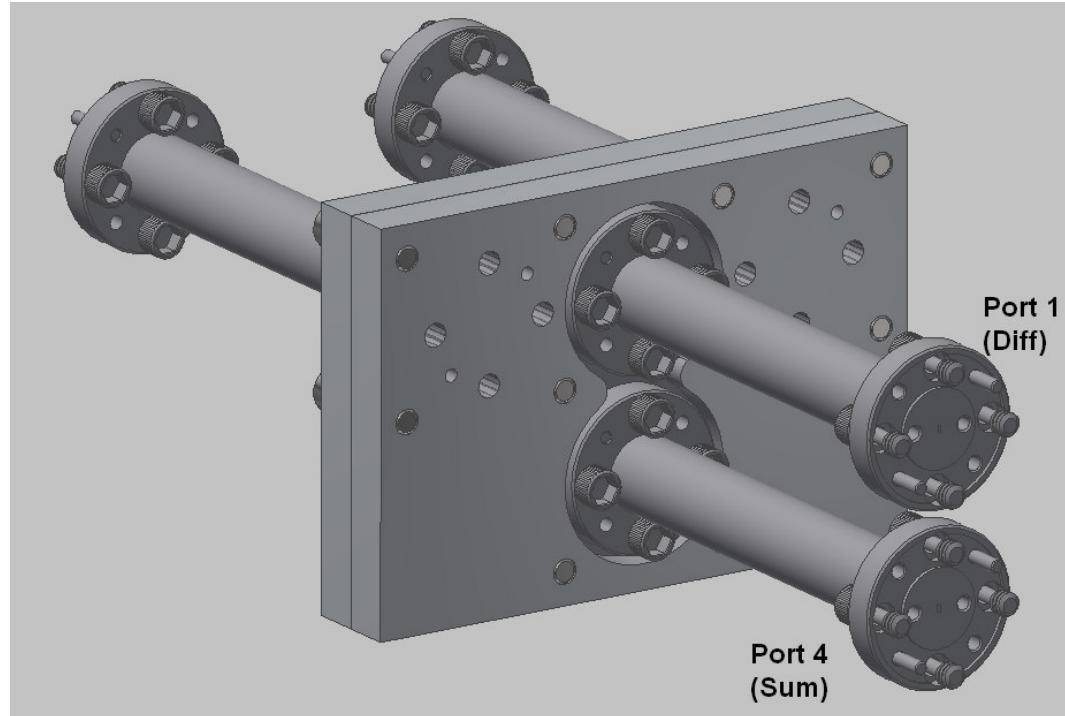- “Magic-T” is a critical component for these platelet-type designs
- 2-layer, all metal; inspired by a paper by Carlos Leal-Sevillano
- Collaborating with Chris Groppi (ASU) to prototype a hybrid-T to test machinability and performance**



Compact Broadband Couplers Based on the Waveguide Magic-T Junction


Carlos A. Leal-Sevillano*, Jorge A. Ruiz-Cruz†, José R. Montejo-Garai*, Jesús M. Rebollar*

*Departamento de Electromagnetismo y Teoría de Circuitos, Universidad Politécnica de Madrid.


†Escuela Politécnica Superior, Universidad Autónoma de Madrid.

Abstract—In this paper, a broadband 180° waveguide directional coupler based on a modified magic-T junction is presented. The well-known magic-T waveguide junction is effectively modified and optimized leading to enhanced performance. Moreover, the volume of the proposed enhanced magic-T is similar to the classic junction. The novel magic-T proposed uses an iris in the E port, a single width step in the H port, a simple post in the PEW port, and a helical slot in the PMW port to couple signals. The bandwidth of the directional coupler can be significantly enlarged with a proper optimization of these four key elements. Different designs are presented covering the full standard rectangular waveguide band, over 40% relative bandwidth, with more than 25 dB return loss in the four ports. In addition, a compact bend with integrated transformer is introduced at the input/output interfaces.

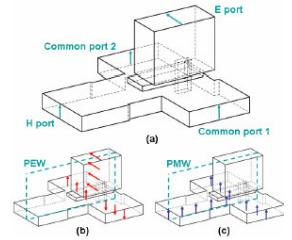Index Terms—Waveguide, magic-T, directional coupler, broadband.



I. INTRODUCTION

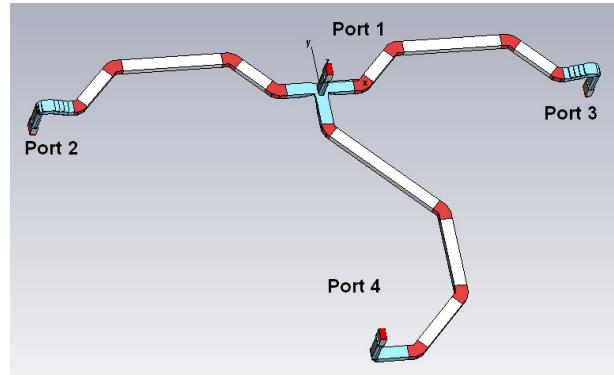


Doug Henke, NRC Herzberg

Summary

- DL2SB “unit cell”

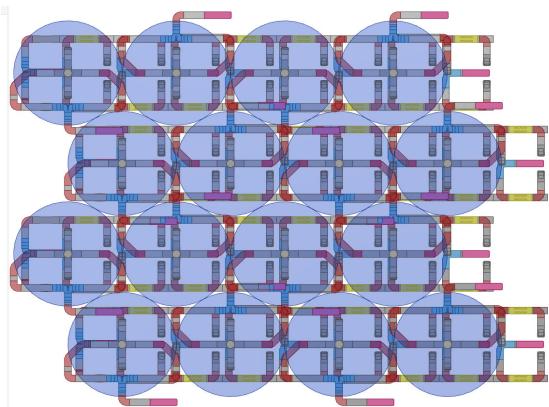- Integrate OMT, power dividers, and LO coupling
- Mixer blocks are separate + split-block
- Platelet assembly
- LO distributed along the array line



Example:
4 x 4 pixel array

